
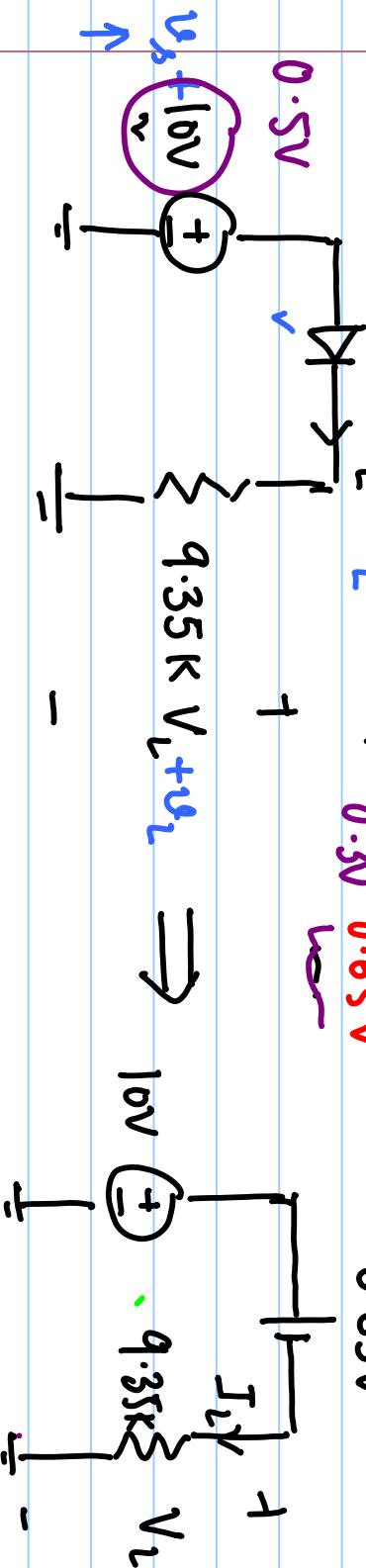


Lecture # 04

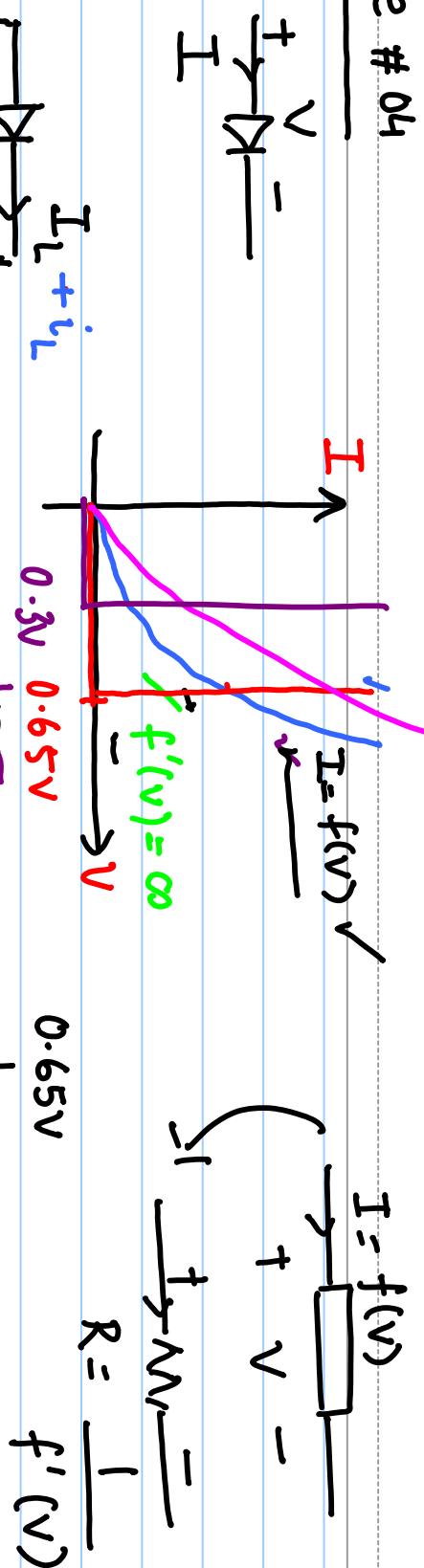

$$-I = I_s \left[\exp\left(\frac{V}{V_T}\right) - 1 \right]$$

$$V_L = 9.35V$$

$$I_L = \frac{9.35V}{9.35K} = 1mA$$


$$f'(V) = \frac{dI}{dV} = I_s \exp\left(\frac{V}{V_T}\right)$$

$$f'(V) = \frac{I}{V_T} = \frac{1mA}{25mV} = \frac{1}{25}$$

$$f'(V) = \frac{I}{V_T} = \frac{1mA}{25mV} = \frac{1}{25}$$


$$R_D = 1/f'(v) = 25\Omega$$
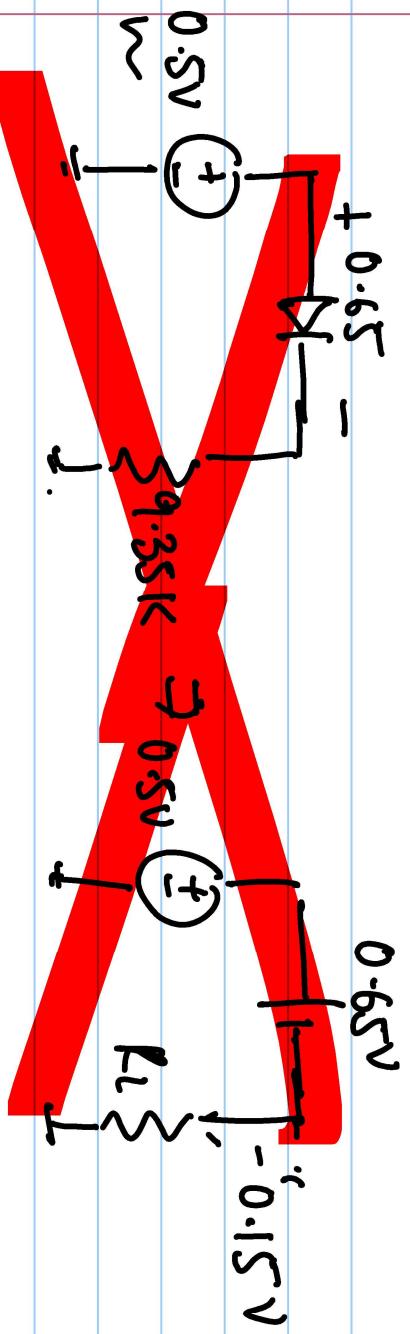
$$\frac{U_L}{U_K} = \frac{R_L}{R_L + R_D} = \frac{9.35k}{9.35k + 25\Omega}$$




- If zeroth-order approx. is valid at 0.65V, don't use it when input voltage is lesser than 0.65V.
- Diodes in different technology can have different potential drop across them for zeroth-order approx.

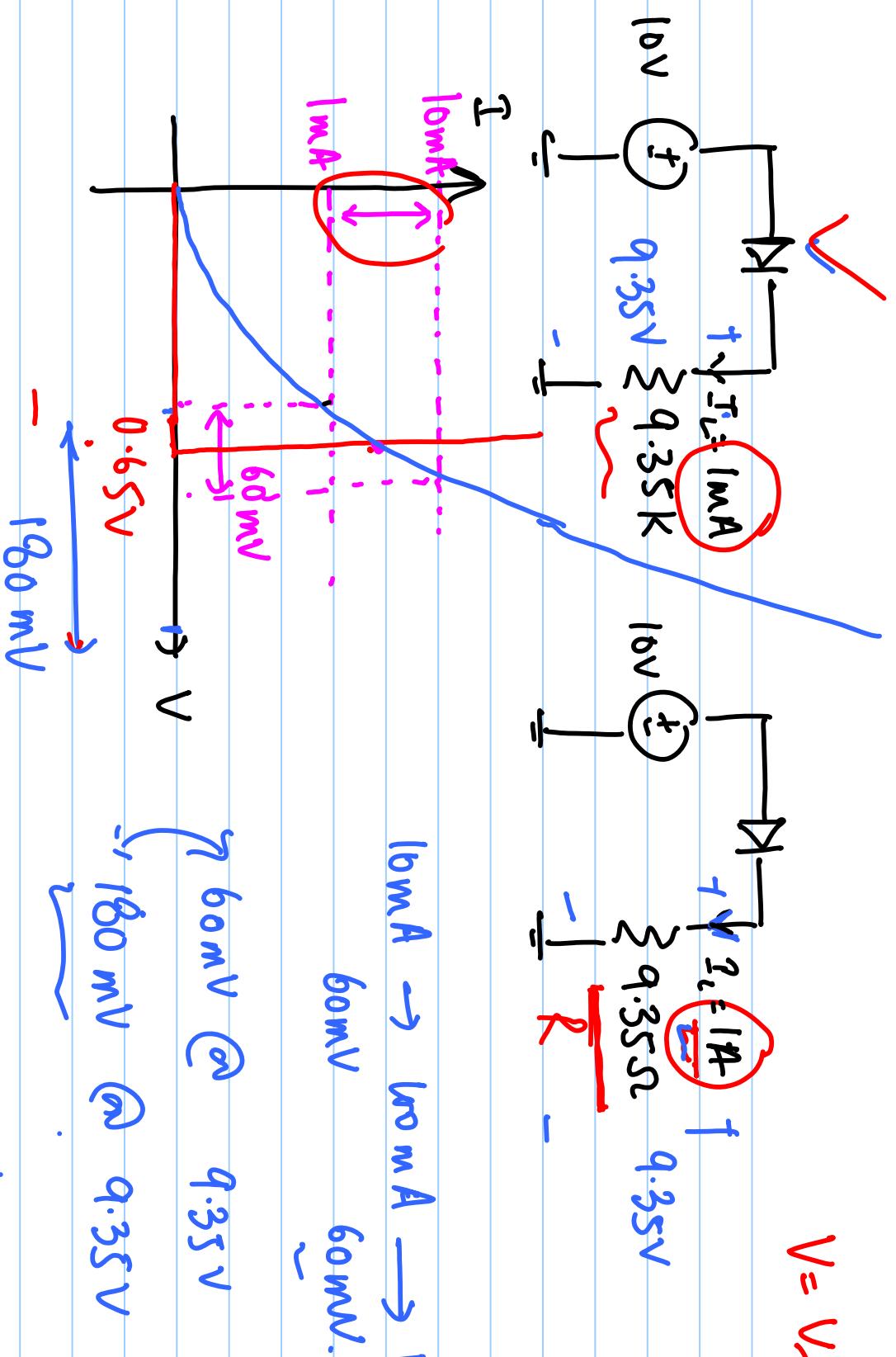
$$V = V_T \ln\left(\frac{I}{I_S}\right)$$



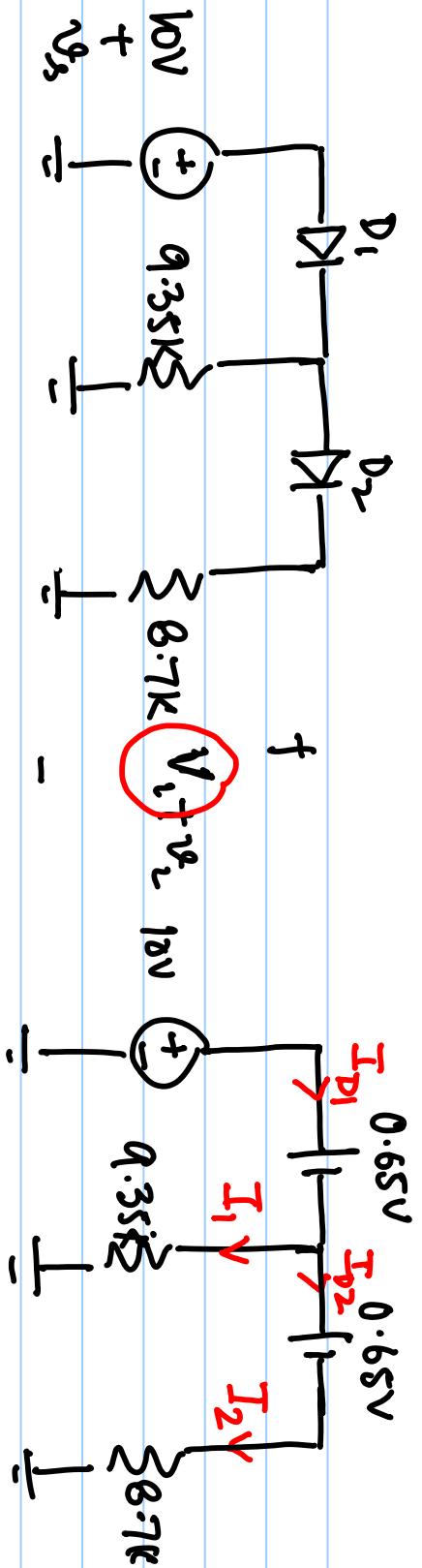- To calculate operating point, use zeroth-order approx.
- To calculate small-signal mode, use actual I vs V relationship.



Small-signal Circuit

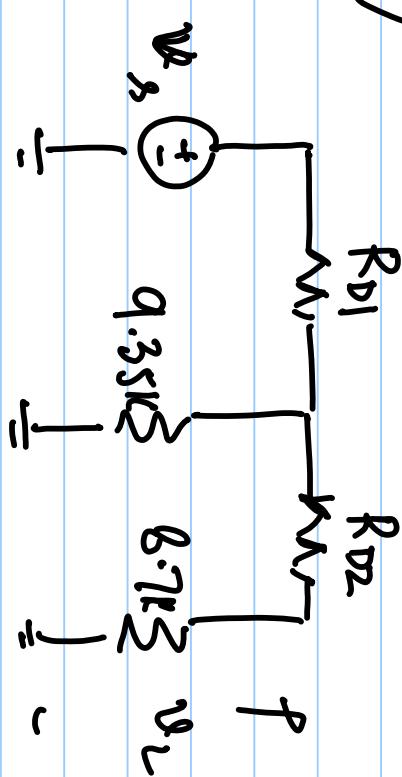

$$\bar{I}_1 = \bar{I}_2 = 1\text{mA}$$

$$\bar{I}_{D2} = \bar{I}_2 = 1\text{mA}, \quad \bar{I}_{D1} = \bar{I}_1 + \bar{I}_{D2} = 2\text{mA}$$

$$R_{D1} = \frac{1}{f(V)} = \frac{25\text{mV}}{2\text{mA}} = 12.5\Omega$$

$$R_{D2} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

$$\frac{V_L}{V_{L_s}} =$$

$$I + V =$$

$$I = f(V)$$


$$I + i = f(V + v)$$

$$I + i = f(V) + f'(V)v + f''(V) \frac{v^2}{2!} + \dots$$

$$i = f'(V)v + f''(V) \frac{v^2}{2!} + \dots$$

$$\int i \approx f'(V)v$$






$$\approx f'(V)v$$

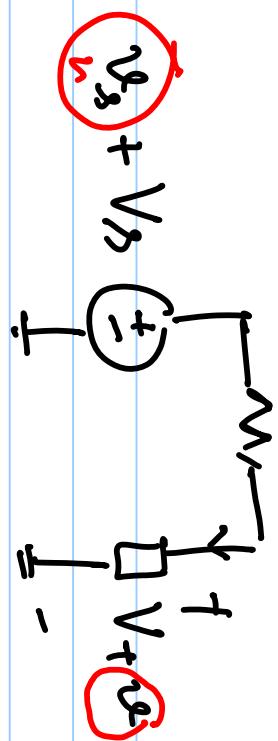

Element in Non-linear Circuit

(operating point ana.)


Circuit for small-signal ana.

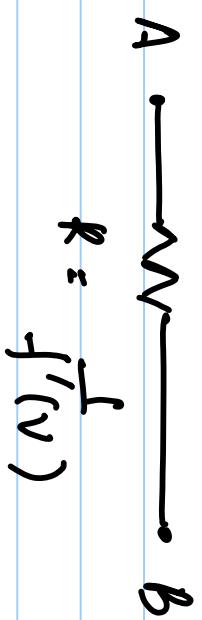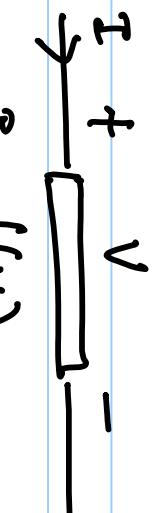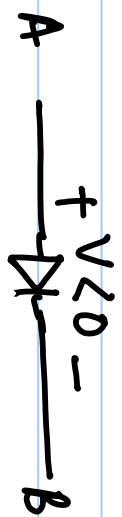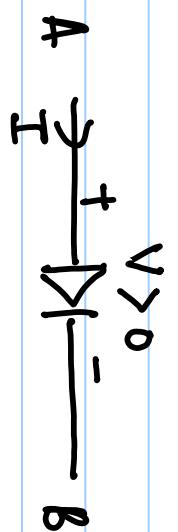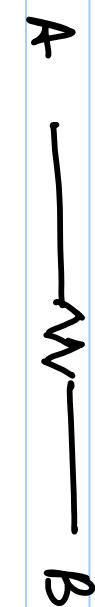

$$I = I_s [\exp(\frac{V}{V_t}) - 1]$$

$I = -I_s$ in reverse bias.

I_s

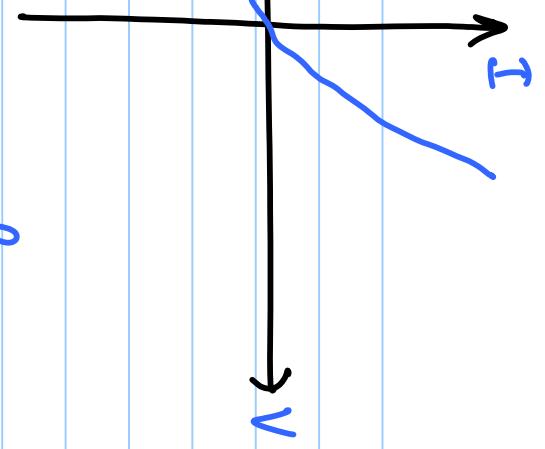

I_s

\curvearrowleft

\curvearrowright

\curvearrowleft