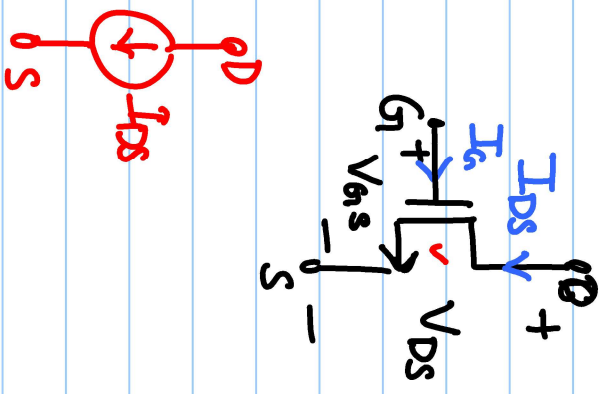


Lecture # 7



i) $V_{gs} \leq V_{th}$: $I_{DS} = 0$, $I_G = 0$

ii) $V_{gs} > V_{th}$, $V_{DS} < V_{gs} - V_{th}$:

$$I_G = 0 , I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

iii) $V_{gs} > V_{th}$, $V_{DS} \geq V_{gs} - V_{th}$


$$I_G = 0 , I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{gs} - V_{th})^2$$

μ_n : mobility of

C_{ox} : Cap. per unit area.



W, L : dimensions of MOSFET

$$I_{DS} = f(V_{gs}, V_{DS})$$

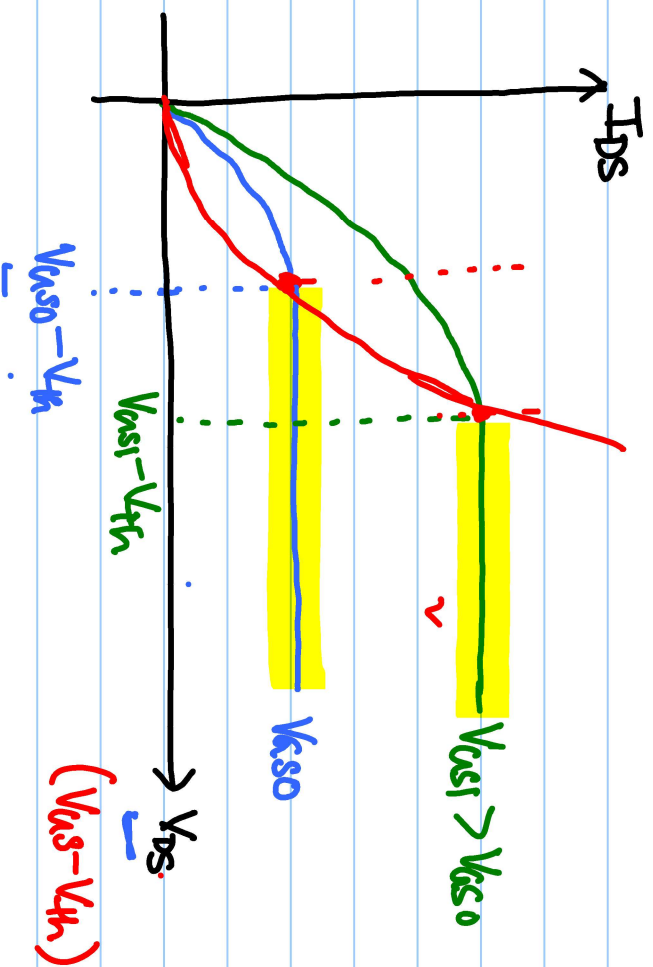

$$V_{GS} - V_{th} \stackrel{qD}{=} I_{DS} \stackrel{D}{=} \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2$$

$$V_{DS} > V_{GS} - V_{th}$$

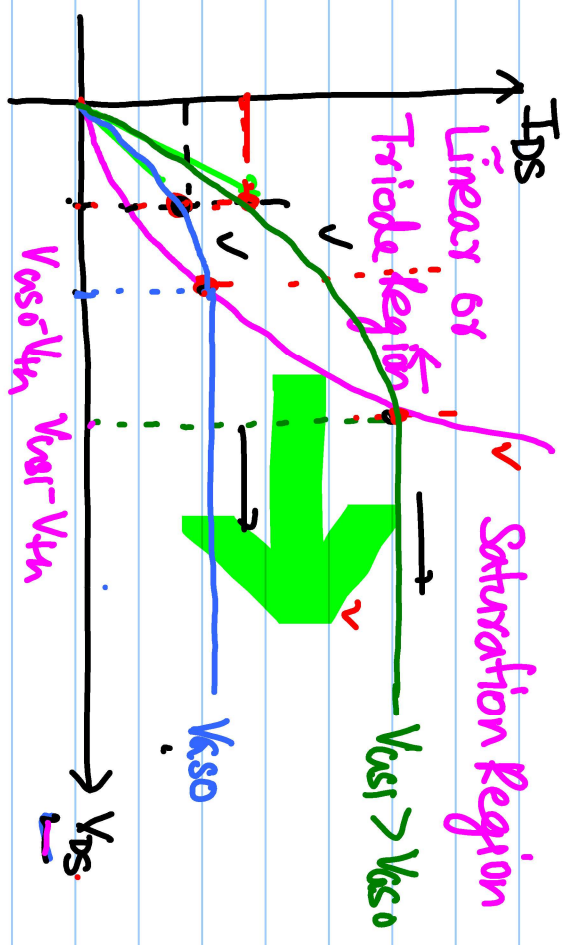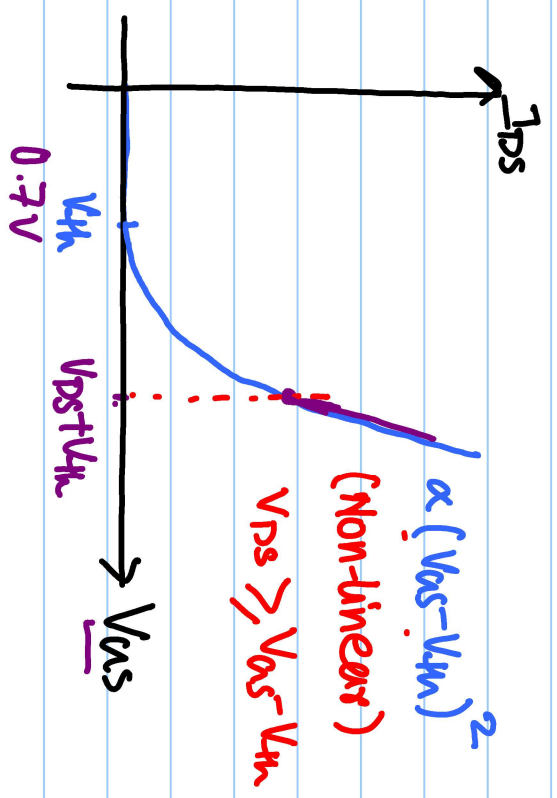


$$I_{DS} = f(V_{GS}, V_{DS})$$

- Control voltage to control current.


$$V_{DS} < V_{GS} - V_{th}$$

$$V_{DS} = 2.5V$$

$$V_{GS} - V_{th} = 2.5V$$

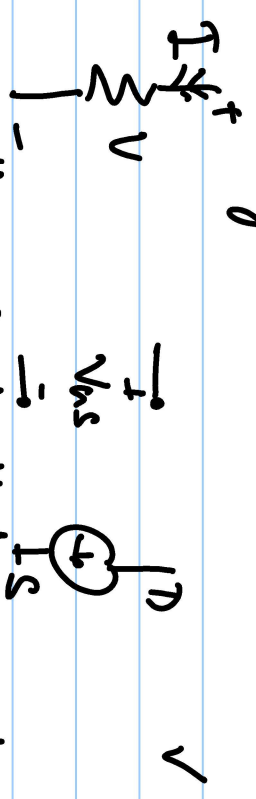

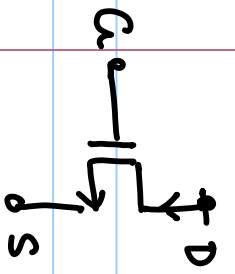W.r.t V_{GS} , Voltage Controlled Current Source




a) current source ✓

Saturation




b) voltage controlled current source

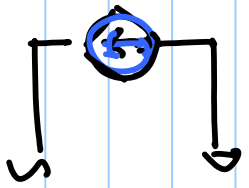

c) resistor : voltage controlled resistor



linear

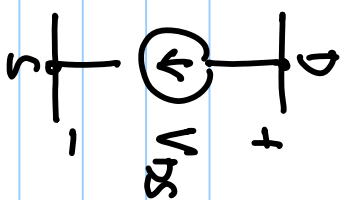

w.r.t \$V_{DS}\$, current source
when \$V_{DS} > V_{GS} - V_{th}\$.

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) - \frac{V_{DS}}{2} \right] \cdot V_{DS}$$

$V_{GS} - V_{th} > V_{DS}$ ✓


\$V_{DS} \ll V_{GS} - V_{th}\$

$$I_{DS} \approx \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}] V_{DS}$$

$$R = \frac{V_{DS}}{I_{DS}} = \frac{1}{\mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}]}$$

MOSFET behaves like a resistor w.r.t \$V_{DS}\$.
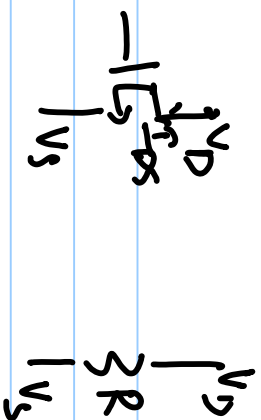
$$I_{DS} = \mu n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



$$R = \frac{V_{DS}}{I_{DS}} = \frac{1}{\mu n C_{ox} \frac{W}{L} \left[V_{GS} - V_{th} - \frac{V_{DS}}{2} \right]}$$

$$R = f(V_{GS}, V_{DS})$$

$$= R_0 + \alpha V_{DS} + \beta \frac{V_{DS}^2}{2}$$

Ex: $V_{th} = 1V$, $\frac{W}{L} = \frac{1\mu m}{1\mu m}$



$\mu n_{tox} = 100 \mu A/V^2$

a) $V_{GS} = 2V$, $V_{DS} = 2V > 2-1=1V$

$I_{DS} = \frac{100 \times 10^{-6}}{2} \frac{1}{1} (2-1)^2 = 50 \mu A$

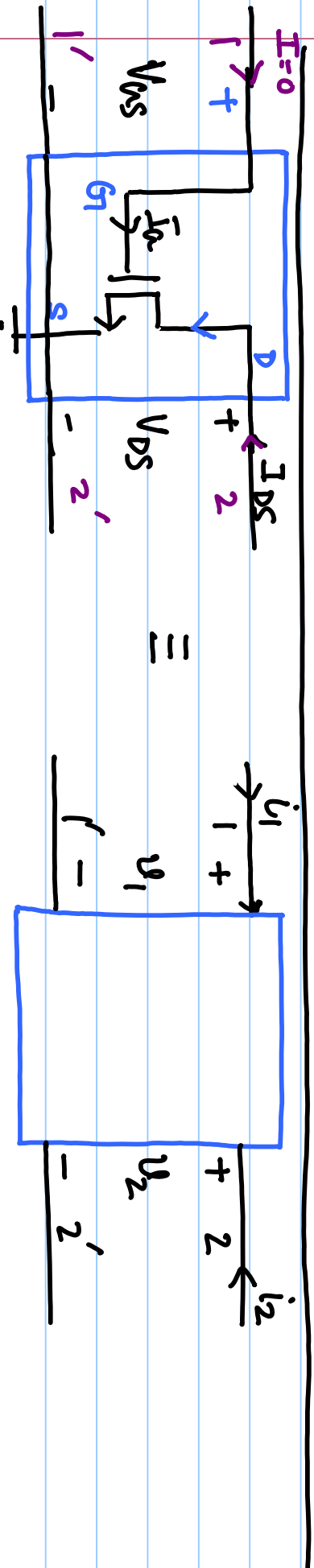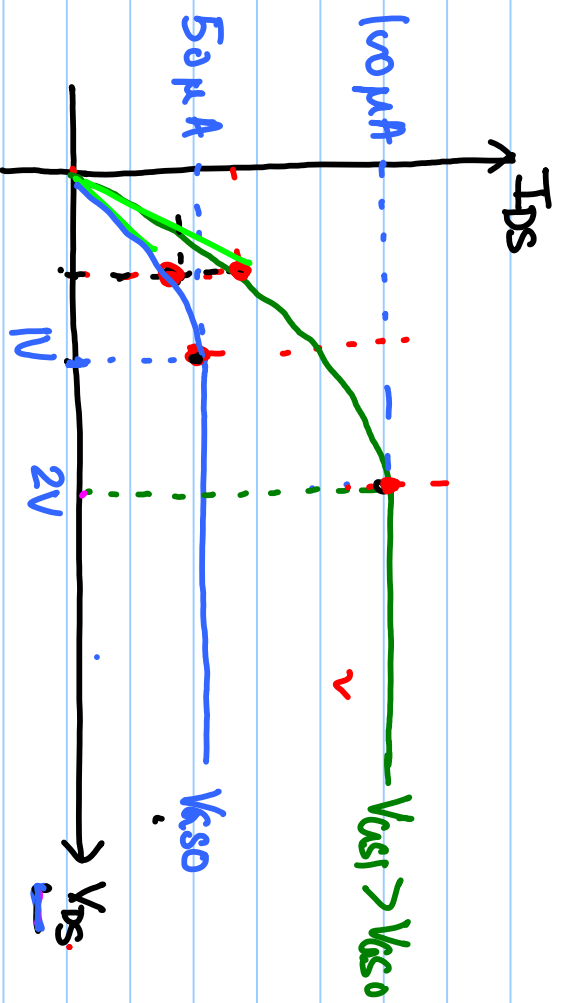
b) $V_{GS} = 3V$

$I_{DS} = \frac{100 \times 10^{-6}}{2} \times \frac{1}{1} \times (3-1)^2 = 200 \mu A$



MOSFET: a non-linear

linear system.

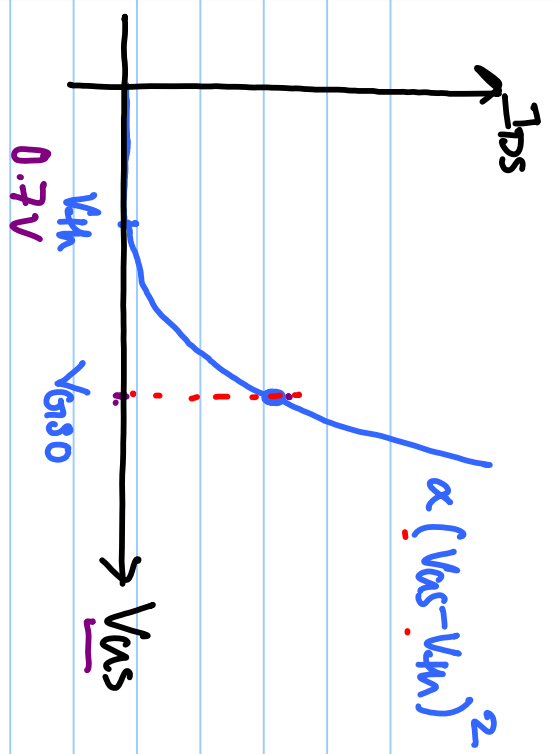

$$I_{DSS} = f(V_{GS}, V_{DS})$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

i_1, i_2 : small changes in i/p & o/p current

v_1, v_2 : " i/p & o/p voltages.

$$\begin{bmatrix} i_{DS} \\ i_{DS} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ y_{21} & 0 \end{bmatrix} \begin{bmatrix} v_{GS} \\ v_{DS} \end{bmatrix}$$

Saturating region

$$I_{DSS} = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{Th})^2$$

$$= f(V_{GS}, V_{DS})$$

$$i_{DS} = \frac{\partial f}{\partial V_{GS}} \cdot v_{GS} + \frac{\partial f}{\partial V_{DS}} \cdot v_{DS}$$

$$y_{21} = \frac{\partial f}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{Th})$$

$$\frac{\partial f}{\partial V_{DS}} = 0$$

$y_{11}, y_{22} : 0$
 $y_{12} : 0$

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{thn}) V_{DS} - \frac{V_{DS}^2}{2}]$$

$$\frac{\partial I}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} V_{DS}$$

$$\frac{\partial I}{\partial V_{DS}} = \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{thn} - V_{DS}]$$

$$\begin{bmatrix} i_{as} \\ i_{os} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ \frac{\partial I}{\partial V_{GS}} & \frac{\partial I}{\partial V_{DS}} \end{bmatrix} \begin{bmatrix} v_{as} \\ v_{os} \end{bmatrix}$$

$$y_{11}, y_{12} : 0$$

$$y_{22} : \text{non-zero}$$

$$y_{21} : \text{non-zero}$$

$$I_{DS} = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{th})^2 = f(V_{GS})$$

$$\cancel{I_{DS} + i_{DS}} = \cancel{f(V_{GS})} + f'(V_{GS})i_{GS} + f''(V_{GS}) \frac{v_{GS}^2}{2!} + \dots$$

$$i_{DS} = f'(V_{GS}) \cdot v_{GS}$$

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right] = f(V_{GS}, V_{DS})$$

$$I_{DS} + i_{DS} = f(V_{GS0}, V_{DS0}) + \left[\frac{\partial f}{\partial V_{GS}} \cdot v_{GS} + \frac{\partial f}{\partial V_{DS}} v_{DS} \right] + \partial^2$$

$$I_{DS} + i_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} + v_{GS} - V_{th}) (V_{DS} + v_{DS}) - \frac{(V_{DS} + v_{DS})^2}{2} \right]$$

$v_{GS}^2, v_{DS}^2, v_{GS} \cdot v_{DS} \dots$