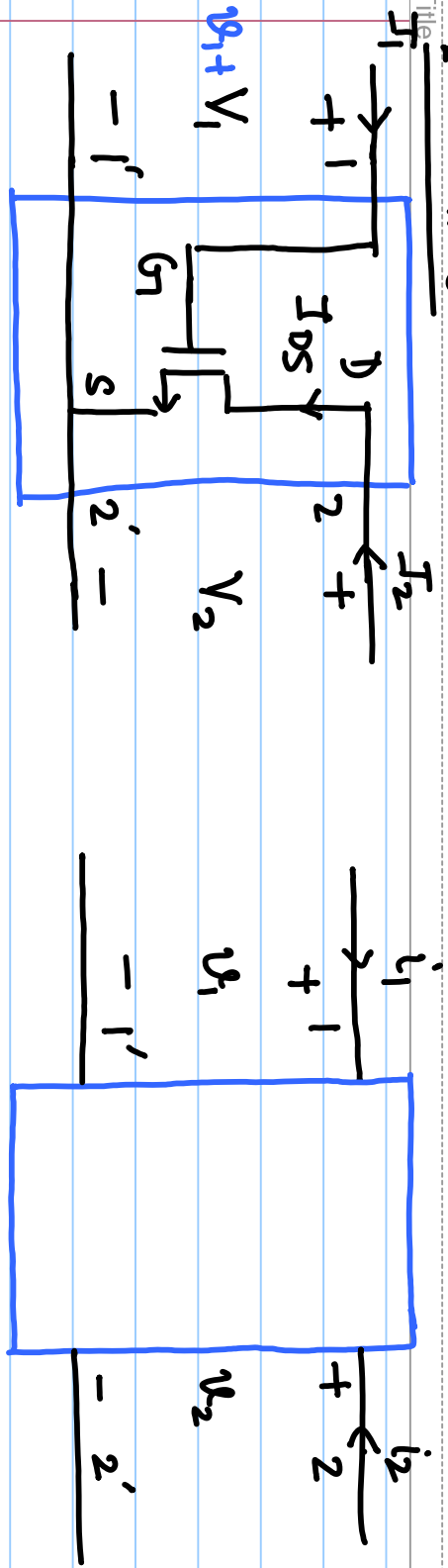


Lecture # 08

Note Title

18-08-2021



MOSFET is in saturation region.

$$I_2 = I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$I_A = I_1 = 0$$

Since, $I_A = 0$ always, $\Rightarrow i_1 = 0$


$$I_2 + i_2 = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} + v_1 - V_{th})^2$$

$$= \frac{\mu_n C_{ox}}{2} \frac{W}{L} ((V_{GS} - V_{th})^2 + v_1^2 + 2v_1(V_{GS} - V_{th}))$$

$$= I_2 + \frac{\mu_n C_{ox}}{2} \frac{W}{L} \{ +2(V_{GS} - V_{th})v_1 + v_1^2 \}$$

$\phi, \sin(x), \cos(x)$
 $\tan(x), \ln(1+x)$

$$\sin(x) = x - \frac{x^3}{3!} + \dots$$

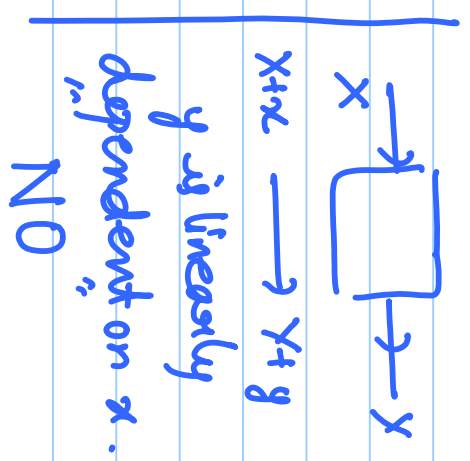

$$i_2 = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left\{ +2 (V_{GS} - V_{thn}) v_1 + v_1^2 \right\} ; v_1^2 \ll 2v_1 (V_{GS} - V_{thn})$$


$$i_2 \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{thn}) v_1$$

$$y_{21}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ y_{21} & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$g_m = y_{21} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{thn})$$

Transconductance "g_m"

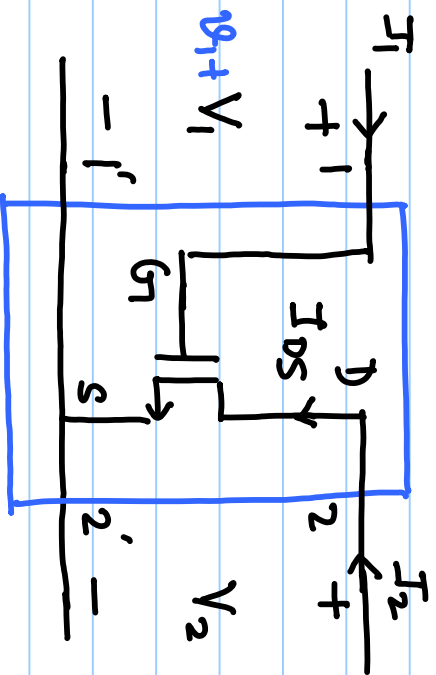


$$I_1 = f_1(v_1, v_2) = 0$$

$$I_2 = f_2(v_1, v_2) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{thn})^2 v_1$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{\partial f_1}{\partial v_1} & \frac{\partial f_1}{\partial v_2} \\ \frac{\partial f_2}{\partial v_1} & \frac{\partial f_2}{\partial v_2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\frac{\partial f_1}{\partial v_1} = 0, \quad \frac{\partial f_1}{\partial v_2} = 0,$$
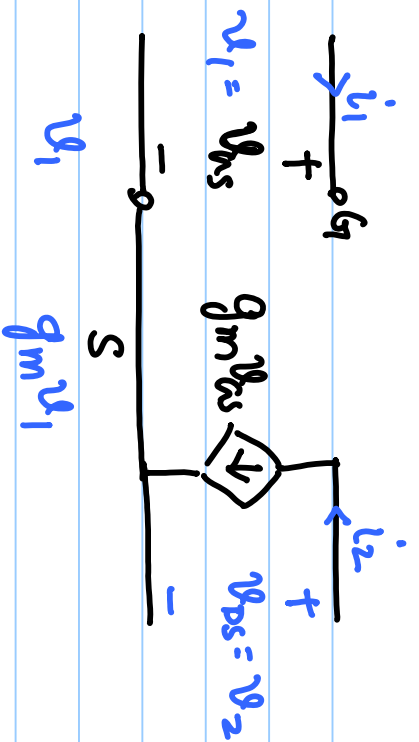
$$\frac{\partial f_2}{\partial v_1} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \times 2 (V_{GS} - V_{thn}), \quad \frac{\partial f_2}{\partial v_2} = 0$$




Small-signal model in saturation region.

In triode region.

$$I_2 = \mu_n C_{ox} \frac{W}{L} \left[(V_{DS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right] = f_2(V_1, V_2)$$

$$I_1 = 0 = f_1(V_1, V_2)$$

$$\frac{\partial f_1}{\partial V_1} = 0, \quad \frac{\partial f_1}{\partial V_2} = 0 \quad \left| \quad \begin{array}{l} I_1 \\ I_2 = \mu_n C_{ox} \frac{W}{L} \left[(V_1 - V_{th}) V_2 - \frac{V_2^2}{2} \right] \end{array} \right.$$

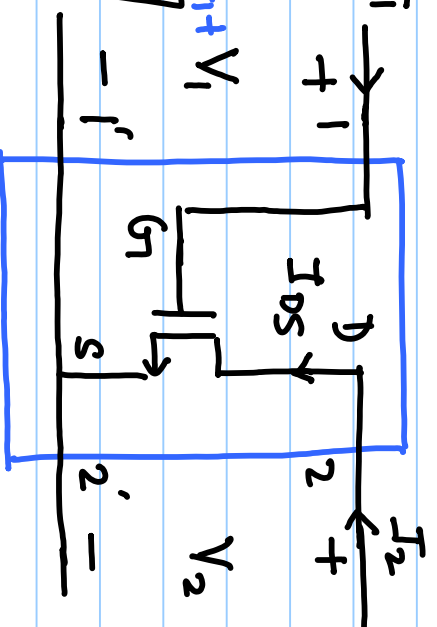


$$V_1 = V_{GS}, \quad V_2 = V_{DS}.$$

$$\frac{\partial f_2}{\partial V_1} = \mu_n C_{ox} \frac{W}{L} (V_{DS}) = y_{21}$$


$$\frac{\partial f_2}{\partial V_2} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) - V_2 \right] = y_{22}$$




$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$r_{ds} = \frac{1}{y_{22}}$$

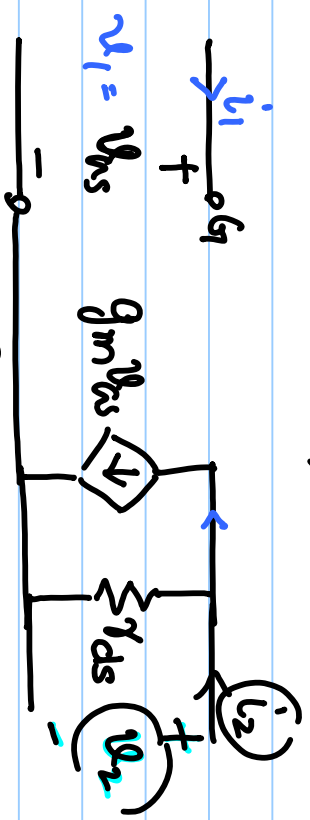

$I_2 (I_{DS})$

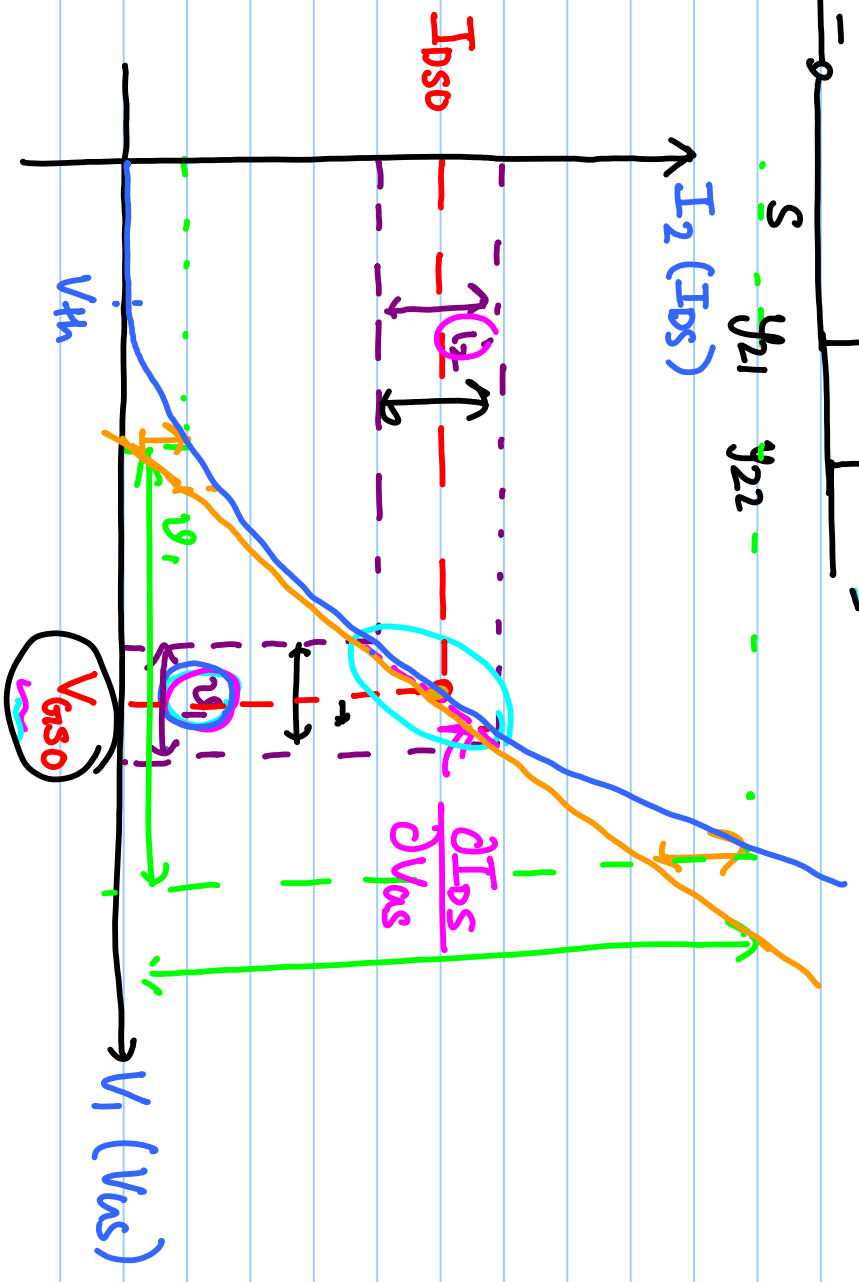

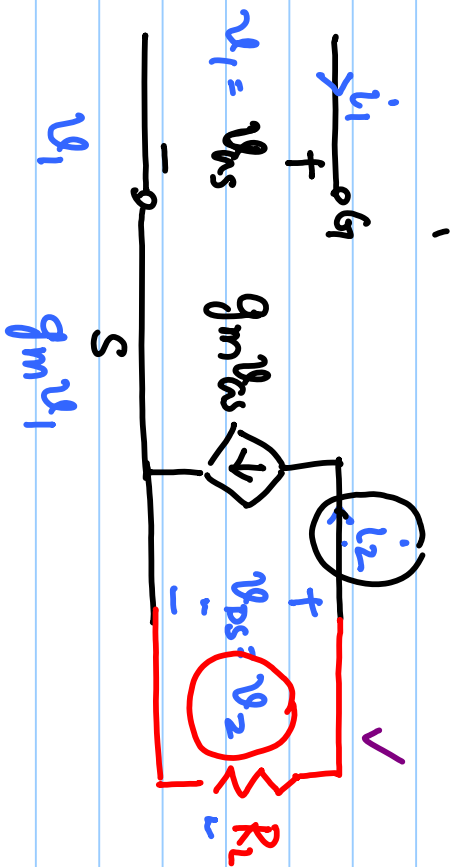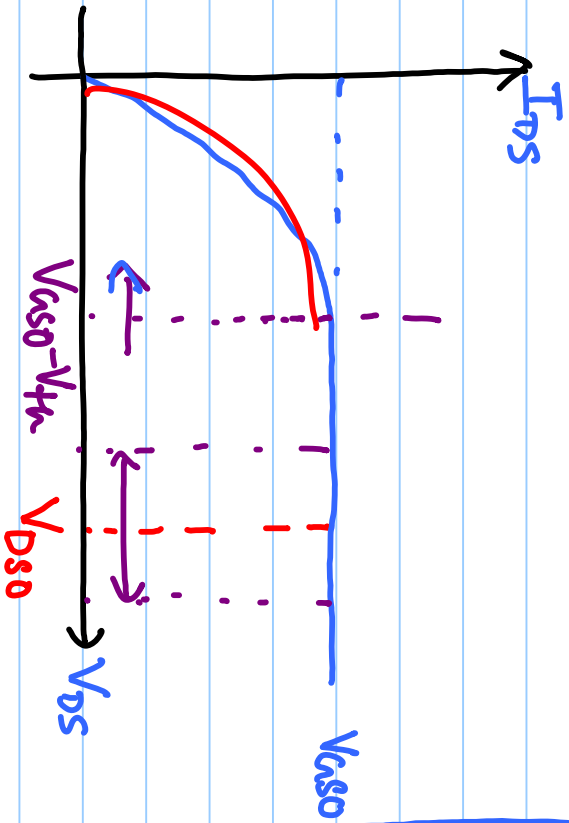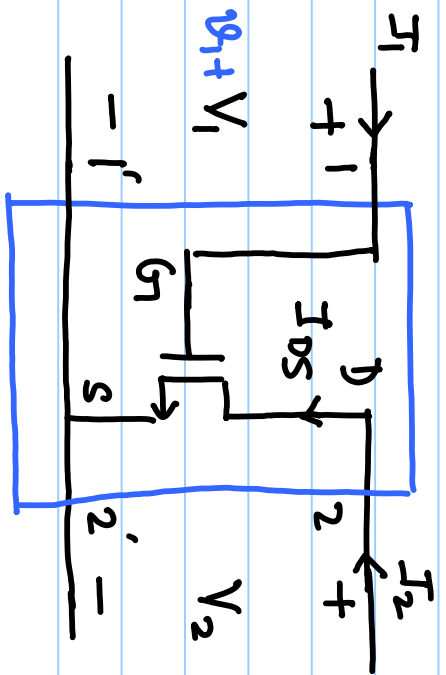

$$\left| \frac{v_2}{v_1} \right| \text{ large value}$$

$$v_2 = -i_2 R_L = -g_m v_1 \cdot R_L$$

$$= -g_m R_L \cdot v_1$$

$$\frac{v_2}{v_1} = -g_m R_L \quad ; \quad \left| \frac{v_2}{v_1} \right| = g_m R_L$$

$$V_{DS} = \underline{V_{DS0} + v_2}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$

Gate-overdrive = $V_{GS} - V_{th}$

$$= \frac{2 I_{DSo}}{V_{GS} - V_{th}}$$

$$I_{DSo}, V_{GS} - V_{th}, \frac{W}{L}$$

$$= \sqrt{2 I_{DSo} \mu_n C_{ox} \frac{W}{L}}$$

$$I_{DSo} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)^2 (V_{GS} - V_{th})^2$$

" 1910 "

Vacuum-Tube : 3 electrodes.

