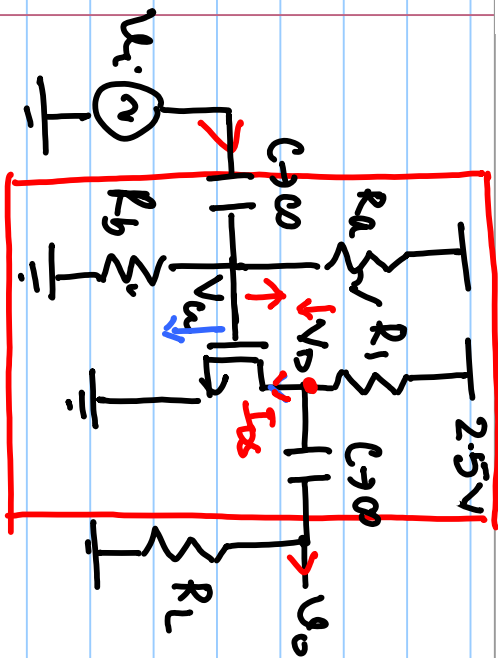


# Lecture # 11



$$\frac{v_o}{v_i} = 1 \quad \frac{v_o}{v_i} = \frac{R_L}{R_L + \frac{1}{sC}} = \frac{sCR_L}{1 + sCR_L}$$

$$\left| \frac{v_o}{v_i} \right| \approx 1 \Rightarrow \left| \frac{sCR_L}{1 + sCR_L} \right| \approx 1$$

$$|sCR_L| \gg 1 \Rightarrow C \gg \left| \frac{1}{\omega_{min}R_L} \right|$$

$$|j\omega_{min}CR_L| = 10$$

$$\text{@ i/f } C \gg \frac{1}{\omega_{min}(R_L || R_b)}$$


$v_o = A v_{in}$   $A$  is the gain of amp.

@ operating point  $A = -2V/V$

- lower limit on  $v_i$ : Small signal.

$V_{in} = 1.2 - v_i \sin(\omega t) \rightarrow I_{CQ} = I_{BQ}$

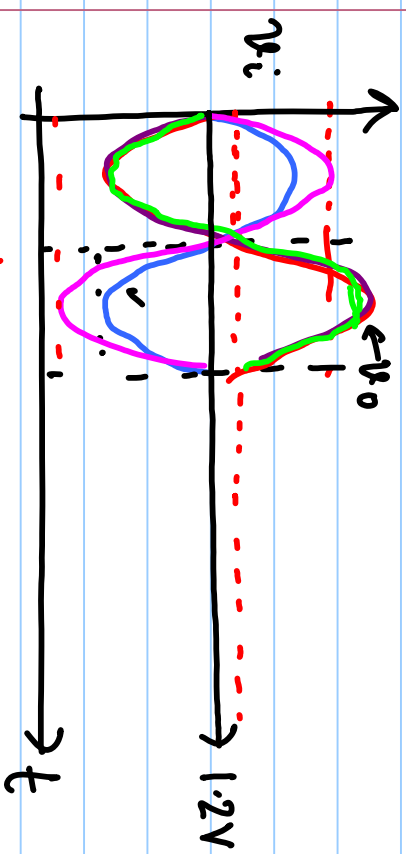- Upper limit on  $v_i$ :  $\Rightarrow$  linear region.




Upper limit: +ve amp ✓  
Lower limit: -ve amp ✓

$$V_{DS} = 1.5V - g_{mR_L} \cdot v_{i} = 1.2 + v_{i} - V_{th}$$


Lower & upper swing limits are evaluated from small-signal model.

$$v_{o}(t) = -2v_{i} \sin(\omega_0 t) + \dots (2v_{i}^3) \quad \text{Negligible. } \times$$

More higher order terms.

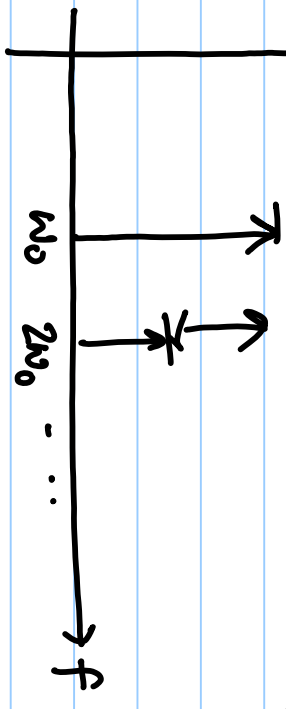

$$V_{GS} = 1.2V - v_{i}$$

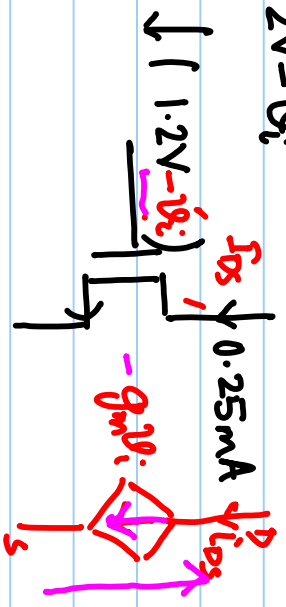



$$0.25mA - g_m v_{i} = 0$$

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L - \Delta L} (V_{GS} - V_{th})^2$$

$$= \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 \left(1 - \frac{\Delta L}{L}\right)^{-1}$$
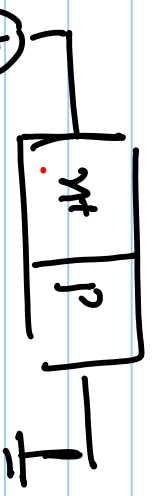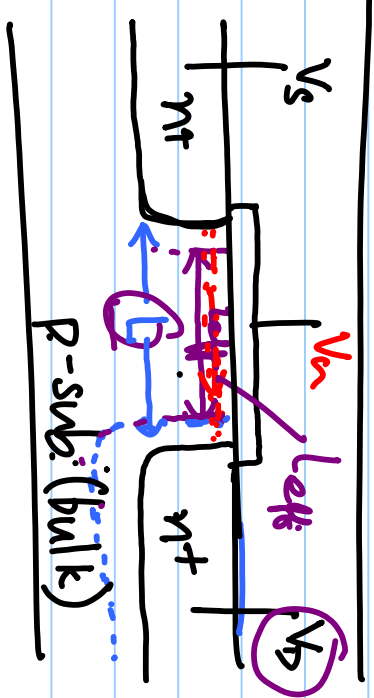
$$\approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 \left(1 + \frac{\Delta L}{L}\right)$$



$$\frac{\Delta L}{L} \propto V_{DS} \Rightarrow \frac{\Delta L}{L} = \lambda V_{DS}$$

In saturation region.


where  $\lambda$  is a constant: channel length modulation


$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \quad \checkmark$$

constant

In linear region.
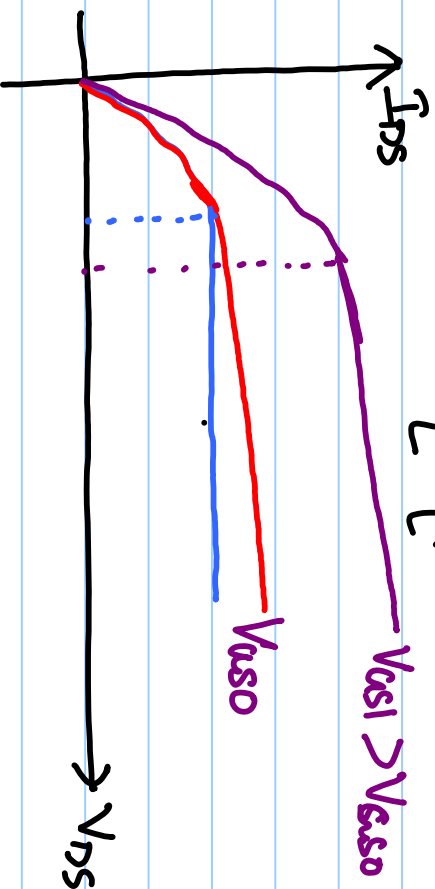
$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



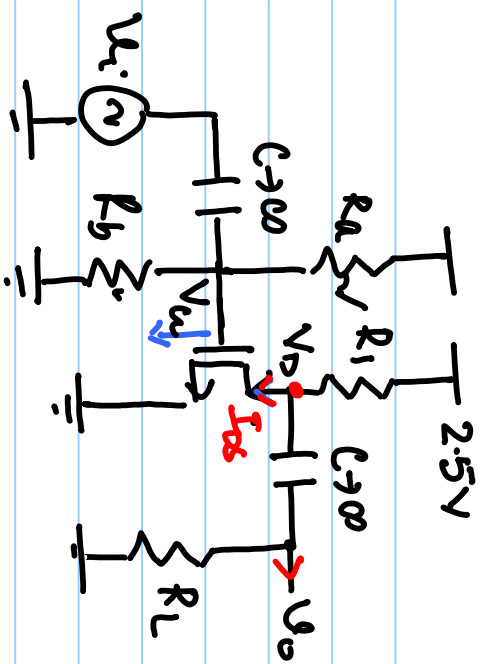

$V_{GS} = 1.2V, \quad V_{th} = 0.7, \quad V_{DS} = 1.5V, \quad \lambda = 0.1$

$\mu_n C_{ox} = 100 \mu A/V^2, \quad \frac{W}{L} = 20, \quad R_1 = 4k$

$I_{DS} = 0.25 \text{ mA} \quad (\text{yesterday})$

$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) = \frac{2.5 - V_{DS}}{4k}$

$= 0.25 \text{ mA} (1 + 0.1 \times 1.5) \quad (\text{Assumption 1})$

$\therefore 0.25 \times 1.15 = 0.2875 \text{ mA}$

Actual  $V_{DS} = 2.5 - 0.2875 \text{ mA} \times 4k$

$0.25 \text{ mA} (1 + 0.1 V_{DS}) = \frac{2.5 - V_{DS}}{4k}$

$1 + 0.1 V_{DS} = 2.5 - V_{DS}$

$V_{DS} = \frac{1.5}{1.1} = 1.36V$

$I_{DS} = \frac{2.5 - 1.36}{4k} = \frac{1.14}{4k} = 0.285 \text{ mA}$

$$I_{DS} = f(V_{GS}, V_{DS})$$


$$\begin{bmatrix} i_{i1} \\ i_{i2} \end{bmatrix} = \begin{bmatrix} i_{iDS} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_{GS} \\ v_{DS} \end{bmatrix}$$



$$y_{11} = 0, \quad y_{12} = 0$$

$$y_{21} = g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) (1 + \lambda V_{DS}) \quad \text{"Accurate"}$$

$$\approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})$$
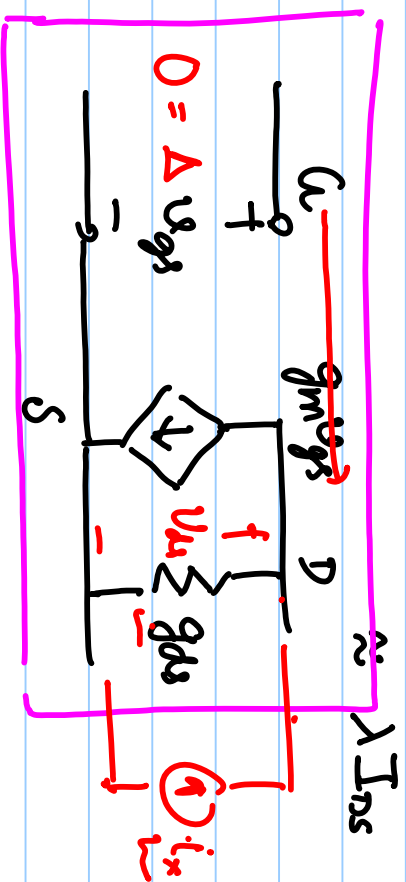
$$y_{22} = g_{ds} = \frac{\partial I_{DS}}{\partial V_{DS}} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 \lambda \quad \text{"Accurate"}$$



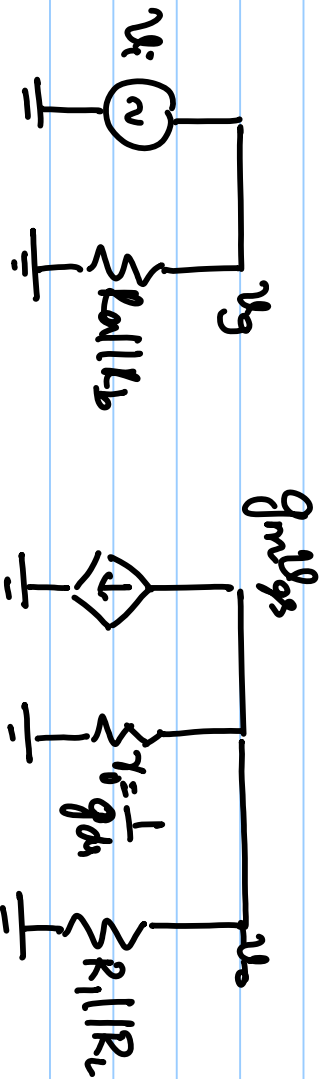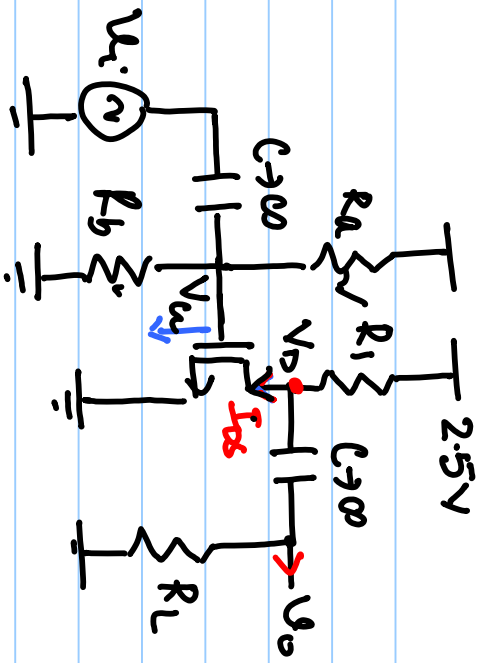

$$\frac{v_o}{v_i} = -g_m (r_o \parallel R_1 \parallel R_2)$$

$$< (R_1 \parallel R_2)$$


To have high gain  $r_o \rightarrow \infty$

$$r_o = \frac{1}{g_{ds}}$$

$$\lambda \propto \frac{1}{L}$$

To increase  $r_o \rightarrow$  increase  $L$
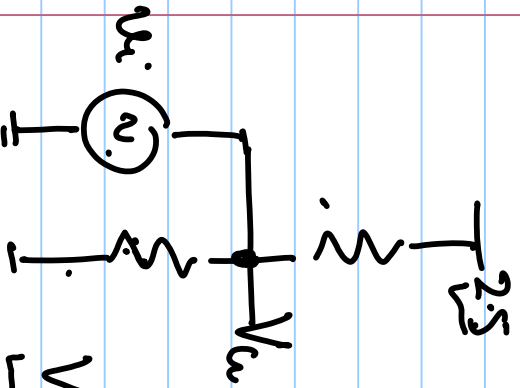
$$\frac{1}{(\mu_n C_{ox} \frac{W}{2L}) (V_{GS} - V_{th})^2} \lambda$$



$$v_o = v_i = A \sin(\omega t)$$

