

Lecture # 12

$$f_{DS} = \frac{\mu_n C_o x \frac{W}{L}}{2} (V_{DS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \mu_n C_o x \frac{W}{L} (V_a - V_g - V_{TH}) \quad (1 + \lambda V_{DS}) \quad (1)$$

$$= \mu_n C_o x \frac{W}{L} (1 + \lambda V_{DS}) \sqrt{\frac{2 f_{DS}}{\mu_n C_o x \frac{W}{L} (1 + \lambda V_{DS})}}$$

$$= \sqrt{2 f_{DS} \cdot \mu_n C_o x \frac{W}{L} (1 + \lambda V_{DS})}$$

$$\approx \sqrt{2 f_{DS} \underbrace{\mu_n C_o x \frac{W}{L}}_{(2)}}$$

$$\frac{V_o}{V_i} = - g_m (R_L || R_L)$$


If MOSFET is biased such that it consumes constant current even

when threshold voltage varies, gain doesn't change.

$$I_{DS} = I_{ref}$$

$$I_{DS} = \frac{\mu_n C_w}{2} \frac{W}{L} (V_{DS} - V_{th})^2 = I_{ref}$$


DC gate voltage, $V_g = 0$

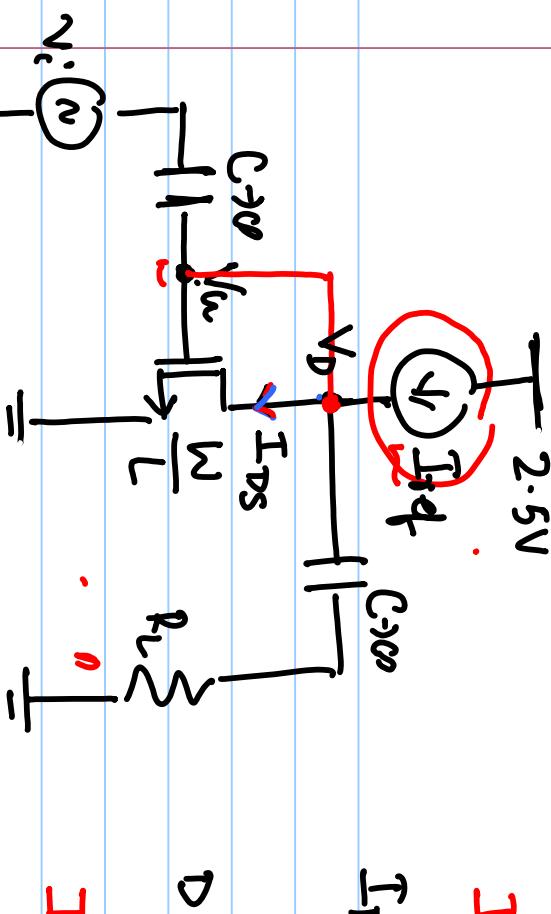

$$I_{DS} = 0$$

- if $I_{ref} > I_{DS}$ then $V_D = V_A \uparrow$

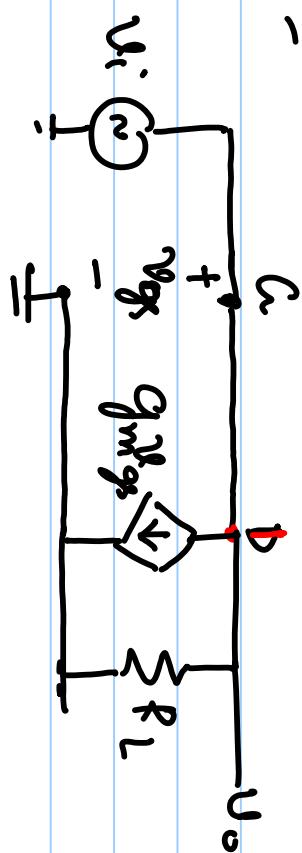- if $V_A \uparrow$ then $I_{DS} \uparrow$



$$\frac{V_D}{V_i} = 1$$

- Inductor is an ideal choice:


$$b/n \propto L D$$

-



for ac.
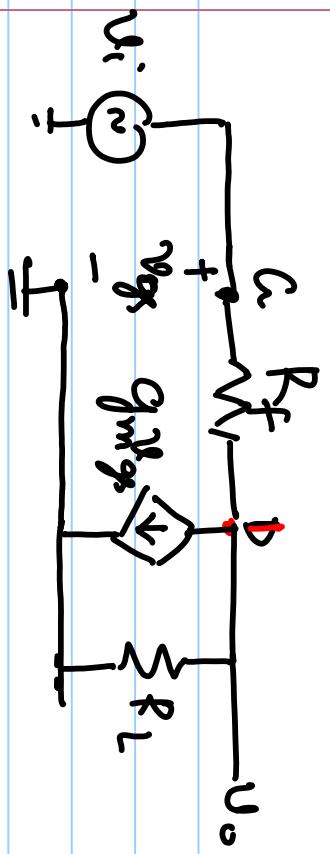
$$- V_a = V_D \text{ at dc, } V_L \& V_D \text{ not connected}$$



$$\frac{U_o}{U_i} = \frac{\left(\frac{1}{R_f} - g_m\right)}{\left(\frac{1}{R_f} + \frac{1}{R_L}\right)} = -g_m R_L$$

$R \rightarrow \infty$