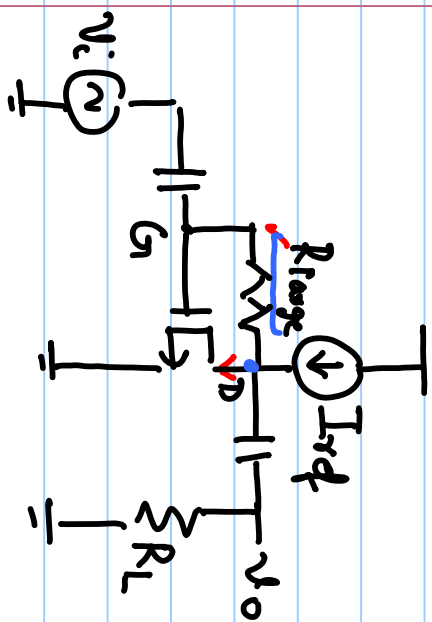


Lecture # 13





$$g_m = \sqrt{2 I_{DS} \frac{\mu_n C_{ox}}{L} \frac{W}{L}}$$

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_G - V_S - V_{th})^2 = I_{req.}$$



$$V_G = \frac{R_B}{R_B + R_{eq}} V_{DD}$$

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left(\frac{R_B}{R_B + R_{eq}} V_{DD} - V_S - V_{th} \right)^2$$
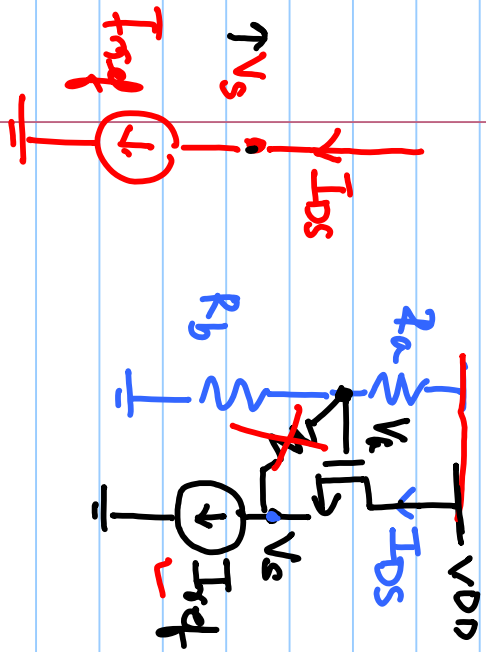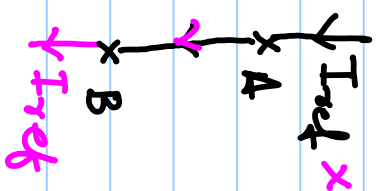
$$= I_{req.} \quad \text{as } \downarrow$$




if $I_{DS} > I_{req}$

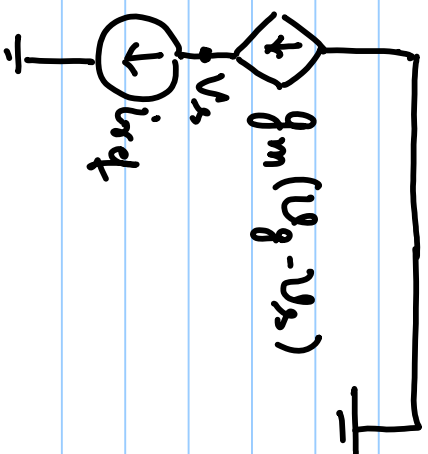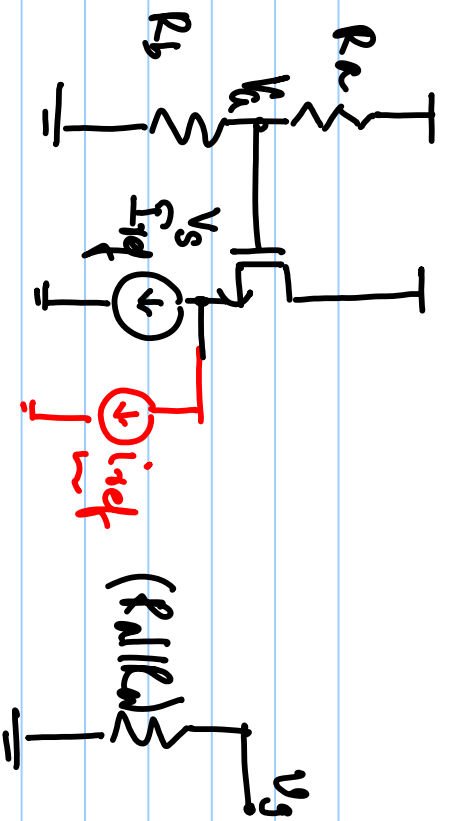

$$V_g = 0,$$

$$g_m(0 - V_s) = I_{req}$$


$$V_s = -\frac{I_{req}}{g_m}$$

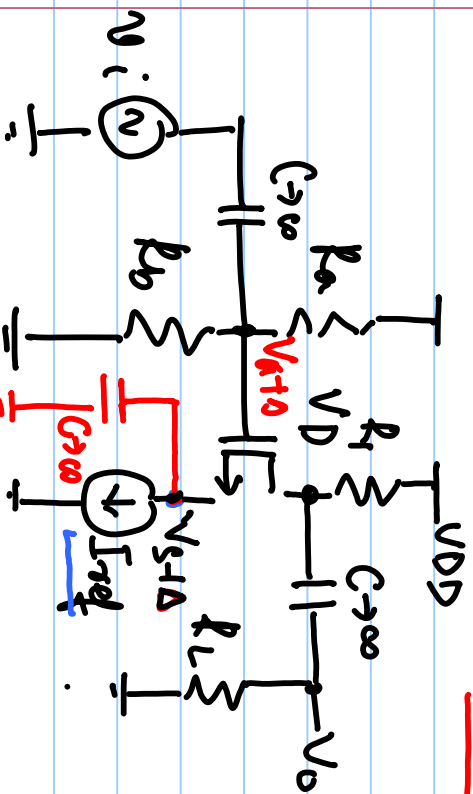

$$V_{gs} = \frac{R_b}{R_b + R_r} V_{DD}, \quad V_D = V_{DD} - I_{req} \cdot R_r$$

$V_D > V_{gs} - V_{th}$ Saturation region

$$I_{DS} = I_{req}$$

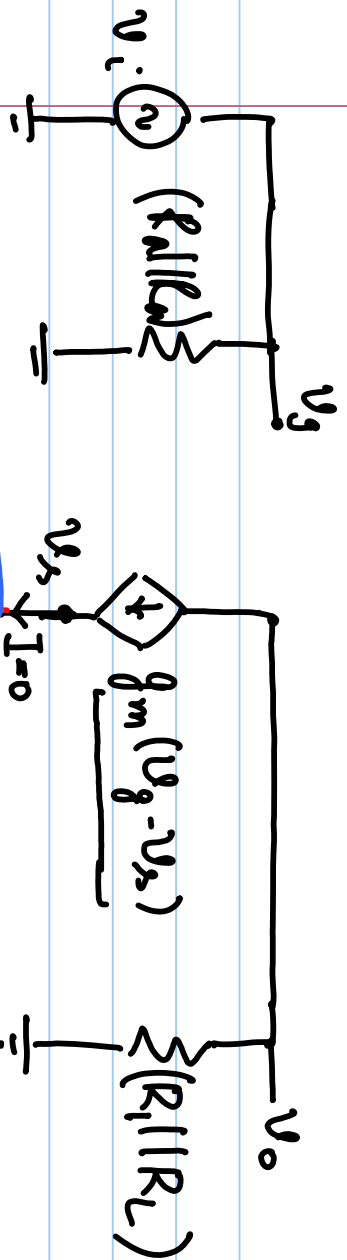

$$v_g = v_i$$


$$g_m(v_g - v_s) = 0 \Rightarrow v_s = v_g = v_i$$

$$v_o = 0$$

"dc"


- MOSFET is biased with fixed current.

- No small signal gain.

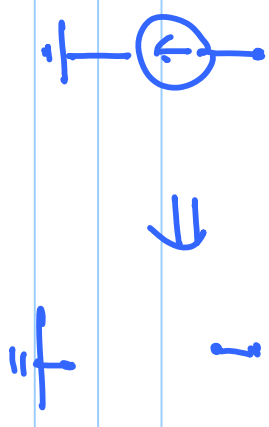

$$g_m(v_i - 0) = -\frac{v_o}{(R_1 || R_2)}$$

$$\frac{v_o}{v_i} = -g_m(R_1 || R_2)$$

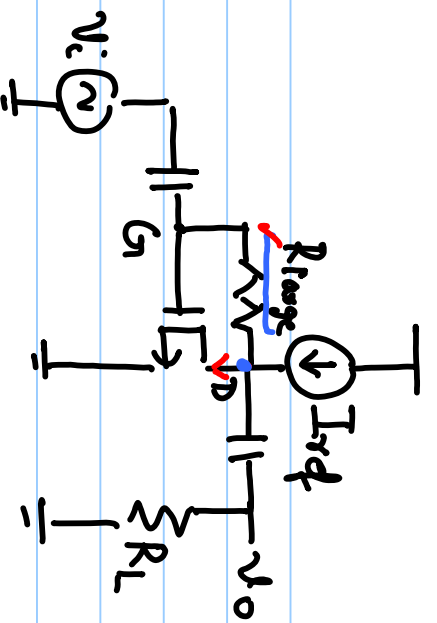


$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (\tilde{V}_{GS} - V_S - V_{th})^2$$


$$= I_{rd}$$

$$\frac{\partial I_{DS}}{\partial V_{th}} = 0$$
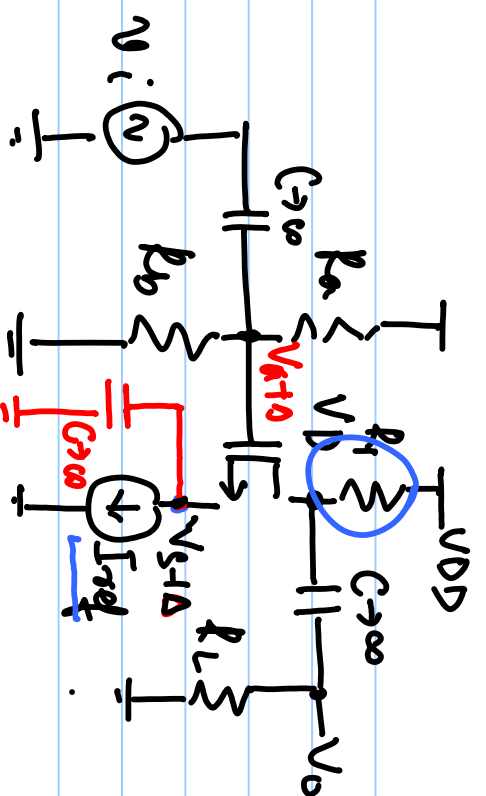
$$\Delta V_{GS} = \Delta V_{th}, \quad \Delta V_G = 0$$


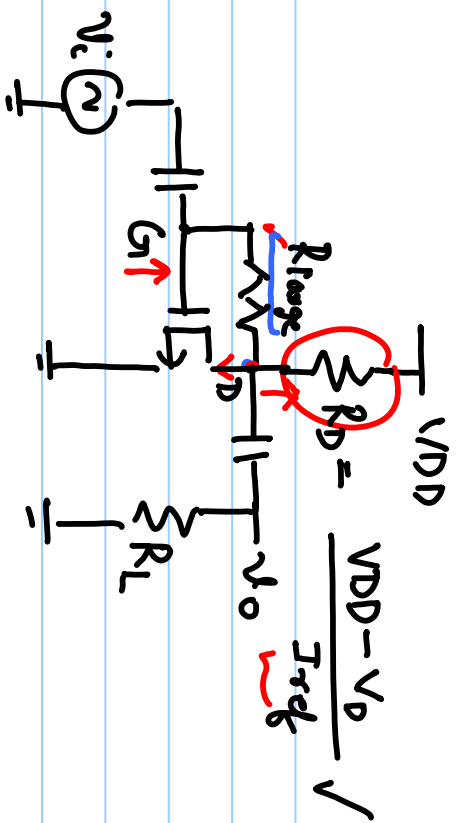
$$\Delta V_{GS} = 0, \quad \Delta V_S = -\Delta V_{th}$$




$$I_{DS} = \frac{M_n C_{ox}}{2} \frac{W}{L} (V_{G1} - 0 - V_{th})^2$$

$$= I_{ref} = \frac{V_{DD} - V_D}{R_D}$$

$$= \frac{V_{DD} - V_k}{R_D}$$

$$\frac{M_n C_{ox}}{2} \frac{W}{L} \times 2 (V_{G1} - V_{th}) \times \left(\frac{\partial V_{G1}}{\partial V_{th}} - 1 \right) = - \frac{\partial V_{G1}}{\partial V_{th}} \times \frac{1}{R_D}$$
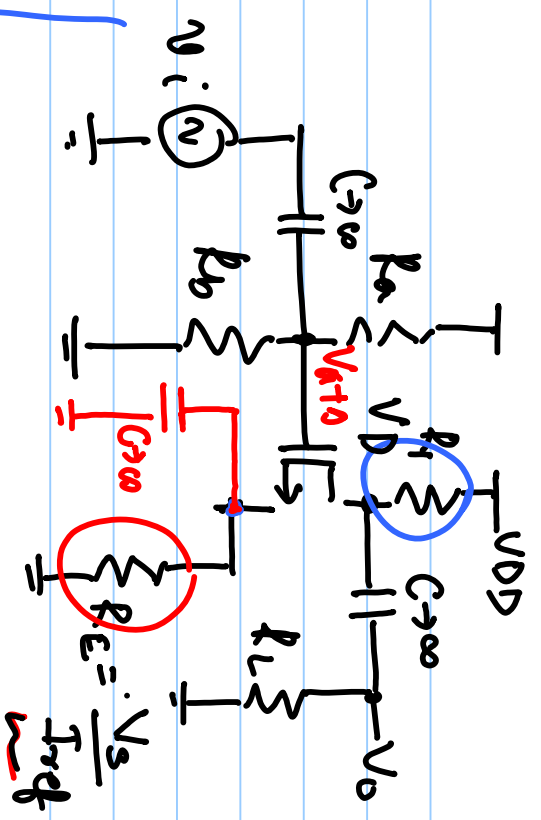
$$\underbrace{\frac{M_n C_{ox}}{2} \frac{W}{L} \times 2 (V_{G1} - V_{th})}_{g_m} \left(\frac{\partial V_{G1}}{\partial V_{th}} - 1 \right) = - \frac{1}{g_m R_D} \frac{\partial V_{G1}}{\partial V_{th}}$$



$$I_{DS} = \frac{M_n C_{ox}}{2} \frac{W}{L} (V_{G1} - V_S - V_{th})^2 = I_{ref}$$

$$= \frac{V_S}{R_E}$$

$$\frac{\partial}{\partial V_{th}} (L.H.S) = \frac{\partial}{\partial V_{th}} (R.H.S)$$

$$g_m (- \frac{\partial V_S}{\partial V_{th}} - 1) = \frac{1}{R_E} \frac{\partial V_S}{\partial V_{th}}$$

$$\frac{\partial V_S}{\partial V_{th}} = - \frac{g_m R_E}{1 + g_m R_E}$$

$$\frac{\partial V_u}{\partial V_{th}} \left(1 + \frac{1}{g_m R_D} \right) = 1$$

$$\frac{\partial V_u}{\partial V_{th}} = \frac{g_m R_D}{1 + g_m R_D}$$

$$\Delta V_s = \frac{-g_m R_E}{1 + g_m R_E} \cdot \Delta V_{th}$$

$$g_m R_E \gg 1$$

$$\neq \frac{\Delta V_u}{\Delta V_{th}} = \frac{g_m R_D}{1 + g_m R_D}$$

$$\Delta V_u = \frac{g_m R_D}{1 + g_m R_D} \Delta V_{th} \checkmark$$

$$\approx \Delta V_{th}$$

$$g_m R_D \gg 1$$