
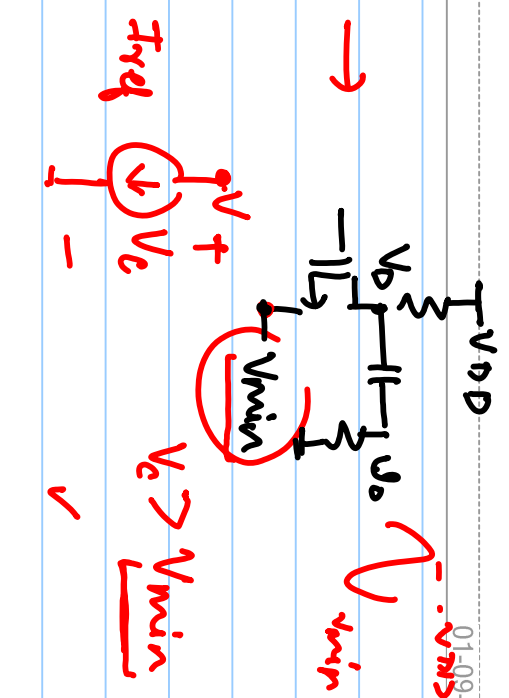
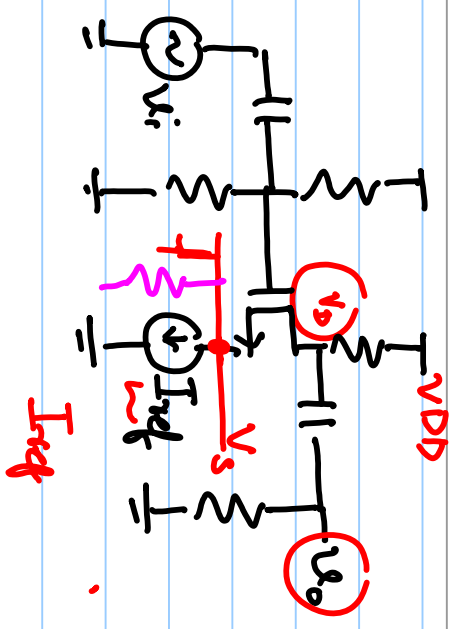


Lecture # 14

#2

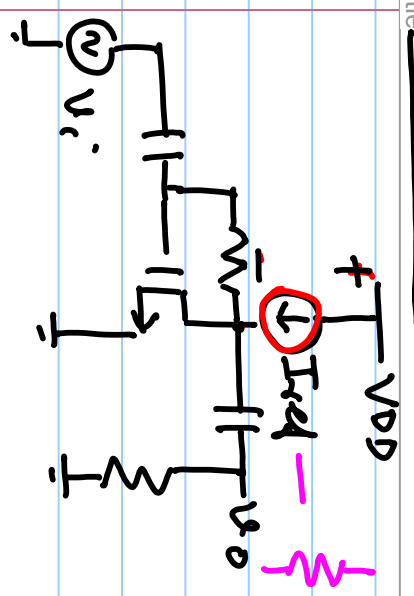




- Real current source will require a potential drop across it.

- It will limit op swing.


$$V_{DS} \geq V_{DS} - V_{th}$$

$$V_{DD} > V_n - V_{th}$$

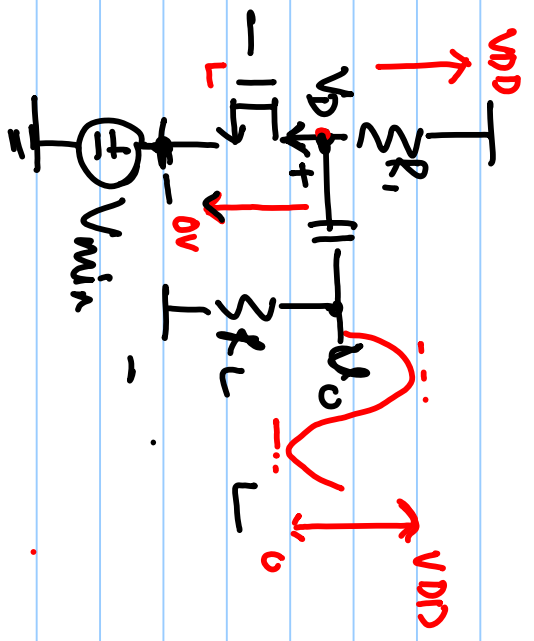

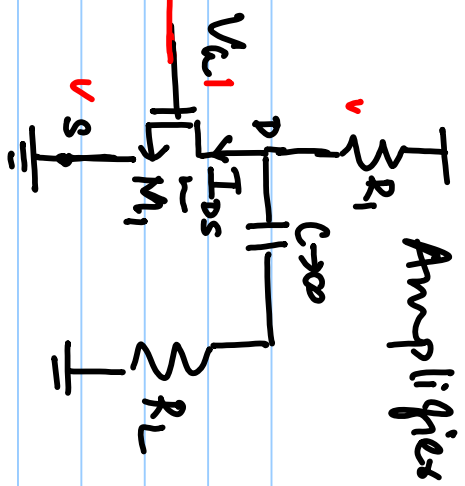
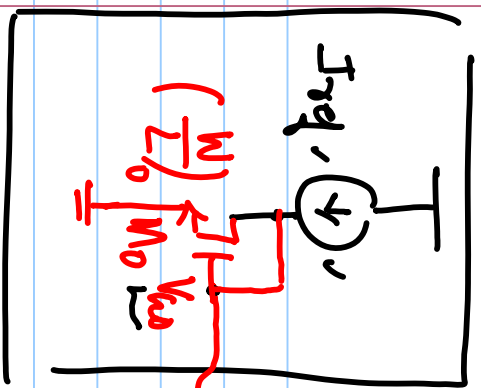



Amplifiers

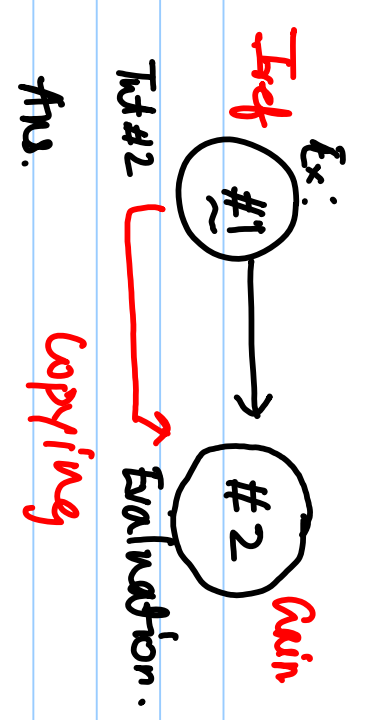

$$I_{DS} = I_{req} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 (V_{GS} - 0 - V_{th})^2$$
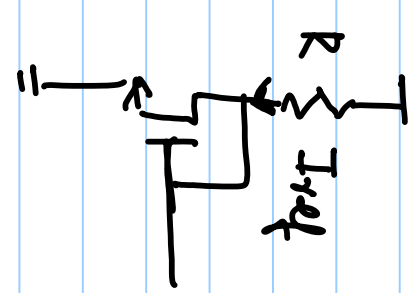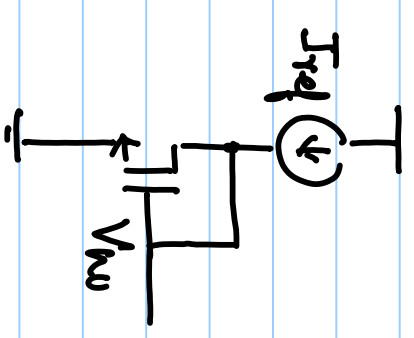
$$\left(\frac{W}{L}\right)_0 = \left(\frac{W}{L}\right)_1$$



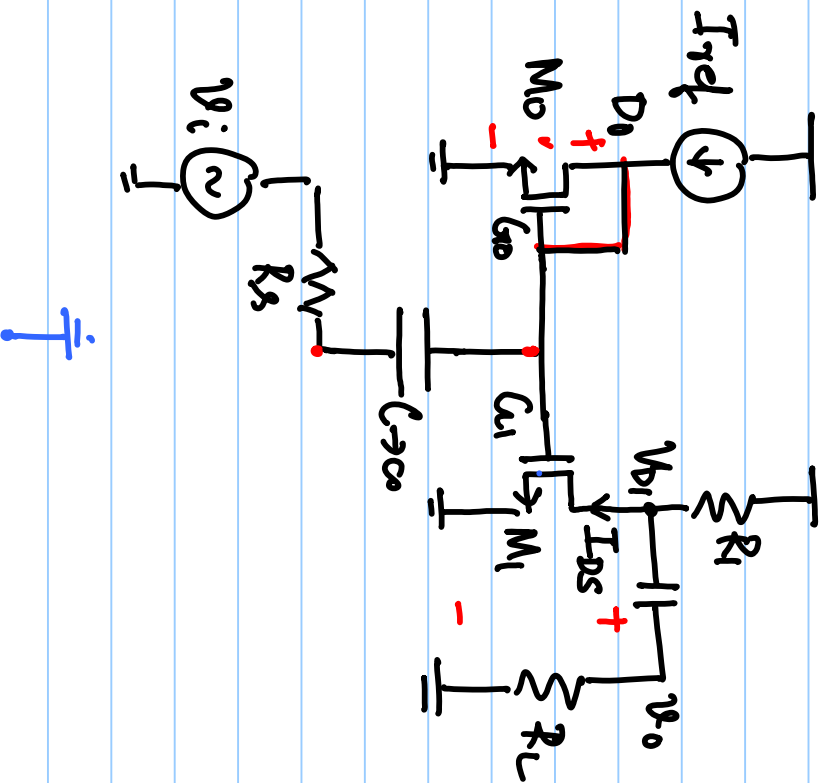


$$V_{D0} = V_{DD} = V_{G1}$$


$$I_{DS} = I_{rdq}$$

$$I_{DS} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{th})^2 \quad (= -I_{rdq})$$
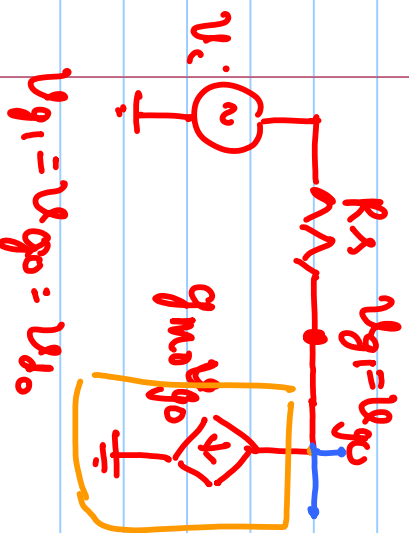
$$v_{g0} \equiv \frac{v_{g0}}{\sqrt{I}} = \frac{v_{g0}}{1/g_{m0}} = g_{m0} v_{g0}$$




$$v_{g1} = v_{g0} = v_{i0}$$

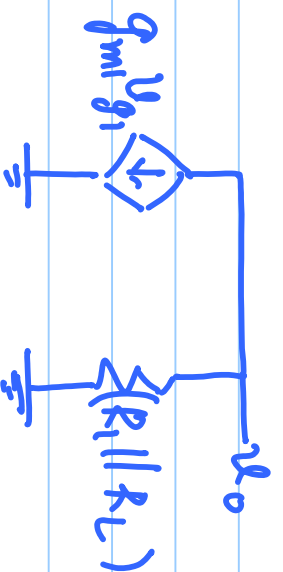




$$v_{g0} = v_{g1} = \frac{1/g_{m0}}{1 + R_s} v_i = \frac{1}{1 + g_{m0} R_s} v_i$$

$$v_o = -g_{m1} v_g \times (R_1 || R_L)$$



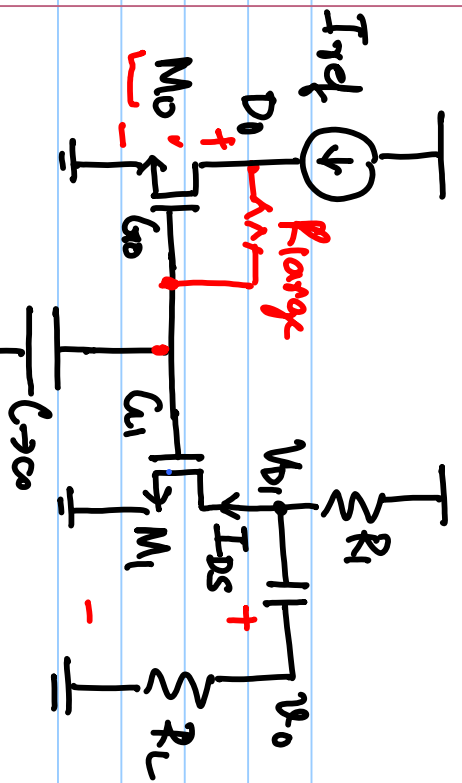


$$\frac{V_o}{V_i} = \frac{-g_m (R_D \parallel R_L)}{1 + g_{m0} R_s}$$
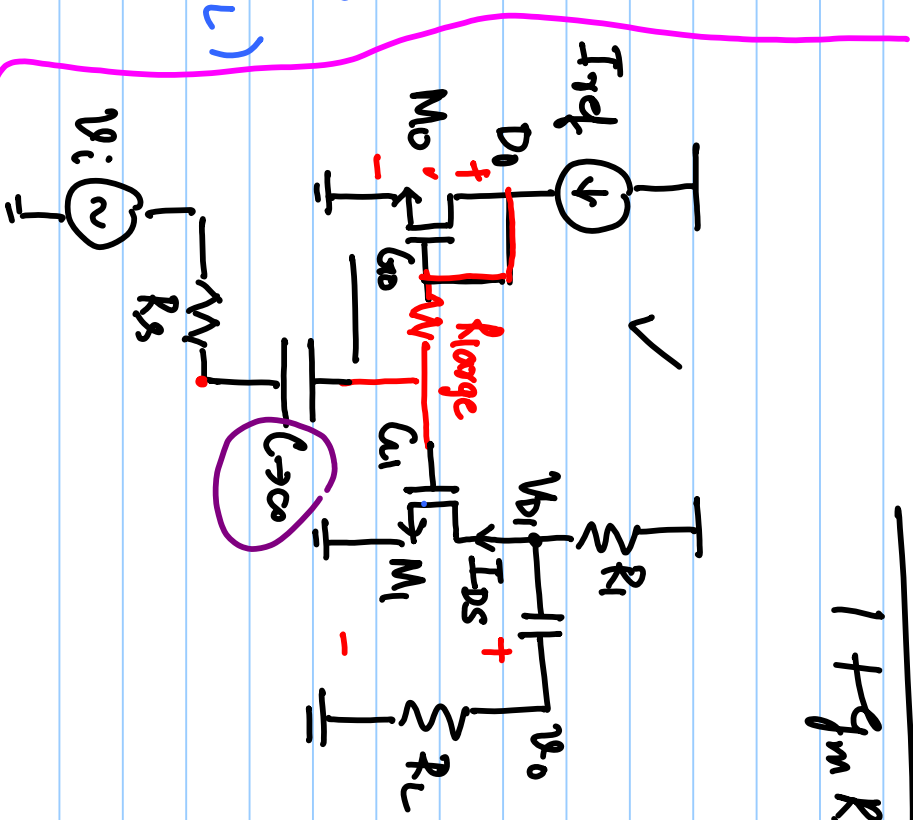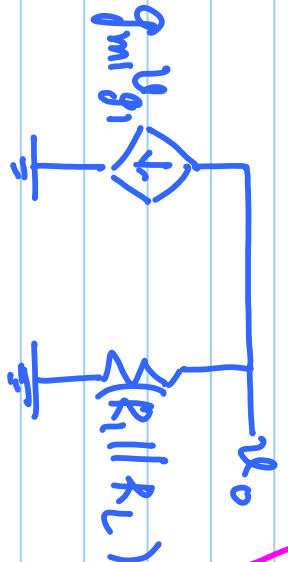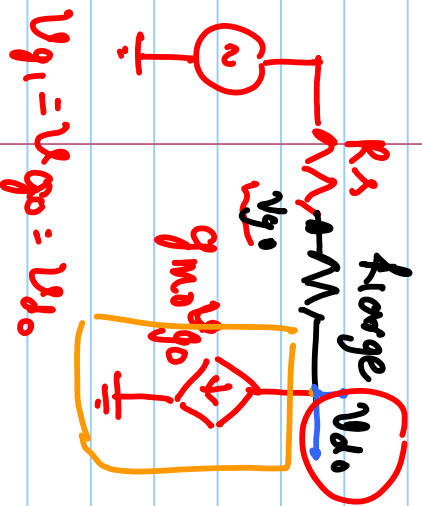
$$= - \frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$$


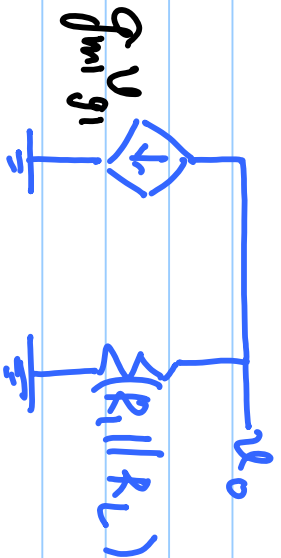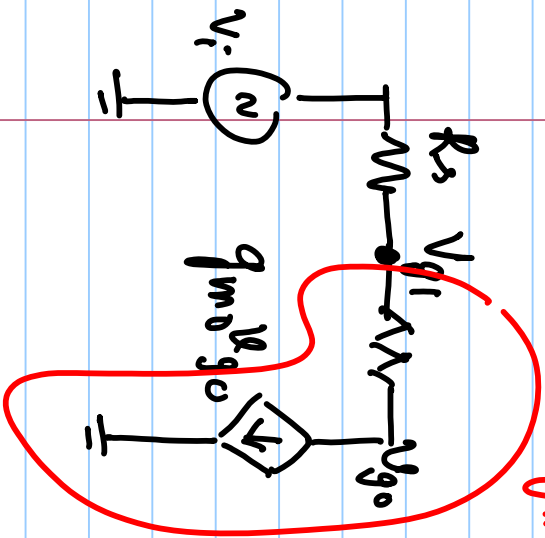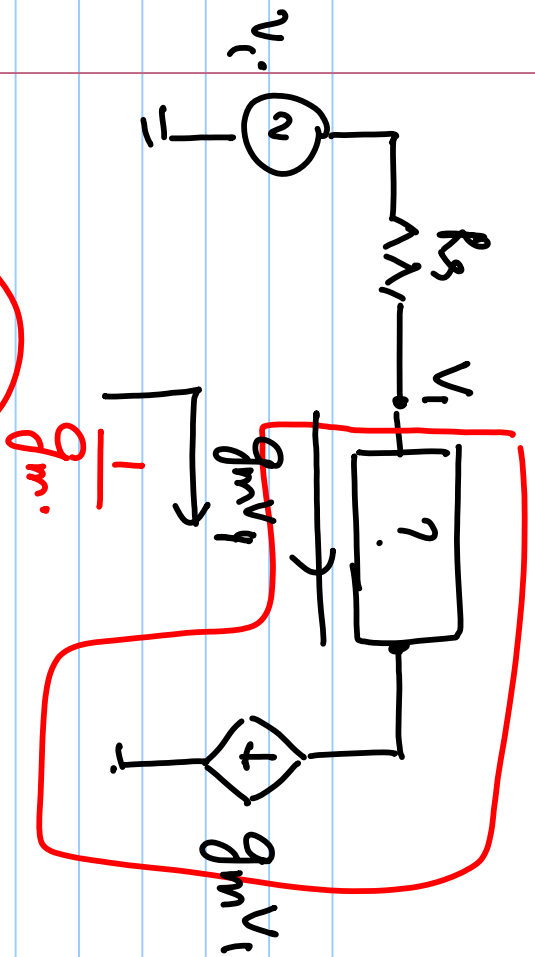
$$\frac{V_i - V_{g0}}{R_s} = g_{m0} V_{g0} \Rightarrow \boxed{V_{g0} = \frac{V_i}{1 + g_{m0} R_s}}$$



$$v_o = -g_m (R_L || R_L) v_{gs}$$

$$\frac{v_o}{v_i} = - \frac{g_m (R_L || R_L) g_m (R_{load} || R_s)}{1 + g_m (R_{load} || R_s)}$$

$$v_{gs} = \frac{\frac{1}{g_m} + R_{load}}{v_i} = \frac{1 + g_m R_{load}}{v_i}$$

$$\approx v_i$$