

$$I_{DS1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{th1})^2 = I_{ref}$$

$$I_{DS2} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{GS} - V_{th2})^2$$

if $\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_1$ and $V_{th2} = V_{th1}$

$$I_{DS2} = I_{DS1} = I_{ref}$$

if $V_{th2} = V_{th1} + \Delta V_{th}$

$$I_{DS2} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_{th1} - \Delta V_{th})^2$$

$$= \frac{K W}{2L} \left[(V_{GS1} - V_{th1})^2 + (\Delta V_{th})^2 - 2 \Delta V_{th} (V_{GS1} - V_{th1}) \right]$$

$$= I_{DS1} + \frac{K W}{2L} \left[-2 (V_{GS1} - V_{th1}) \cdot \Delta V_{th} + (\Delta V_{th}^2) \right]$$


$$= I_{req} + \frac{K_N}{L} (V_{a1} - V_{tn1}) \times (-\Delta V_{tn}) + \frac{K_N}{2L} (\Delta V_{tn}^2) \quad \checkmark$$

$$\approx I_{req} + \frac{K_N}{L} (V_{a1} - V_{tn1}) \times (-\Delta V_{tn})$$

$$I_{DS2} = I_{req} + g_{m1} (-\Delta V_{tn})$$

$$g_{m2} = \sqrt{\frac{2 I_{DS2} \mu_n C_{ox} W}{L}} = \sqrt{(I_{req} - g_{m1} \Delta V_{tn}) \mu_n C_{ox} \frac{W}{L}}$$
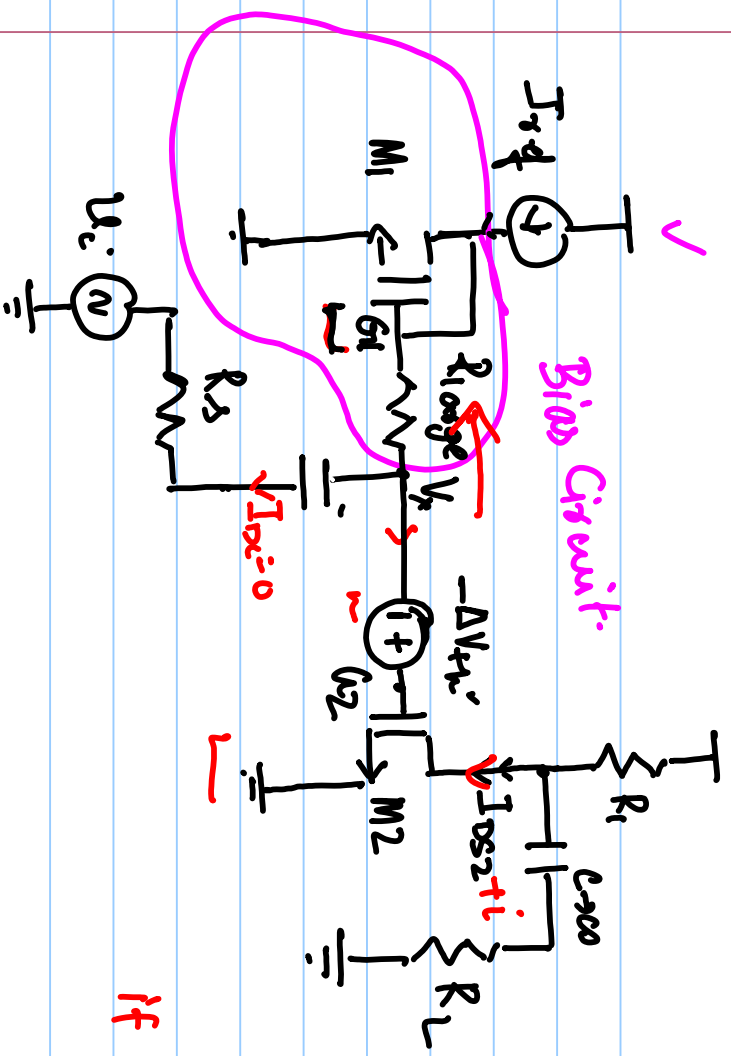
$$\begin{aligned} V_{GS2} - V_{tn2} &= V_{a1} - (V_{tn1} + \Delta V_{tn}) = (V_{a1} - V_{tn1}) - (\Delta V_{tn}) \\ &= (V_{a1} - \Delta V_{tn}) - V_{tn1} \end{aligned}$$



$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$

$$V_{th1} = V_{th2}$$


$$V_{gs2} = V_{gs1} - \Delta V_{th}$$

if $\Delta V_{th} = 0$ then $I_{ds2} = I_{ds1} = I_{ref}$


if $\Delta V_{th} \neq 0$ then $I_{ds2} = I_{ds1} + g_{m2} (-\Delta V_{th})$

$$I_{ds2} = I_{ref} - g_{m2} \cdot \Delta V_{th}$$

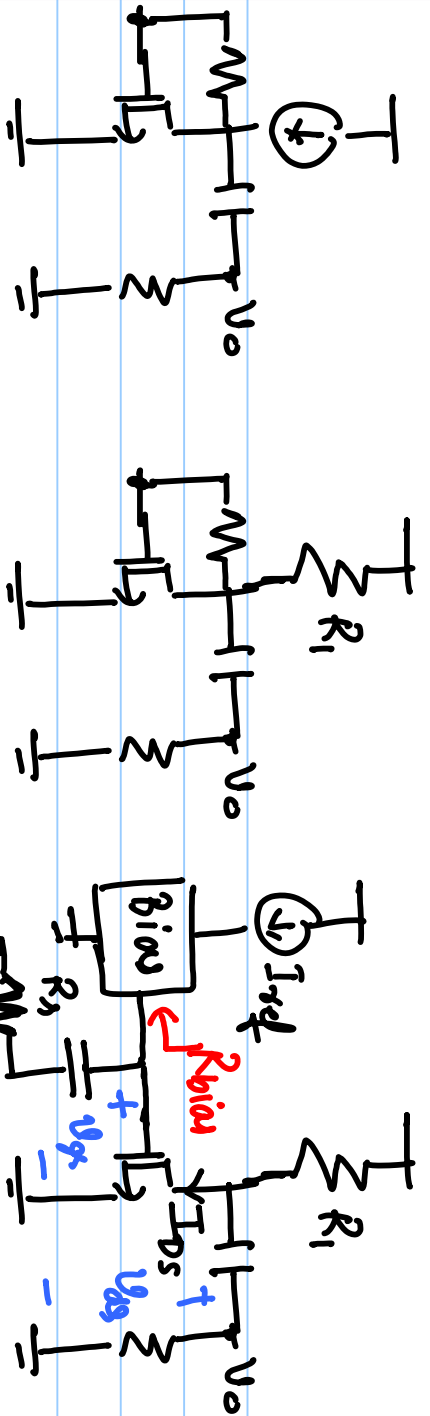- Change in threshold voltage can be represented as change in gate voltage w/ -ve sign.



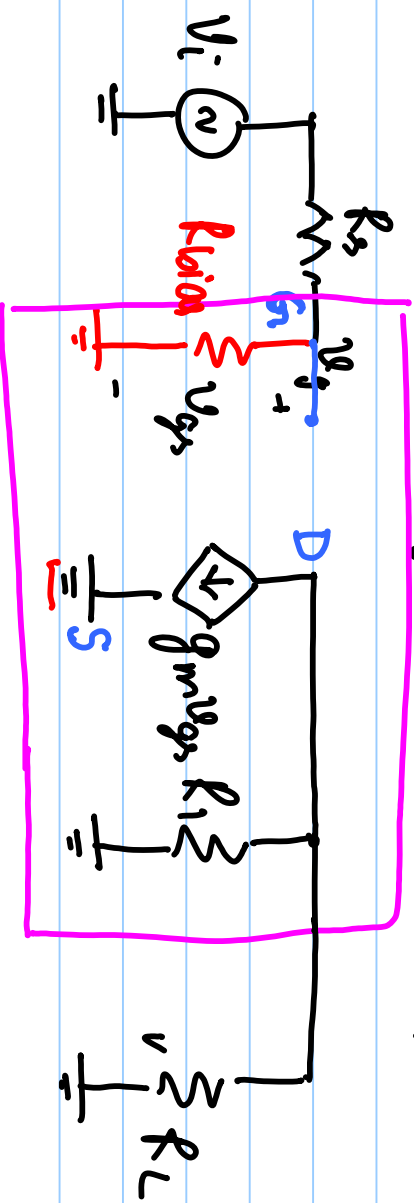-NMOSFET biased with fixed current I_{rd} .




"Common Source Amplifier" (CS)


$$\frac{v_o}{v_i} = -g_m (R_1 || R_L)$$

$$g_m = \sqrt{2 I_{rd} \mu_n C_{ox} \frac{W}{L}}$$

-Gain depends on R_L .

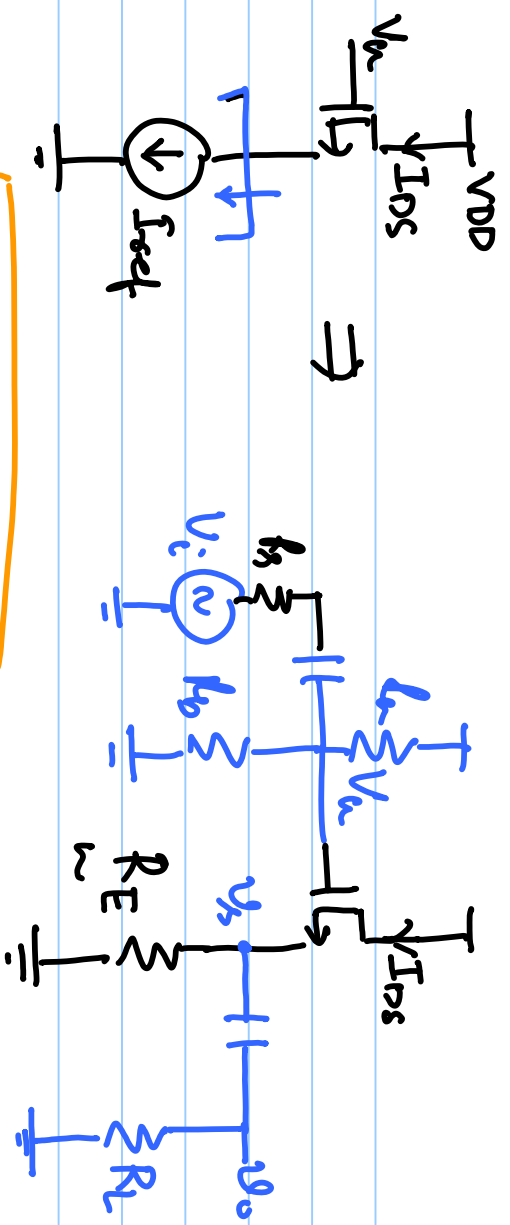

"Common Drain" Amplifier

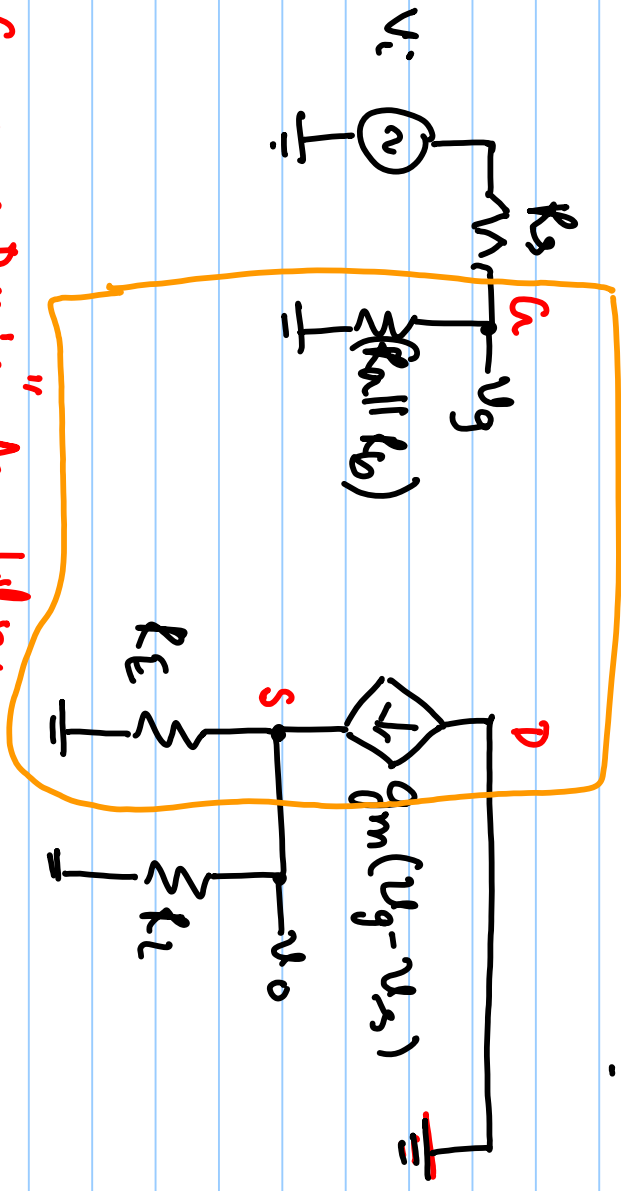

$$R_{g1} || R_{g2} \gg R_s$$

$$v_g = v_i$$

$$g_m(v_i - v_o) = \frac{v_o}{(R_E || R_L)}$$

$$\frac{v_o}{v_i} = \frac{g_m (R_E || R_L)}{1 + g_m (R_E || R_L)}$$

$$\frac{v_o}{v_i} = \frac{1}{(R_E || R_L) g_m}$$


$$\frac{v_o}{v_i} = 1$$

$$\frac{v_o}{v_i} = \frac{1}{\frac{1}{g_m} + (R_E || R_L)}$$


CS : Large gain, Gain depends on R_L ($A_v = -g_m(R_{L1} || R_L)$)

CD : Unity gain (≈ 1), Gain doesn't depend on R_L ($\frac{1}{g_m} \ll (R_{L1} || R_L)$)

Ideal Amplifiers

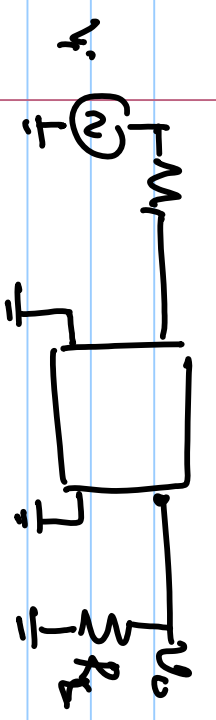

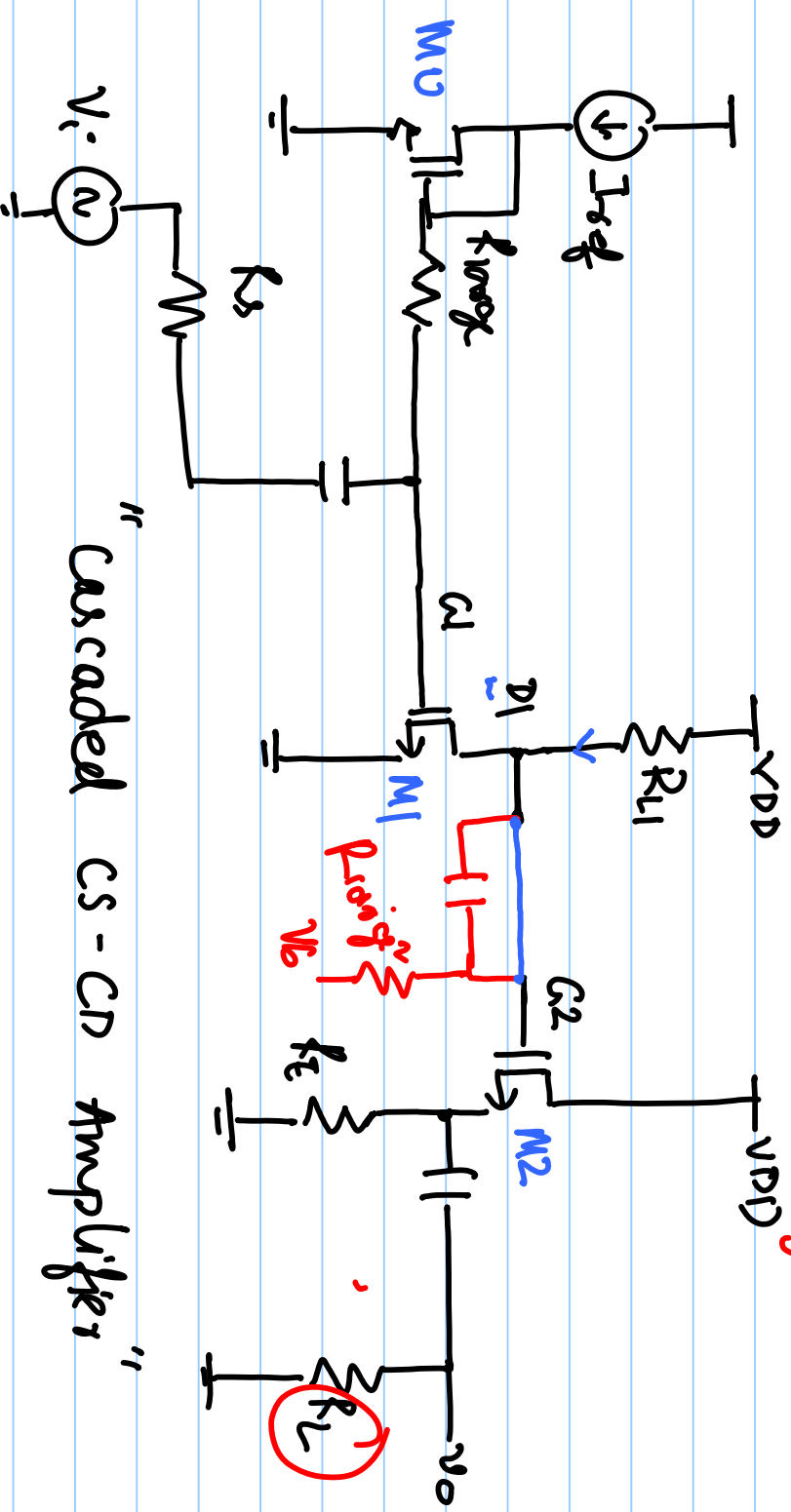$\frac{V_o}{V_i} =$ large and independent of R_L
First-Stage *Second-Stage.*



"Cascaded CS-CD Amplifier"

$$\frac{V_o}{v_i} = -g_{m1}R_{L1} \cdot \frac{g_{m2}(R_{E1}||R_{L2})}{g_{m2}(R_{E1}||R_{L2})+1}$$

$$\frac{V_o}{v_i} \approx -g_{m1}R_{L1}$$