
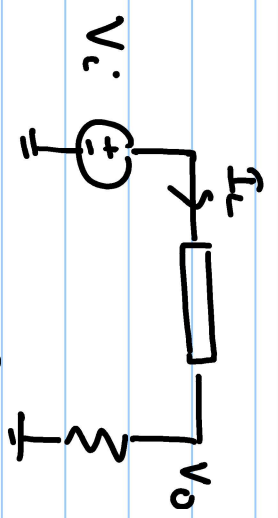


Lecture # 16



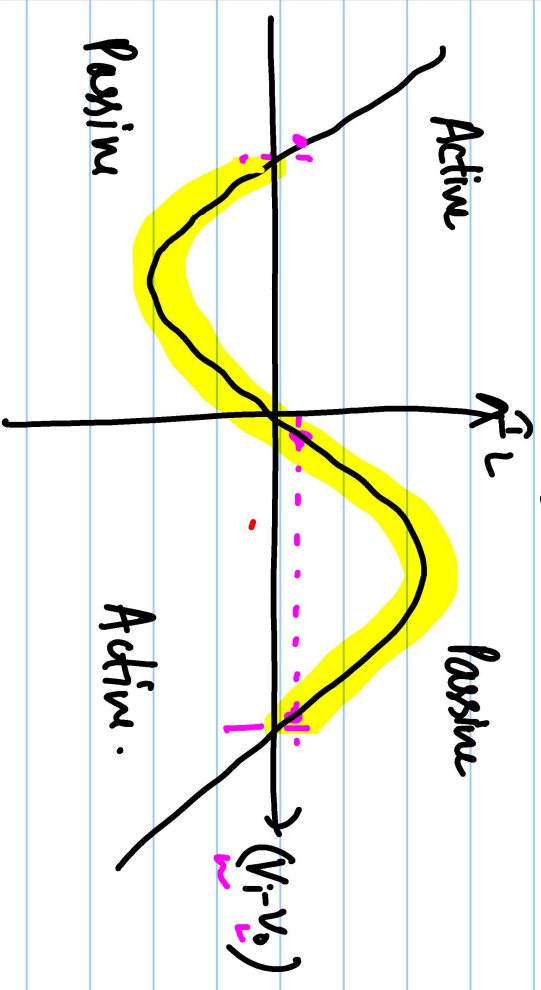


$$I_L = \alpha_1 (V_i - V_o) - \alpha_2 (V_i - V_o)^3 = \frac{V_o}{R_L}$$

$$V_o =$$



CS-CD amplifier

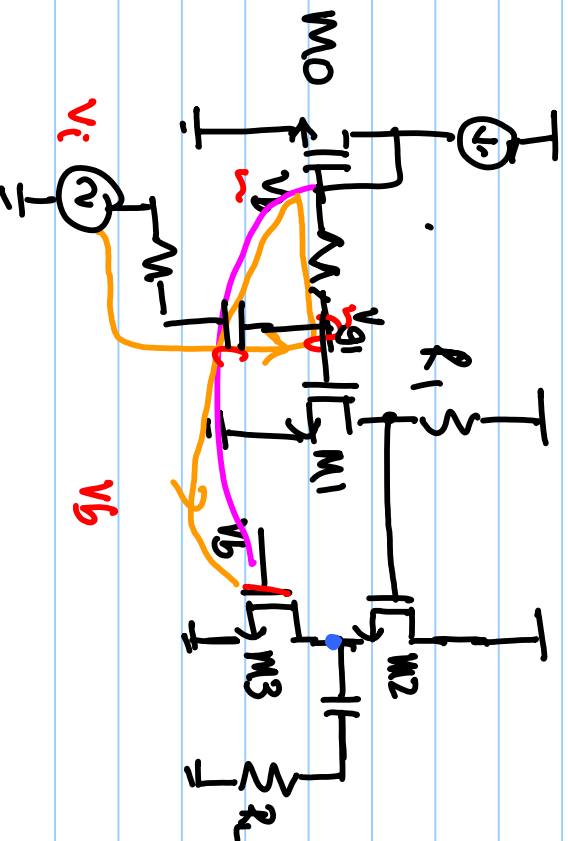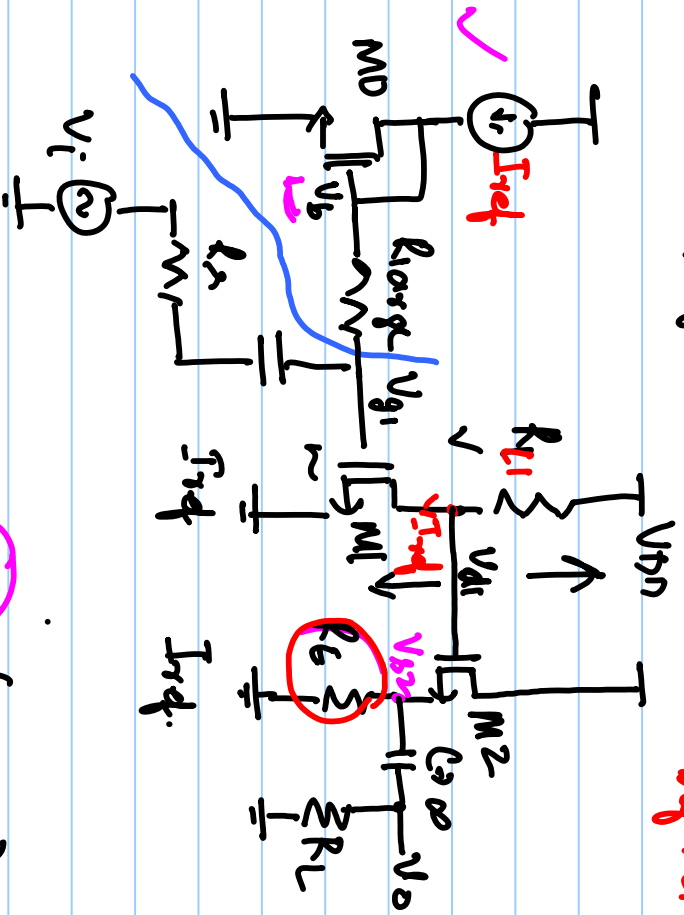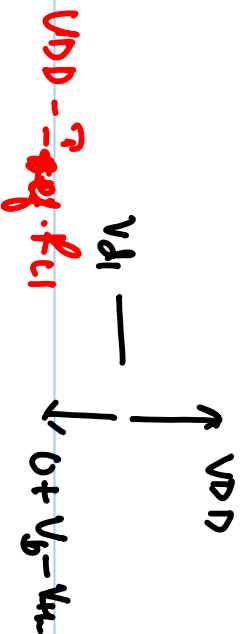


$$\frac{v_o}{v_i} = -g_{m1} R_L \times \frac{g_{m2} (R_{C1} \parallel R_L)}{1 + g_{m2} (R_{C1} \parallel R_L)}$$


$M0, M1, M2$ (W/L)

$$\approx \frac{g_{m2} K_C}{1 + g_{m2} K_C}$$
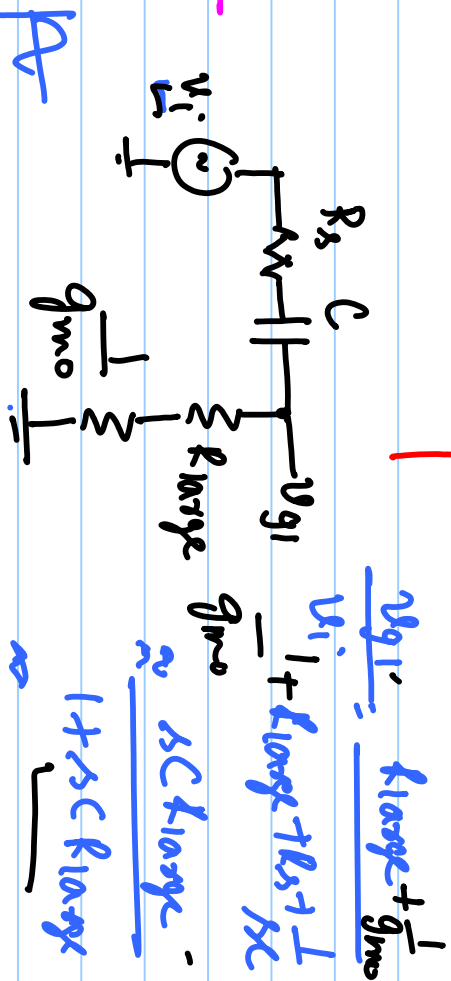
$$v_b + v_{g1} \quad \downarrow \quad I_{ref} + g_{m1} v_{g1}$$





$$\approx \frac{1}{1 + sC R_{C1}}$$

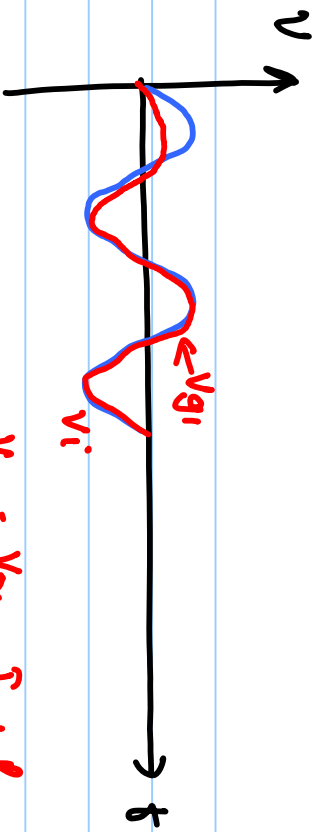

$$v_{o1} = v_{DD} - I_{req} \cdot R_{L1}$$


$$v_i = \sin(\omega t) \quad \omega(t)$$
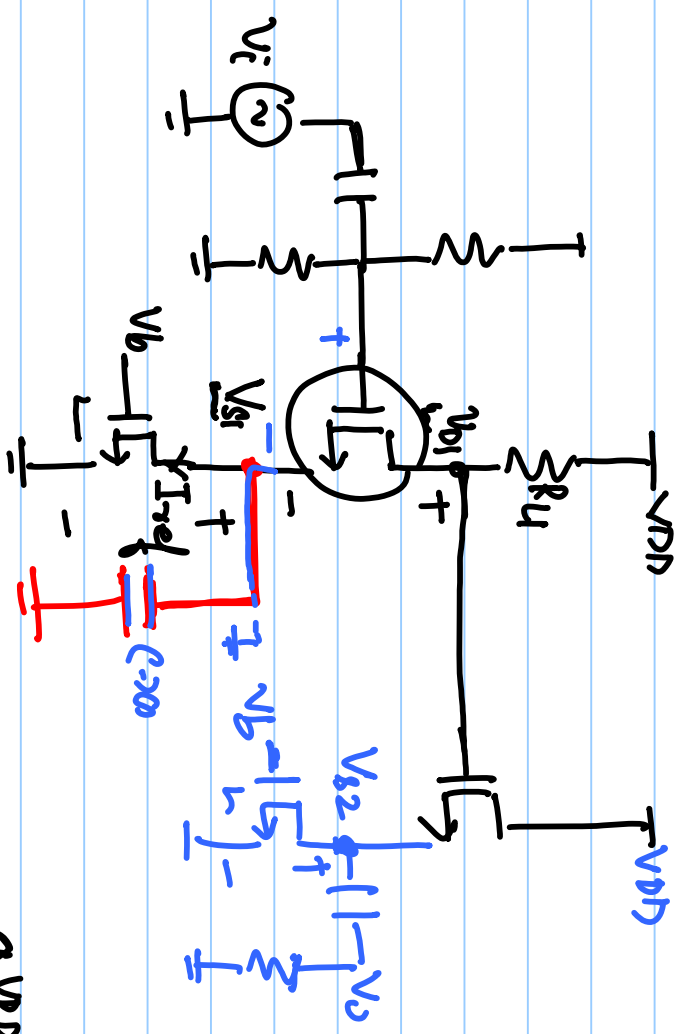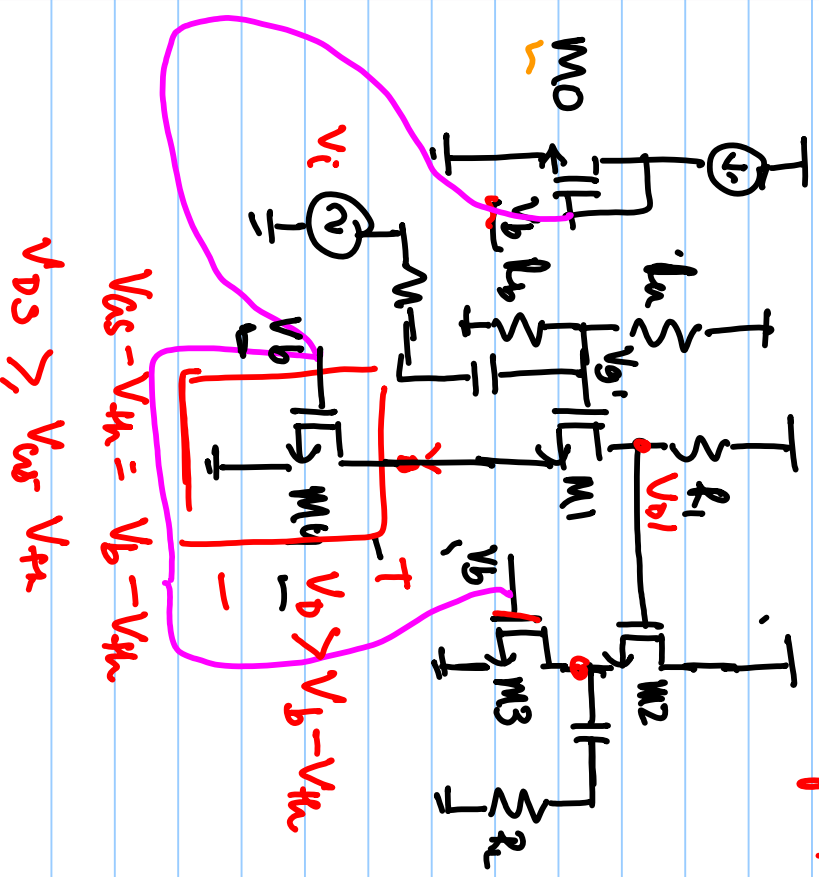
$$H(s) = \frac{v_{o1}}{v_i} = \frac{\beta S C R_{1req}}{1 + \beta S C R_{1req}}$$



$$\frac{v_{o1}}{v_i} = -g_{m1} \cdot R_{L1} \quad v_{GS1} = \frac{V_{DD}}{2(V_B - V_{th})}$$
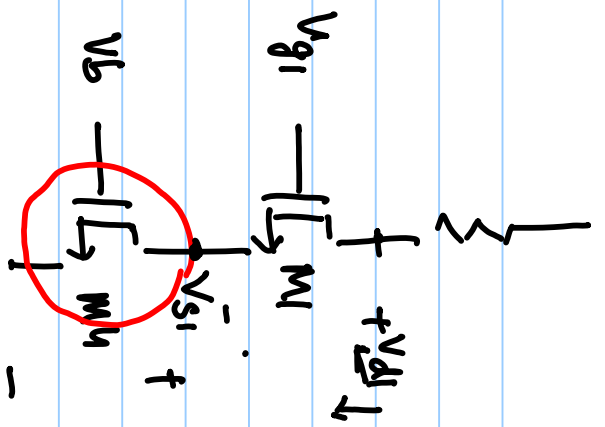
$$v_{o1} = v_{DD} - I_{req} \cdot R_{L1} - g_{m1} \cdot v_i \cdot R_{L1}$$



Mh: $V_{as} - V_{th} = V_b - V_{th}$


$V_{s1} = 0 > V_{as} - V_{th}$

$V_{s1} > V_b - V_{th}$


M1: $V_{g1} - V_{s1} - \cancel{\gamma_{th}} = V_b - \cancel{\gamma_{th}}$

$V_{d1} - V_{s1} > V_{g1} - V_{s1} - V_{th}$

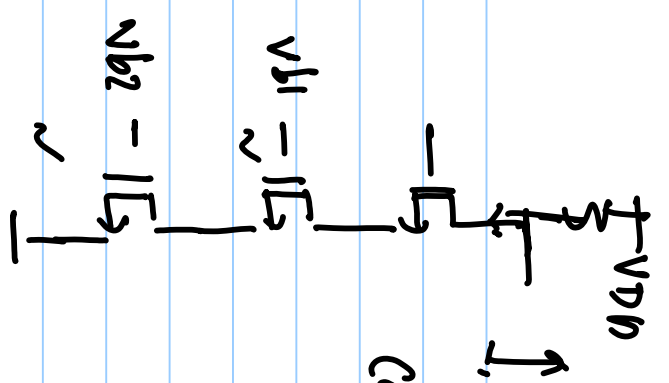$V_{d1} > V_{g1} - V_{th} = V_{s1} + V_b - V_{th}$



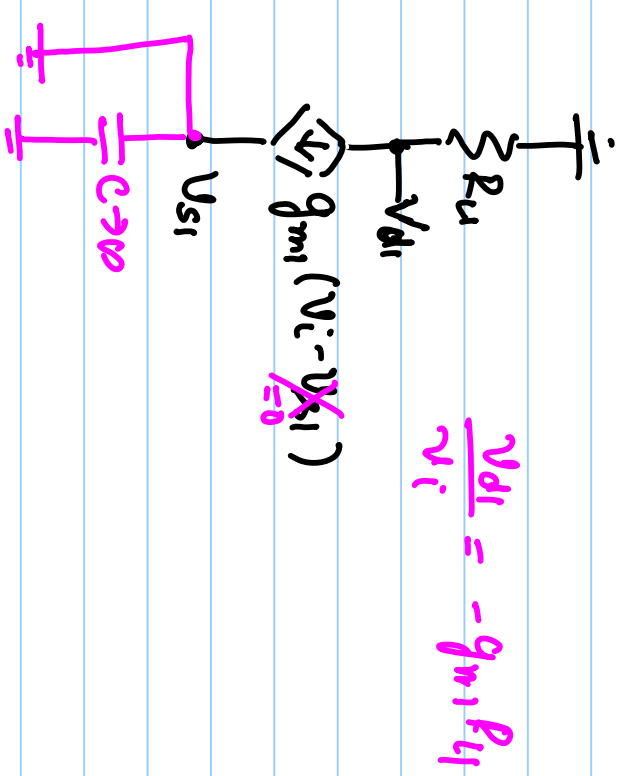Cascoding more transistors in same branch, output swing limits reduces.



$\frac{v_{d1}}{v_i} = -g_{m1} R_{L1}$

