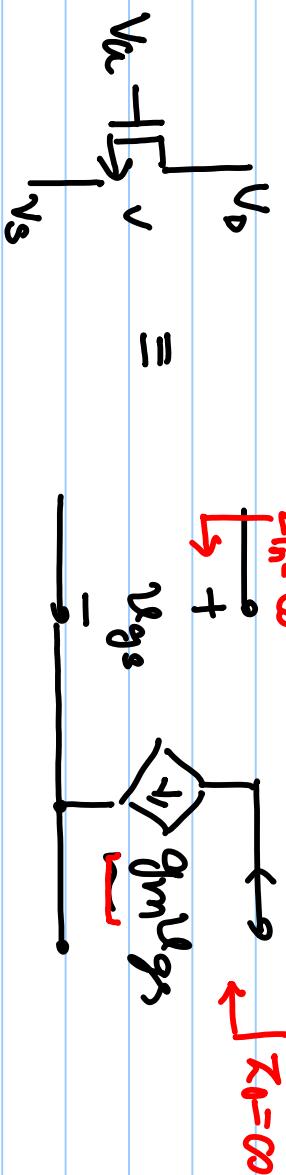


Lecture # 20


Note Title

17-09-2021

Voltage Controlled Current Source (VCCS)




$$i_{out} = g_m v_{gs}$$

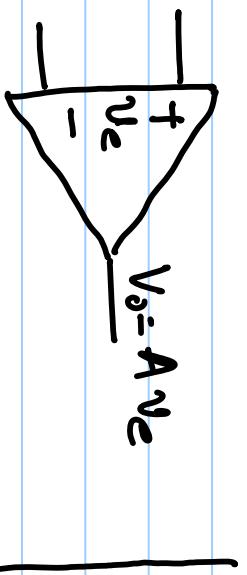



$$\frac{V_o}{V_{in}} = K f(\lambda \mu)$$

$\approx K$

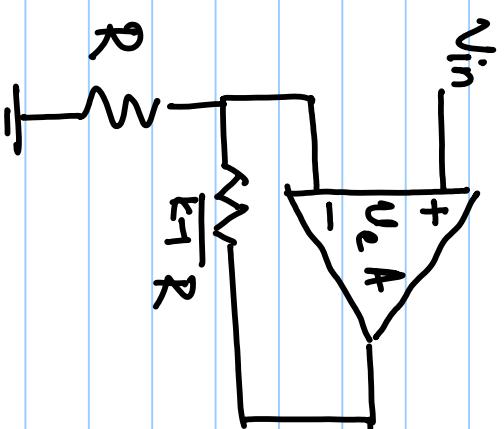


$$R \gtrsim \frac{1}{K} R$$


Ideal VCCS ✓

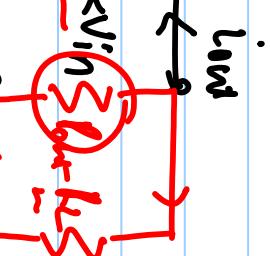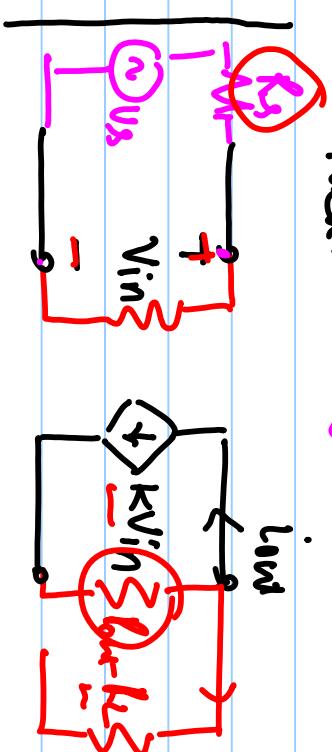

$$i_{out} = f(v_{in}) \quad v_{in}$$

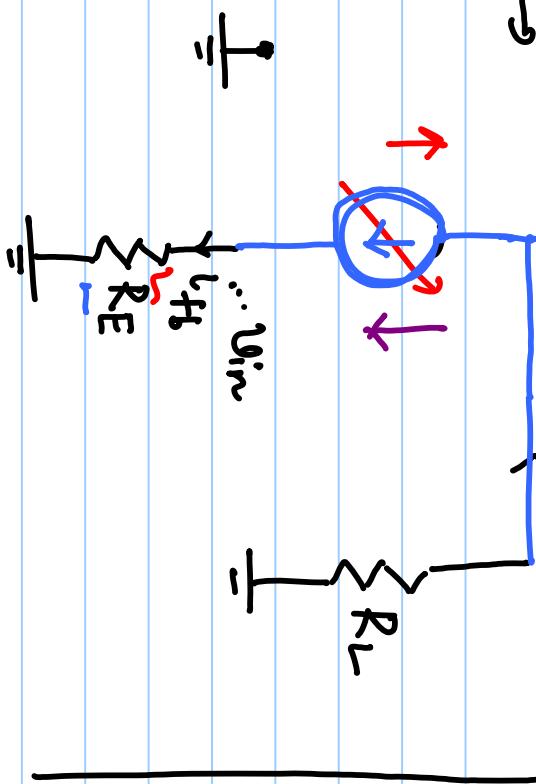

$$i_{out} = f(v_{in}) \quad v_{in}$$

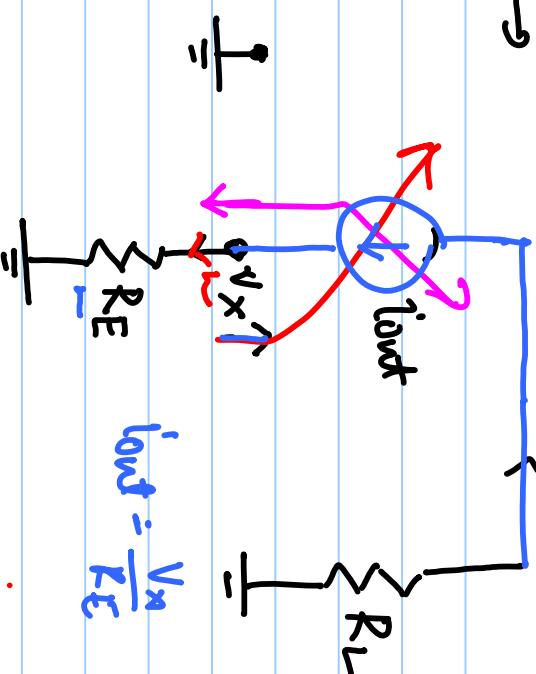

Compare i_{tb} w/ i_{out} .


$$i_{tb} = \frac{v_{in}}{R_E}$$

$$i_{out} < \frac{v_{in}}{R_E} \Rightarrow v_x < v_{in}$$


If $i_{out} > i_{tb}$ $\Delta i = i_{out} - i_{tb}$

$i_{out} < i_{tb}$ $\Delta i = -(i_{out} - i_{tb})$

$$i_{out} = f(v_{in}) \quad v$$

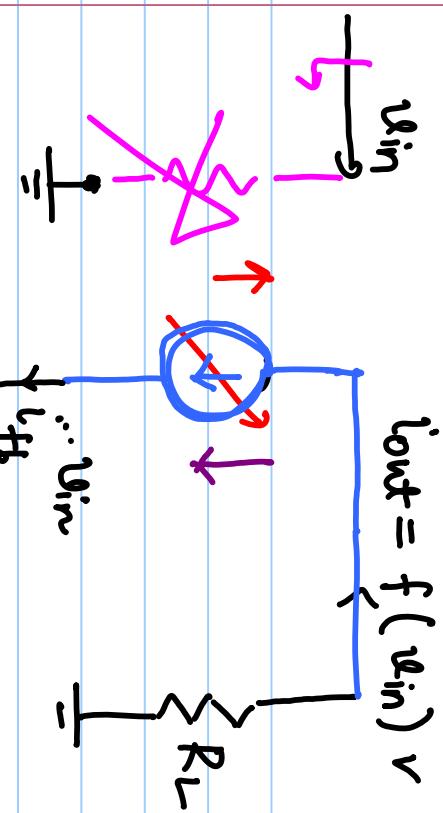

$$i_{out} = f(v_{in}) \quad v$$

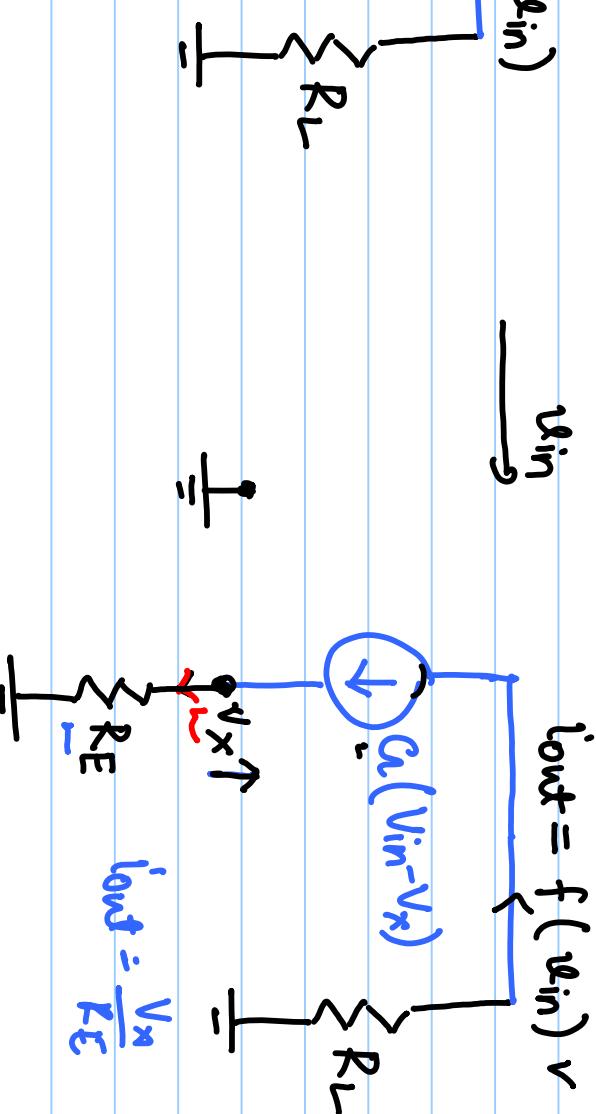


$$I_{out} = C(V_{in} - V_x)$$

$$I_{out} = \frac{V_x}{R_E}$$


Compare last w/
i_H
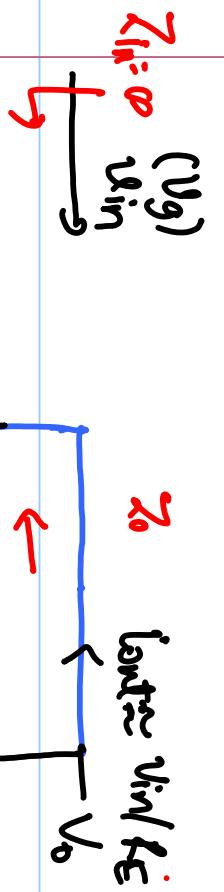
$$V_x = \frac{C R_E}{1 + C R_E} V_{in} \xrightarrow{C \rightarrow \infty} V_n = V_{in}$$



$$g_m(v_{in} - v_s) = \frac{v_s}{R_E}$$
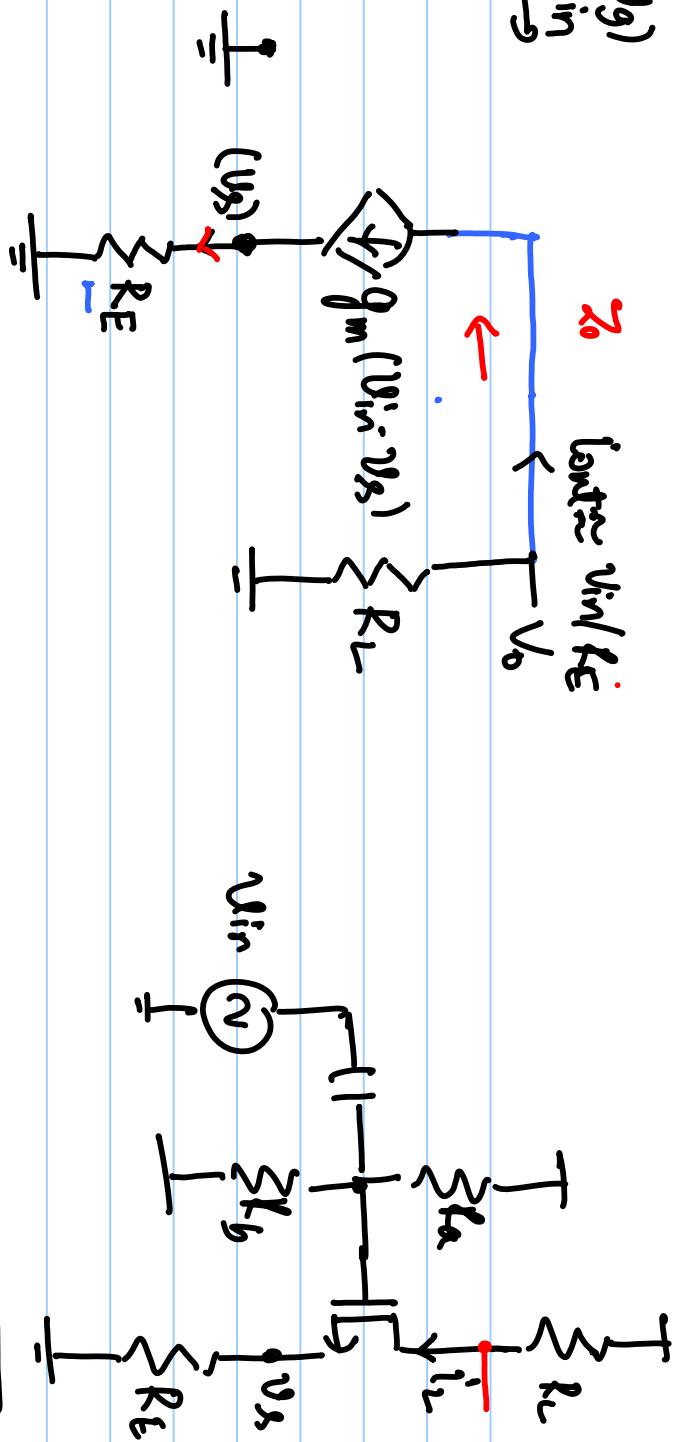
$$\left[i_c = \frac{v_{in}}{R_E} \right] \text{ VCS.}$$



$$v_R = \frac{g_m R_E}{1 + g_m R_E} v_{in}$$

$$i_L = \frac{v_s}{R_E} = \frac{g_m}{1 + g_m R_E} \cdot v_{in}$$

$$i_L \approx \frac{g_m}{R_E} v_{in} = \frac{v_{in}}{R_E}$$



$$-g_m V_s = \frac{V_b}{R_E} \Rightarrow V_b = 0$$

$$Z_0 = \frac{V_b}{I_{TEST}} = \infty$$