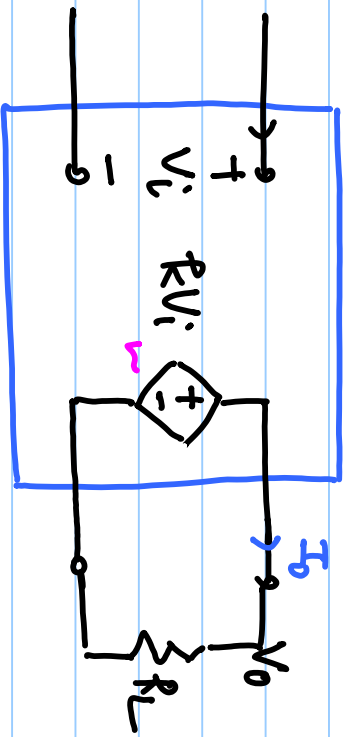


Lecture # 21

- Voltage controlled current source (VCCS)

- Voltage controlled voltage source (VCVS)


Ideal



$$Z_i = \infty, \quad Z_o = 0$$

$$I_o = \frac{V_o}{R_L} = \frac{kV_i}{R_L}$$
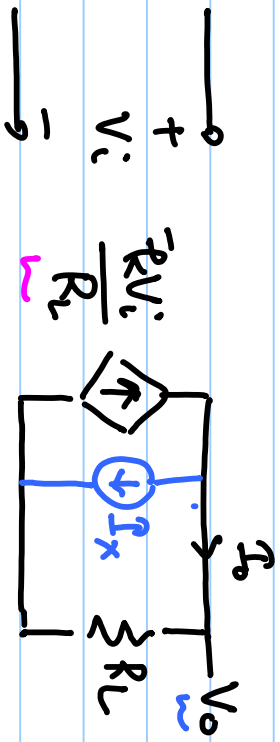
$$\left. \begin{matrix} R_{u1} \\ R_{u2} \end{matrix} \right\} V_o = kV_i$$



$$V_o = \frac{kV_i}{R_L} \cdot R_L = kV_i$$

if $V_o > kV_i$ then $I_x = g(V_o - kV_i)$

$V_o < kV_i$ then $I_x = -g(V_o - kV_i)$

$$\left(\frac{kV_i}{R_L} - I_x \right) R_L = V_o$$

$$\left\{ \frac{K V_i}{R_L} - g(V_o - K V_i) \right\} R_L = V_o$$

$$\left\{ K V_i \left(\frac{1}{R_L} + g \right) - g V_o \right\} R_L = V_o$$



$$i_g \quad K=1 \quad \left\{ V_i \left(\frac{1}{R_L} + g \right) - g V_o \right\} R_L = V_o$$

g is very large

$$g(V_i - V_o) \cdot R_L = V_o$$


$$V_o = \frac{g R_L}{1 + g R_L} V_i$$


$$\approx V_i$$

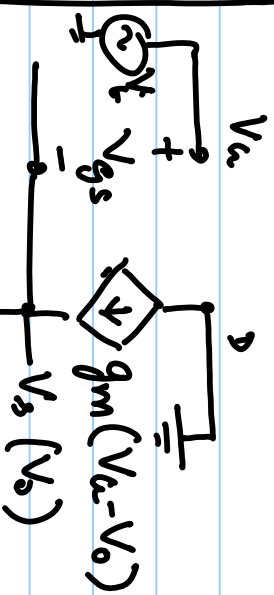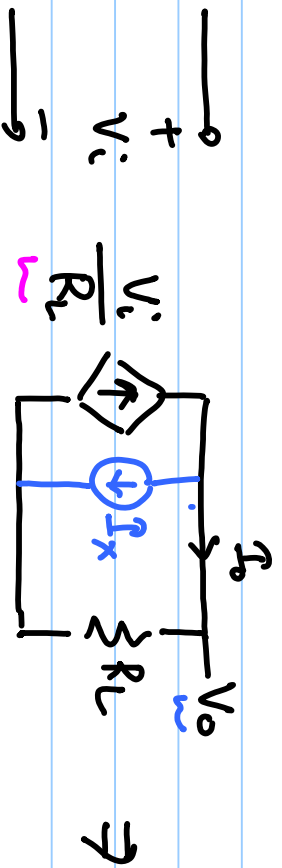



$$g_m(V_i - V_o) = \frac{V_o}{R_L}$$
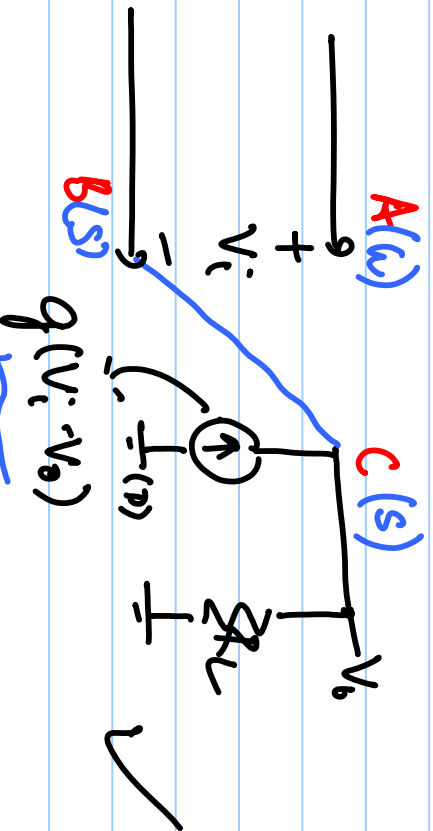
$$V_o = \frac{g_m R_L}{1 + g_m R_L} V_i$$



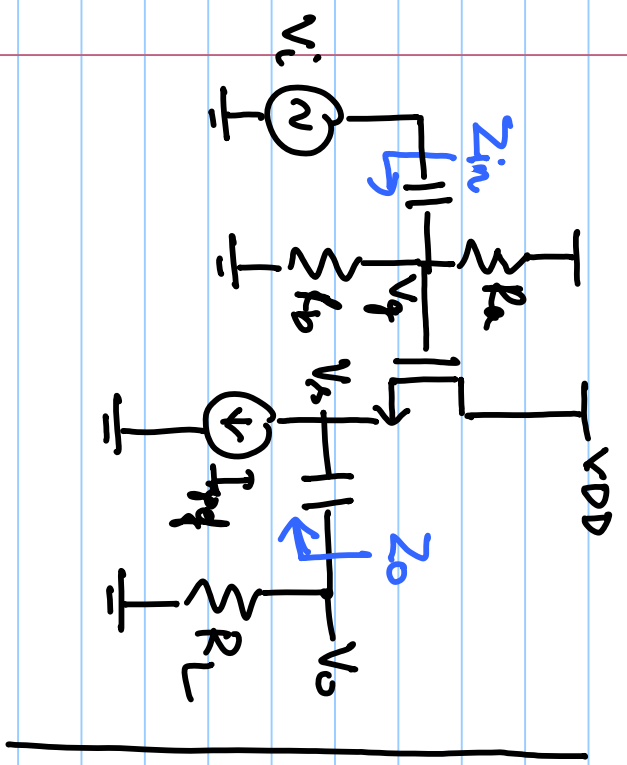


NCVS

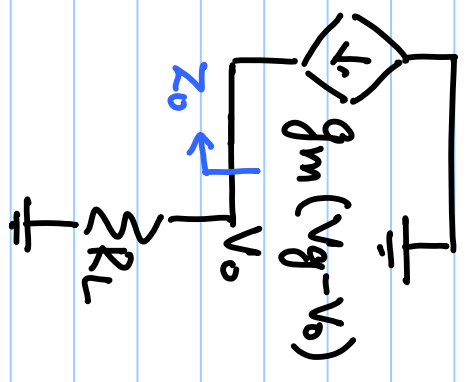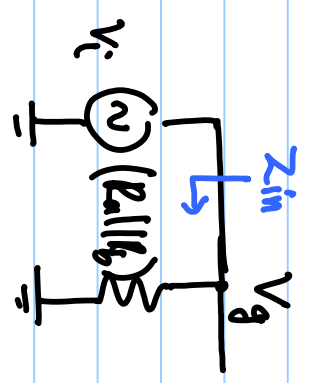

- $Z_{in} = (R_a || R_b)$ ✓

- $Z_o = \frac{1}{g_m} \xrightarrow{g_m \rightarrow \infty} Z_o = 0$


- $\frac{V_o}{V_i} \approx 1$

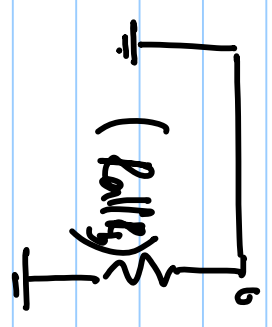


$I_T = - (-g_m V_T)$

$= g_m V_T$

$Z_o = V_T / I_T = 1 / g_m$

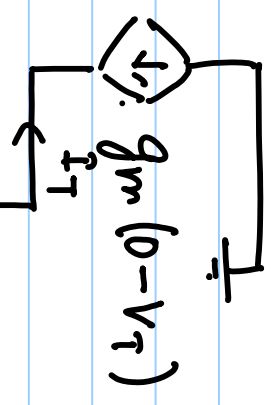


Current Controlled Current Source (CCCS)

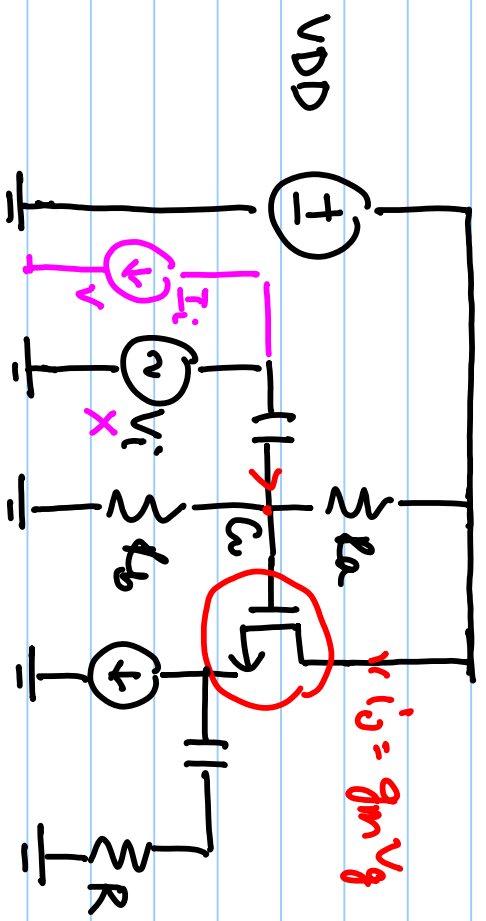


$$r_{i_s} = g_m V_g$$

$$V_g = -I_i (R_b || R_b)$$


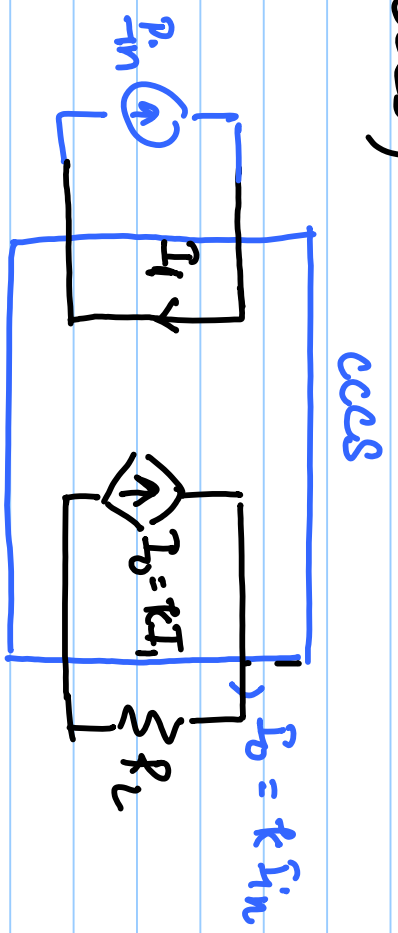


CCCS

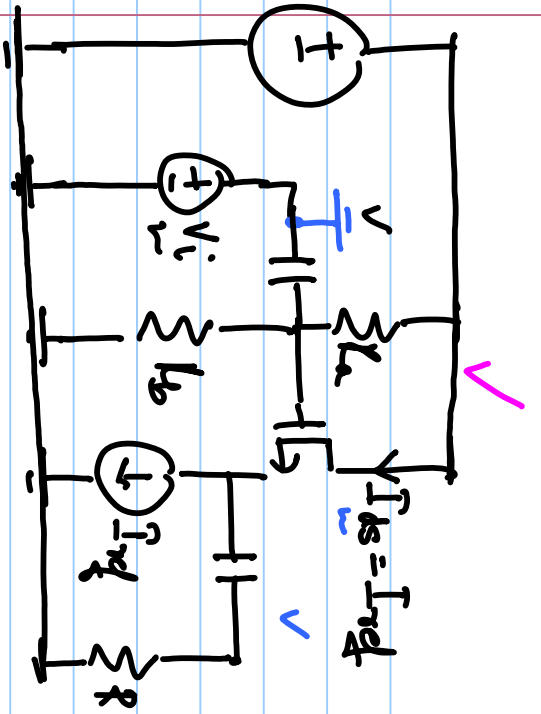

$\Delta I_{DS} = f(V_i)$


Analysis ✓

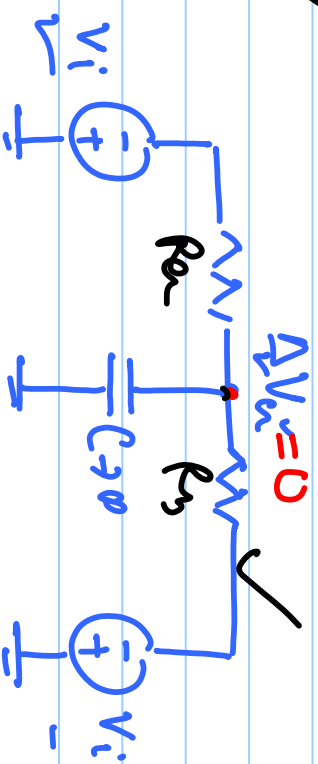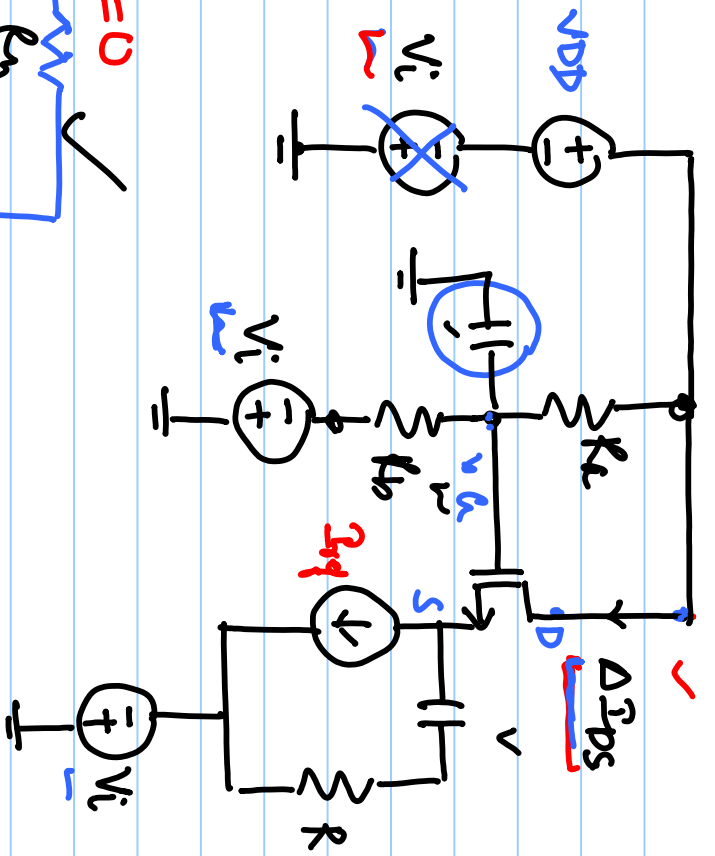

$i_o = -g_m V_s = \frac{V_s - V_i}{R}$


$\Rightarrow V_s = \frac{1}{1 + g_m R} V_i$

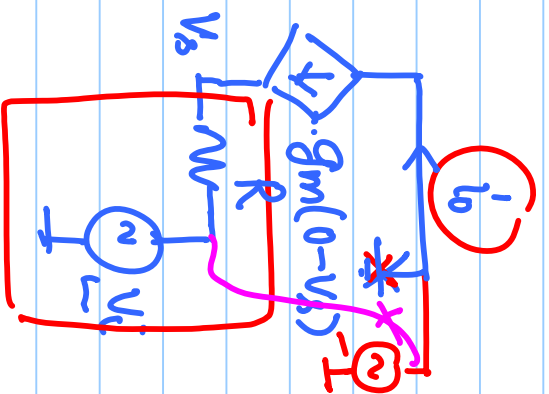$i_o = -\frac{g_m}{1 + g_m R} V_i \xrightarrow{g_m R \rightarrow \infty} i_o = -\frac{V_i}{R}$




$$i_o = -\frac{g_m}{(1+g_m R)} v_i \longrightarrow i_o = -\frac{v_i}{R}$$

$$i_o = -i_{in}$$

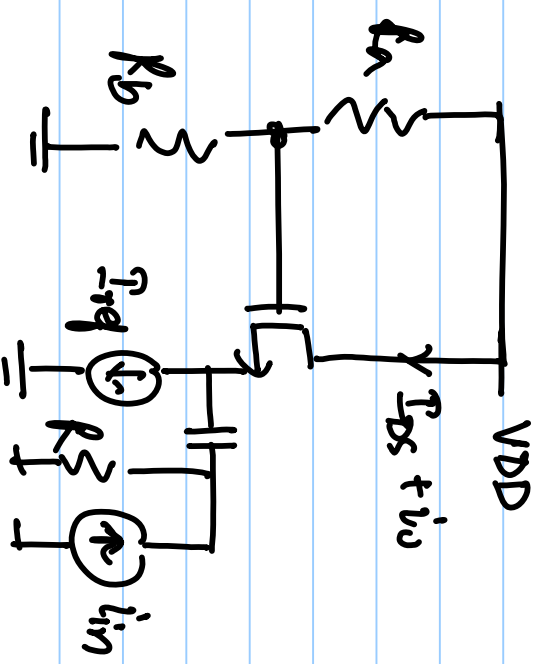

Common-Gate Amplifier (CCG)

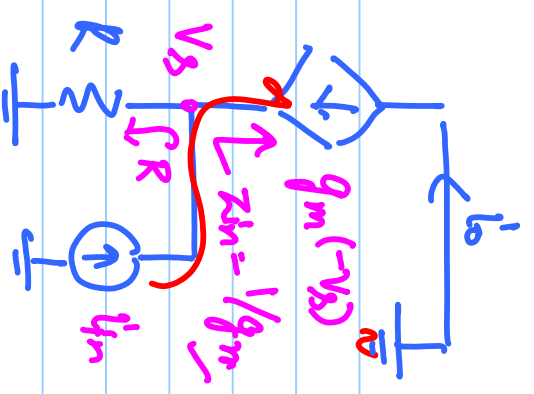

$$i_o = i_{in} \frac{R}{R + \frac{1}{g_m}}$$