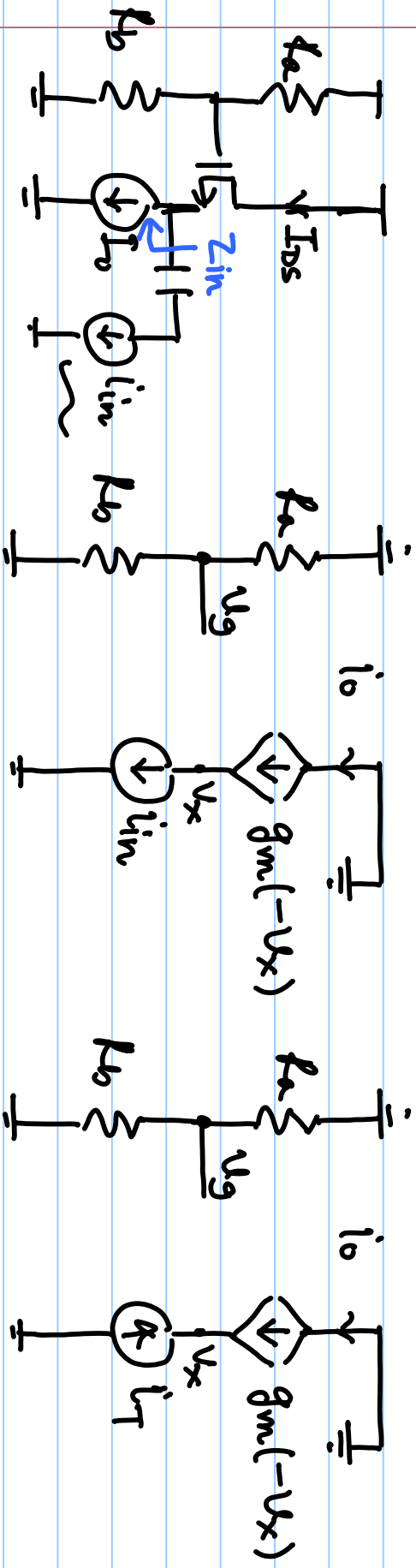


lecture # 22

CCCS



Common-Gate Amp.


$$i_o = -g_m V_x = i_{in}$$

$$i_T = +g_m V_x$$



$$Z_{in} = \frac{V_x}{i_T} = \frac{+1}{g_m}$$

$$Z_{in} \xrightarrow{g_m \rightarrow \infty} 0$$


$$\frac{i_o}{i_{in}} = 1$$

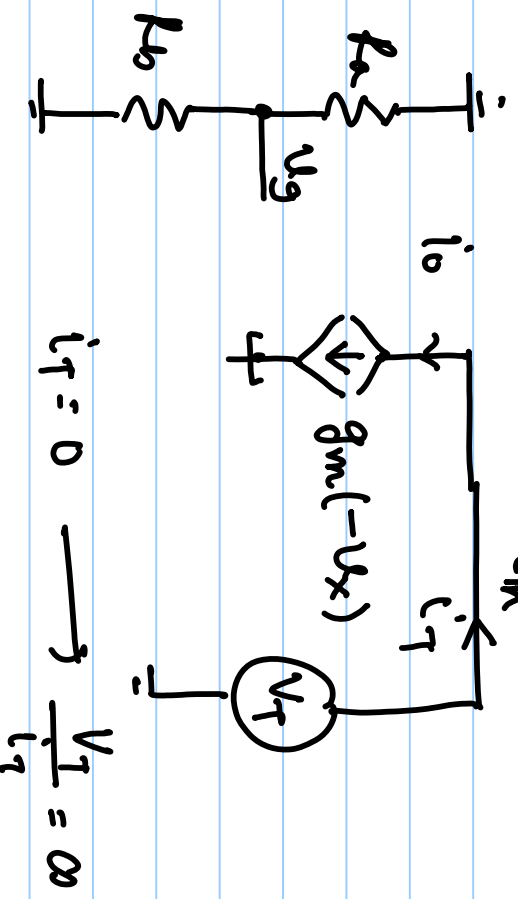
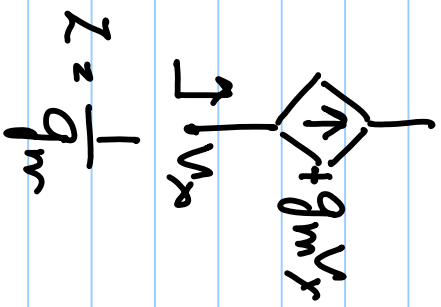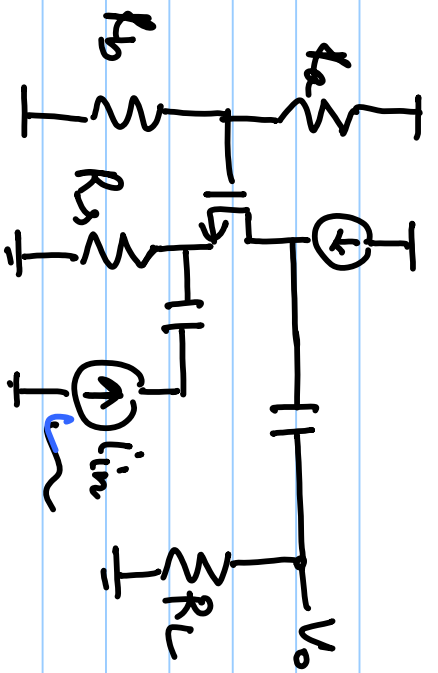
$$i_T = 0 \rightarrow \frac{V_T}{i_T} = \infty$$





$$Z = \frac{1}{g_m}$$

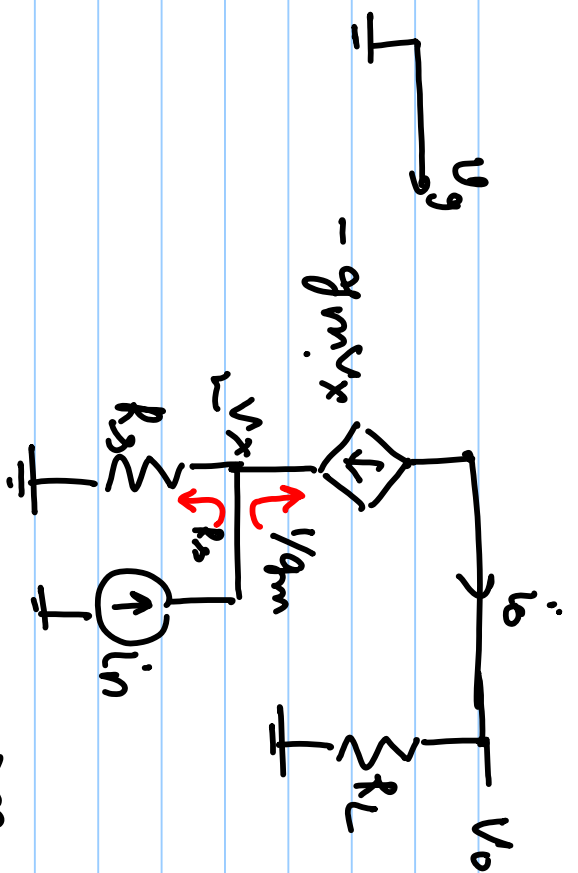


$$i_o = \left(\frac{R}{\frac{1}{g_m} + R} \right) i_{in} \xrightarrow{g_m \rightarrow \infty} i_o = i_{in}$$
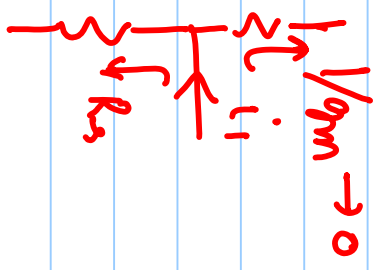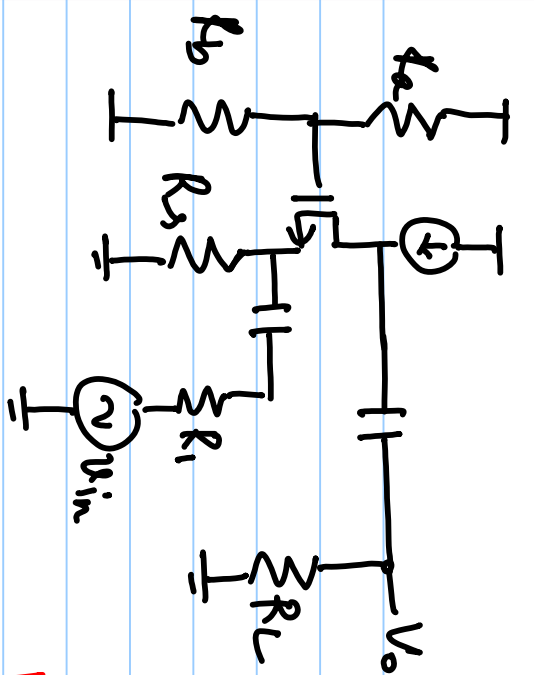
$$v_o = \frac{g_m R}{1 + g_m R} i_{in} R_L \xrightarrow{g_m \rightarrow \infty} i_{in} \cdot R_L$$


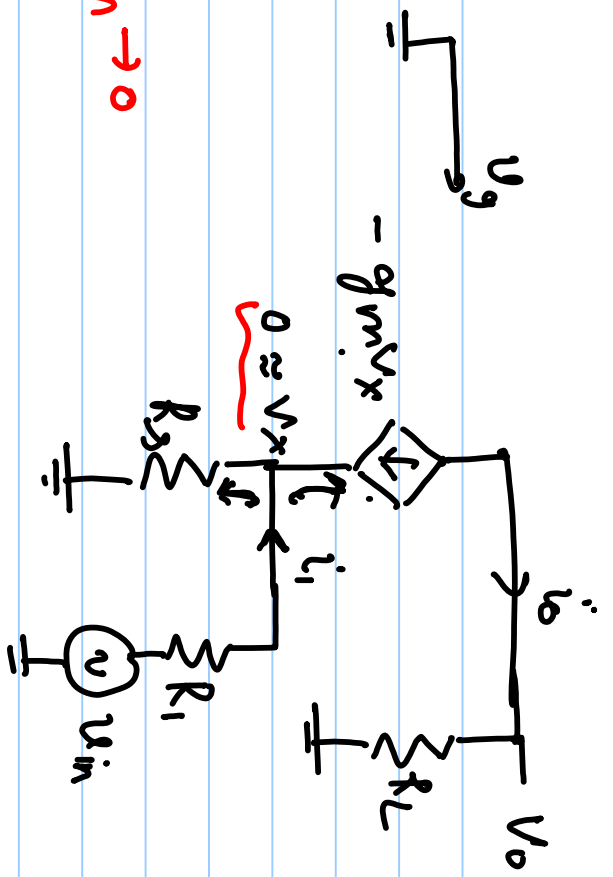
$$i_{up} = \frac{R_3}{R_3 + \frac{1}{g_m}} \times i_i$$



$$i_i = \frac{v_{in}}{R_1}$$

$$i_o = i_i$$

$$v_o = v_{in} \cdot \frac{R_L}{R_1}$$


$$\frac{v_o}{v_{in}} = \frac{R_L}{R_1}$$

$g_m \rightarrow \infty$


$$v_x = v_{in} \times \frac{\frac{1}{g_m} || R_3}{\left(\frac{1}{g_m} || R_3\right) + R_1}$$

$$v_o = g_m v_x \cdot R_L$$

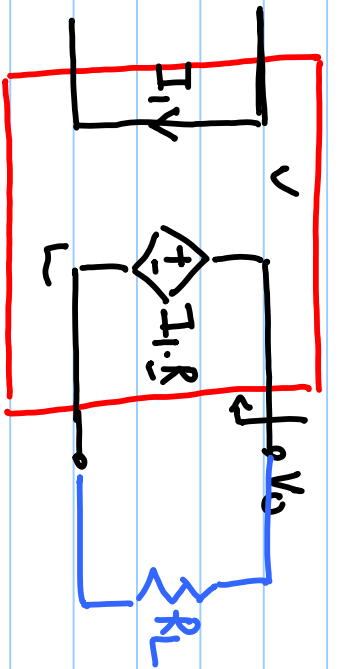
Current Controlled Voltage Sources (CCVS)



$Z_{in} = 0, Z_0 = 0$

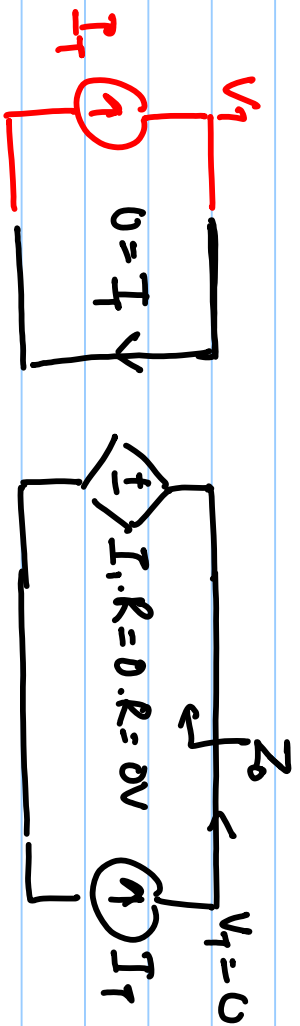

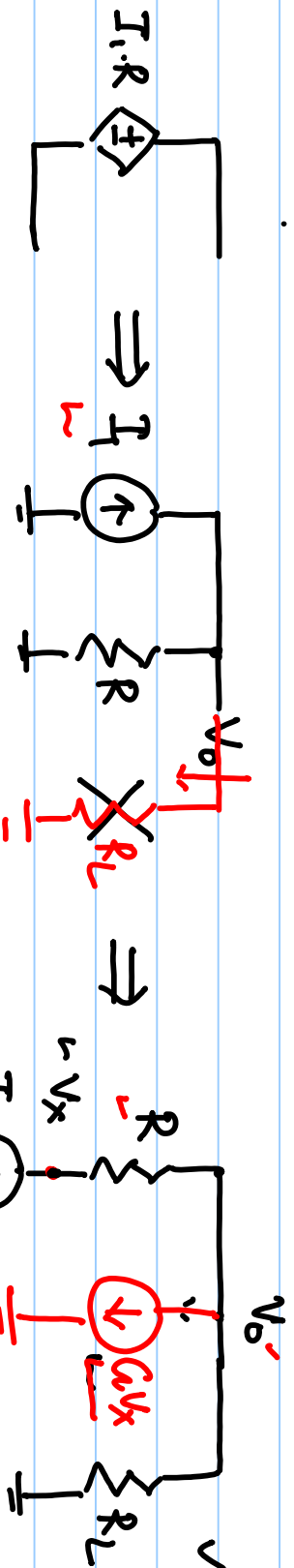$Z_0 = \frac{V_1}{I_1} = \frac{0}{I_1} = 0 \Omega$



$G.V_x + I_1 + \frac{V_0}{R_L} = 0 \quad (1)$

$V_0 = V_x + I_1 \cdot R \quad (2)$

$V_0 = V_x + I_1 \cdot R \xrightarrow{V_x \rightarrow 0} V_0 = I_1 \cdot R$

$V_x > 0$

$V_x < 0$




$$u (V_0 - I_1 \cdot R) + I_1 + \frac{V_0}{R_L} = 0$$

$$V_0 \left(u + \frac{1}{R_L} \right) = I_1 \cdot R \cdot u - I_1 = I_1 R \left(u - \frac{1}{R} \right)$$

$$V_0 = I_1 \cdot R \frac{\left(u - \frac{1}{R} \right)}{\left(u + \frac{1}{R_L} \right)} \xrightarrow{u \rightarrow \infty} V_0 = I_1 \cdot R$$



$$V_K = V_0 - I_1 \cdot R = I_1 \cdot R \frac{\left(u - \frac{1}{R} - u - \frac{1}{R_L} \right)}{u + \frac{1}{R_L}}$$
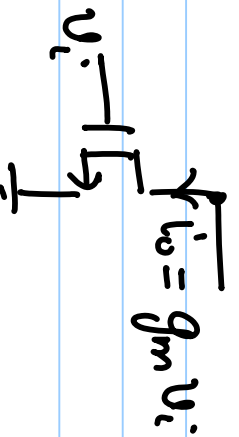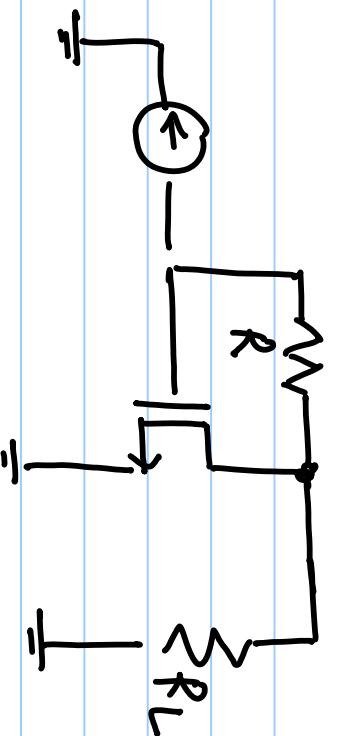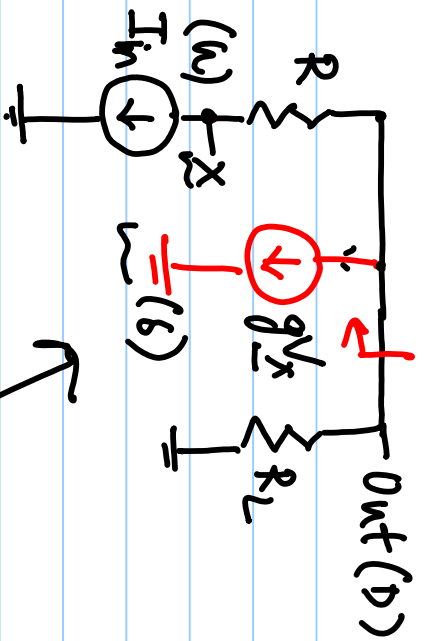
$$= I_1 \cdot R \frac{\left(-\frac{1}{R} - \frac{1}{R_L} \right)}{\left(u + \frac{1}{R_L} \right)} \xrightarrow{u \rightarrow \infty} V_K = 0$$



$$\frac{i_o}{v_i} = g_m$$


Trans-Conductance

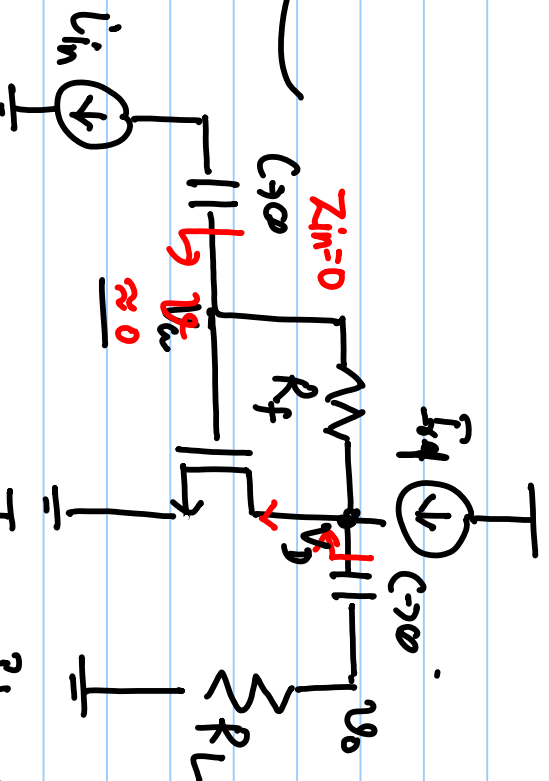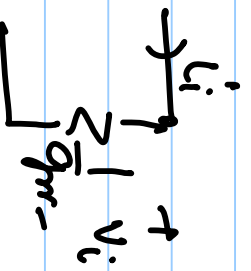

Trans-Impedance Amp.

$$v_o = i_{in} \cdot R_f$$

$$\frac{v_o}{i_{in}} = R_f$$

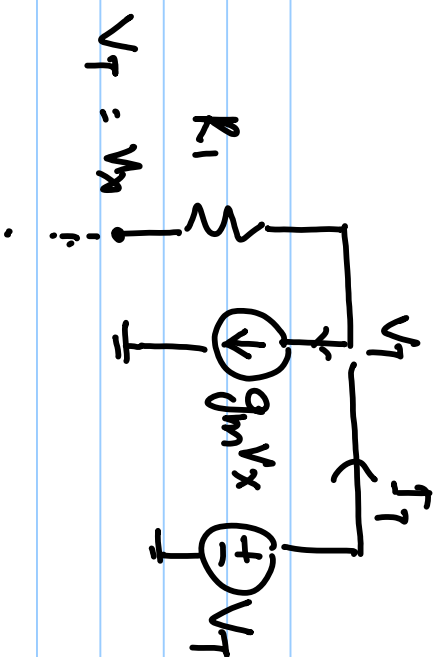

$$I_T = g_m V_n$$

$$\frac{V_n}{I_T} = \frac{1}{g_m} \rightarrow 0$$

- Common Source (CS) Amp.
- Common Drain (CD) Amp.
- Common Gate (CG) Amp.

- VCCS
- VCVS
- CCCS
- CCVS

- Transimpedance Amp.