

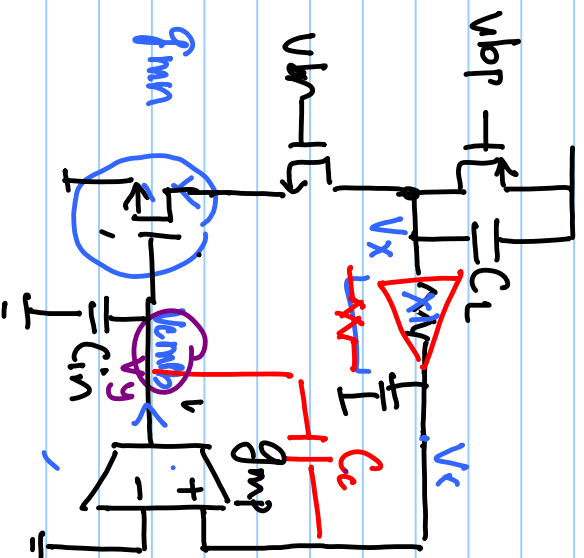


Lecture # 38


Common mode Feedback Inop

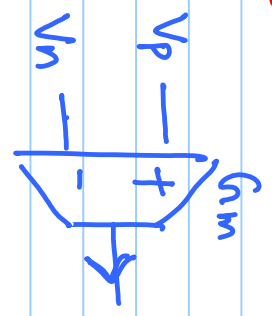
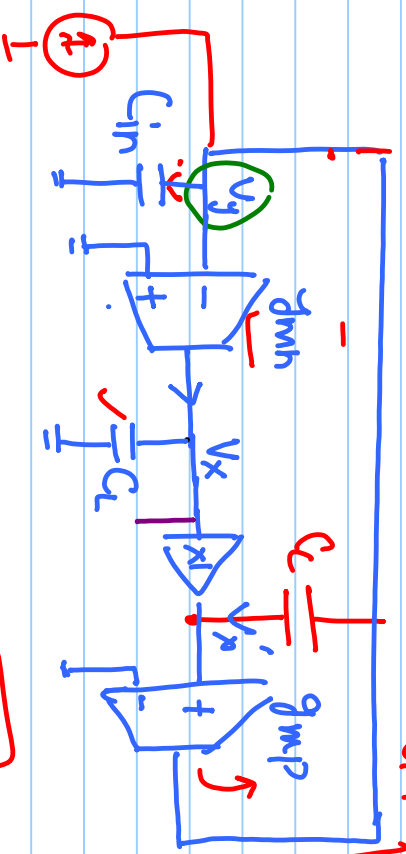
$$i_{out} = \frac{V_y}{1/2C_{in}} - g_{mp}V_x = \frac{V_y}{1/2C_{in}} + g_{mp} \left(-\frac{g_{mn}V_y}{2C_c} \right)$$




$$i_{out} = g_m (V_p - V_n)$$

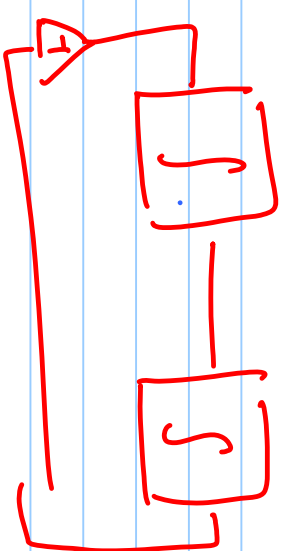

$$V_x = \frac{g_{mn}V_y}{2C_c}$$

$$i = V_y/R = \frac{g_{mn}V_y}{1/2C_c} = g_{mn}V_y \frac{C_c}{1/2C_c}$$
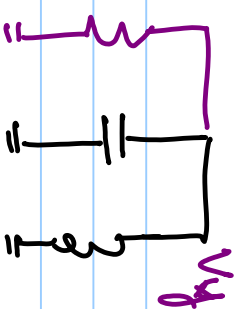
$$= v_y \left[s C_{in} + \frac{1}{s C_L / g_m g_{mn}} \right]$$





$$= \frac{v_y}{1/s C_{in}} + \frac{v_y}{s L_o}$$

$$v_y \sum_k r_{i_k}$$

$$i = \frac{v_y}{R}$$

$$v_x = \frac{g_{mn} v_y}{s C_L}$$

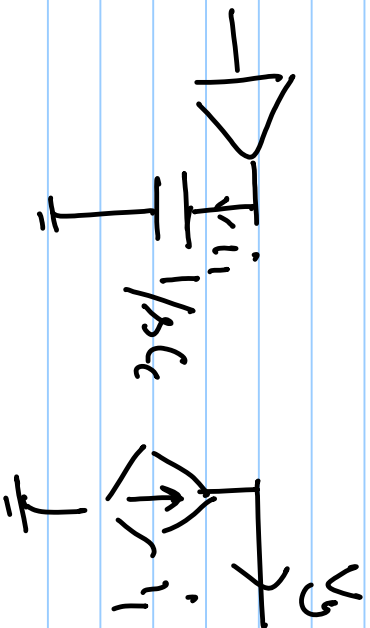

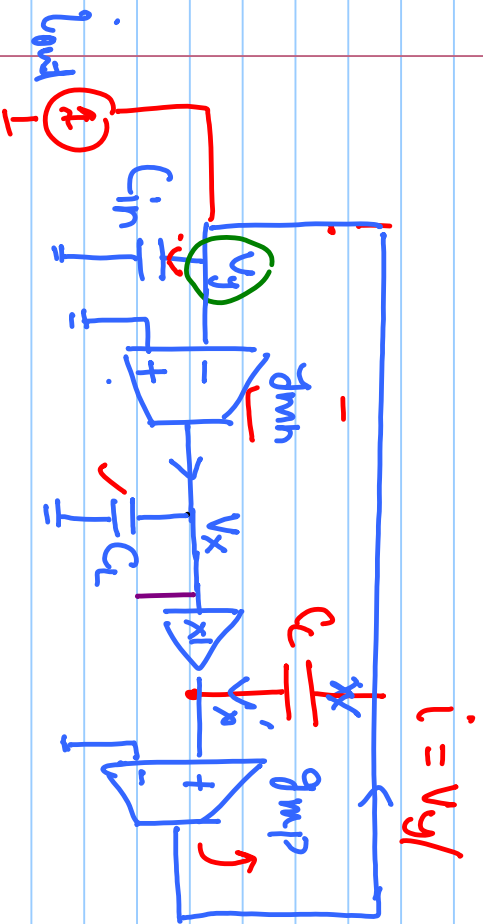

$$i = \frac{V_y}{R}$$


$$\frac{V_x'}{V_x} = \frac{1/sC_L'}{1/sC_L' + R}$$

$$i_{out} = \frac{V_y}{1/sC_{in}} + \frac{V_y - V_x'}{1/sC_c} - g_{mp} V_x'$$

$$= \frac{V_y \cdot sC_{in} + V_y - \left(\frac{-g_{mn} V_y}{sC_c} \right) - g_{mp} \left(\frac{-g_{mp} V_y}{sC_c} \right)}{1/sC_c}$$



$$= V_y (sC_{in} + sC_c) + \frac{V_y}{sC_c} + \frac{V_y \cdot g_{mn} C_c}{sC_c}$$

Transimpedance Amp.

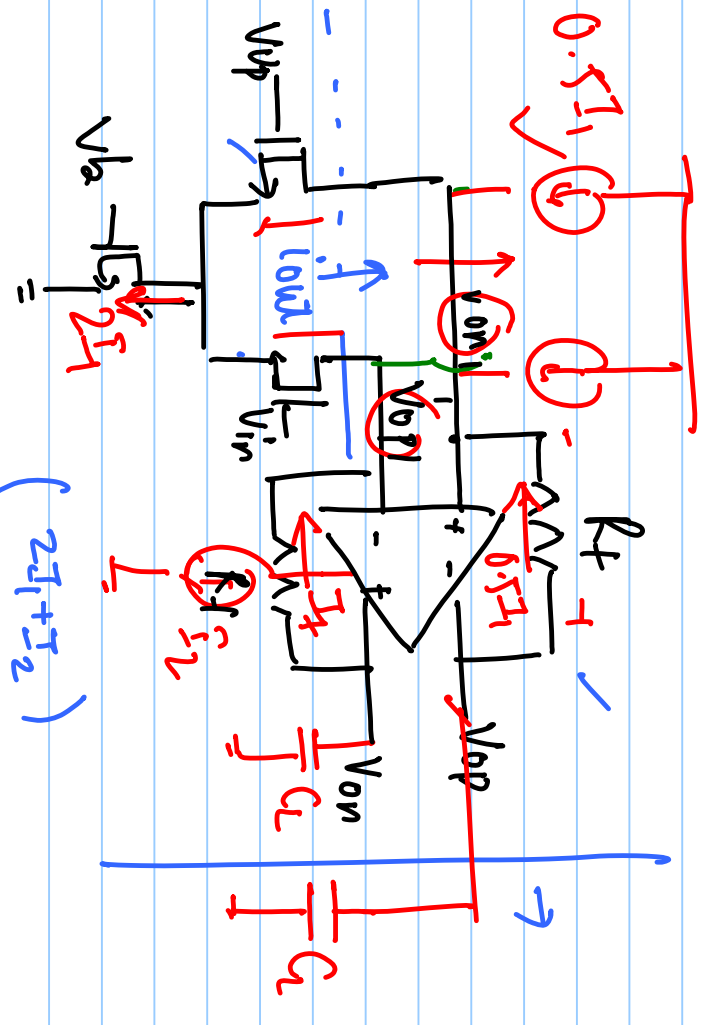

$$I_{out} = g_{m1} (V_{ip} - V_{in}) = g_{m1} V_{sig}$$
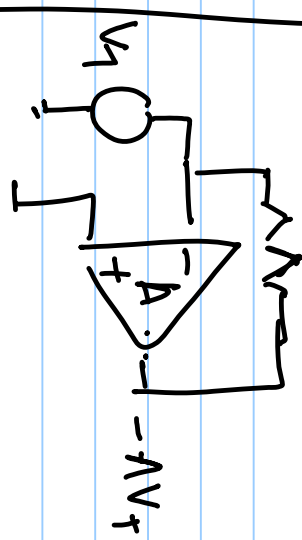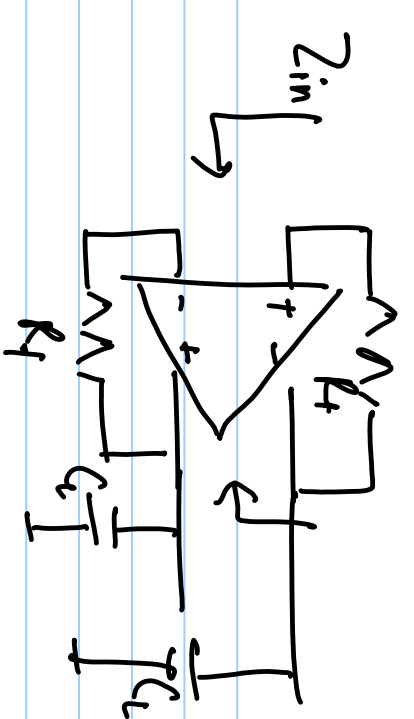
$$V_{op} - V_{on} = g_{m1} V_{sig} \times R_f$$



$$I = \frac{V_1 - (-AV_1)}{R_f}$$

$$Z = \frac{V_1}{I} = \frac{R_f}{1+A}$$

