
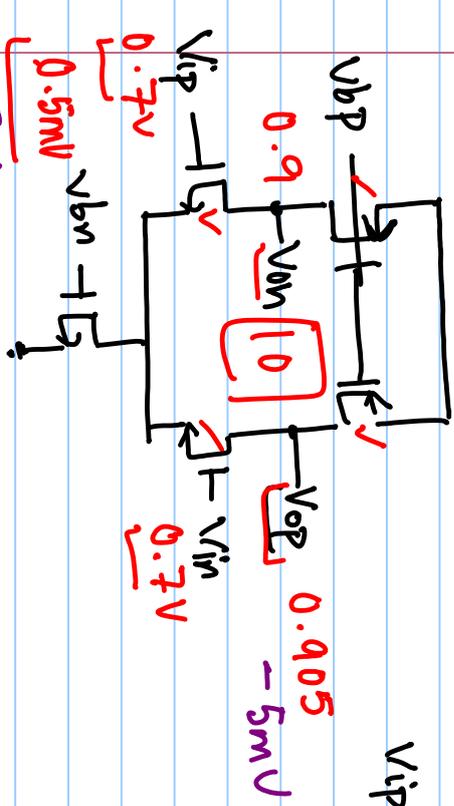


Lecture # 4b


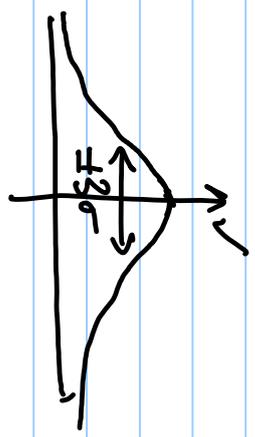


$V_{ip} = V_{in} \rightarrow V_{op} \neq V_{on}$

$\Delta V_{out} = V_{op} - V_{on} \sigma_{os}$
 $V_{ip} = V_{in}$



Input referred offset —

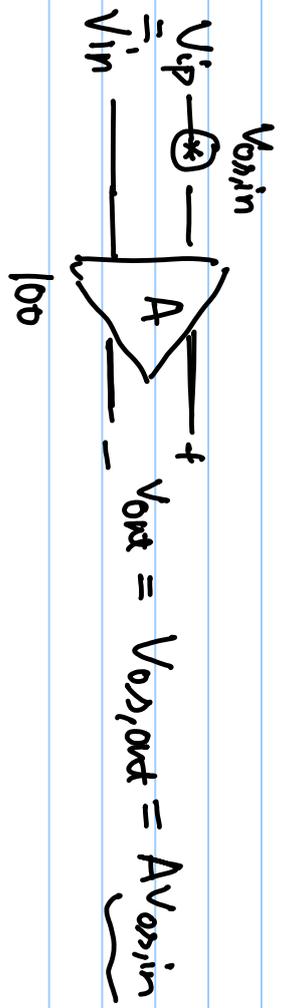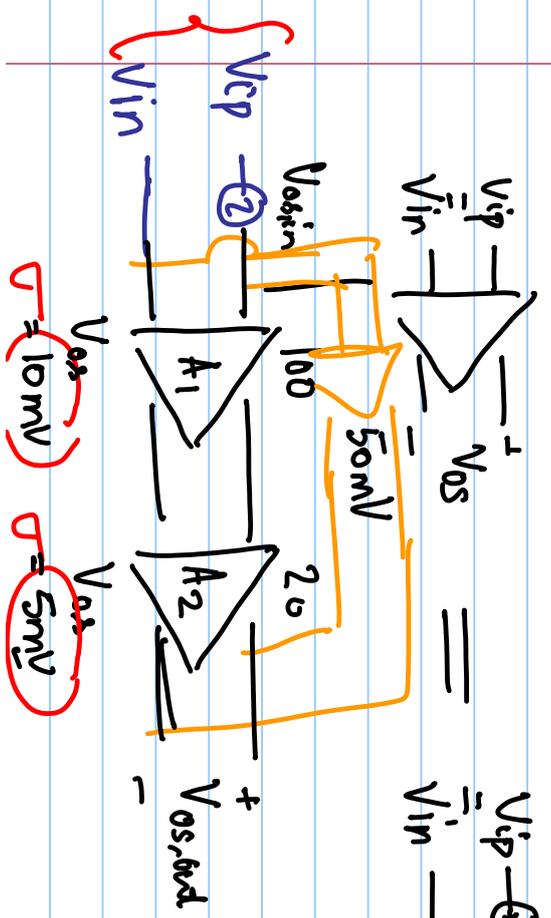

$V_{os,out} = A_1 \cdot A_2 \cdot V_{os,in}$

$V_{os,out} = 5 \text{ mV} + A_2 \cdot 10 \text{ mV}$


$\sigma_{os,out}^2 = \sigma_{os,avg2}^2 + A_2^2 \cdot \sigma_{os,avg1}^2$

$$V_{\text{output}} = V_{\text{os}, \text{amp}2} + A_2 \cdot V_{\text{os}, \text{amp}1}$$


$$V_{\text{O}, \text{out}} = A_1 \cdot A_2 \cdot V_{\text{O}, \text{in}}$$

$$\sigma_{\text{O}, \text{out}}^2 = A_1^2 A_2^2 \sigma_{\text{O}, \text{in}}^2$$
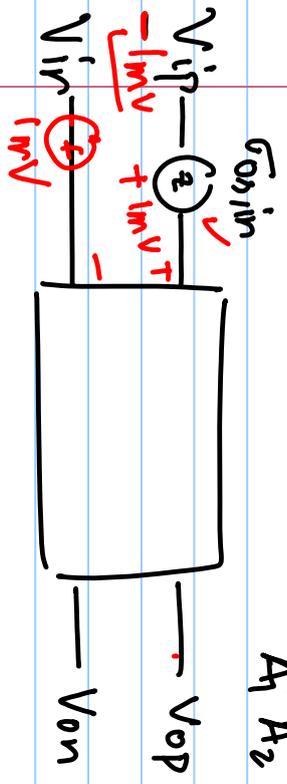
$$\sigma_{\text{O}, \text{in}}^2 = \frac{\sigma_{\text{O}, \text{amp}2}^2}{A_1^2 A_2^2} + \frac{1}{A_1^2} \sigma_{\text{O}, \text{amp}1}^2$$





$$|V_{\text{os}, \text{in}}| < 3\sigma$$

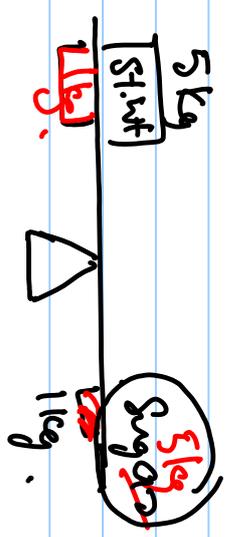

$$V_{\text{ip}} = \frac{V_{\text{diff}}}{2} = \frac{0.5 \text{ mV}}{2} = 0.25 \text{ mV}$$

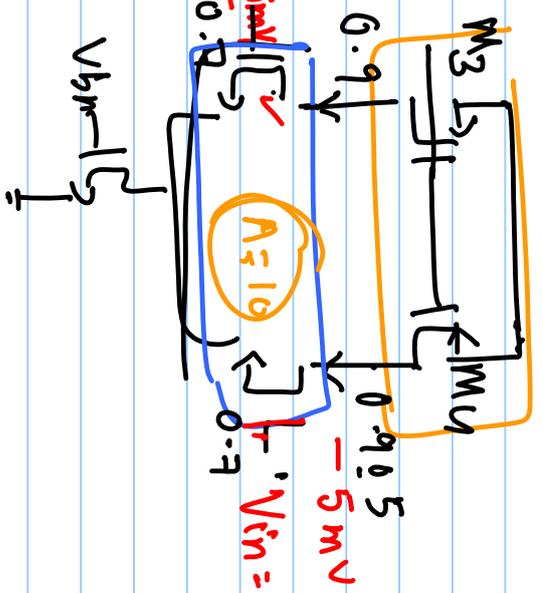
$$V_{\text{in}} = -\frac{V_{\text{diff}}}{2}$$



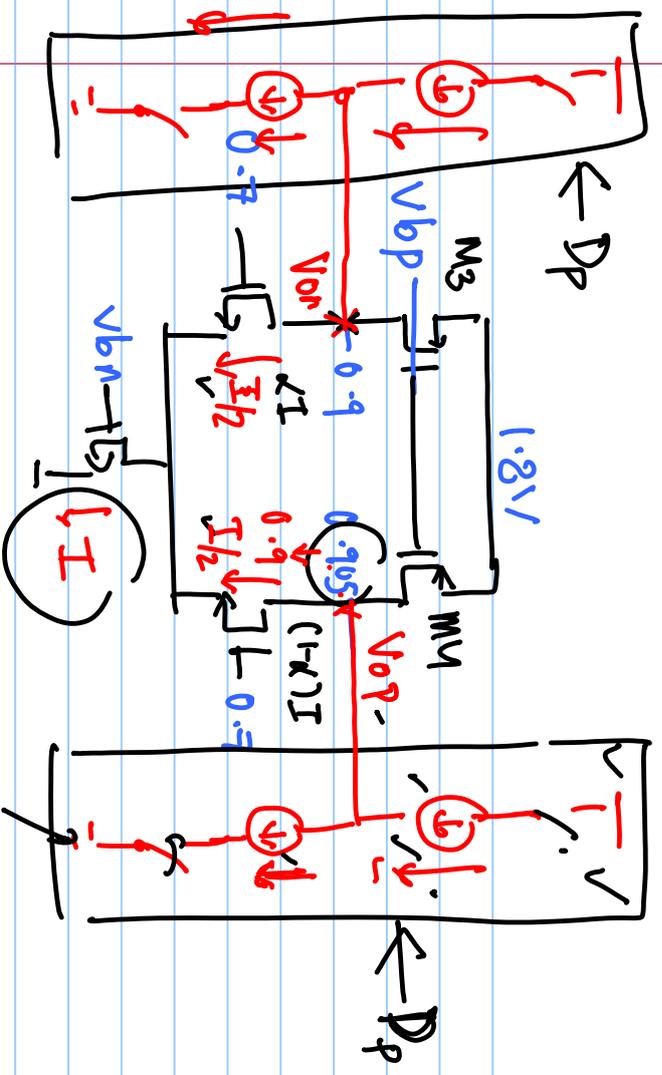

$$V_{op} = V_{on}$$

$$V_{op} - V_{on} \neq 0$$

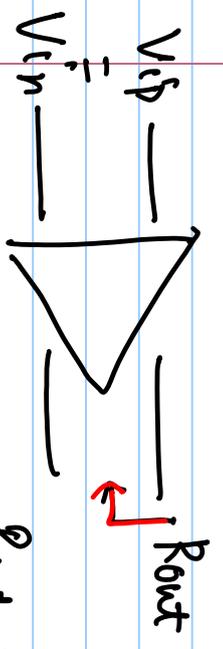

$$R_{out} \times I_{DACLSB} = \underline{V_{res}}$$

$$\sigma_{\text{resout}} = 10 \text{ mV}$$


$$V_{op} - V_{on} \left| \begin{array}{l} V_{ip} = V_{in} \\ \leq 3\sigma = \pm 30 \text{ mV} \end{array} \right.$$




$$-30 \text{ mV} < \underline{V_{\text{resout}}} < 30 \text{ mV} \rightarrow$$

$$\text{Range} = \underline{64 \text{ mV}}$$

Resolution of offset cancellation
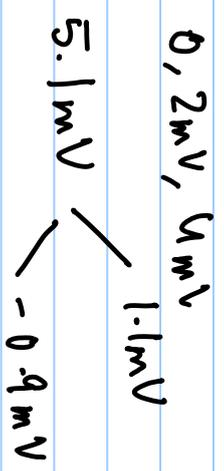
$$= \underline{2 \text{ mV}} \leftarrow \text{Residual offset}$$




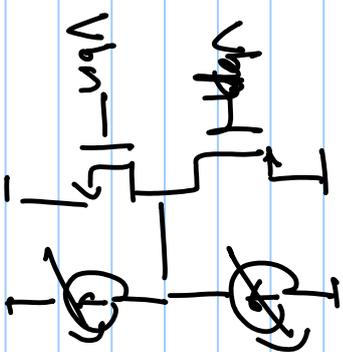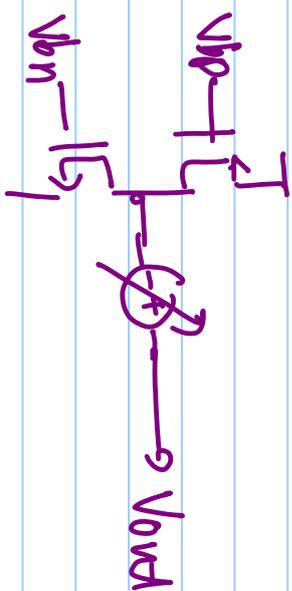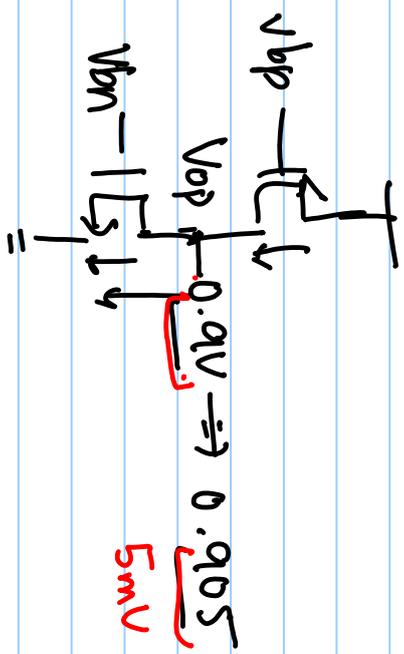

$$I_p = \frac{K_p}{2} \left(\frac{W}{L} \right)_p (V_{DD} - V_{CEP} - |V_{TP}|)^2 (1 + \lambda (V_{DD} - V_{out}))$$

$$I_n = \frac{K_n}{2} \left(\frac{W}{L} \right)_n (V_{in} - V_{in})^2 (1 + \lambda (V_{out})) + \Delta I = I_p$$

$$\Delta V = \Delta I \cdot R_{out}$$

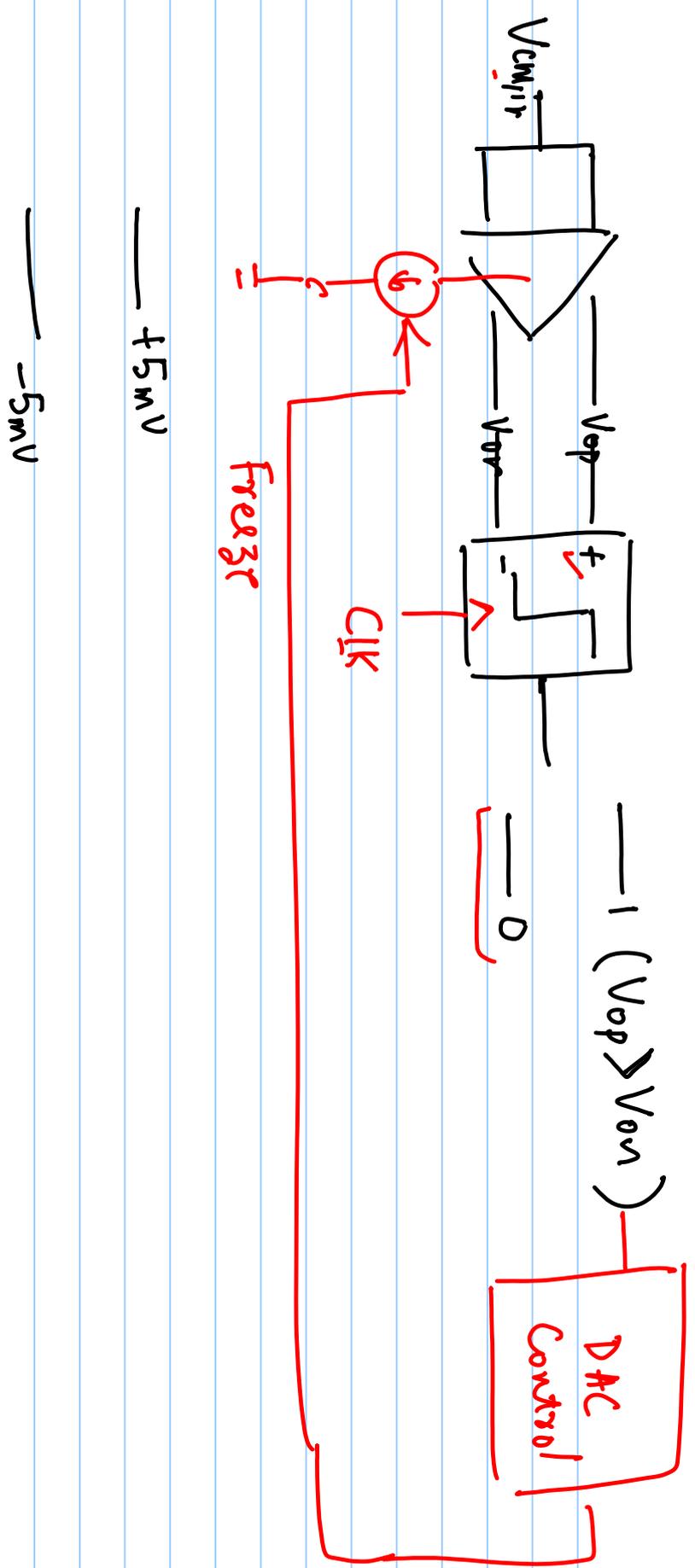

$1 (V_{op} > V_{on})$

0

$+5mV$

$-5mV$