

Lecture # 43

Switched capacitor Circuits.





$$\frac{V_{out}}{V_{in}} = \frac{1}{1+sRC}$$

$$\omega_{-3dB} = \frac{1}{RC}$$

$$= \frac{1}{\underbrace{R_{nom} C_{nom}}_{200\text{fHz} - 20\text{MHz}}}$$


R, C: PVT variations.

RF Tx & Rx

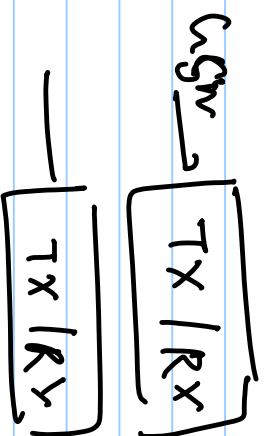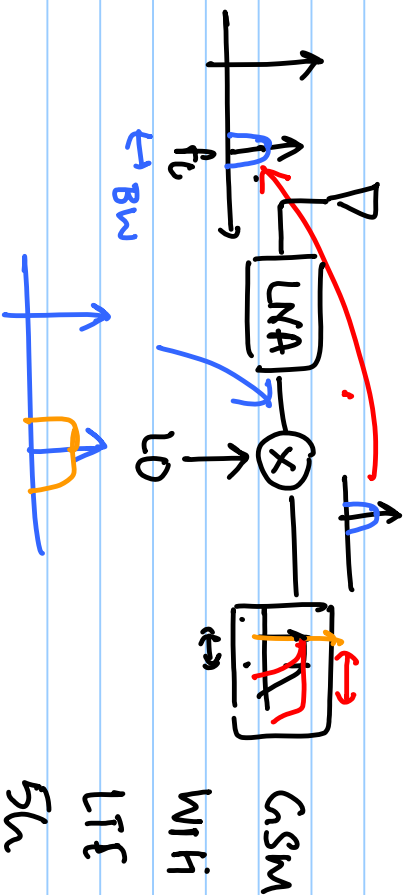


CGM
WIFI
LTE
5G
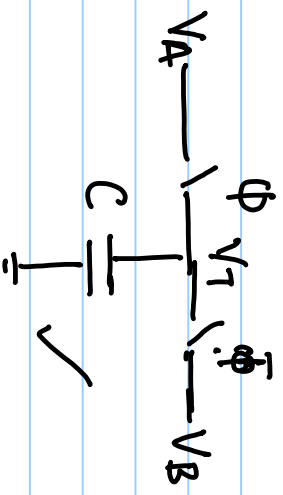
$$i = \frac{V_A - V_B}{R} \Rightarrow R = \frac{V_A - V_B}{i_{avg}}$$



ϕ is high: $V_T = V_A$

$$q_V(T/2) = C V_A$$

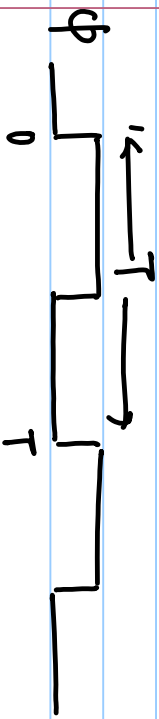


ϕ is low: $V_T = V_B$

$$q_V(T) = C V_B$$

$$i_{avg} = \frac{C(V_A - V_B)}{T}$$

$$= \frac{V_A - V_B}{(T/C)} = \frac{V_A - V_B}{R}$$
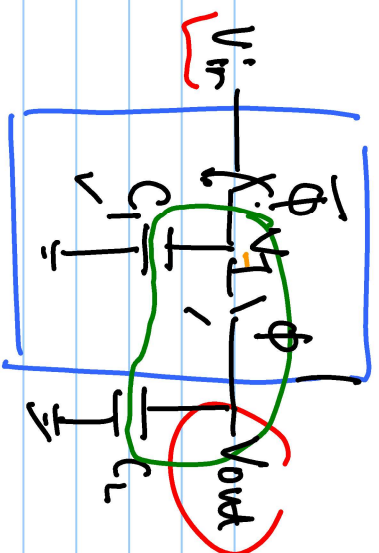
$$\Rightarrow R = T/C = \frac{1}{C f_s}$$



$$R_2 \approx \frac{1}{f_s C_1}$$

$$N=3dB = \frac{1}{RC}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{1}{1+sRC} \approx \frac{1}{1+j\omega RC}$$

$$= \frac{f_s C_1}{C_L}$$

→ Bandwidth tuning with

$$= f_s \cdot \left(\frac{C_1}{C_L} \right)$$

clock frequency.
→ Bandwidth $\propto \frac{C_1}{C_L}$

$$\phi \text{ is low: } V_T(nT + T/2) = V_{in}(nT + T/2)$$


$$V_{out}(nT + T/2) = V_{out}(nT)$$

$$q_1(nT + T/2) = C_1 V_T(nT + T/2)$$

$$= C_1 V_{in}(nT + T/2)$$

$$q_2(nT + T/2) = C_L V_{out}(nT + T/2)$$

$$= C_L V_{out}(nT)$$

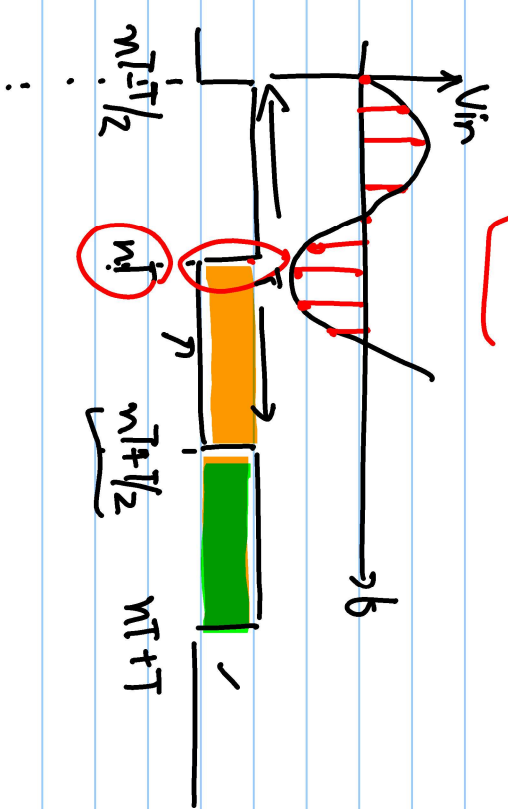

ϕ is high:

$$C_1 V_{in}(nT + T/2) + C_L V_{out}(nT) = (C_1 + C_L) V_{out}(nT + T)$$

$$z \left(V_{out}(nT) \right) = \frac{C_1}{C_1 + C_L} V_{in}(nT + T) + \frac{C_L}{C_1 + C_L} V_{out}(nT)$$

$$z V_{out}(z) = \frac{C_1}{C_1 + C_L} V_{in}(z) + \frac{C_L}{C_1 + C_L} V_{out}(z)$$

$$z = e^{j\omega T}$$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1}{C_1 + C_L} \left(z - \frac{C_L}{C_1 + C_L} \right)$$

$$= \frac{C_1 / (C_1 + C_L)}{\left(1 - \frac{C_L}{C_1 + C_L} \right) + j\omega T}$$




$$V_{in} \xrightarrow{R} \frac{1}{C} V_{out}$$

$$V_{out}(t) =$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + sRC}$$

$$z = e^{j\omega T} \approx 1 + j\omega T \quad (|\omega T| \ll 1)$$
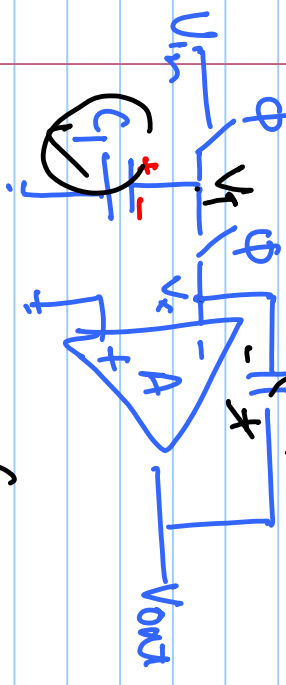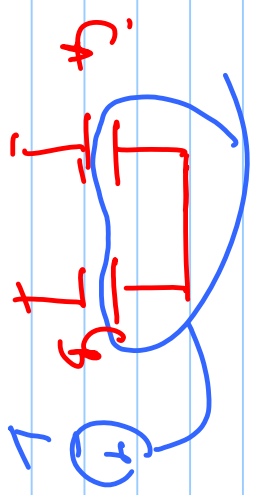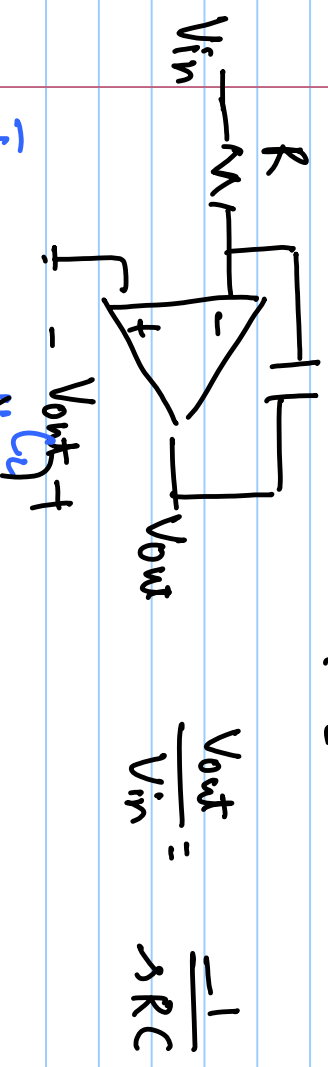
$$= \frac{C_1 / (C_1 + C_L)}{\frac{C_1}{C_1 + C_L} + j\omega T} = \frac{1}{1 + j\omega T \frac{C_L}{C_1}} = \frac{1}{1 + j\omega RC}$$




ϕ is high:

$$\phi \text{ is low: } V_T(nT + T/2) = V_{in}(nT + T/2)$$

$$V_{out}(nT + T/2) = V_{out}(nT)$$

$$C_1 V_{in}(nT + T/2) - C_L V_{out}(nT) = -C_L V_{out}(nT + T)$$
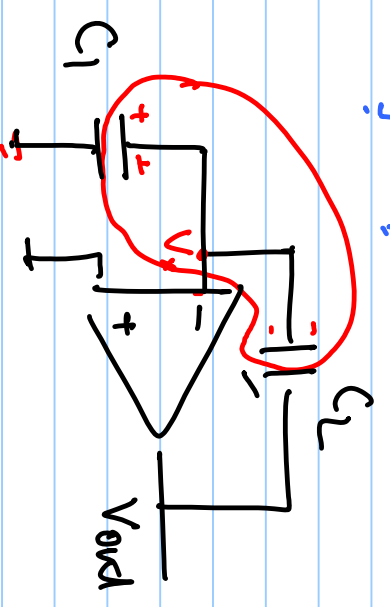
$$V_{out}(nT + T) = V_{out}(nT) - \frac{C_1}{C_L} V_{in}(nT)$$



$$z^{-2} V_{out}(z) - V_{out}(z) = -\frac{C_1}{C_2} V_{in}(z)$$

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{-C_1}{C_2} \frac{1}{z-1} \stackrel{z=e^{j\omega T} \approx 1+j\omega T}{\approx} -\frac{C_1}{C_2} \frac{1}{j\omega T}$$

$$= -\frac{1}{j\omega C_2 (T/C_1)} = \frac{1}{j\omega C_1 R} \quad \checkmark$$

$$R = \frac{T}{C_1}$$