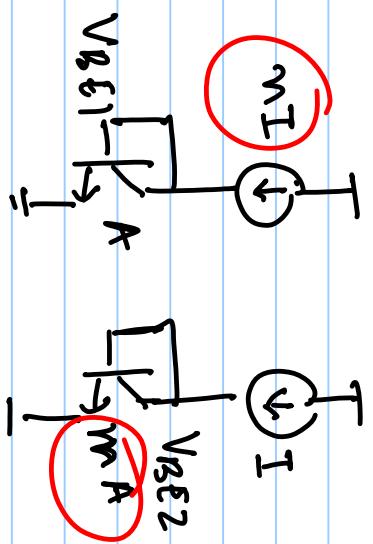


Lecture # 48

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right)$$

$$\frac{dV_{BE}}{dT} = -1.5 \text{ mV/}^{\circ}\text{C}$$



$$\Delta(V_{BE}) = V_T \ln(nm)$$

$$\begin{aligned} V_{RE} &= \alpha_1 \underbrace{V_{BE}} + \alpha_2 \underbrace{(\Delta V_{BE})} \\ &= 1 \cdot V_{BE} + \alpha_2 V_T \ln(\underline{nm}) \end{aligned}$$

$$I$$

$$I$$

$$V_{BE1} = V_{BE2} + I \cdot R$$

$$IR = V_{BE1} - V_{BE2}$$

$$= V_T \ln(n)$$

$$\frac{V_{BE1}}{-} \frac{V_{BE2}}{=} R$$

$$V_{BE1} = V_{BE2} + (V_T \ln(n)) = 0.75 + 0.025 \times 17.2$$


$$V_{REF} = V_{O2} = V_{BE1} =$$

$$\frac{dV_{BE2}}{dT} < 0 \quad \frac{dV_T}{dT} > 0$$


Curve

$$\frac{dV_{BE1}}{dT} = 0 \Rightarrow \ln(n) = 17.2$$

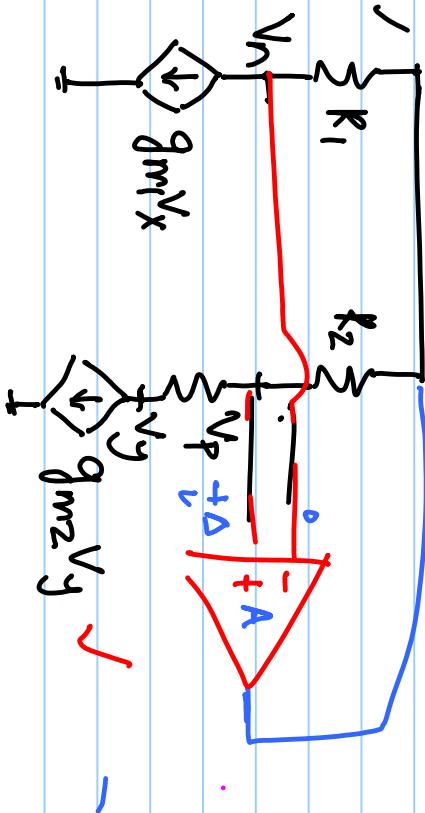
$$-1.5 \text{ mV/K} + 17.2 \times 0.087 = 0$$






$$V_p - V_n = +\Delta \rightarrow$$

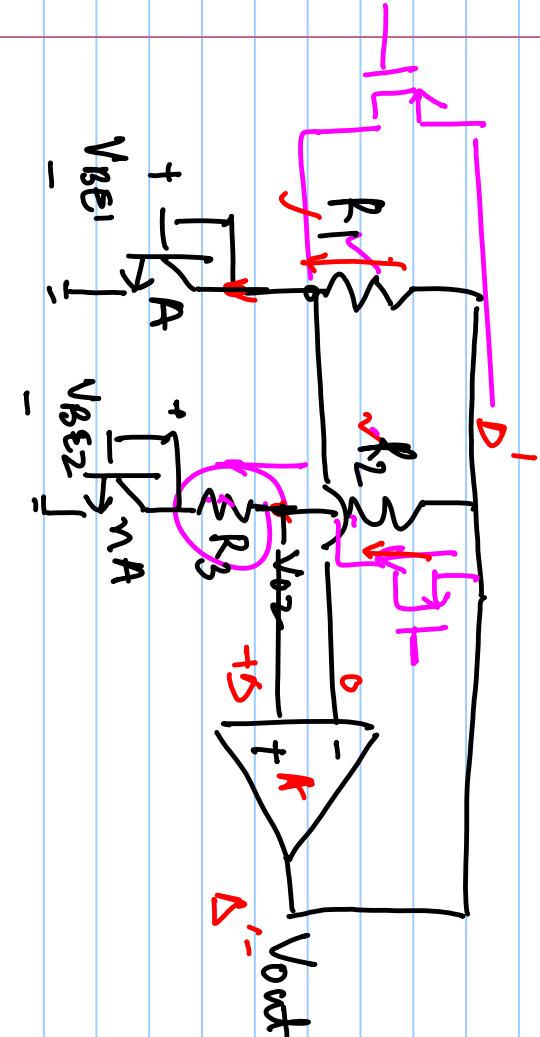
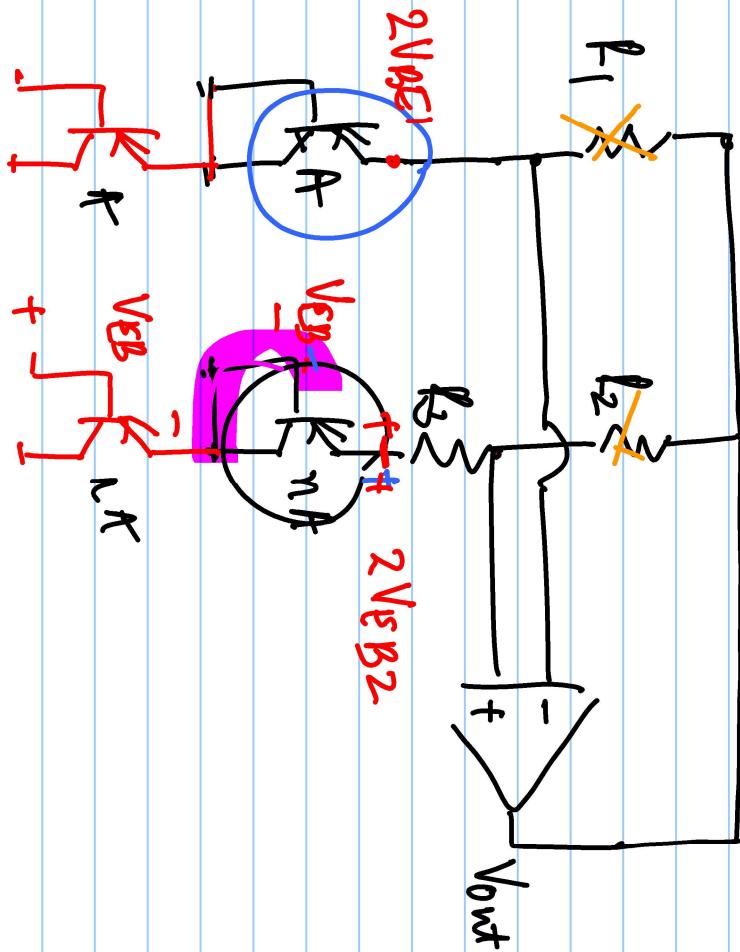
$$\begin{aligned} V_{out} &= V_{BE2} + I (R_2 + R_3) \\ &= V_{BE2} + \frac{V_T \ln(n)}{R_3} (R_2 + R_3) \\ &\approx V_{BE2} + V_T \left(1 + \frac{R_2}{R_3}\right) \ln(n) \end{aligned}$$



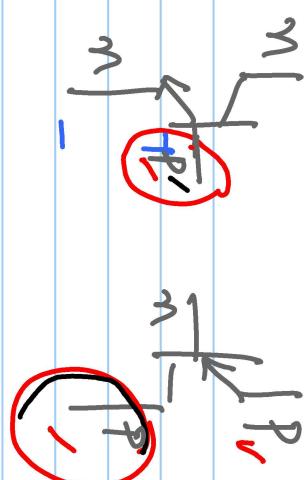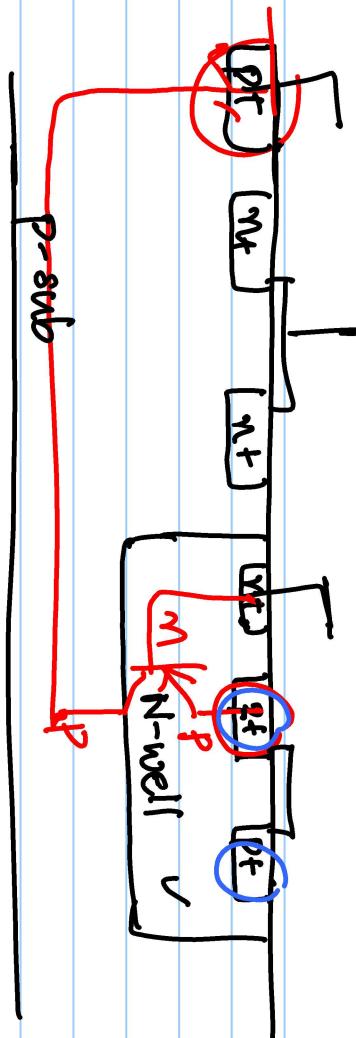
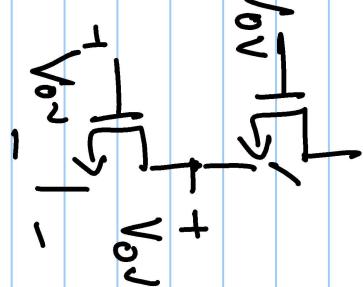
$$2 \times \left[V_{EB} + V_t \ln(n) \left(1 + \frac{R_2}{R_1} \right) \right]$$




$$2V_{ER1} = 2V_{ER2} + I \cdot R_3$$

$$I = \frac{2(V_{EB1} - V_{EB2})}{R_3} = \frac{2V_1 \ln(n)}{R_3}$$
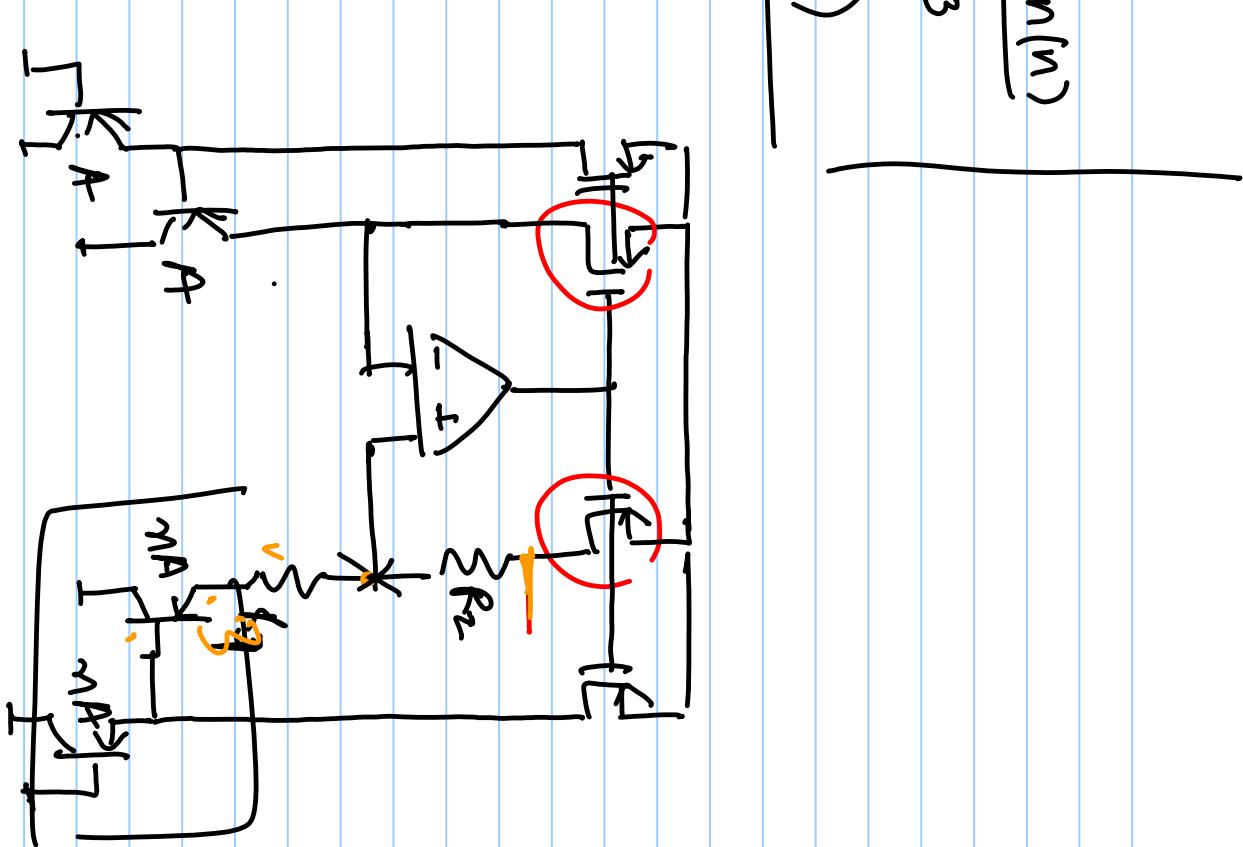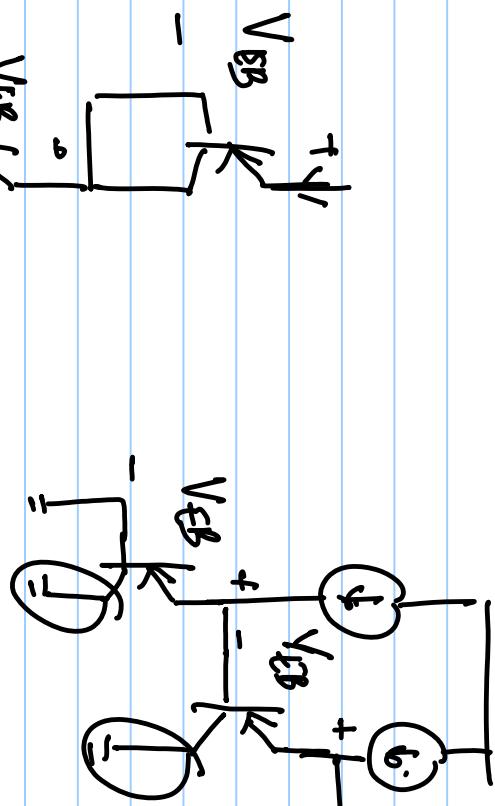
$$V_{ond} = 2 \sqrt{t_B z} + 2 \frac{\sqrt{t_1 \ln(n)}}{R_3} \left(R_2 + R_3 \right)$$



PTAT Current Source

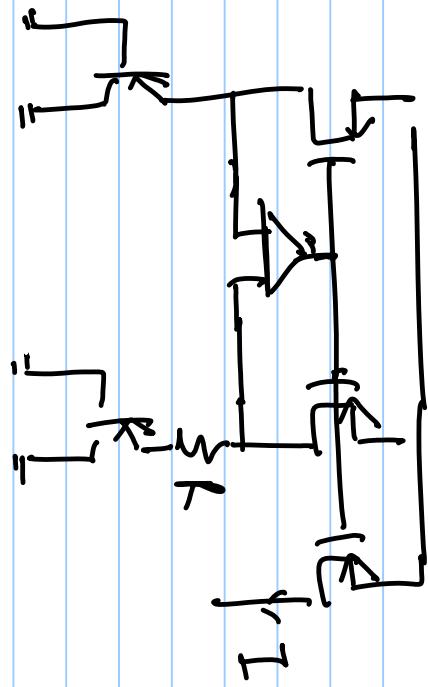

$$\frac{2V_{BE2} + V_T \ln(n)}{R_3} \times (k_3 + k_2)$$