

Lecture 34

Equalization in Serial Links


On Tx Side — FIR (FFE) $\left\{ \begin{array}{l} \text{CML Equalizer} \\ \text{VM Equalizer} \end{array} \right.$

PWM — CML/VM

On Rx Side — FIR (FFE)


Linear Equalization $\left\{ \begin{array}{l} \text{Active} \\ \text{Passive} \end{array} \right.$
DFE (Non-Linear Equalizer)

IIR Equalization

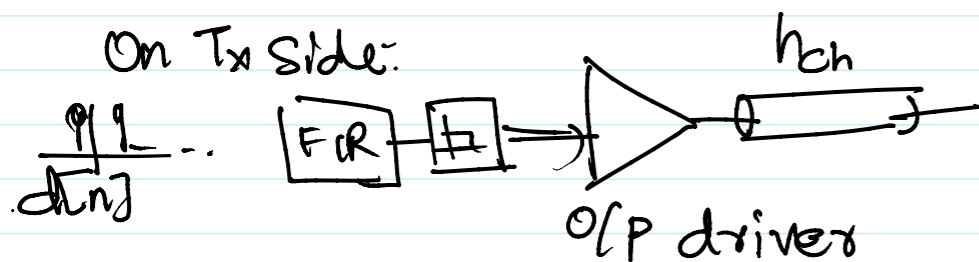

$$H_{eq}(s) = \frac{1}{H_{ch}(s)}$$

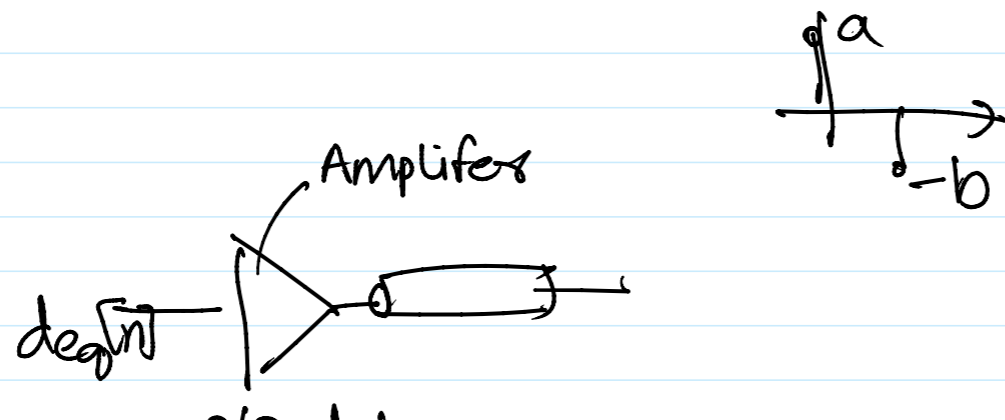
O/P of FIR filter, $d_{eq}[n] = d[n] * h_{eq}[n] = \sum d[k] h[n-k]$




req'd /
O/P drives

Amplifier — Linear gain, wide bandwidth

2)

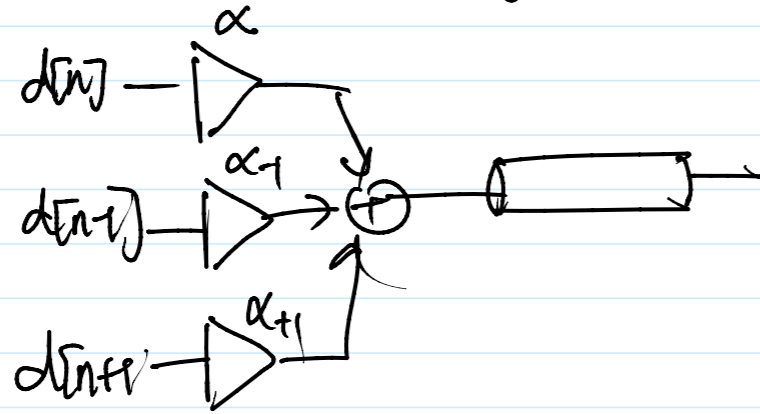

OML o/p driver

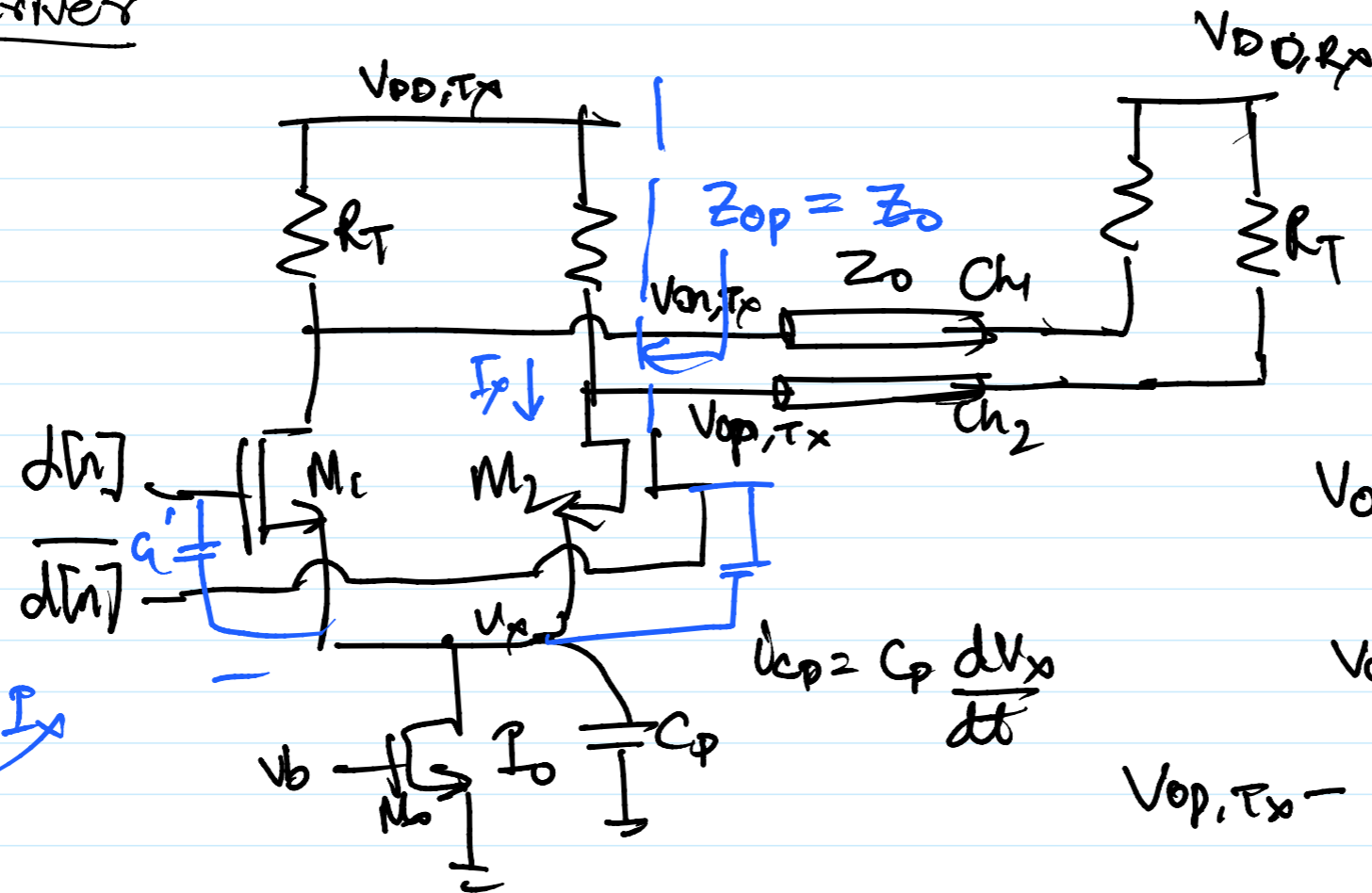

$$V_{DD, TX} = V_{DD, RX} = V_{DD}$$

$$V_{on, TX} = V_{DD, TX} - \frac{I_0}{2} \times \frac{R_T}{2}$$

$$d[n] = 1, \overline{d[n]} = 0$$

$$V_{on, TX} = V_{DD} - \frac{I_0 R_T}{2}$$

$$V_{op, TX} = V_{DD}$$

$$V_{op, TX} - V_{on, RX} = \pm \frac{I_0 R_T}{2}$$

$$V_{out, pk-pk} = I_0 R_T$$

$$I_0 + C_p \frac{dV_{Xo}}{dt} = I_{Xo}$$

$$I_{cp} = C_p \frac{dV_{Xo}}{dt}$$








$$M_1, M_2, \frac{I_0}{2}, V_{cm} - V_X - V_T = V_{OV}$$

$$\overline{d[n]} = 0 \Rightarrow M_2 \rightarrow \text{cut off}$$

Large $C_p \rightarrow$ data dependent V_X

$d[n] = 0 \Rightarrow M_2 \rightarrow \text{cut off}$
 $d[n] = 1 \Rightarrow M_1$

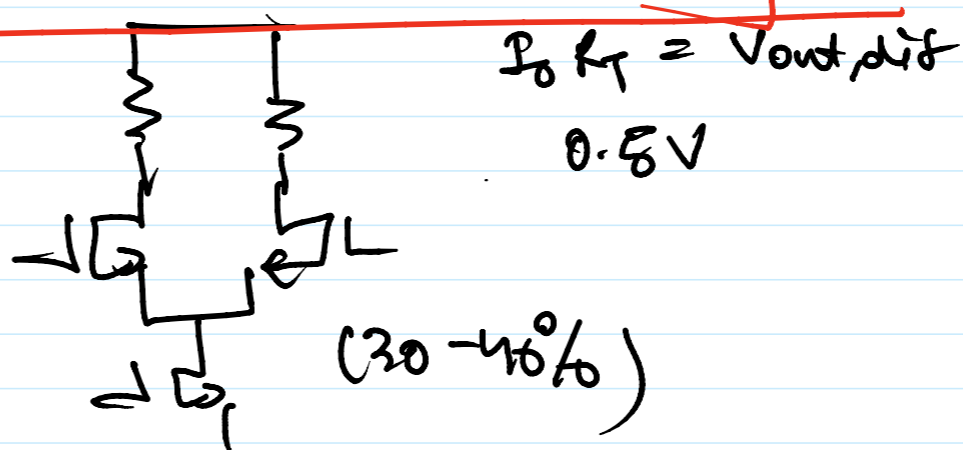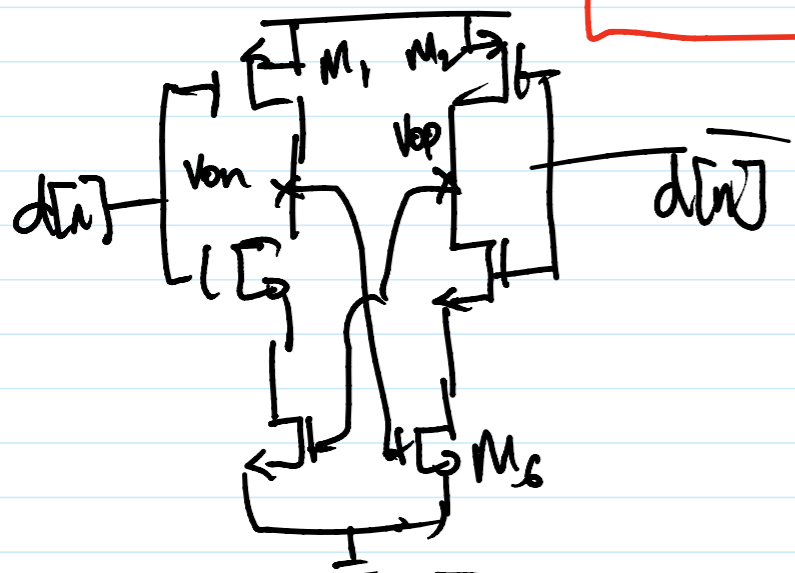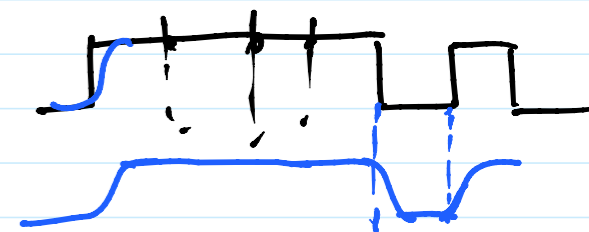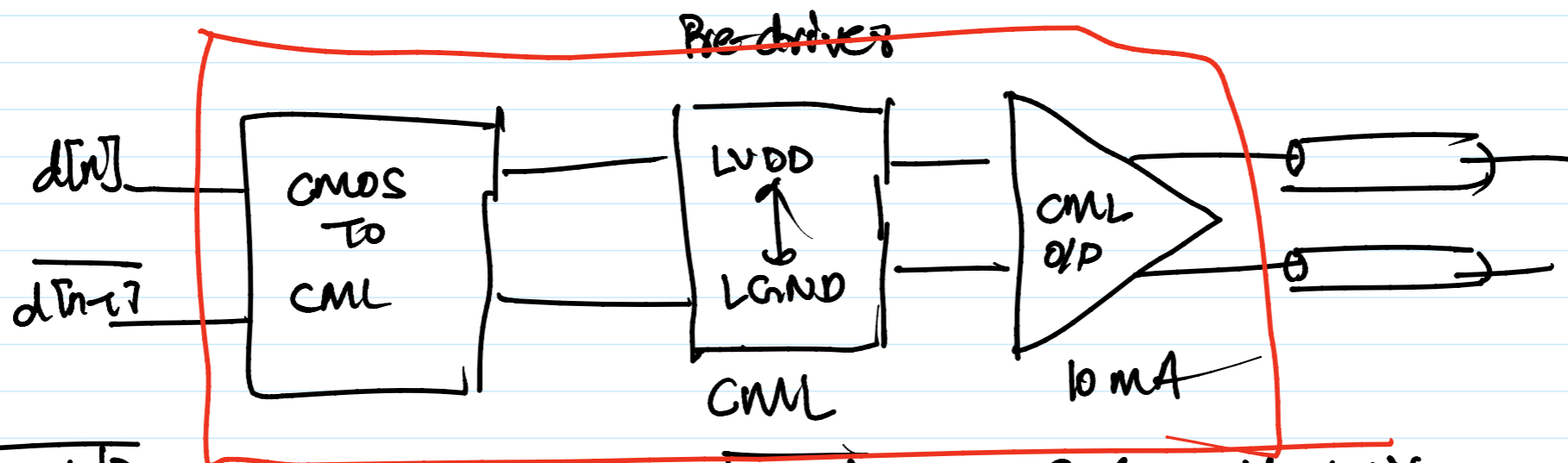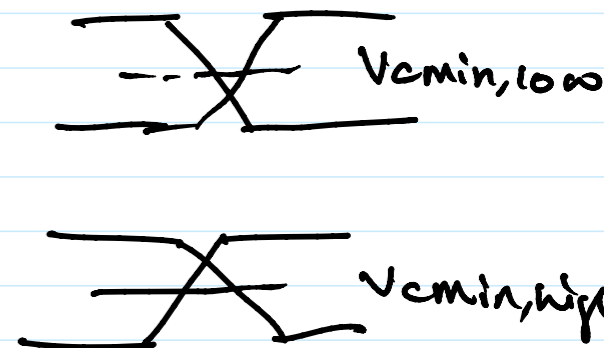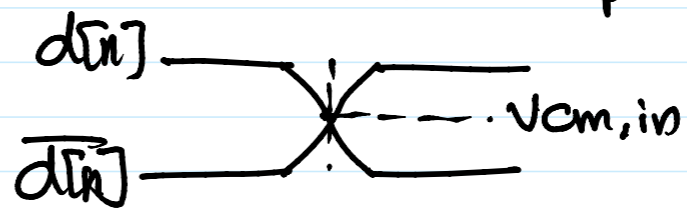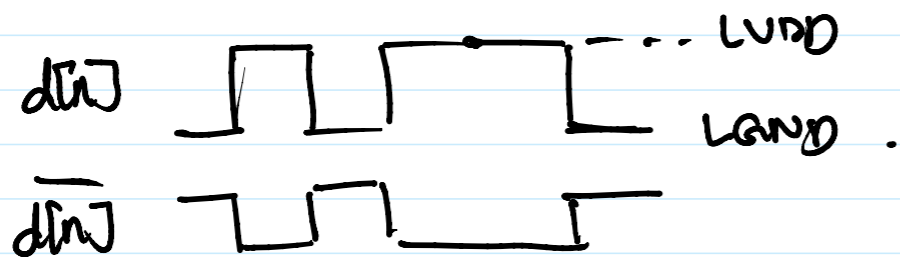Large $C_p \rightarrow$ data dependent V_{cm}
 Small $C_p \rightarrow$ smaller length M_0



$\frac{I_0}{2} \rightarrow I$
 V_{ov}

$d[n] = 1, \overline{d[n]} = 0,$
 $\overline{d[n]} = 0$

$V_{on} = 0, V_{op} = 1$

