
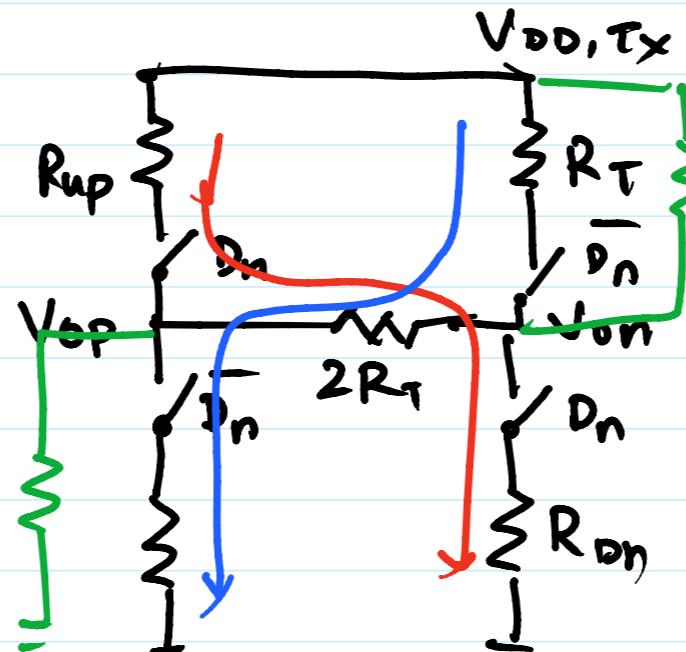


Lecture - 36


High Swing VM o/p driver

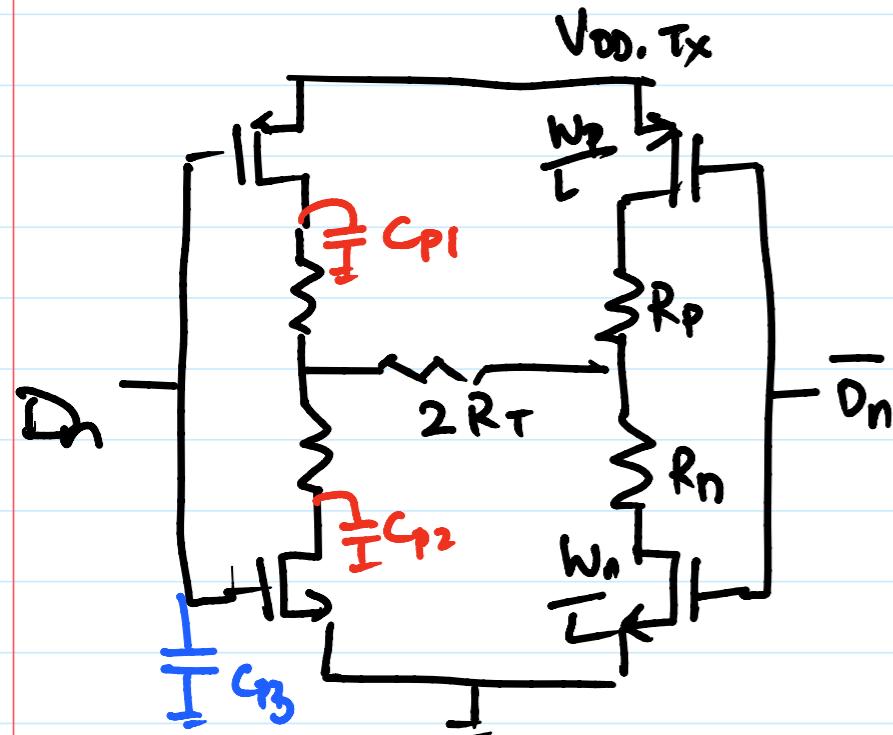

$$V_{op} - V_{on} = \pm \frac{V_{DD,Tx}}{2}$$

$$\begin{aligned} R_T &= R_{PMOS} + R_P \\ &= R_{NMOS} + R_P \end{aligned}$$

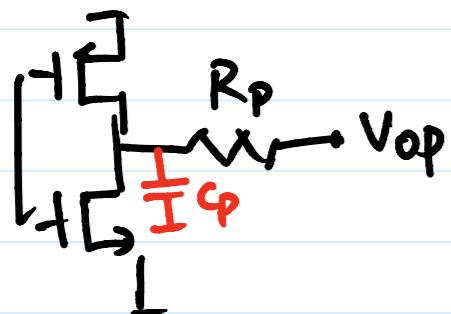$R_P \gg R_{MOS}$ Process variation negligible
Parasitic cap large



$$R_{PMOS} + R_P = R_{NMOS} + R_{P2} = R_T \quad (\text{Typ. } 27^\circ\text{C, 1V})$$

$\downarrow \pm 20\%$ $\downarrow \pm 10\%$

To compensate PVT variation

Vary size

Vary Vctrl (fixed VDD, Cload)



$$R_T = \frac{(R_{MOS} + R_{POLY})}{N}$$

(Typical)

'ss', 'tt', 'ff', 'ff', 'ff'

$$= \frac{(R_{\text{mos}0} + R_{\text{poly}0})}{M (> N)}$$

(ss)

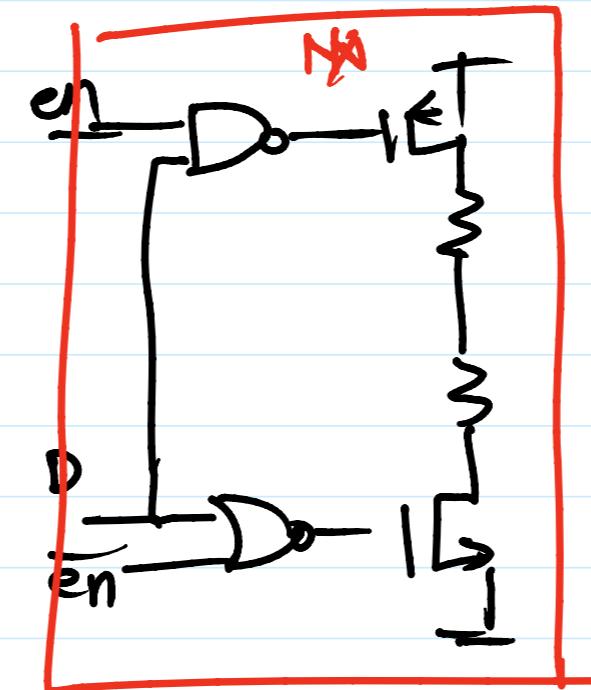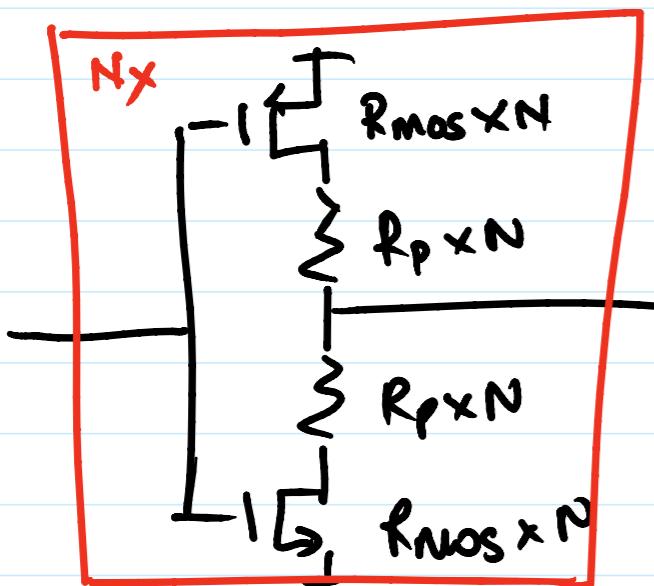


PMOS	NMOS
slow	fast
Higher V_t	Lower V_f

$en = 1$

en	0	PMOS	NMOS
0	0	OFF	ON
0	1	off	OFF
1	0	off	ON
1	1		

$N = 1000$



Higher r_{reso}

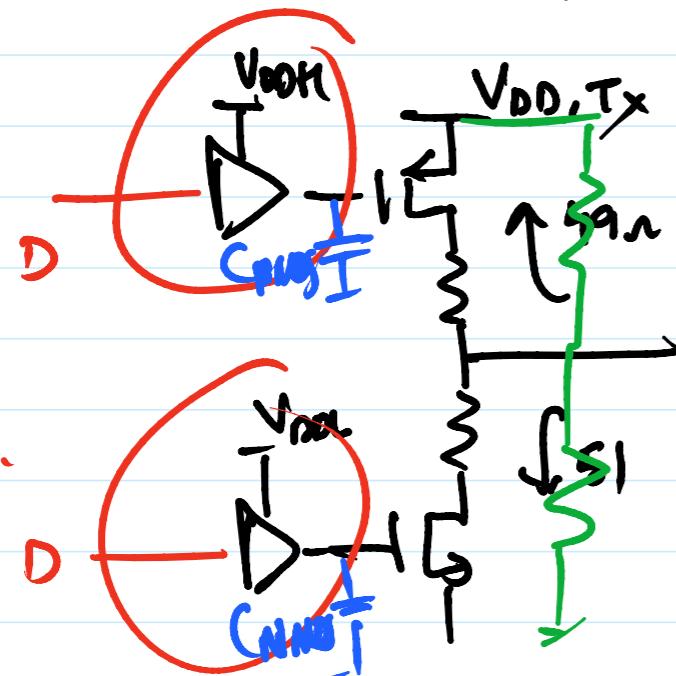


Vary $V_{DD,TX}$, $V_{VDD,TX}$ for $R_T = 50$

$P_{\text{cell}} = 64$

$N_{\text{cell}} = 32$

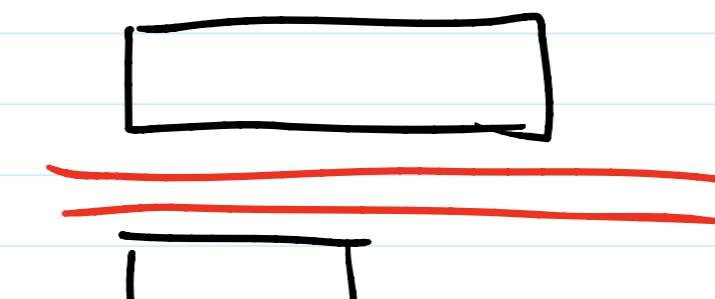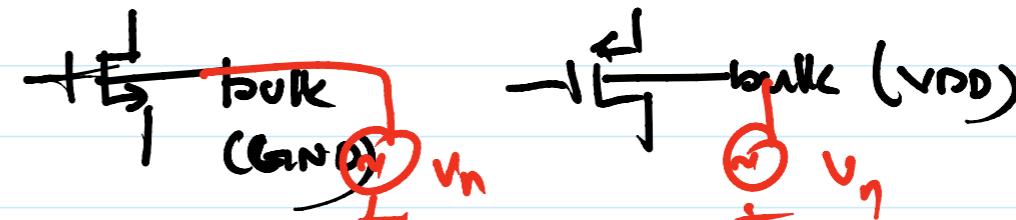


Ncell = 32

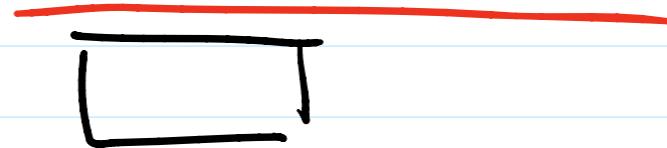

$$V_{out, min} = \frac{1}{2} (\max(|V_{Th,p}|, V_{Th,n}))$$

PMOS gets cut off $\Rightarrow V_{DD,Tx} = |V_{Th,p}|$

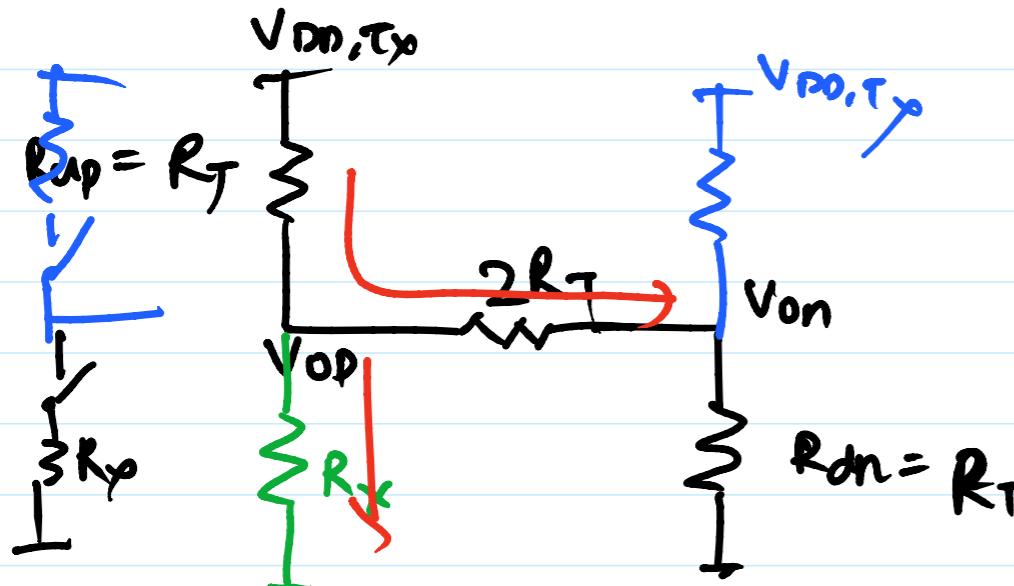NMOS "", "" $\Rightarrow V_{DD,Tx} = V_{Th,n}$





$$V_{op} = \frac{3}{4} V_{DD,Tx}$$

$$V_{on} = \frac{1}{4} V_{DD,Tx}$$

$$(V_{op} - V_{on}) \downarrow$$

$$R_{up} \parallel R_x = R_T$$

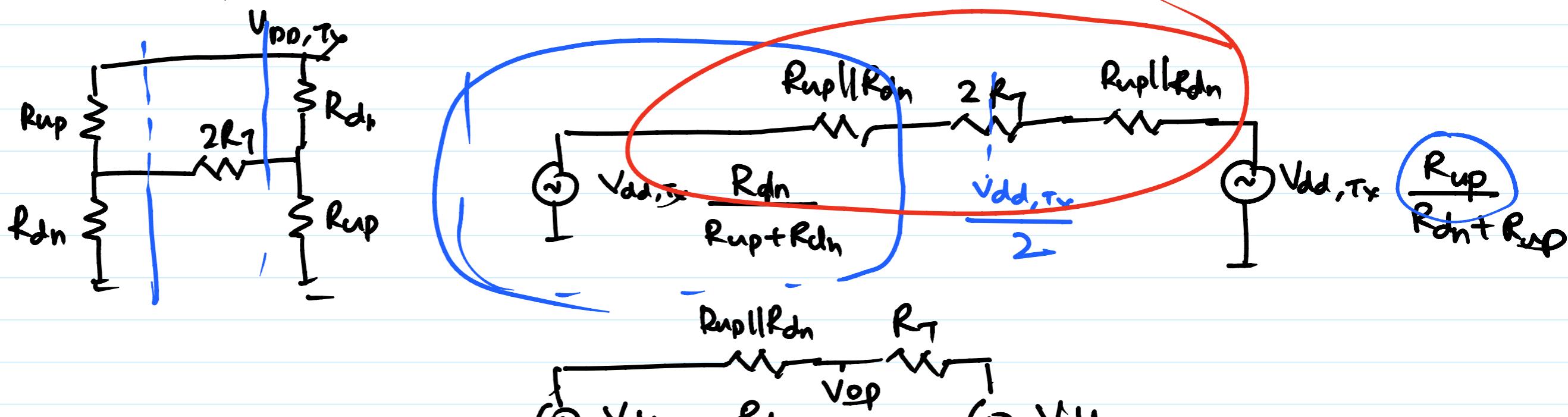

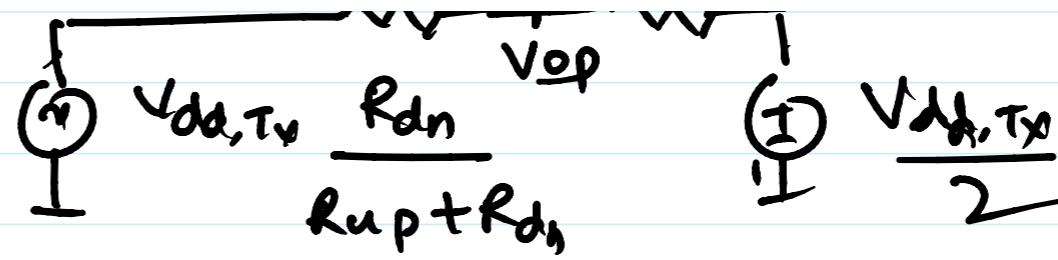

$$V_{op} = \frac{R_T}{R_T + R_{up} \parallel R_{dn}} \underbrace{\frac{V_{dd,Tx}}{R_{dn}}}_{R_{up} + R_{dn}} + \underbrace{\frac{R_{up} \parallel R_{dn}}{R_T + R_{up} \parallel R_{dn}} \frac{V_{dd,Tx}}{2}}$$

$$V_{cm} = \frac{R_T + (R_{up} \parallel R_{dn})}{2(R_T + R_{up} \parallel R_{dn})} \times \frac{R_{dn}}{(R_{dn} + R_{up})} V_{dd,Tx}$$

$$+ \frac{R_T + (R_{up} \parallel R_{dn})}{2(R_T + (R_{up} \parallel R_{dn}))} \times \frac{R_{up}}{R_{dn} + R_{up}} V_{DD,Tx}$$

$$R_{up} \parallel R_{dn} = R_T \quad \text{Channel term}$$

$$V_{op} = \frac{R_T \cdot R_{dn}}{R_T (R_{up} + R_{dn})} \frac{V_{DD,Tx}}{2} + \frac{R_T}{2R_T} \frac{V_{dd,Tx}}{2}$$

$$= \frac{R_{dn}}{R_{up} + R_{dn}} \frac{V_{DD,Tx}}{2} + \frac{V_{DD,Tx}}{4}$$

$$V_{on} = \frac{R_{up}}{R_{up} + R_{dn}} \frac{V_{dd,Tx}}{2} + \frac{V_{dd,Tx}}{4}$$

$$\begin{aligned} V_{op} - V_{on} &= \left[\frac{R_{dn} - R_{up}}{R_{up} + R_{dn}} \right] \frac{V_{dd,Tx}}{2} = \frac{\frac{R_{up} \cdot R_{dn}}{R_{up} + R_{dn}}}{\frac{R_{up} \cdot R_{dn}}{R_{up} + R_{dn}}} \left[\frac{1}{R_{up}} - \frac{1}{R_{dn}} \right] \frac{V_{dd,Tx}}{2} \\ &= \frac{V_{dd,Tx}}{2} \cdot R_T \left[\frac{1}{R_{up}} - \frac{1}{R_{dn}} \right] \end{aligned}$$

$$R_{dn} \rightarrow \infty, R_{up} = R_T \Rightarrow V_{op} - V_{on} = \frac{V_{dd,Tx}}{2}$$