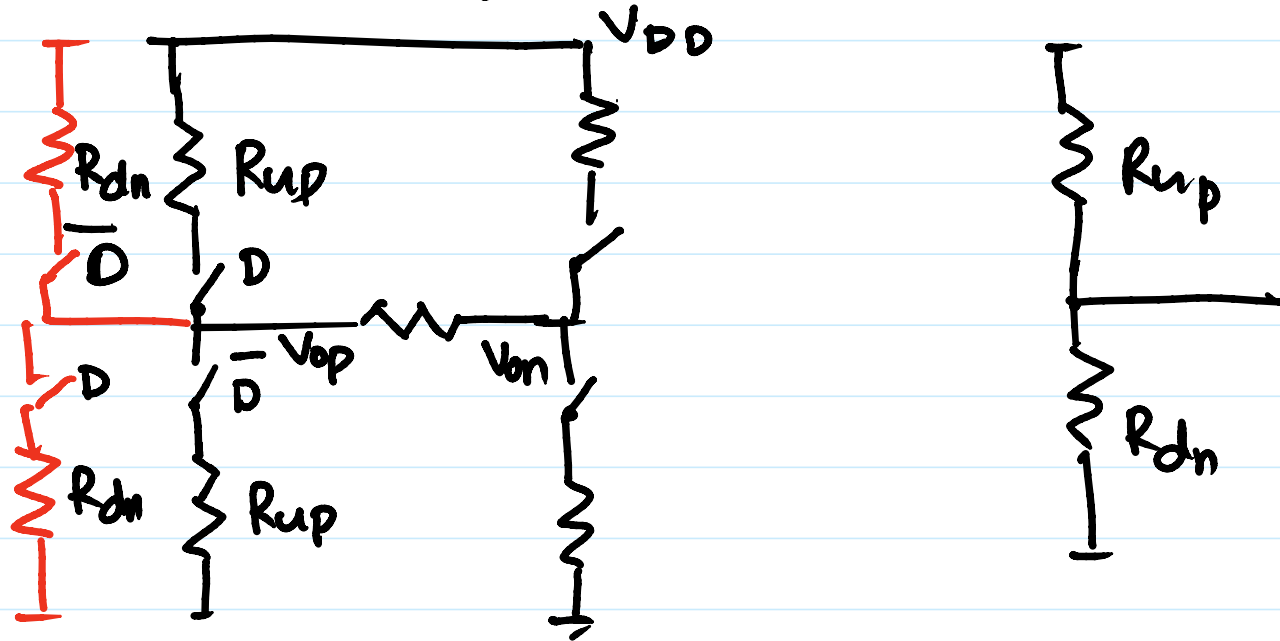


# Lecture 37

High swing VM o/p driver



$$V_{out} = V_{op} - V_{on} = \frac{V_{DD}}{2} R_T \left[ \frac{1}{R_u} - \frac{1}{R_d} \right]$$


$$\frac{1}{R_u} + \frac{1}{R_d} = \frac{1}{R_T} \quad (\text{Chan. term.})$$

$$\frac{1}{R_u} - \frac{1}{R_d} = \frac{V_{out}}{V_{DD}/2} \frac{1}{R_T}$$

$$\frac{1}{R_u} = \frac{1}{2R_T} \left[ 1 + \frac{V_{out}}{V_{DD}/2} \right]$$

$$\frac{1}{R_d} = \frac{1}{2R_T} \left[ 1 - \frac{V_{out}}{V_{DD}/2} \right]$$
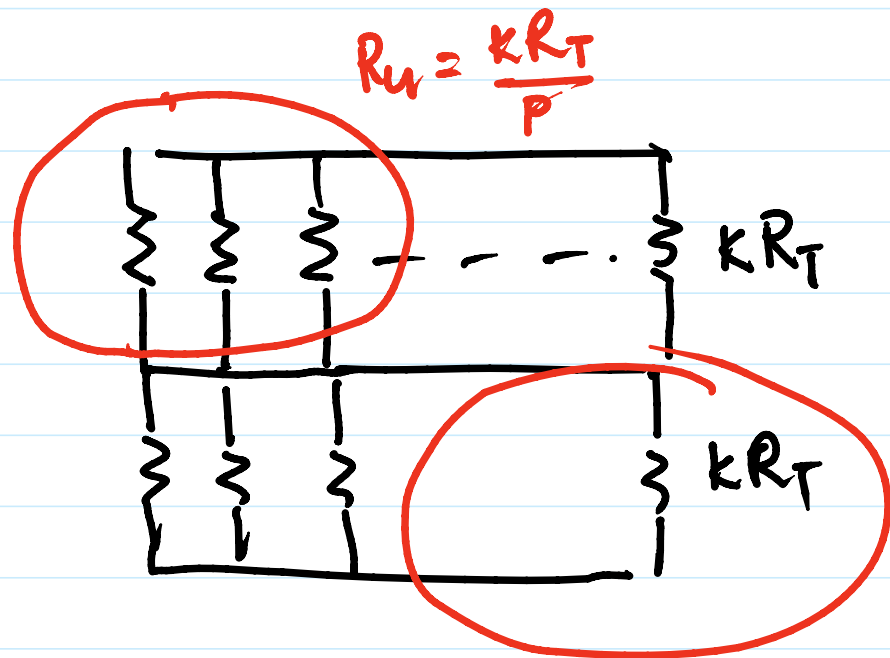
$$G_m = \frac{1}{R_u} = \frac{G_T}{2} \left[ 1 + \frac{V_{out}}{V_{DD}/2} \right]$$





$$R_u = \frac{kR_T}{p}$$

$$R_d = \frac{kR_T}{(k-p)}$$


$$I = \frac{V_{DD} - V_{op}}{p} + \frac{V_{DD} - V_{on}}{p_1} = \frac{V_{DD} - \left( \frac{V_{DD}}{2} + \frac{V_{out}}{2} \right)}{p} + \frac{V_{DD} - \left( \frac{V_{DD}}{2} - \frac{V_{out}}{2} \right)}{p_1}$$

$$\begin{aligned}
 I &= \frac{V_{DD} - V_{op}}{R_u} + \frac{V_{DD} - V_{on}}{R_d} = \frac{V_{DD} - \left(\frac{1}{2} \cdot \frac{V_{DD}}{2}\right)}{R_u} + \frac{V_{DD} - \left(\frac{1}{2} \cdot \frac{V_{DD}}{2}\right)}{R_d} \\
 &= \frac{V_{DD}}{2} \left( \frac{1}{R_u} + \frac{1}{R_d} \right) - \frac{V_{out}}{2} \left( \frac{1}{R_u} - \frac{1}{R_d} \right) \\
 &= \frac{V_{DD}}{2R_T} - \frac{V_{out}}{2} \frac{V_{out}}{V_{DD}/2 \cdot R_T} \\
 &= \frac{V_{DD}}{2R_T} \left[ 1 - 2 \left( \frac{V_{out}}{V_{DD}} \right)^2 \right]
 \end{aligned}$$

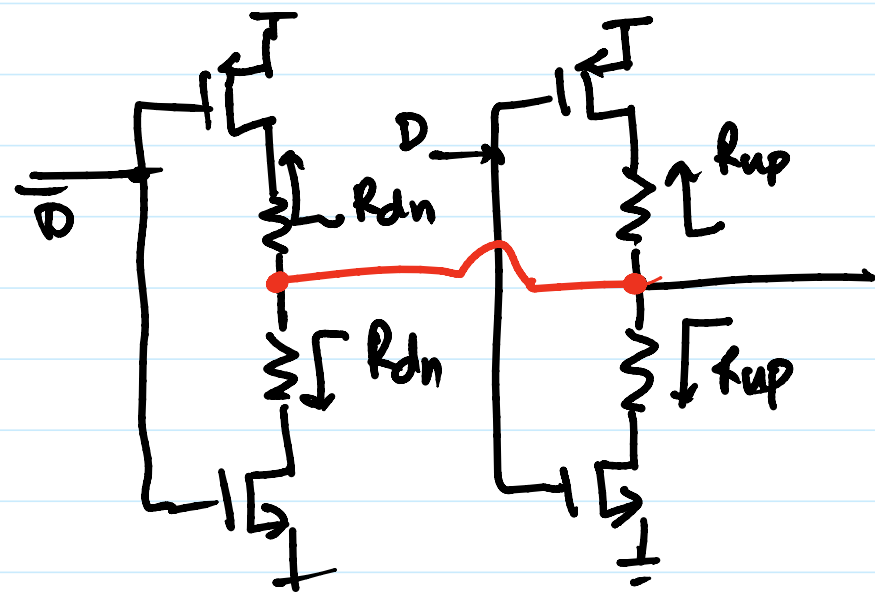
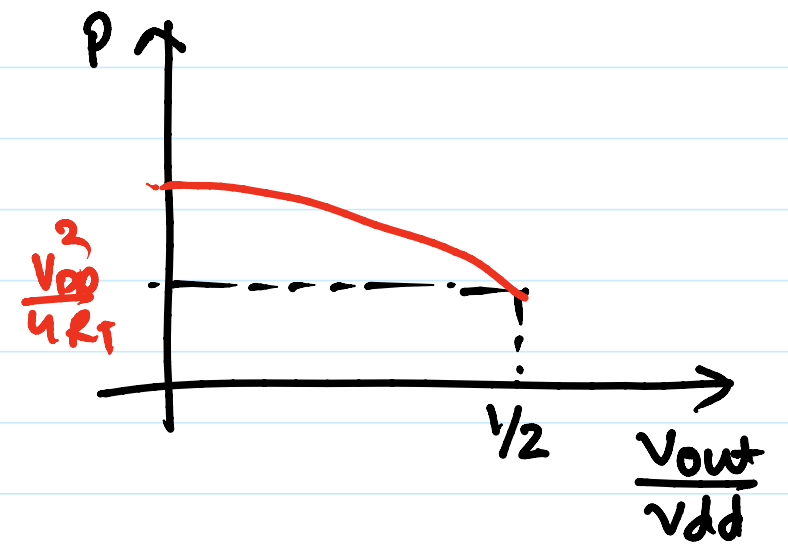
$$\begin{aligned}
 P &= V_{DD} I = \frac{V_{DD}^2}{2R_T} \left[ 1 - 2 \left( \frac{V_{out}}{V_{DD}} \right)^2 \right] \\
 \text{max swing, } & V_{out} = \frac{V_{DD}}{2} \Rightarrow P = \frac{V_{DD}^2}{4R_T} \\
 \text{min swing} & V_{out} = 0 \Rightarrow P = \frac{V_{DD}^2}{2R_T}
 \end{aligned}$$



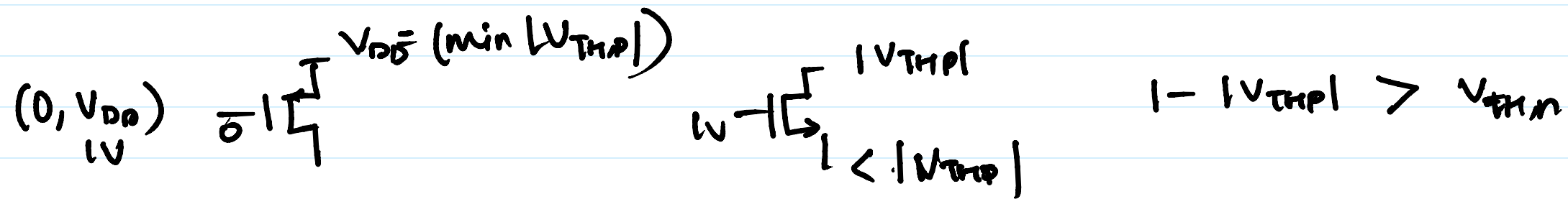
Drawback: Resistive divider more power consumption



Low swing o/p driver (Nover-N)

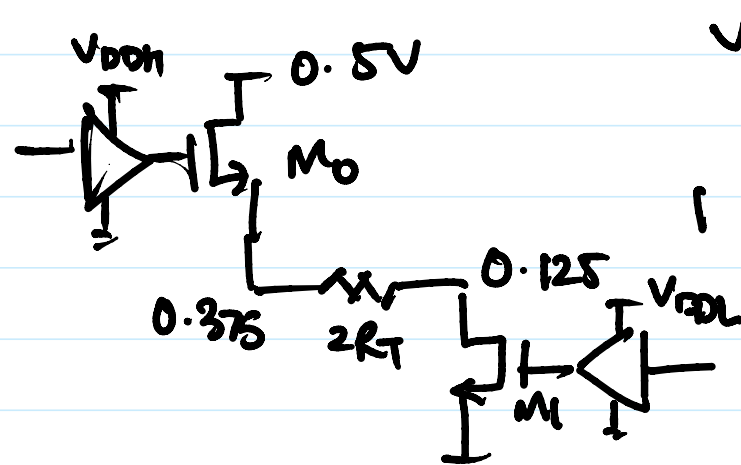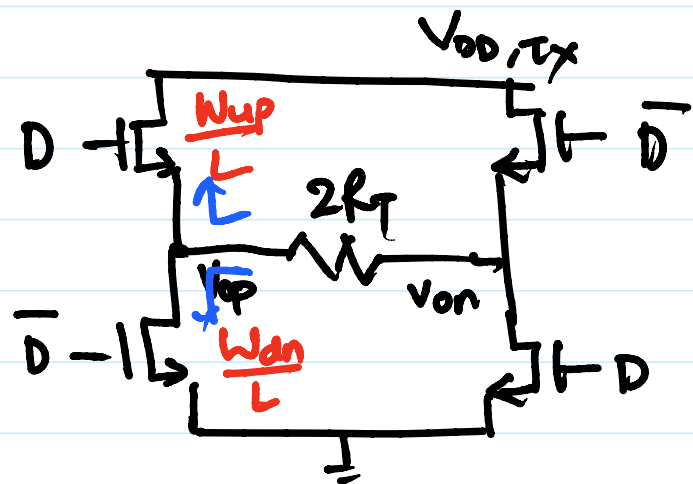

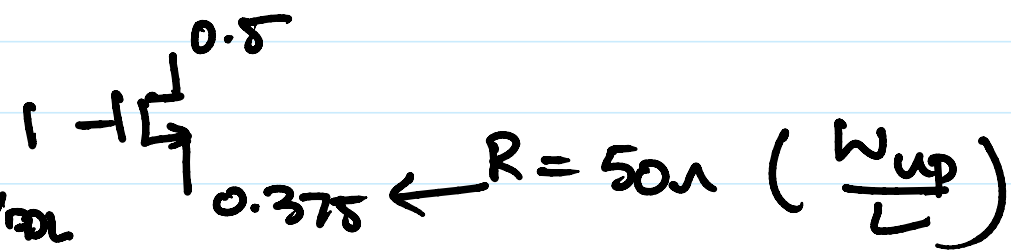$V_{DS} = 0.125, v_o = 0.5V, v_g = 0.375V$



$0.5 \rightarrow 0.4V$

$R_T = 50\Omega, V_{DDH}, \frac{W_{up}}{L}$


\* Different control voltage for  $M_0, M_1$  s.t.  $R_{up} = R_{dn} = 50\Omega$

\* Same control voltage,

$M_0 = \frac{W_{up}}{L}$

$W_{up} > W_{dn}$

$M_1 = \frac{W_{dn}}{L}$

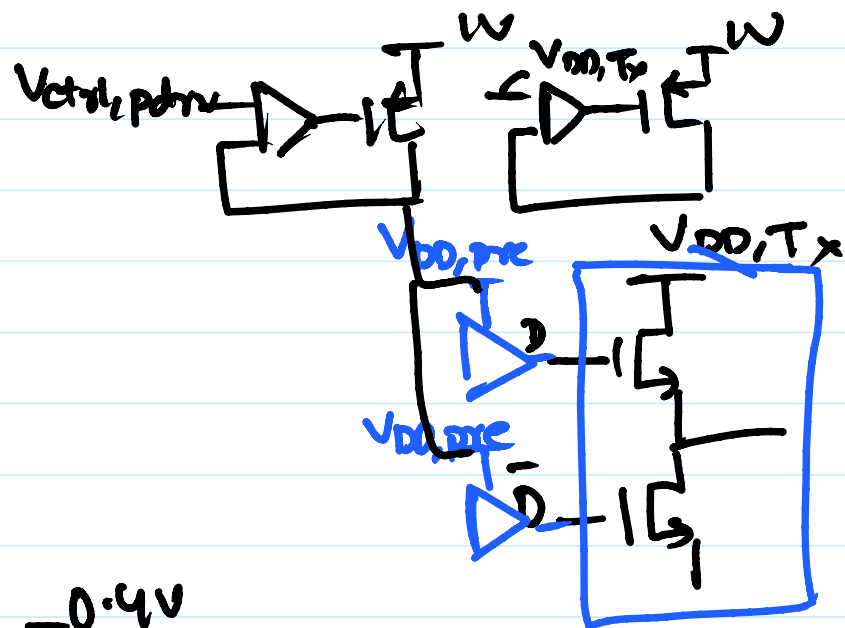


Output swing  $= \frac{V_{DD,Tx}}{2}$


vary o/p swing

$T_{0.5V}$

$T_{0.4V}$


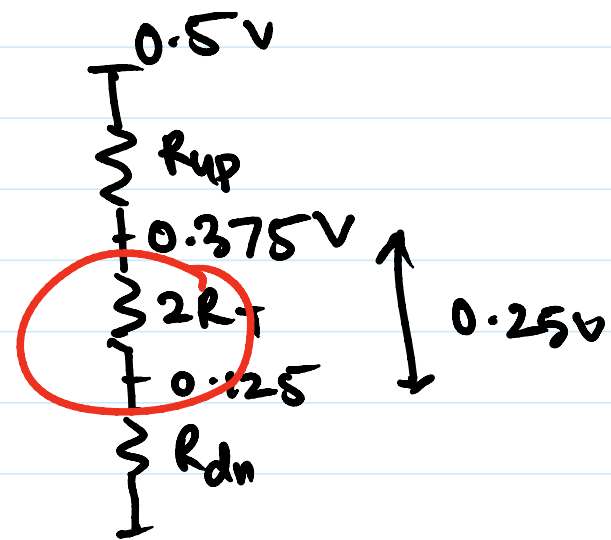


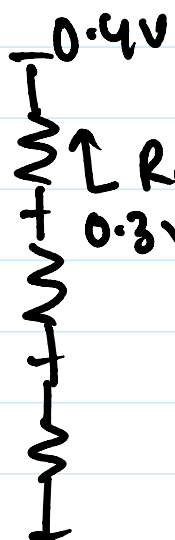$V_{ctrl} = 1V$   
 $V_{gs} = 0.625V$   
 $I = 2.5mA$



$I = 2mA$   
 $V_{gs} = 0.625V$   
 $V_g = 0.925V$

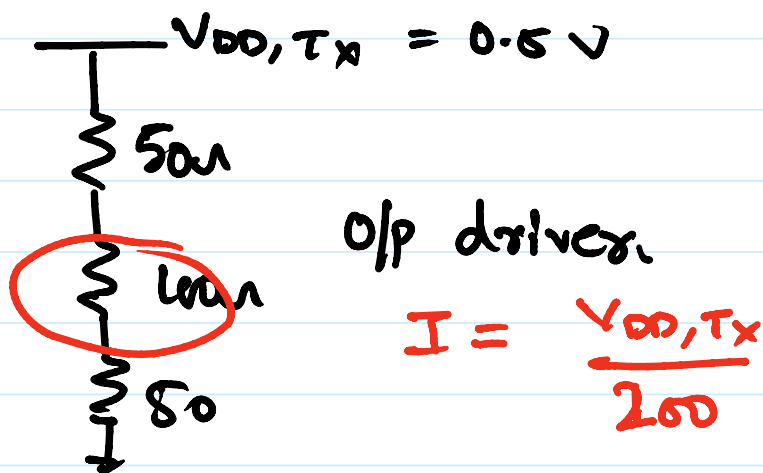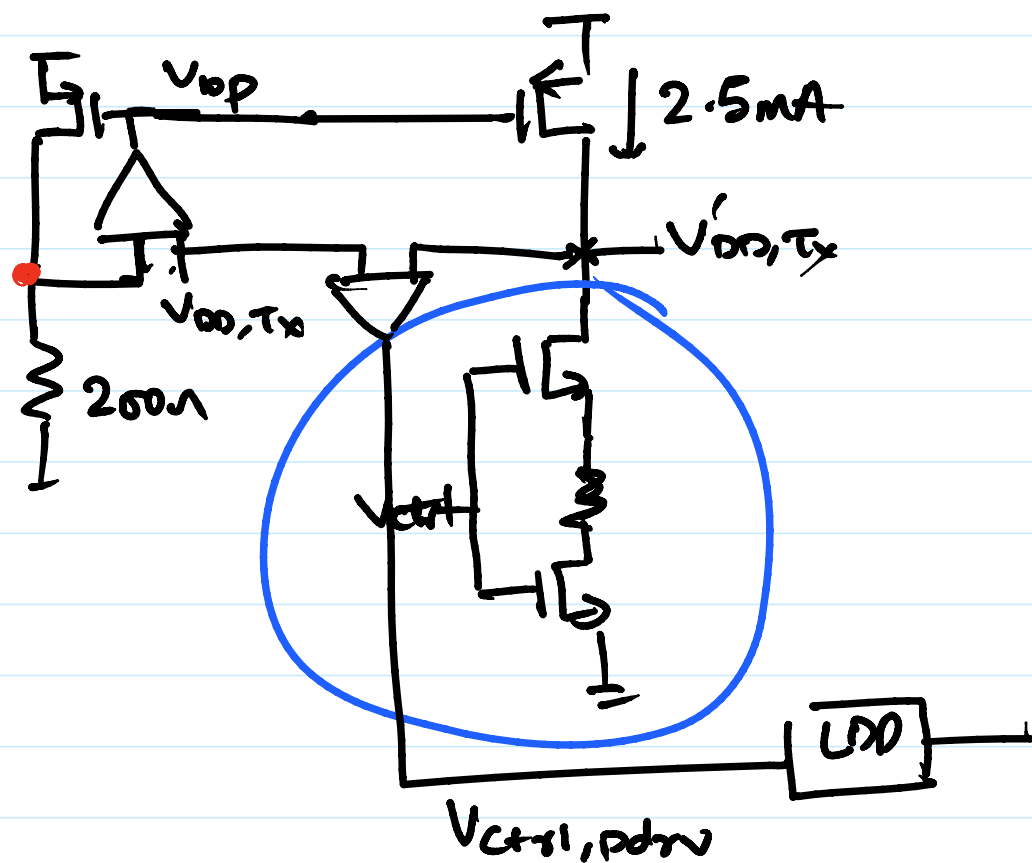$R_{up} \neq 50\Omega$ , if  $R_{up} = 50\Omega \Rightarrow V_{out} = \pm 0.2V$



Power ( $\pm 0.25V$  from high-swing o/p driver) =  $\frac{V_{DD}^2}{2R_T} \left[ 1 - 2 \left( \frac{V_{out}}{V_{DD}} \right)^2 \right]$   
 $= \frac{V_{DD}^2}{2} [1 - 2 \times 1] = \frac{V_{DD}^2}{2}$

$$\begin{aligned}
 &= \frac{V_{DD}^2}{2R_T} \left[ 1 - 2 \times \frac{1}{16} \right] = \frac{7}{8} \frac{V_{DD}^2}{2R_T} = \frac{7}{16} \frac{V_{DD}^2}{R_T} \\
 \text{Power } (\pm 0.25V \text{ from N-over-N}) &= \frac{0.5}{4R_T} \times V_{DD} = \frac{V_{DD}}{4R_T} = \frac{V_{DD}}{8R_T} = \frac{1}{8R_T} = \frac{2}{16R_T}
 \end{aligned}$$