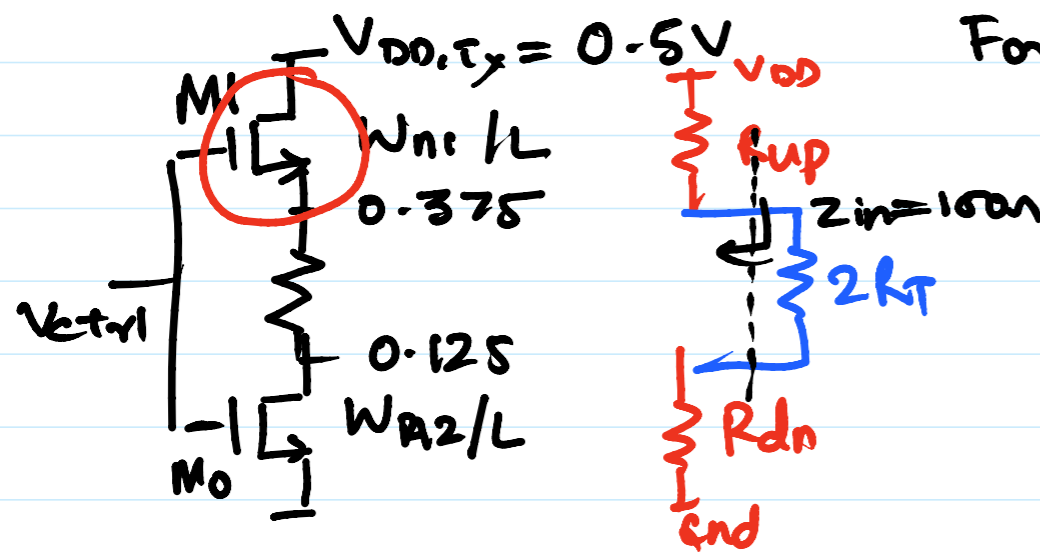


Lecture 38



For M1,  $R_{up} = \frac{1}{k \left( \frac{W_{n1}}{L} \right) (V_{ctrl} - 0.375 - V_T)}$

For M0,  $R_{dn} = \frac{1}{k \left( \frac{W_{p2}}{L} \right) (V_{ctrl} - 0 - V_T)}$

$R_{up} = R_{dn} = 50 \Omega$



Same  $V_{ctrl}$  for M0, M1  $\Rightarrow$  Differential o/p impedance of 100  $\Omega$



Equalization in VM o/p driver

$heq[n] = 0.8 s[n] - 0.2 s[n-1]$

o/p of Tx =  $d[n] * heq[n] = 0.8 d[n] - 0.2 d[n-1] = y[n]$




$d[n]$	$d[n-1]$	$y[n]$
1	1	0.6
1	-1	1.0
-1	-1	-1.0
-1	1	-0.6

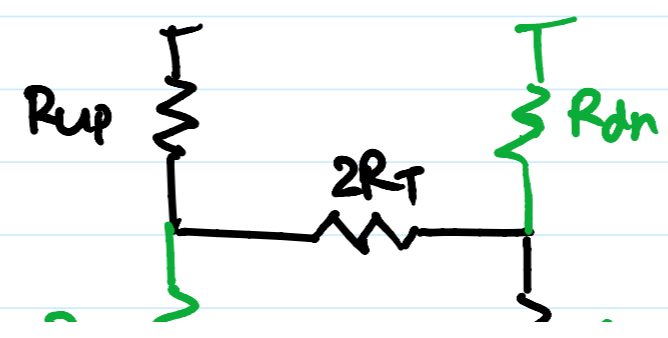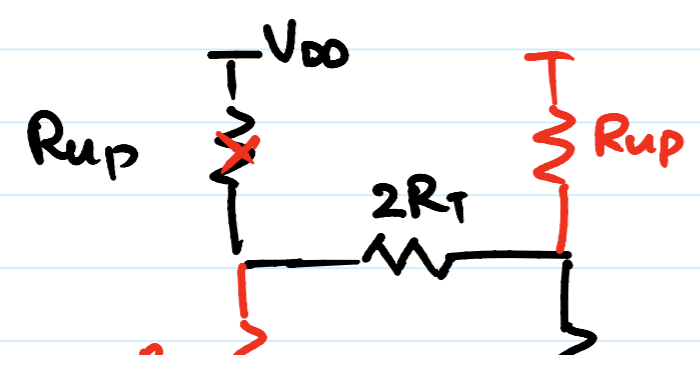

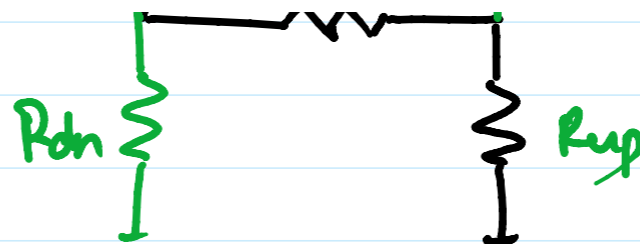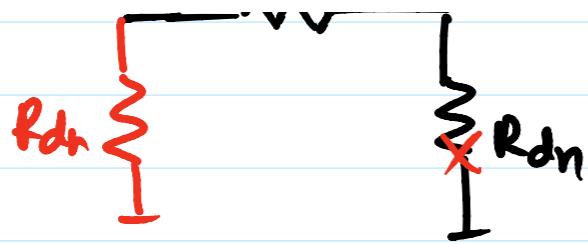

$$R_{up} = R_{dn} = r_T$$


$$V_{out} = \pm \frac{V_{dd}}{2}$$

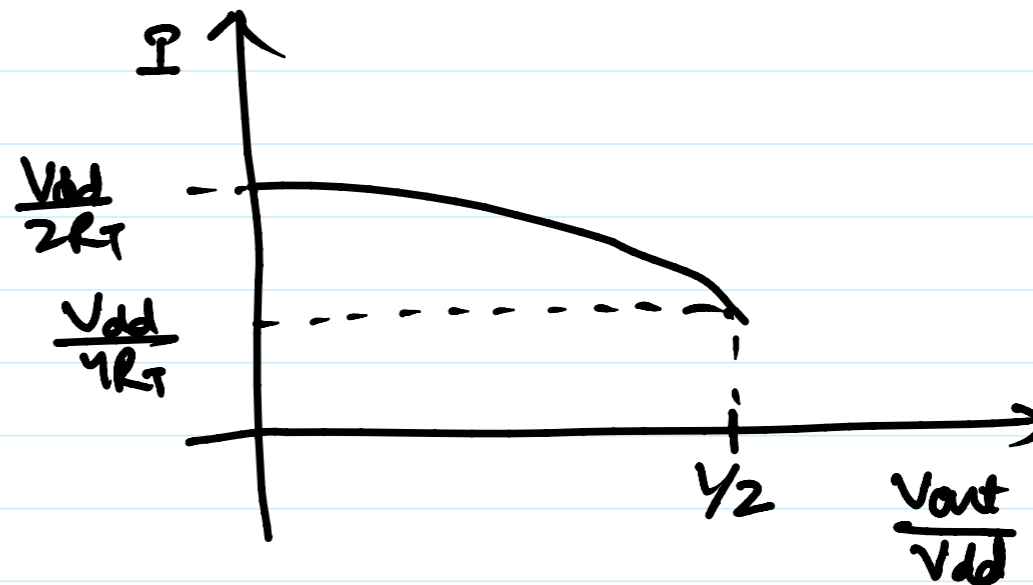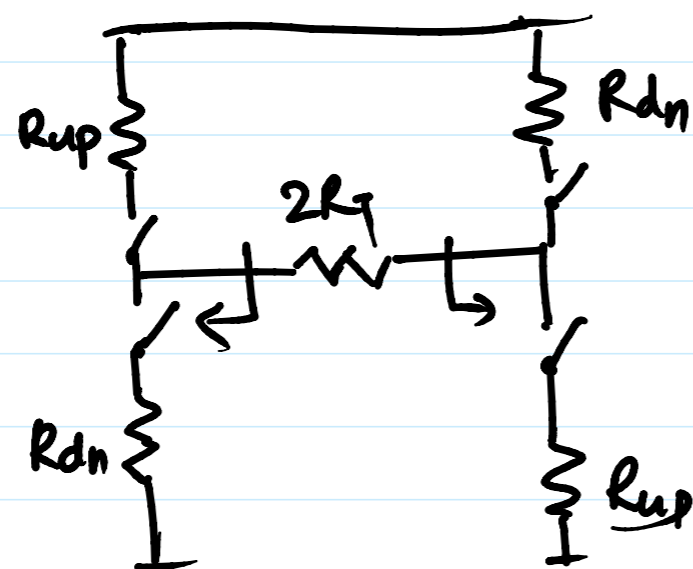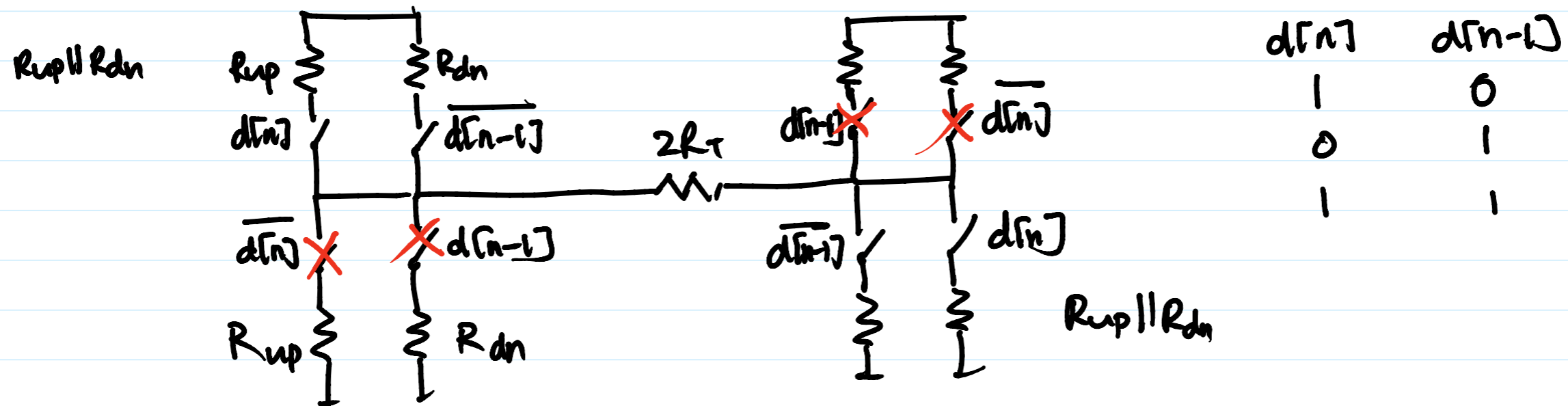

- \* More current in VM o/p driver w/ equalization
- \* Switching current

→ Switching current


Uniformly Segmented VM of driver

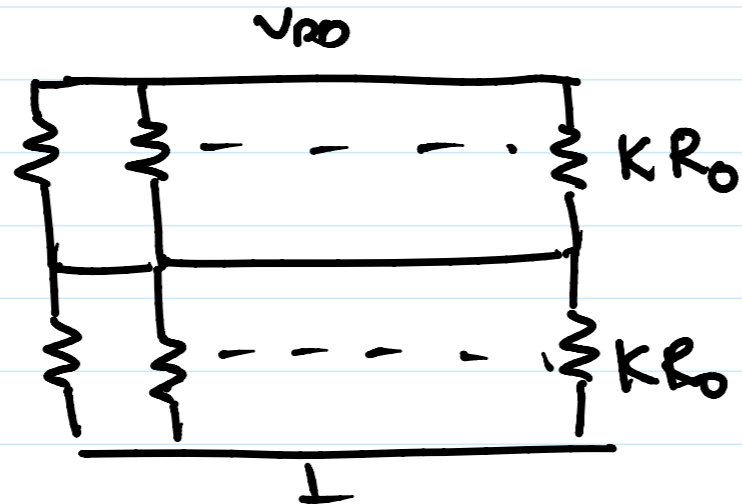

Depending on PVT variations, choose N seg.

$$\frac{KR_0}{N} = R_T$$

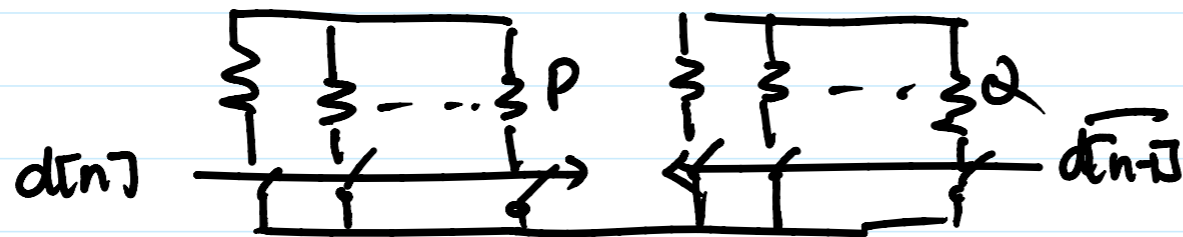
$\left\{ \begin{array}{l} P \text{ (Main cursor)} \\ Q \text{ (Post cursor)} \end{array} \right.$



For ex.  $N = 16 = P + Q$

min.  $Q = 1, P = 15$

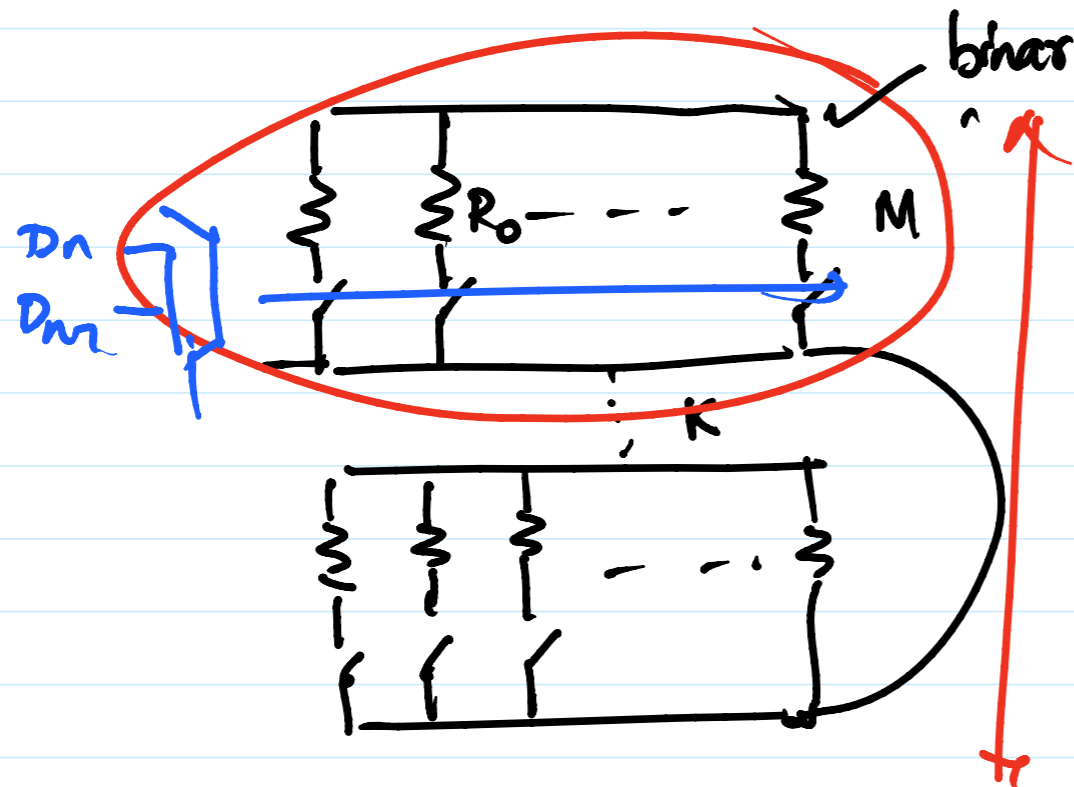$N \rightarrow 14, \text{ min. } Q = 1, P = 13$




$$\frac{R_0}{M}$$

$$x (< k) \text{ s.t. } \frac{R_0}{M \cdot x} = R_T$$


min. Post cursor 1 fM

$$\frac{R_0}{M \cdot k} = R_T$$

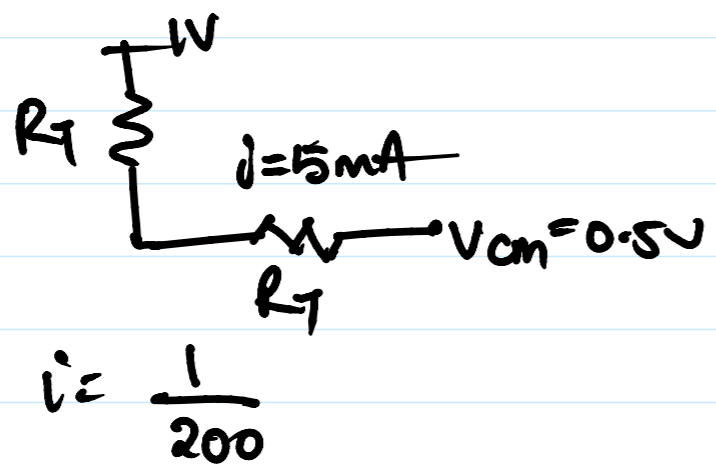


$i_{up} = i_{sig} + i_{dn}$

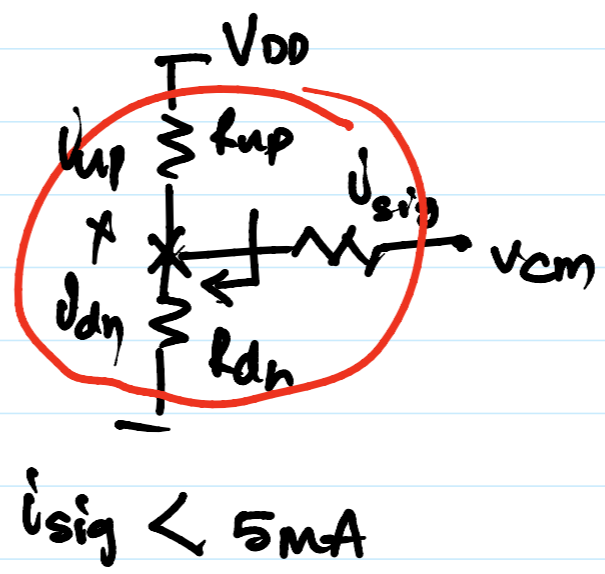
$\Rightarrow R_{up} \uparrow \quad R_{dn} \uparrow$



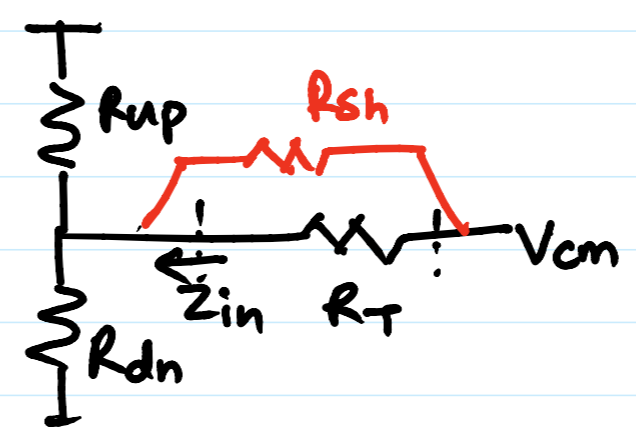Goal - lower current from supply -  
 Maintain channel termination



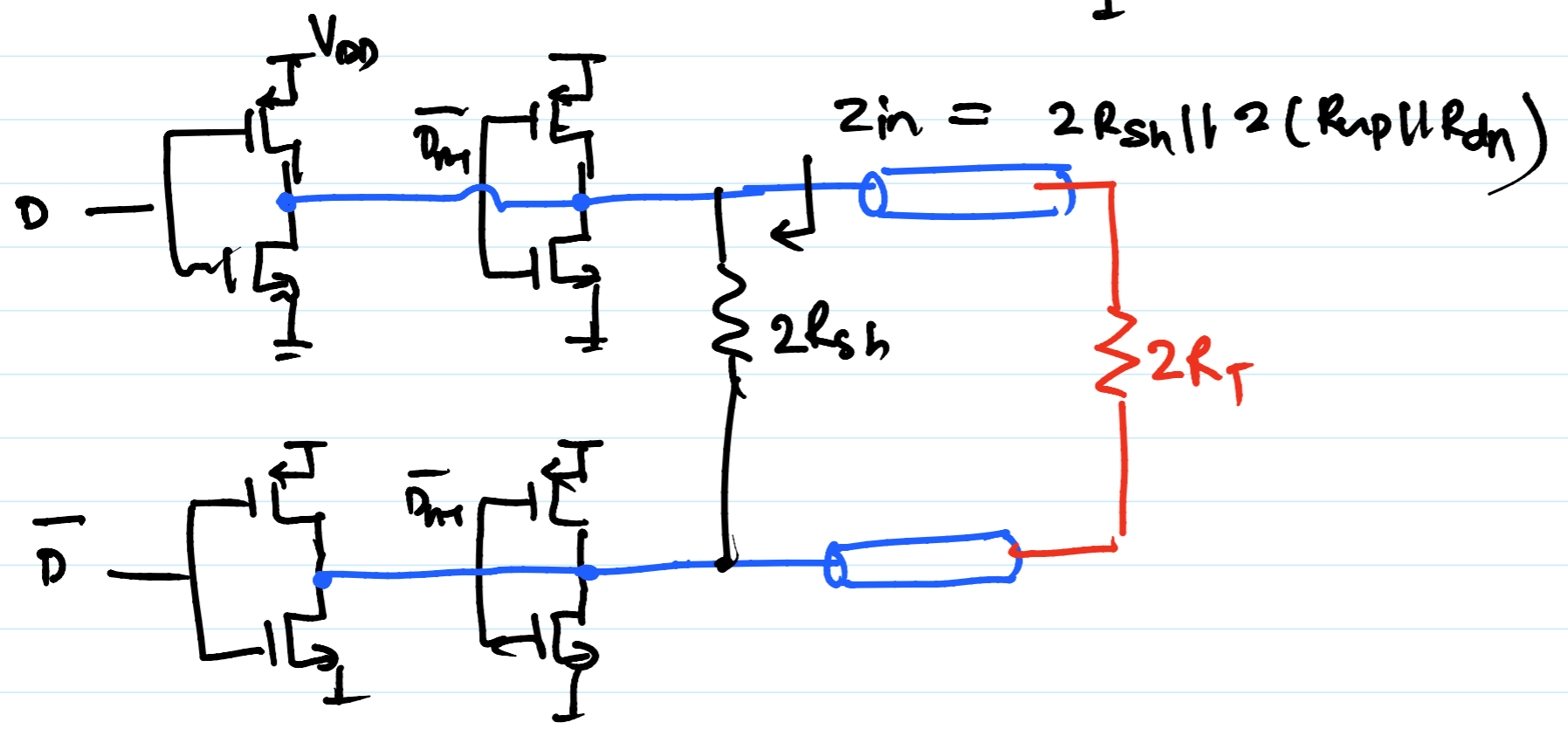$Z_{in} = R_{up} \parallel R_{dn} \parallel R_{sh}$



channel term  $\rightarrow \frac{1}{\dots} + \frac{1}{\dots} + \frac{1}{\dots} \geq \frac{1}{\dots}$

\* Channel term.  $\Rightarrow \frac{1}{R_{up}} + \frac{1}{R_{dn}} + \frac{1}{R_{sh}} = \frac{1}{R_T}$

\*  $\frac{dI_{sup}}{dV_{out}} = 0$

\*  $V_{out}$  depends on equalization