

Lecture #4




V_{ctrl1} , V_{out} : Non-linear


f_{out} , V_{ctrl1} : $f_{out} = f_0 + K_{VCO} \cdot V_{ctrl1}$

$$[K_{VCO}] = \text{Hz/V}$$



$$\omega_{out} = 2\pi (f_0 + K_{VCO} \cdot V_{ctrl1})$$
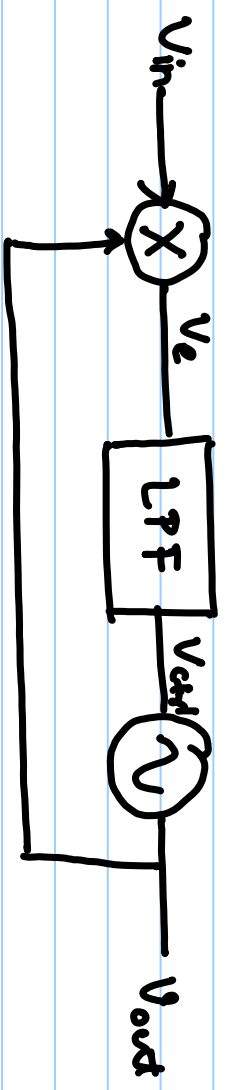
$$\phi_{out} = \int 2\pi (f_0 + K_{VCO} \cdot V_{ctrl1}) dt$$





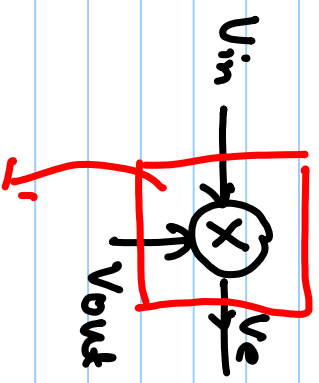
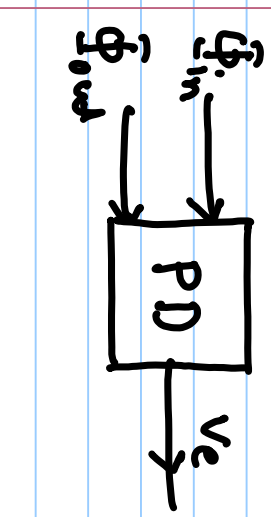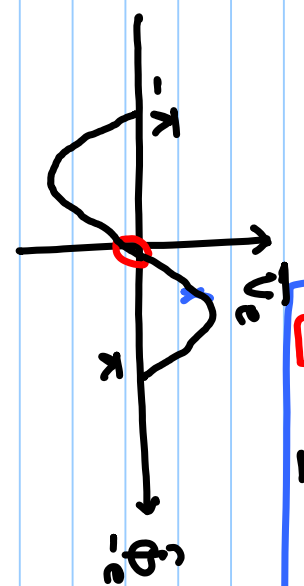
$$V_e = \frac{1}{2} \sin(\Delta \omega \cdot t + \tilde{\phi}_e) + \sin(\omega_{diff} \omega_c t + \tilde{\phi}_e)$$



$$K_{pd} \Big|_{\phi_e=0} = \frac{1}{2} \cos(\tilde{\phi}_e) \Big|_{\phi_e=0} = \frac{1}{2}$$

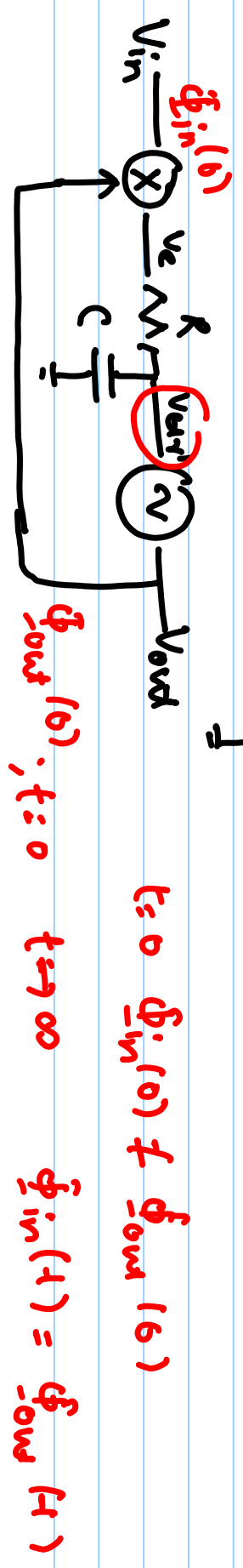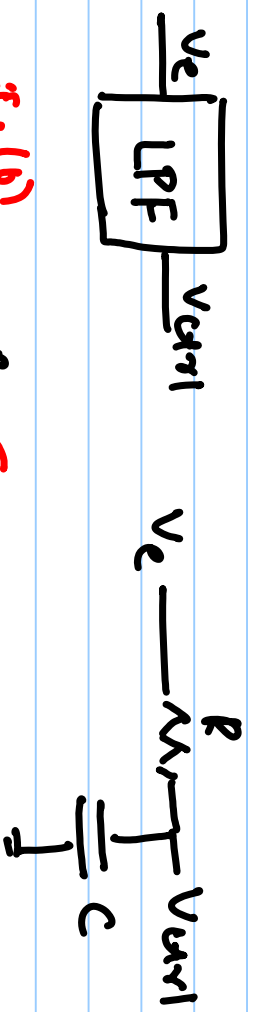

$$t=0 \quad \phi_{in}(0) \neq \phi_{out}(0)$$

$$t \rightarrow \infty \quad \phi_{in}(t) = \phi_{out}(t)$$

$$V_{in} = 1. \sin(2\pi \cdot 100 \text{ MHz} \cdot t)$$

$$V_{out} = 1. \cos(2\pi \cdot 100 \text{ MHz} \cdot t + \Delta\dot{\phi}(t) + 2\pi \int K_{VCO} \cdot V_{var} dt)$$

$$V_e = V_{in} \times V_{out} = \frac{1}{2} \left[\sin(2\pi \cdot 200 \text{ MHz} \cdot t + \Delta\dot{\phi}(t)) + \sin(\Delta\dot{\phi}(t)) \right]$$

$$V_{carrier} = \frac{1}{2} \sin(\Delta\dot{\phi}(t))$$

$$V_{out} = \cos(2\pi \cdot 100 \text{ MHz} \cdot t + \Delta\dot{\phi}(t) + 2\pi \int K_{VCO} \cdot \frac{1}{2} \sin(\Delta\dot{\phi}(t)) dt)$$

$$\Delta\dot{\phi}(t) + 2\pi \times K_{pd} \times K_{vco} \int \sin(\Delta\dot{\phi}(t)) dt$$

$$\text{Sol: } \Delta\dot{\phi}(t) = 0 \Rightarrow V_e = 0 \Rightarrow V_{var} = 0$$

V_{out} locks to V_{in} w/ phase offset $\pi/2$


* V_{in} , V_{out} in above PLL locks to zero steady state phase error provided ref. & free running clock freq. are same.

$$V_{in} = \sin(\omega_d t)$$

$$V_{out} = \sin(\omega_c t + \Delta\phi(0))$$

at $t=0$
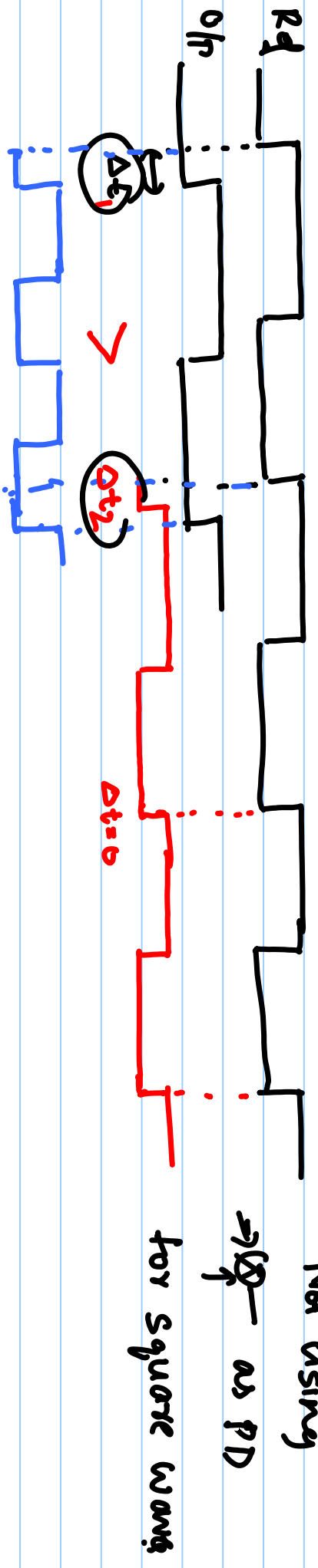
$$t=0 \left\{ \begin{aligned} \omega_{in} &= 100 \text{ MHz} & \phi_{in}(0) &= 0 \\ \omega_{out} &= 100 \text{ MHz} & \phi_{out}(0) &= \pi/3 \end{aligned} \right.$$





$$\underline{V_{in}(t)}, \underline{V_{out}(t)}$$

$$\text{At } \omega_c(t) = 0 \Rightarrow V_c = \sin(\phi_c)$$

$$\sin(\omega_1 t) \cdot \sin(\omega_1 t) = \frac{1}{2} (1 + \cos(2\omega_1 t))$$


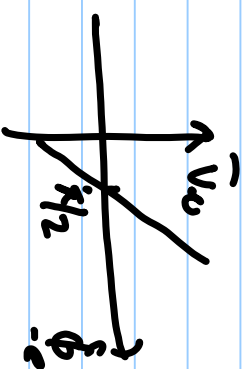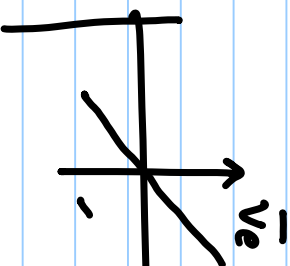
$$\left. \begin{array}{l} \sin(\omega_1 t) \\ \cos(\omega_1 t) \end{array} \right\} V_c = 0$$



$$f_c = 0 \left\{ \begin{array}{l} V_{in} = \sin(2\pi \cdot \underbrace{100 \text{ MHz}}_{\omega_0} t) \quad \omega_0 = 100 \text{ MHz} \\ V_{out} = \cos(2\pi \cdot 99 \text{ MHz} t + \Delta\phi(0)) \quad \Delta\omega = 1 \text{ MHz} \end{array} \right.$$

$$V_c = \frac{1}{2} [\sin(2\pi \cdot 2\omega_0 \cdot t - 2\pi \cdot \Delta\omega \cdot t + \Delta\phi(0)) + \sin(2\pi \cdot \Delta\omega \cdot t - \Delta\phi(0))]]$$

$$V_{\text{err1}} = \frac{1}{2} \sin(2\pi \cdot \Delta\omega \cdot t - \Delta\phi(0))$$

$$V_{\text{out}} = \cos(2\pi \cdot \omega_0 \cdot t - 2\pi \cdot \Delta\omega \cdot t + 2\pi \int K_{\text{VCO}} \cdot V_{\text{err1}} \cdot dt + \Delta\phi(0))$$

$$\phi_{\text{in}}(t) = 2\pi \cdot 100 \text{ MHz} \cdot t$$

$$\phi_{\text{out}}(t) = 2\pi (\omega_0 - \Delta\omega) t + 2\pi \int K_{\text{VCO}} \cdot V_{\text{err1}} \cdot dt + \Delta\phi(0)$$

$$\phi_e(t) = \phi_{\text{in}} - \phi_{\text{out}}$$

$$\phi_e(t) = 2\pi \cdot \Delta\omega \cdot t - 2\pi \int K_{\text{VCO}} \cdot V_{\text{err1}} \cdot dt - \Delta\phi(0)$$

$$\checkmark \phi_e(t) = 2\pi \cdot \Delta\omega \cdot t - 2\pi K_{\text{VCO}} \int K_{\text{PD}} \sin(2\pi \cdot \Delta\omega \cdot t - \Delta\phi(0)) \cdot dt - \Delta\phi(0)$$

$$\sin(\phi_e(t - \tau)) \checkmark$$

$$2\pi K_{vco} \cdot K_{pd} \int \sin(2\pi \Delta\omega t - \Delta\hat{\phi}(t)) dt = 2\pi \Delta\omega t - \Delta\hat{\phi}(t) - \hat{\phi}_e(t)$$

$$\frac{d\hat{\phi}_e(t)}{dt} = 2\pi \Delta\omega - 2\pi K_{vco} K_{pd} \sin(2\pi \Delta\omega t - \Delta\hat{\phi}(t))$$

$$2\pi \Delta\omega - 2\pi K_{vco} \cdot K_{pd} \sin(\hat{\phi}_e(t+\omega)) = 0$$

$$\Rightarrow \sin(\hat{\phi}_e(t+\omega)) = \frac{\Delta\omega}{K_{vco} K_{pd}} \leq 1$$

$$\Rightarrow \Delta\omega \leq K_{vco} K_{pd}$$

