
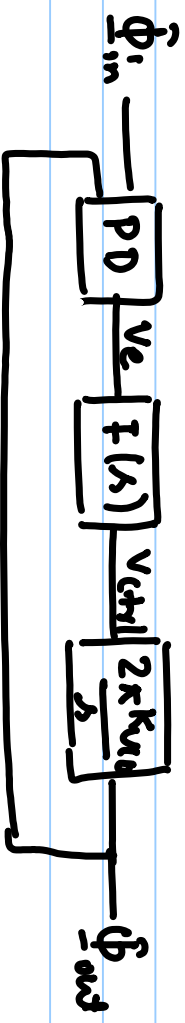


Lecture # 6

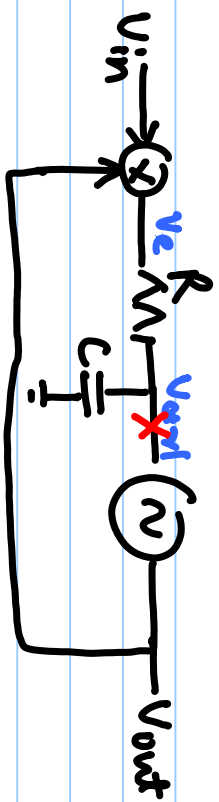

at $t=0$ $v_{in} = A_{in} \sin(\omega_{in} t)$


$$v_{out} = A_{out} \cos(\int \omega_{free} + 2\pi K_{vo} v_{err} dt)$$

$$v_e = 0, \quad v_{err} = 0, \quad A_{in} = A_{out} = 1$$

$$v_e = v_{in} \times v_{out} = \frac{1}{2} \left[\sin(\omega_{in} t + \omega_{free} t + \int 2\pi K_{vo} v_{err} dt) + \sin(\omega_{in} t - \omega_{free} t - \int 2\pi K_{vo} v_{err} dt) \right]$$

$$v_e = \frac{1}{2} \left[\sin(\omega_{in} t) + \sin(\Delta \omega t - \int 2\pi K_{vo} v_{err} dt) \right]$$
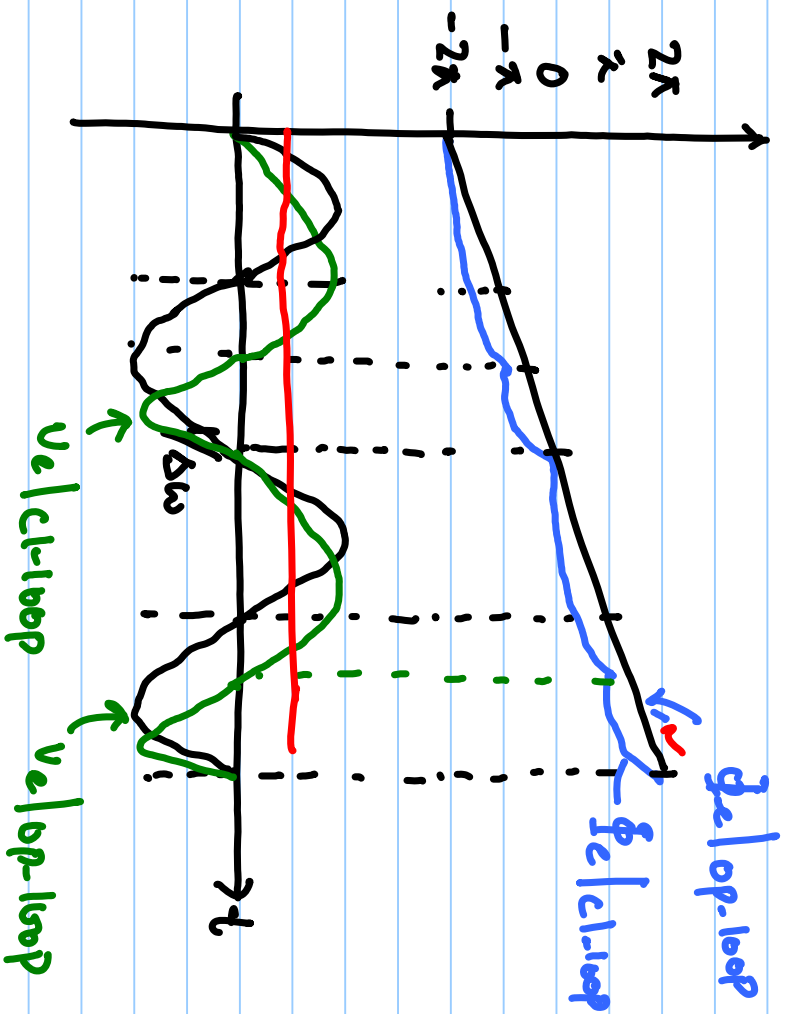
$$\dot{\Phi}_e = \Delta\omega t - 2\pi \int K_{vco} \cdot U_{ctrl} dt$$



$$v_e = \frac{1}{2} \sin(\Phi_e)$$

$$\dot{\Phi}_{ows} = \omega_{free} t + 2\pi K_{vco} \cdot K_{pd} \int \sin(\Phi_e) dt$$

$$\dot{\Phi}_e(t) = \Delta\omega \cdot t - 2\pi K_{vco} \cdot K_{pd} \int \sin(\Delta\omega t) dt$$

$$\dot{\Phi}_e(t) = \Delta\omega \cdot t - \frac{2\pi K_{vco} \cdot K_{pd}}{\Delta\omega} (1 - \cos(\Delta\omega t))$$

$$\dot{\Phi}_e(0) = \Delta\omega \cdot 0$$


$$\dot{\Phi}_e\left(\frac{1}{\Delta\omega}\right) = \Delta\omega \cdot \frac{1}{\Delta\omega} - 0$$

$$\dot{\Phi}_e\left(\frac{1}{2 \cdot \Delta\omega}\right) = \pi - \frac{\pi}{2}$$

$$v_e = \frac{1}{2} \sin(\Phi_e)$$

$\dot{\Phi}_e$ | open loop

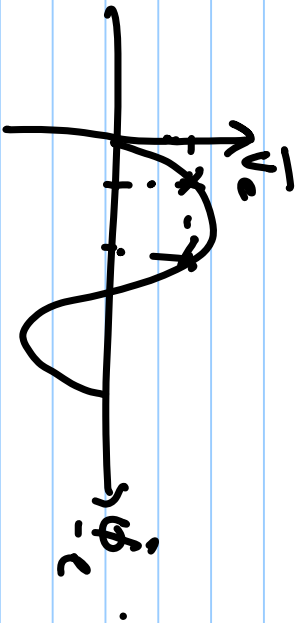In steady state, $\bar{V}_e = \frac{1}{2} \sin(\dot{\Phi}_e)$ ✓
 $V_{ctrl} = \frac{\Delta \omega}{2\pi K_{vco}}$
 $K = 2\pi K_{vco} \cdot K_{pd}$




$$\dot{\Phi}_e = \Delta \omega \cdot t - \underbrace{2\pi K_{vco} \cdot K_{pd}}_K \int \sin(\dot{\Phi}_e) dt$$

$$\Delta \omega' = \frac{d\dot{\Phi}_e}{dt} = \Delta \omega - K \sin(\dot{\Phi}_e)$$

$$\frac{\Delta \omega'}{K} = \frac{\Delta \omega}{K} - \sin(\dot{\Phi}_e)$$

at NULL: $\frac{\Delta \omega'}{K} < 0$

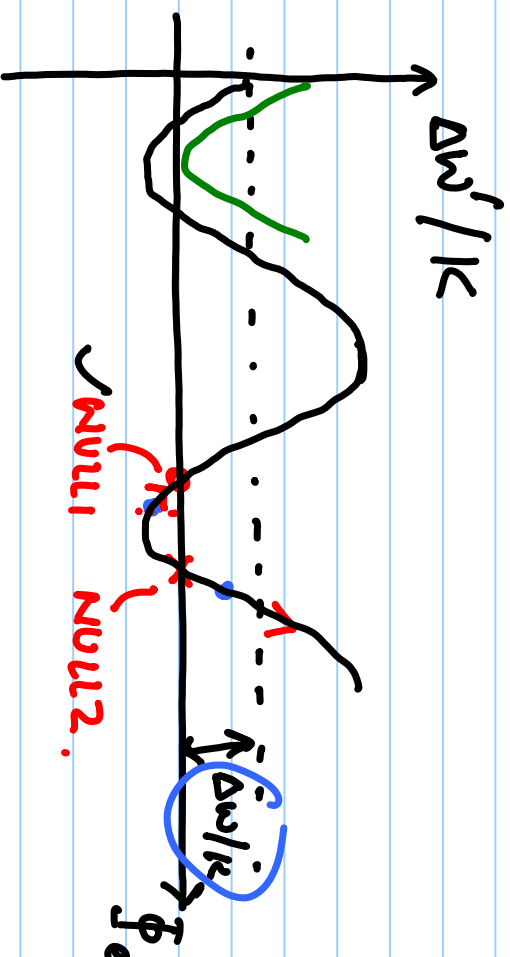


$$\Phi_e = \int \Delta \omega' dt$$

$$\frac{\Delta \omega}{K} = \sin(\Phi_e) \leq 1$$

To increase $\Delta \omega \rightarrow$ increase K .

PLL Type / Order
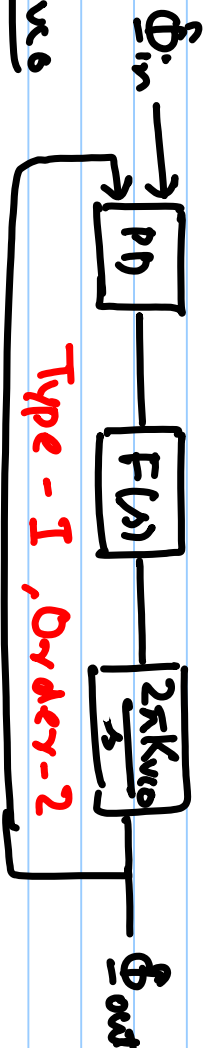
$$L_c(s) = K_{pd} \cdot F(s) \cdot \frac{2\pi K_{vco}}{s}$$



$$\text{if } F(s) = \frac{1}{1+s\tau}, \quad K_{pd} = \frac{1}{2}$$

Type: No. of integrators in PLL loop.

Order: No. of poles in PLL loop transfer function.


Type $\left\{ \begin{array}{l} > \\ \leq \\ = \end{array} \right.$ Order

Type \leq Order

$$\frac{\Delta \omega}{\omega} = \sin(\phi_2) \leq 1$$

For large $\Delta \omega \Rightarrow$ large K

$$\frac{K}{s}$$

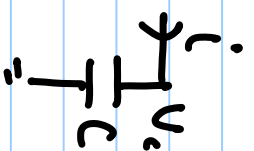

$$V_c = i \times \frac{1}{Cs} = \frac{i}{s}$$

$$F(s) = \frac{A_o}{s}$$




$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sRC}$$



$$\frac{V_{out}}{V_{in}} = \frac{A_o}{s}$$


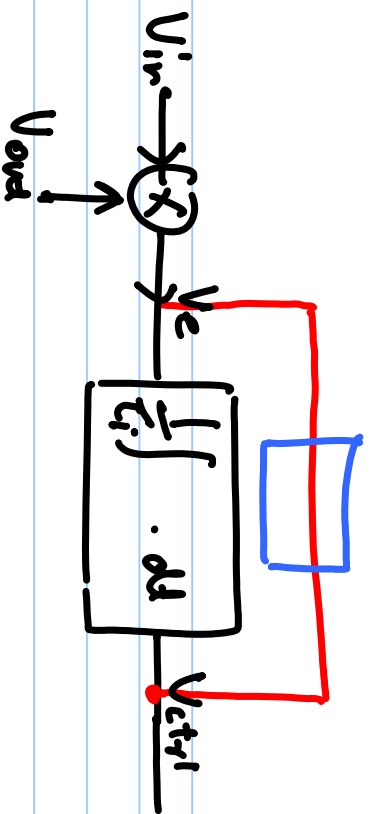
$$L_G(s) = K_{pd} \cdot \frac{A_o}{s} \frac{2\pi K_{vco}}{s}$$



$$V_e = \frac{1}{2} \sin(\Delta\omega \cdot t)$$

$$V_{ctrl} = \int_0^{1/\Delta\omega} V_e \cdot dt$$



In locked state:

$$\Delta\omega = 0, \quad \phi_e = 0 \quad \therefore V_{ctrl} = \frac{\Delta\omega}{2\pi K_{vco}}$$

Prop. + Int. ✓

Prop. ✗

Int. ✓

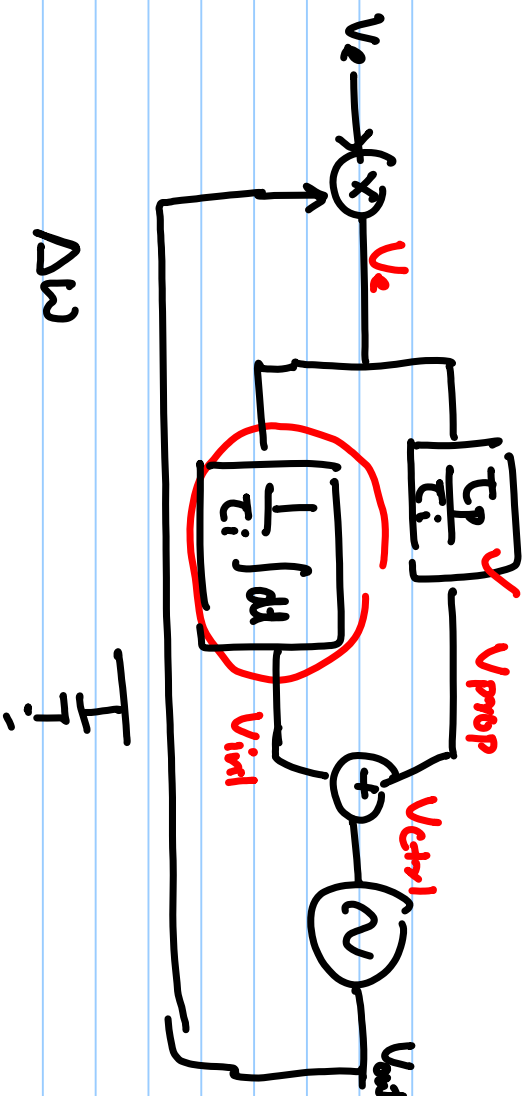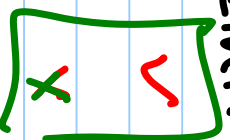

$$V_{ctrl} = V_{prop} + V_{int} = \frac{\Delta\omega}{2\pi K_{vco}}$$

$$= \frac{\tau_p}{\tau_i} V_e + \omega \times V_e =$$

$$V_e = 0$$