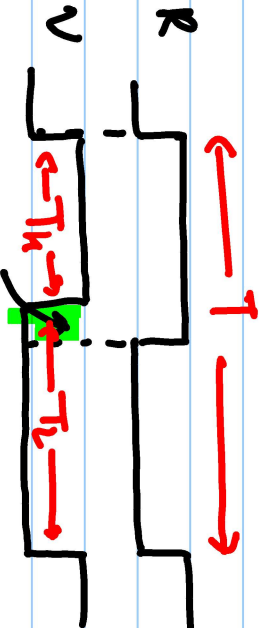


Lecture #14


DFF based PD

Digital Phase Error Det. — EXOR based PD

EXOR PD





$$D = \frac{T_H}{T_H + T_L}$$

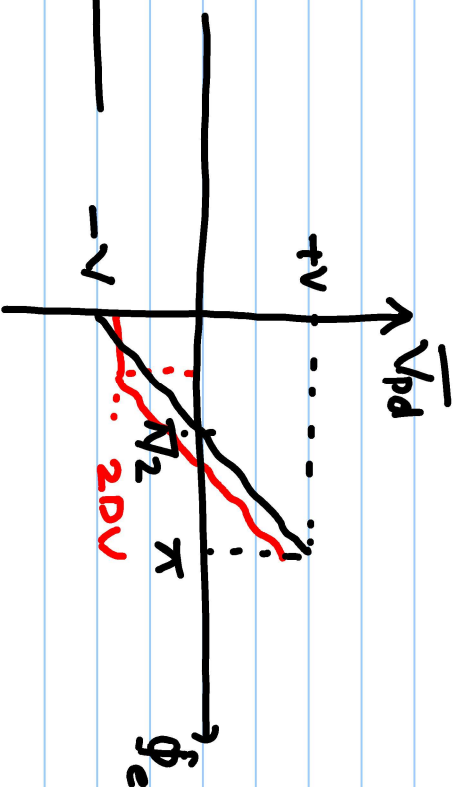

$$K_{pd} = \frac{2V}{\pi} \quad [V/rad]$$




Linear range: 0 to π

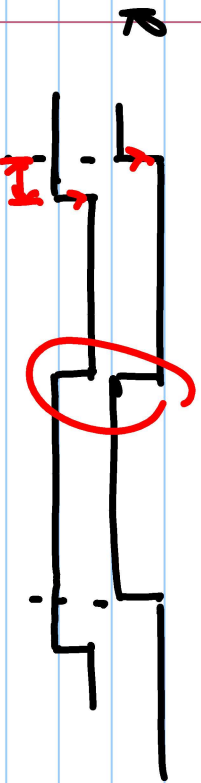


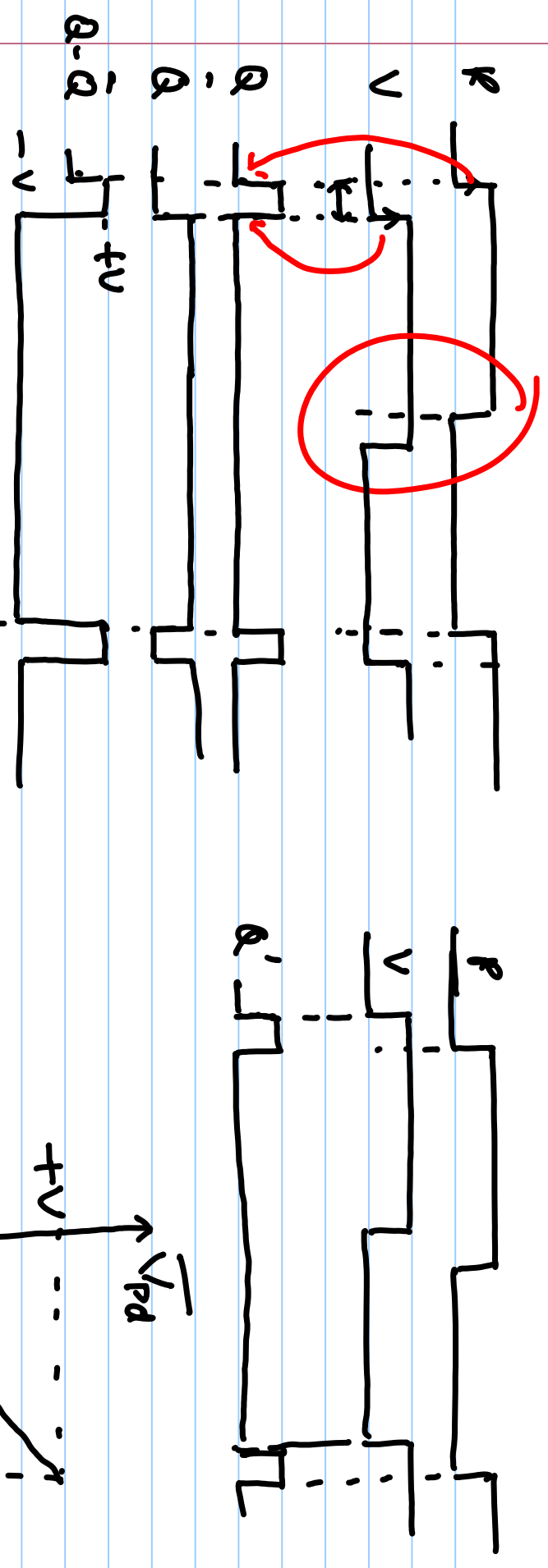


$$\overline{V_{pd}} = \frac{V \cdot \Phi_e - v(2\pi - \Phi_e)}{2\pi}$$

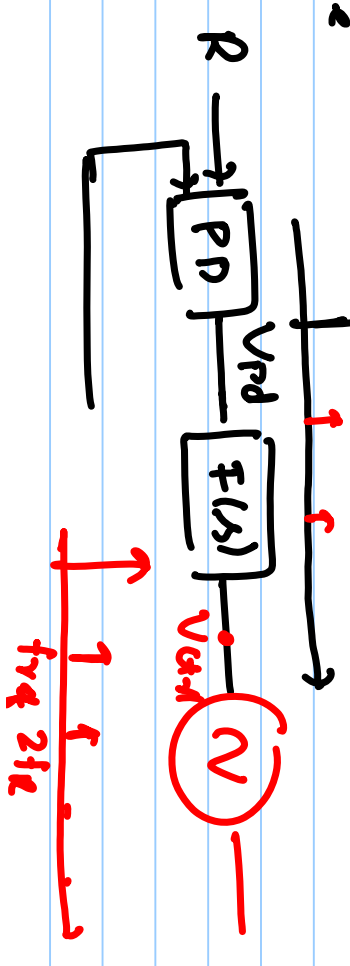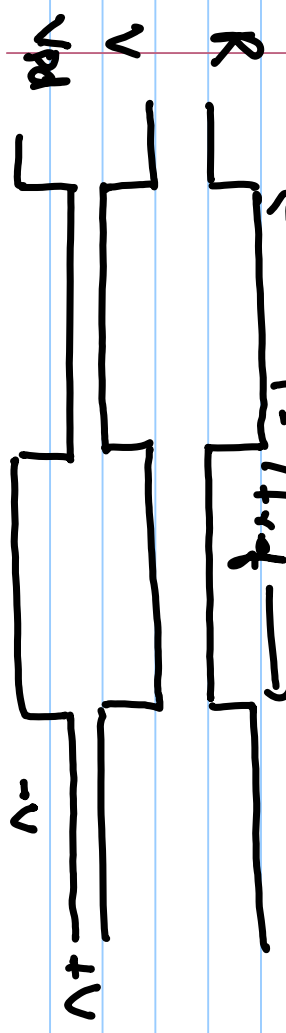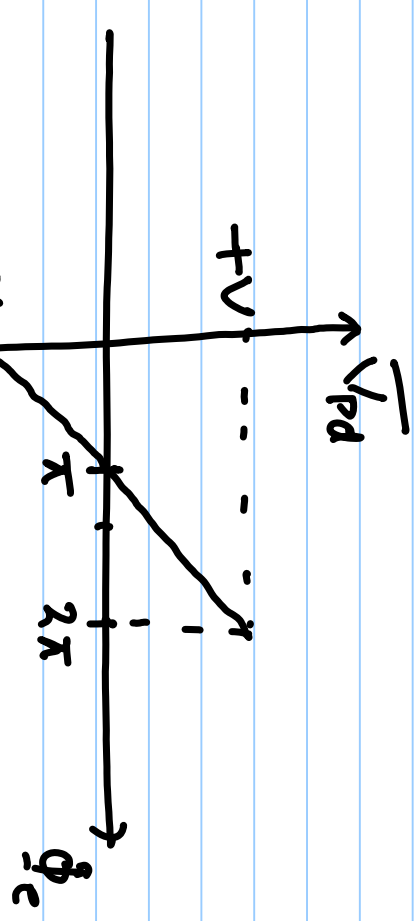
$$= \frac{2V}{2\pi} (\Phi_e - \pi) = \frac{V}{\pi} (\Phi_e - \pi)$$



SR latch-based PD


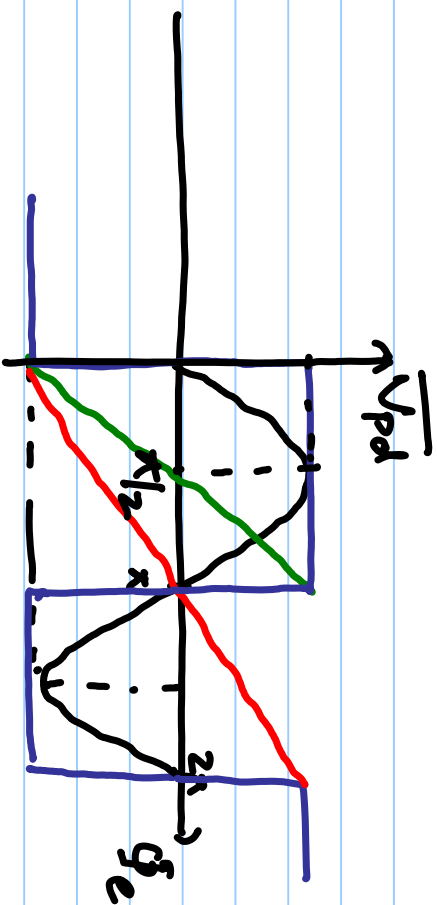
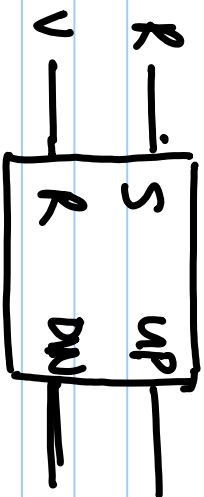

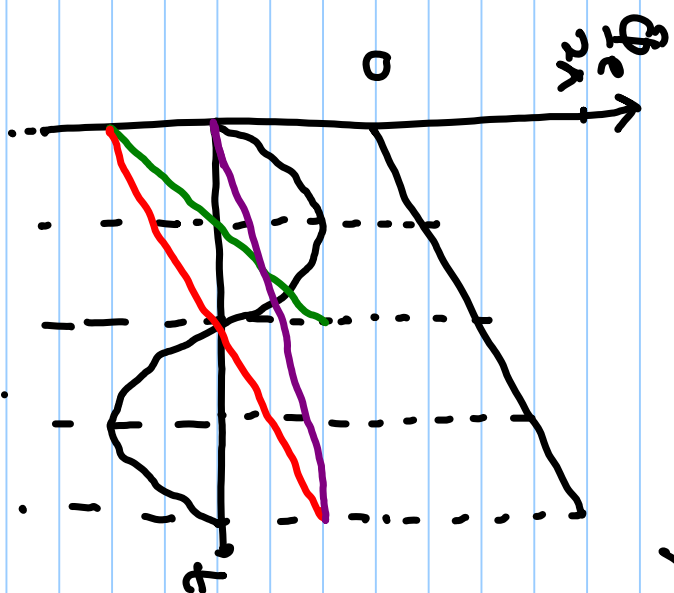
$$\Delta \omega = \omega_{in} - \omega_{out} \neq 0 > 0$$








PD o/p is both +ve & -ve for same freq. error

3-state PFD (Phase Frequency Detector)

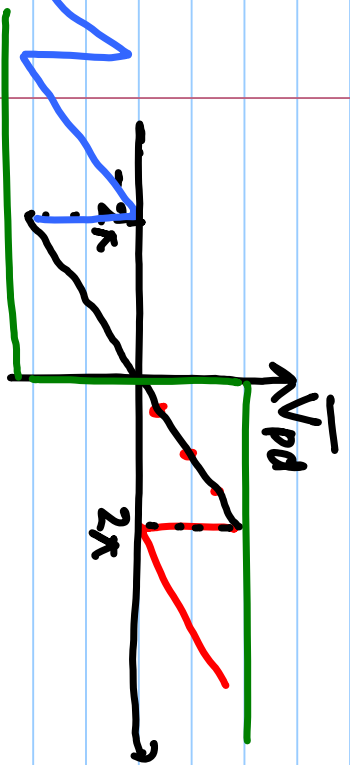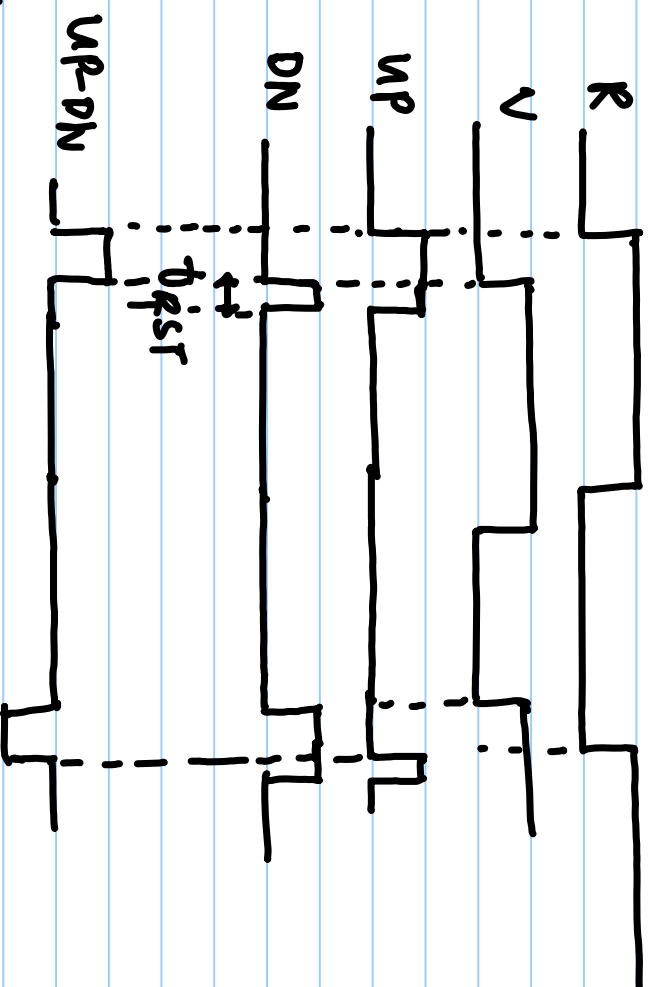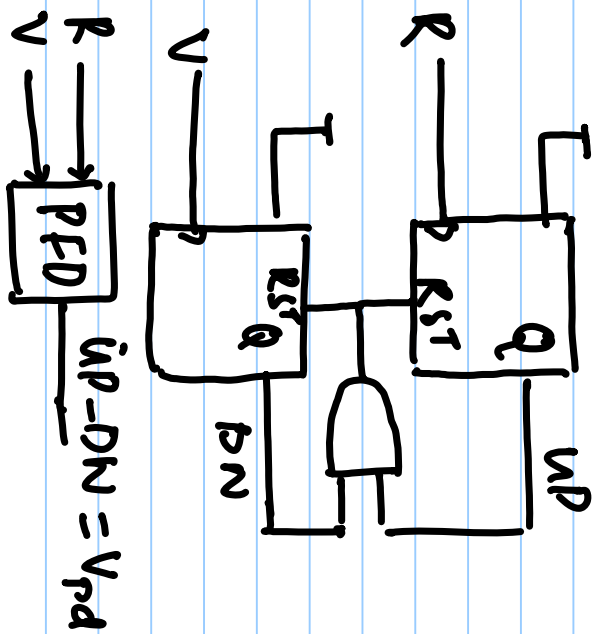
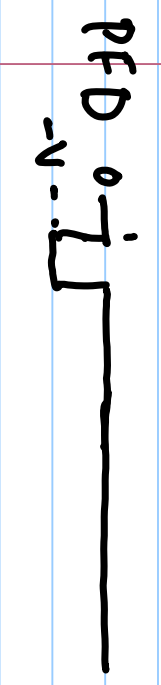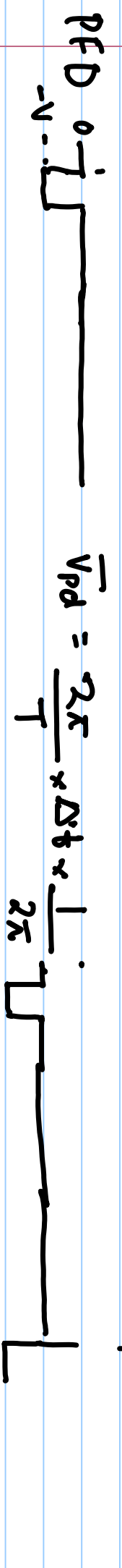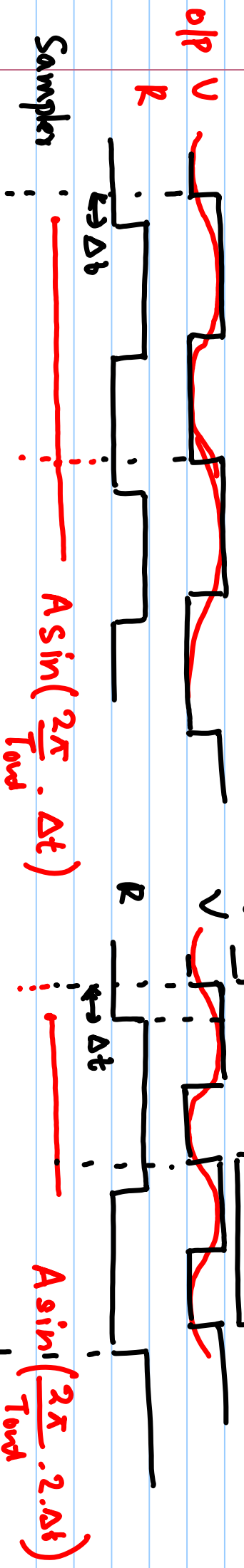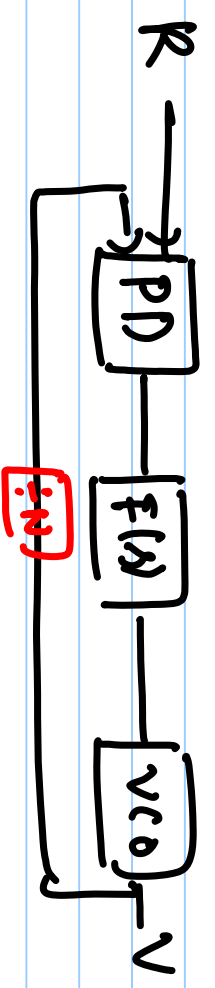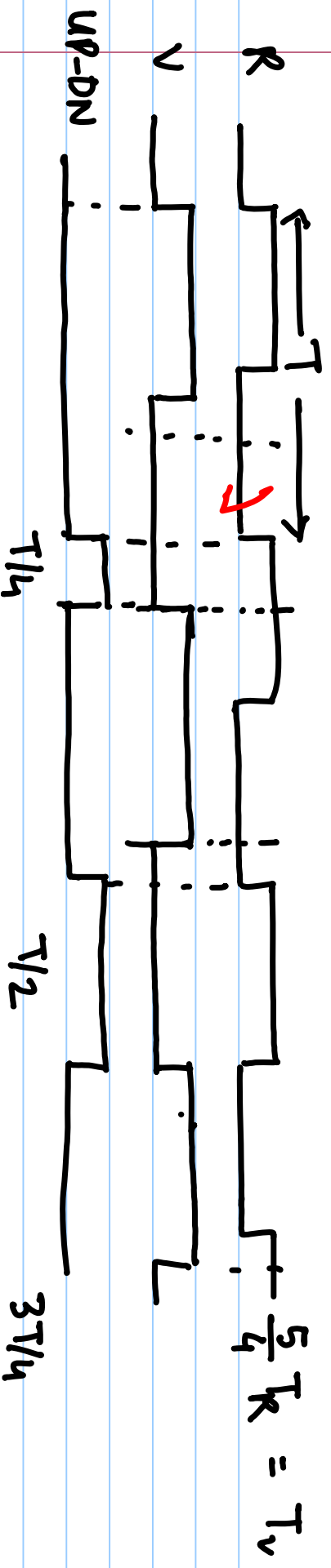
$$V_{pd} = +V \times \frac{\phi}{2\pi} = \frac{\phi}{2\pi} \cdot V$$





$$V_{pd} = \frac{2\pi}{T} \times \Delta t \times \frac{1}{2\pi}$$

