

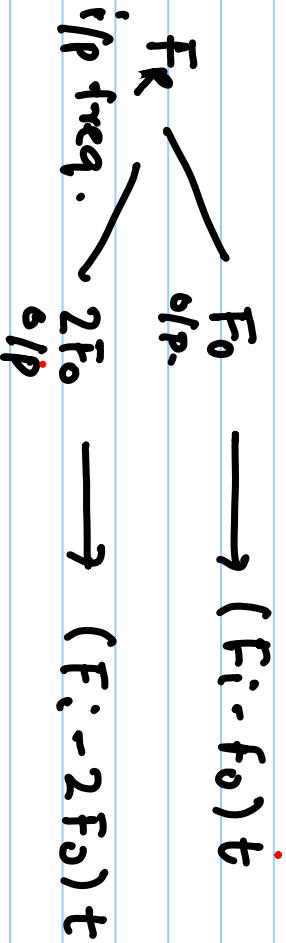


Lecture #15







Phase Frequency Detector (PFD)

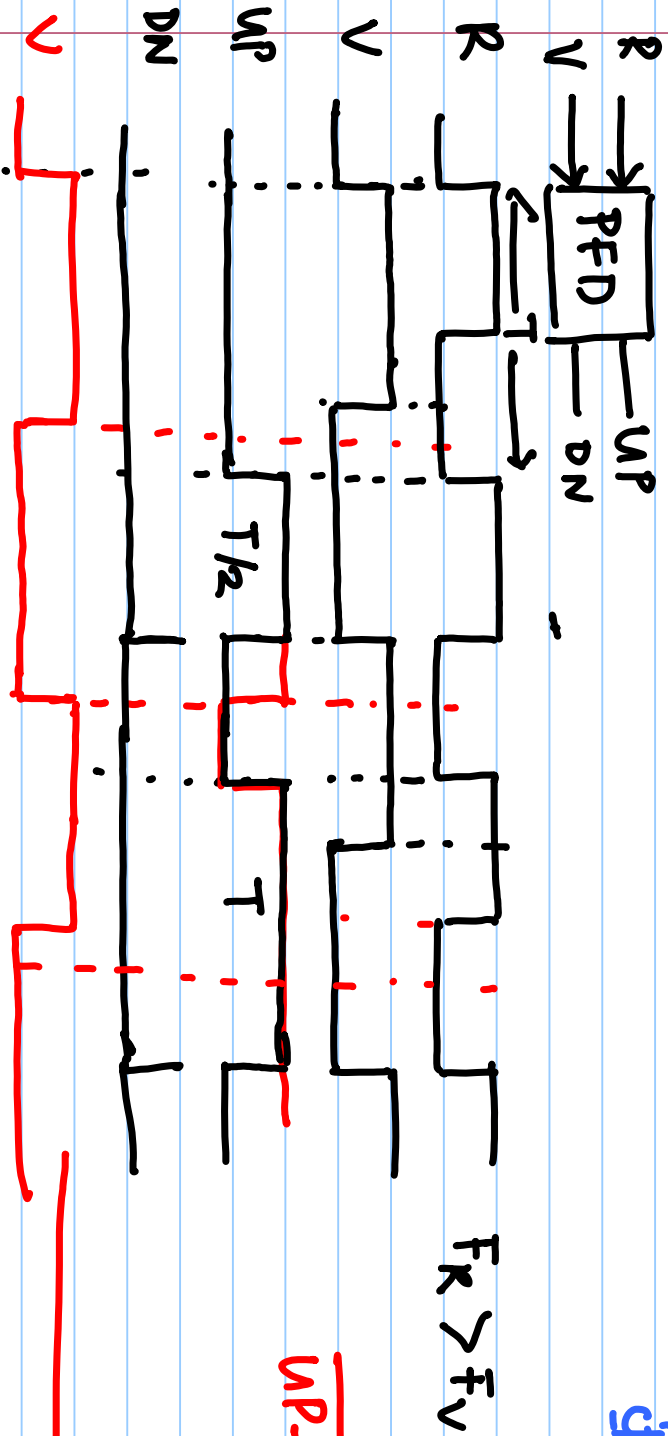


$\overline{UP - DN}$

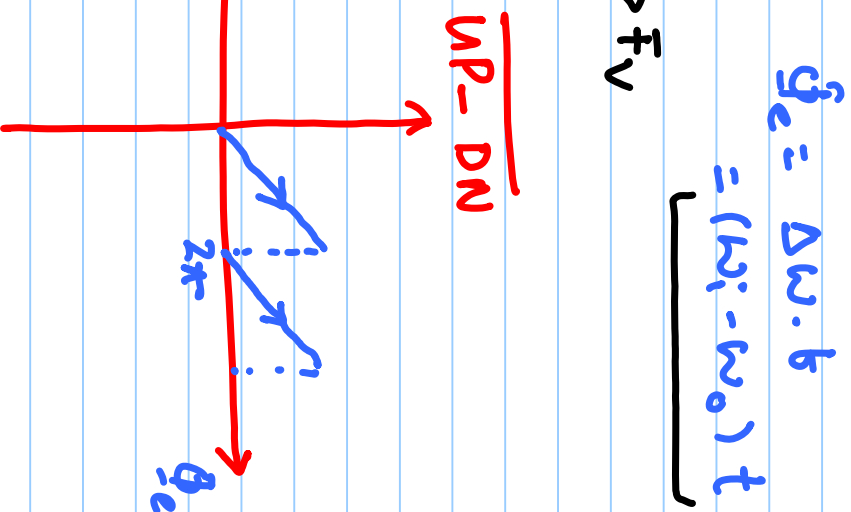

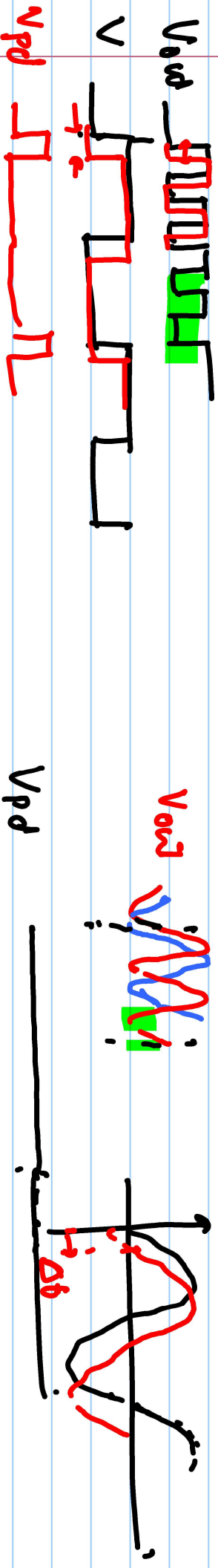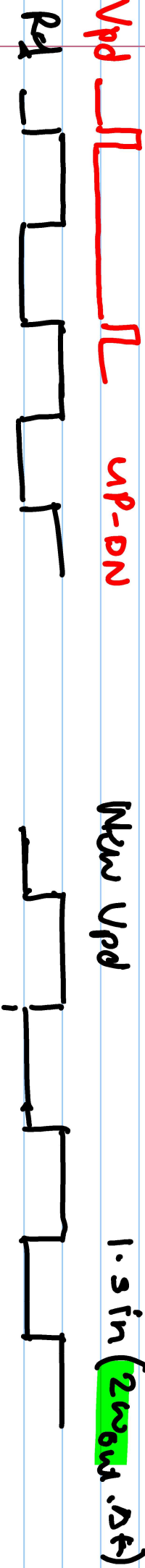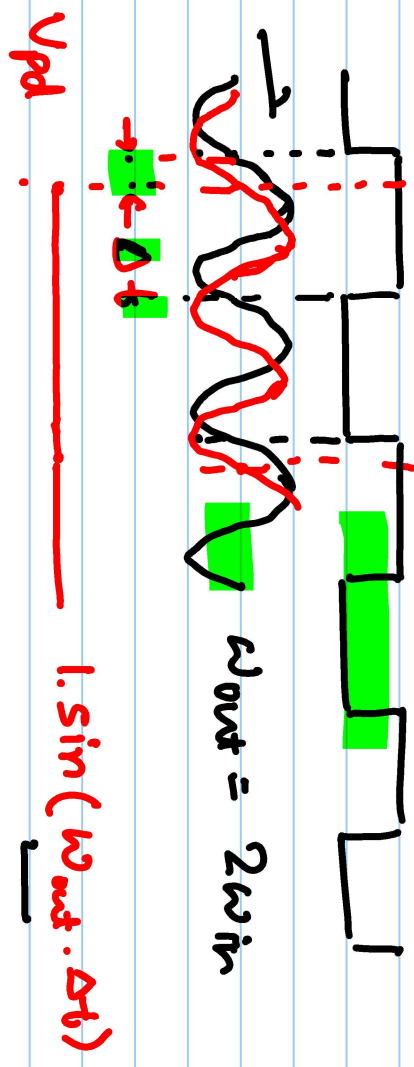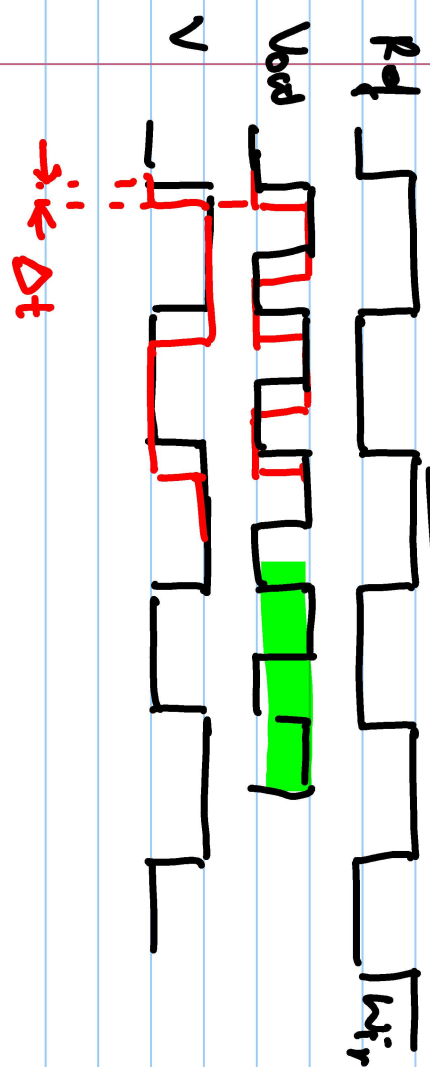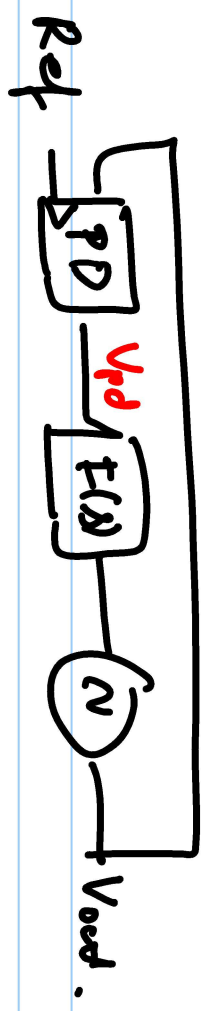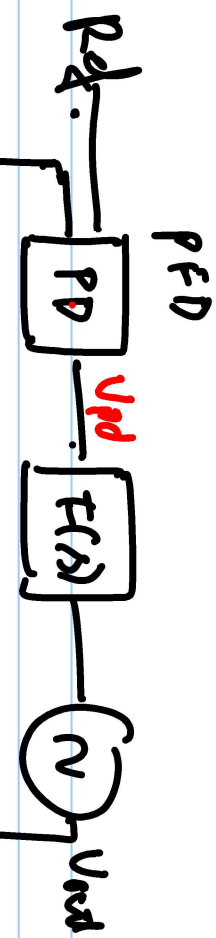
$$\theta_e = \Delta \omega \cdot t = (\omega_i - \omega_o) t$$



At shift in o/p clock.

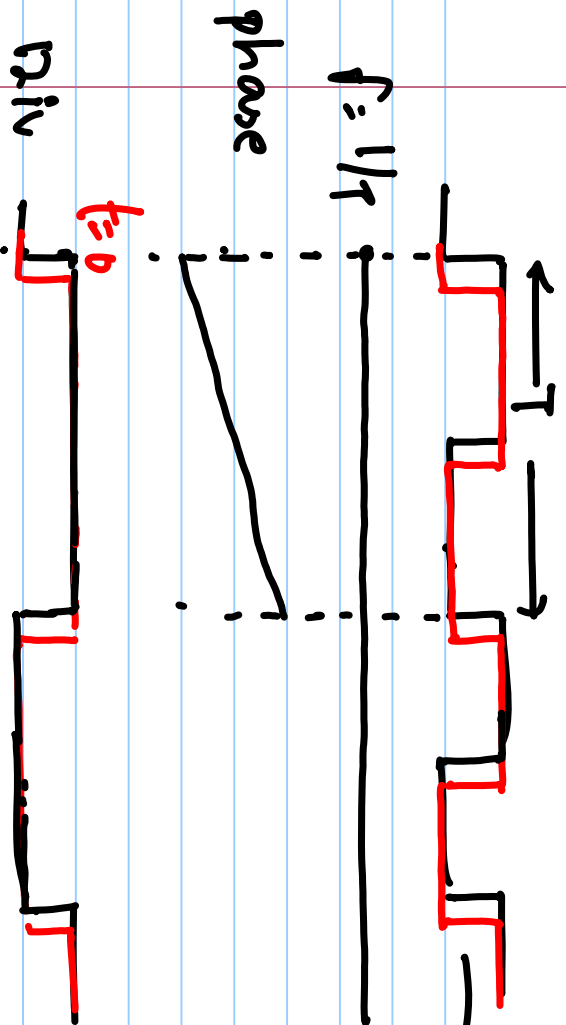

Δt

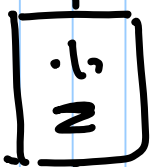

Δt

$$f = \frac{1}{NT}$$

$$\Phi_{in} = \frac{2\pi}{T} \Delta t$$

$$\Phi_{out} = \frac{2\pi}{NT} \Delta t$$

T is VCO period

$$= \frac{\Phi_{in}}{N}$$




PFD as frequency detector

F_R : Ref. clock freq. $F_R = 1/T_R$
 F_V : O/p clock freq. $F_V = 1/T_V$



$$\Delta t = T_V - T_R \quad ; \quad F_R > F_V$$
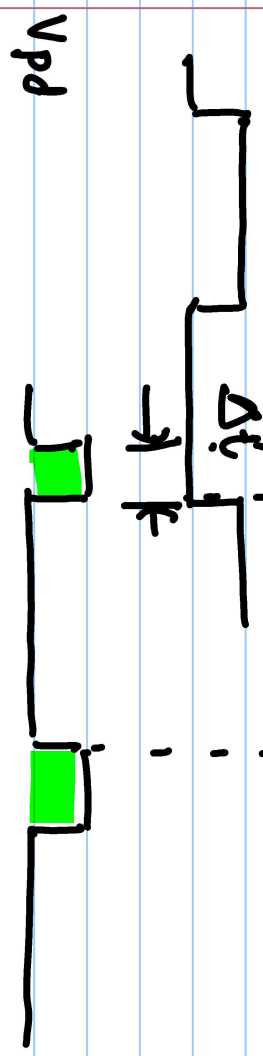
$$\frac{F_R}{F_V} = \frac{5}{4} \quad \Rightarrow \quad \frac{T_V}{T_R} = \frac{5}{4}$$



For 1st Ref. cycle. $4T_V = 5T_R$

$$\Delta t(1) = T_V - T_R = \frac{5}{4}T_R - T_R = \frac{T_R}{4}$$

$$\Delta t(2) = 2T_V - 2T_R = \frac{T_R}{2}$$

$$\overline{V_{pd}} = \frac{1}{N \cdot T} (\Delta t + 2 \cdot \Delta t + \dots + N(\Delta t))$$

$$N(\Delta t) = T$$

$$\overline{V_{pd}} = \frac{1}{N \cdot T} \Delta t \frac{N(N+1)}{2}$$


$$\bar{V}_{pd} = \frac{\Delta t}{T} \frac{1}{N} \frac{N(N+1)}{2}$$

$$\Delta t = T_V - T_R \quad ; \quad F_R > F_V$$

$$= \frac{\Delta t}{T} \frac{1}{N} \cancel{N} 0.5 \cancel{N} (N+1)$$

$$\frac{F_R}{F_V} = \frac{3}{2} \Rightarrow \frac{T_V}{T_R} = \frac{3}{2}$$

$$2T_V = 3T_R$$

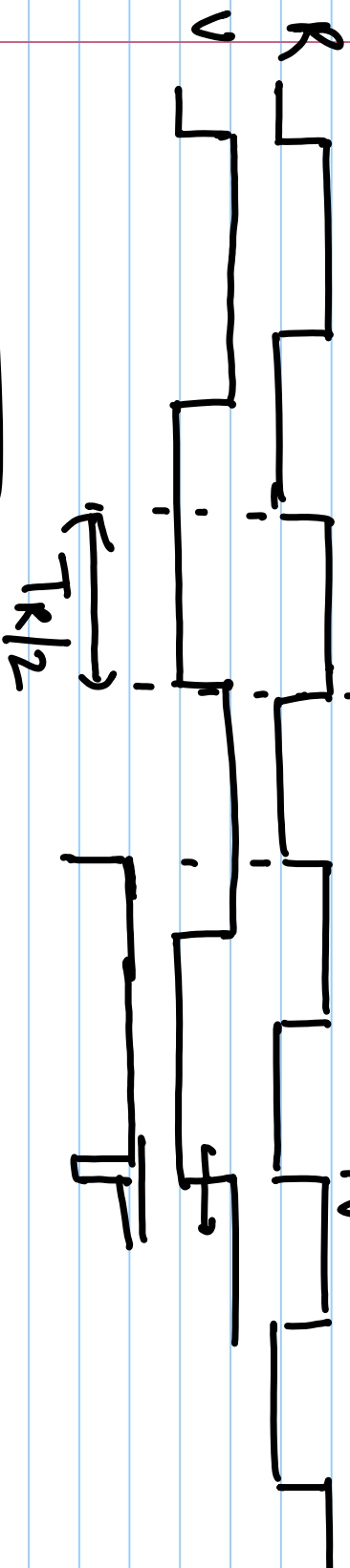

$$\boxed{\Delta t \cdot N = T_R}$$

$$V_{pd} = 0.5 \left(\frac{N+1}{N} \right) = 0.5 \left(1 + \frac{\Delta t}{T_R} \right)$$

$$= 0.5 + 0.5 \frac{(T_V - T_R)}{T_V} =$$