
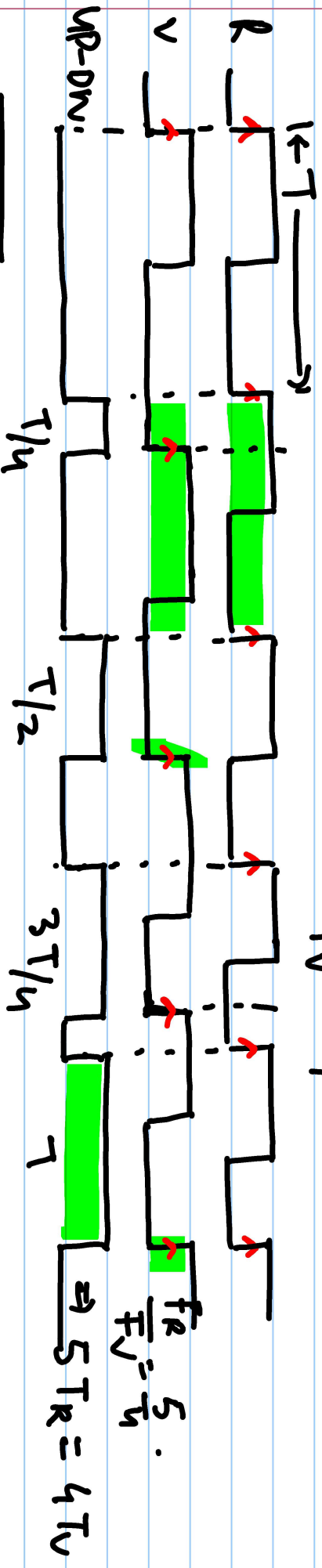


# Lecture # 16

PFN as frequency detector:

$$\frac{f_R}{f_V} = \frac{5}{4}$$

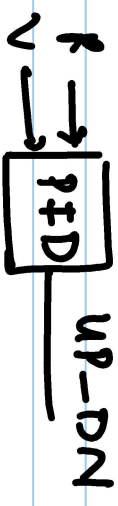


$$UP-DN = \frac{1}{5T} (T/4 + T/2 + 3T/4 + T) = 0.5$$

$$f_R > f_V \Rightarrow T_R < T_V$$


P (V ↑ transition during one  $T_R$  period) =  $\frac{T_R}{T_V} = \alpha = \frac{f_V}{f_R}$

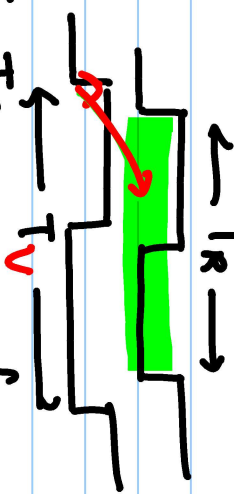P (no V ↑ transition happen during 1  $T_R$  period) =  $1 - \alpha$





$$\overline{UP-DN} = 1$$

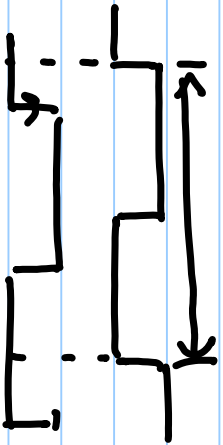

$$\overline{UP-DN} = \frac{\Delta t}{T_R}$$

$\overline{UP-DN}$  when  $V$  transition happens during  $1 T_R$  period

$$= 0.5 \int_0^{T_R} \frac{1}{T_R} \cdot \left(\frac{\Delta t}{T_R}\right) \cdot d(\Delta t)$$


$$\overline{UP-DN} = P(V \uparrow \text{ happens}) \times 0.5 + P(V \uparrow \text{ doesn't happen}) \times 1$$

$$= 0.5 \alpha + (1 - \alpha) \times 1$$

$$= 1 - 0.5 \alpha$$

$$\overline{UP-DN} = 1 - 0.5 \frac{f_v}{f_R} \quad ; \quad f_R > f_v$$
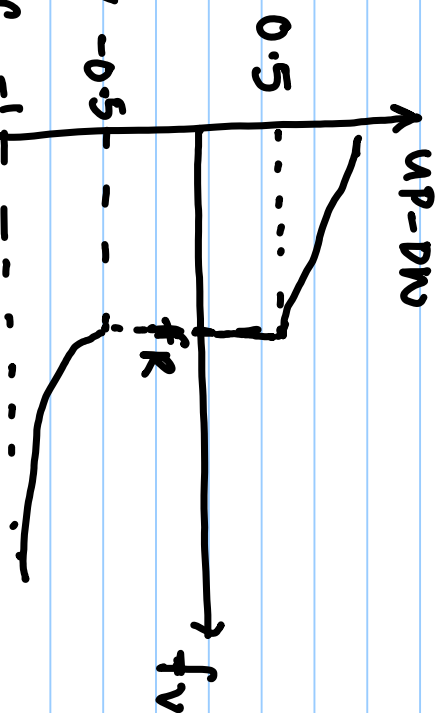
$$\overline{UP-DN} = 0.5 \frac{f_R}{f_v} - 1 \quad ; \quad f_v > f_R$$




## Frequency Detectors



$$\frac{f_R}{f_V} = \frac{5}{4} \Rightarrow 5 T_R = 4 T_V \Rightarrow 5 \text{ ref. time period} = 4 \text{ o/p time period.}$$

R as reference / known clock.
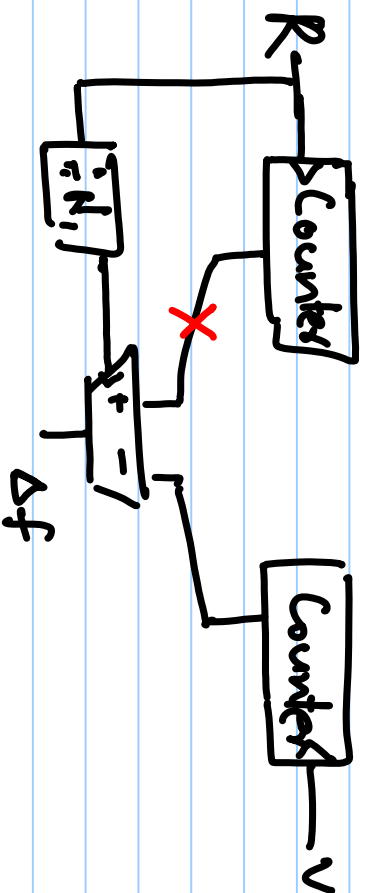
$$N \times T_R = M T_V \Rightarrow f_V = \frac{M}{N} f_R$$





# Divider based freq. error detector

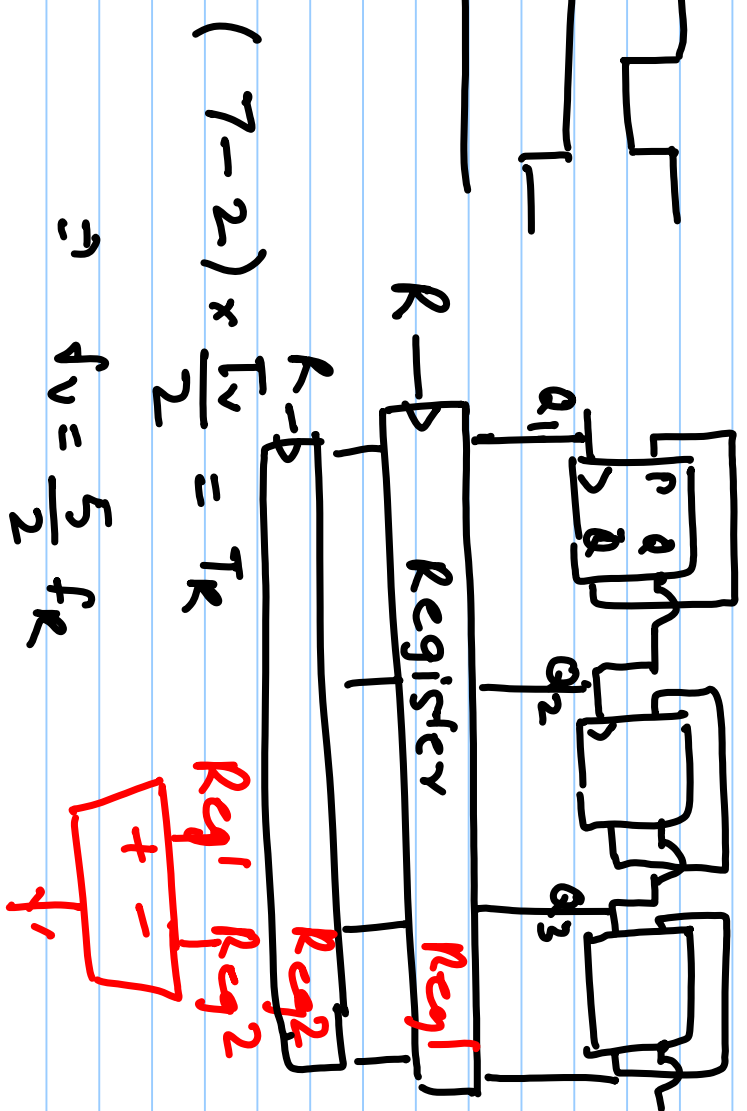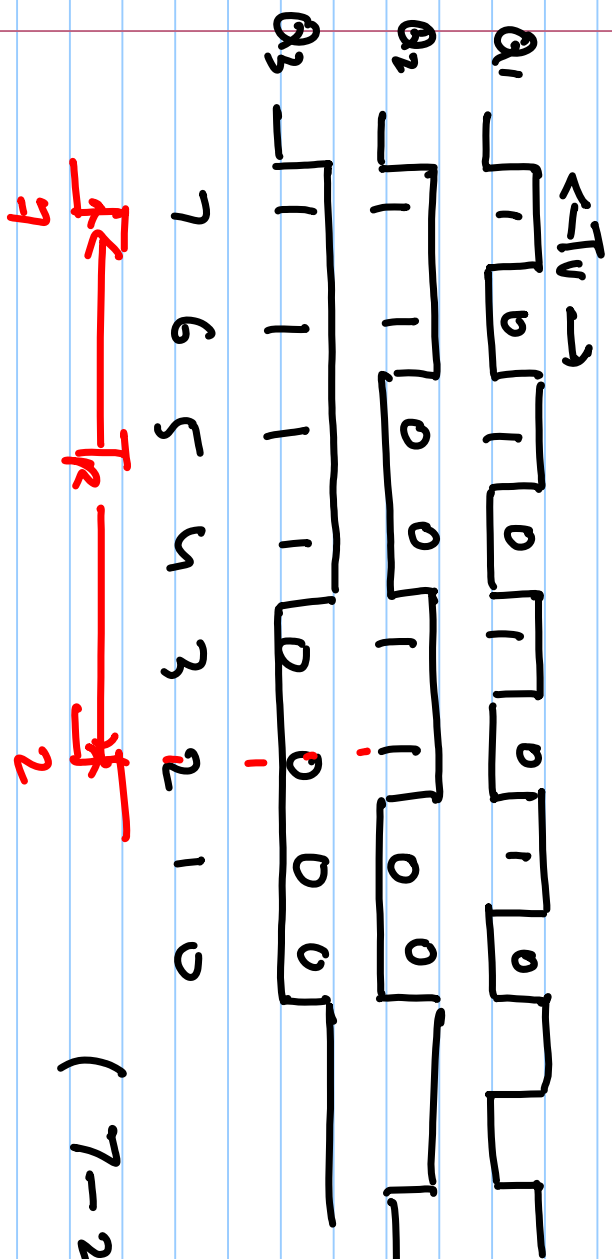

$$(7-2) \times \frac{T_v}{2} = T_R$$
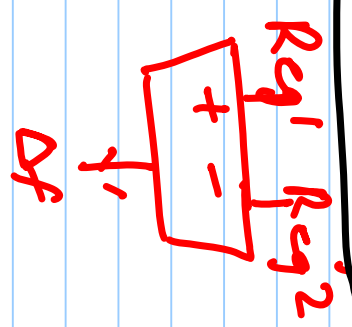
$$\Rightarrow \Delta v = \frac{5}{2} f_R$$



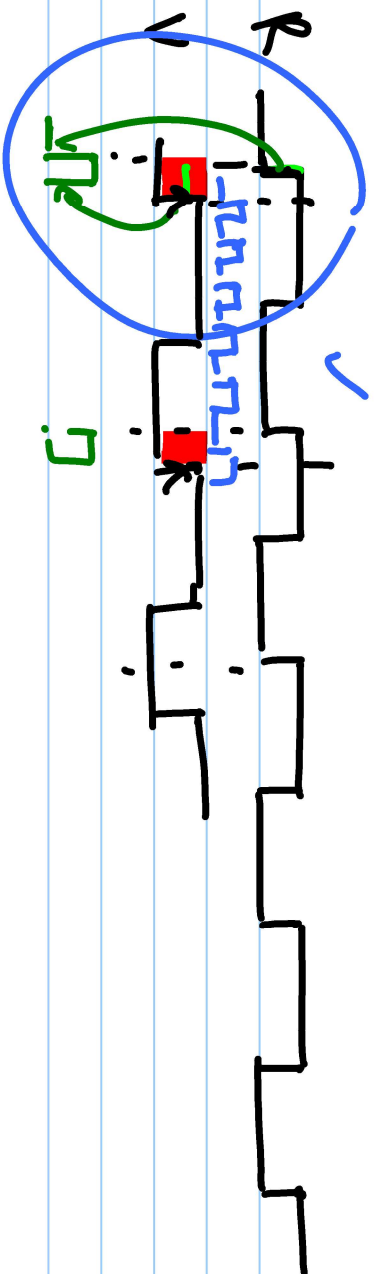

$$f_R = \frac{1023}{2041}$$


$$2041 T_V = 1023 T_R$$

Time-to-Digital Converter (TDC)

$R$   $V$   $\rightarrow$  TDC  $\rightarrow$  digital output of Counter


Ex:  $R_{ref} = 100 \text{ MHz}$ .  $5.001 \text{ GHz}$ .
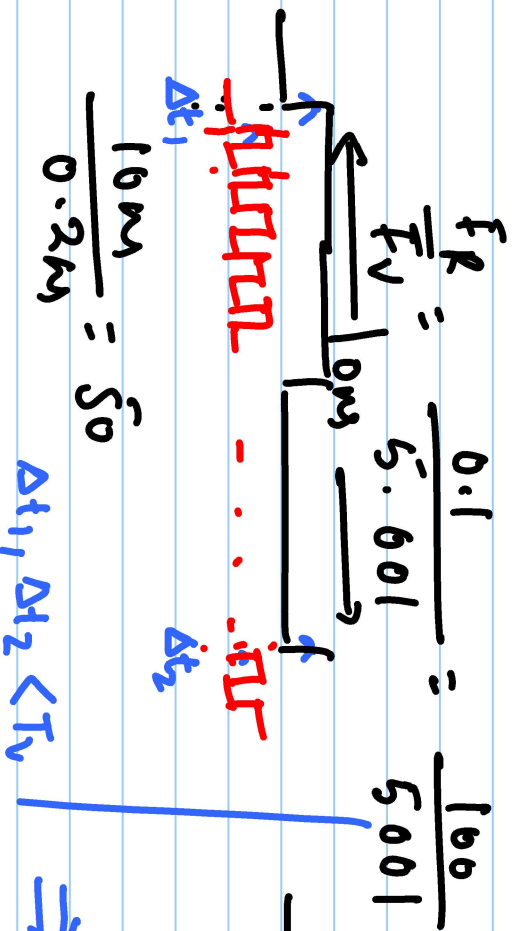
$$T = \frac{1}{5.001 \text{ GHz}} = 199.96 \text{ ps}$$



$$\frac{10 \text{ ns}}{0.2 \mu\text{s}} = 50$$

$\Delta t_1, \Delta t_2 < T_V$

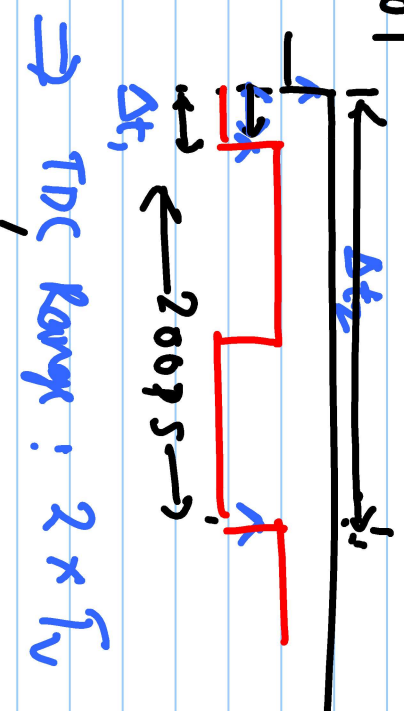

$\Rightarrow$  TDC Range:  $2 \times T_V$

---

$$50 \times T_v + \underbrace{\Delta t_1} + \underbrace{\Delta t_2} = T_R$$

.