
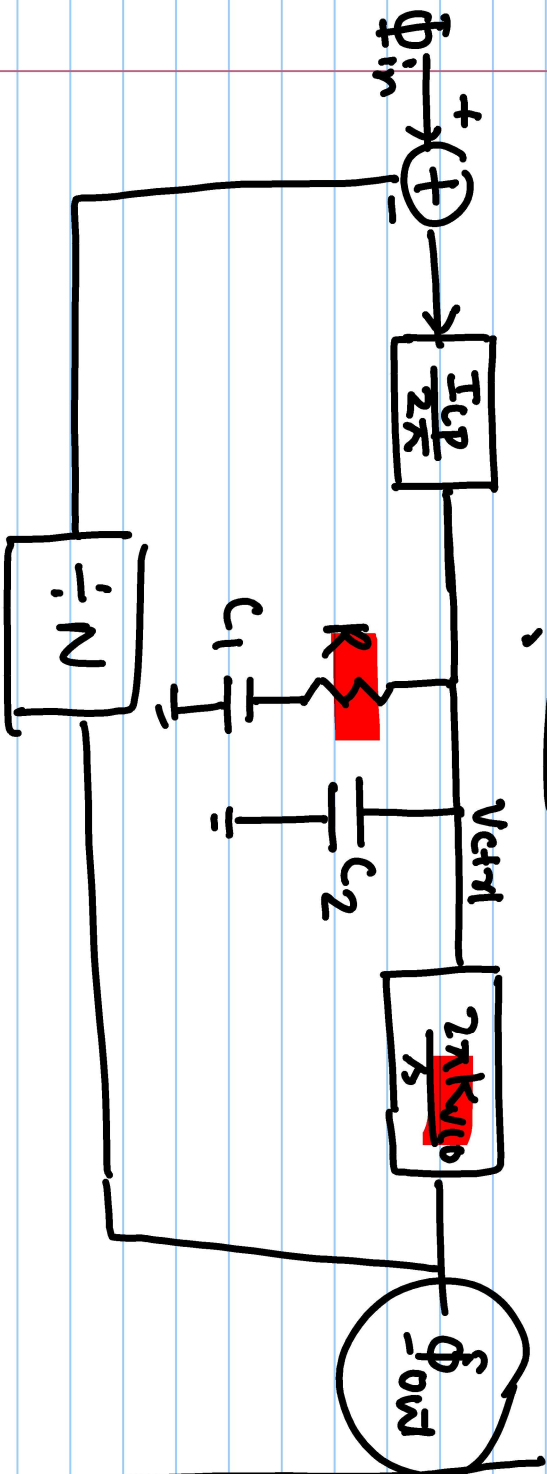


Lecture # 20

Charge-pump PLL

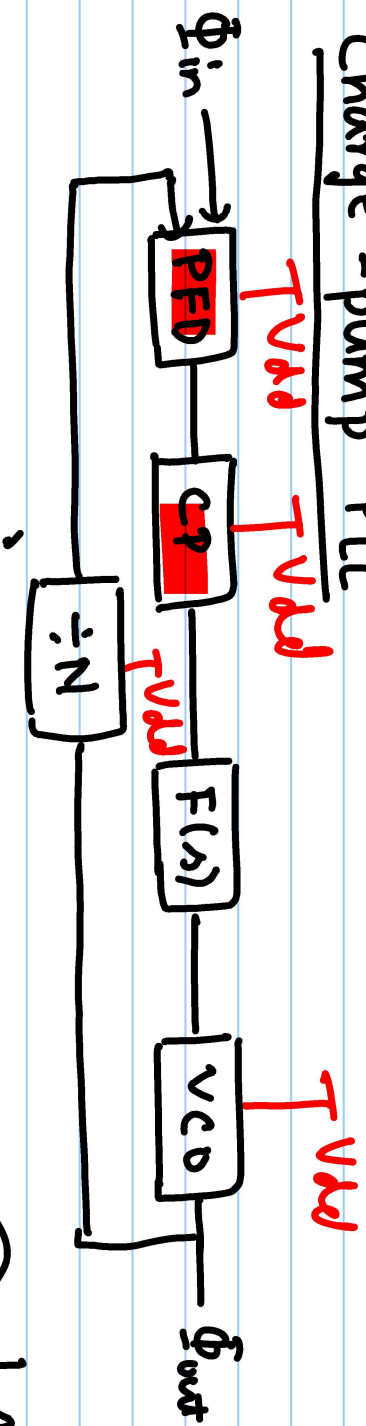

$$\omega_{p1} = \omega_{p2} = 0, \quad \omega_{p3} = \frac{1}{RC_1C_2/C_1K_2}$$

$$\omega_z = 1/RC_1$$

1. ω_u : unity gain
freq. Phase margin
2. $\frac{C_1}{C_2} = f(\tan(\phi_m)) = K_c$
 $\omega_u^2 = \omega_z \cdot \omega_{p3}$
3. Choose R.
 $C_1 = \frac{1}{\omega_z \cdot R}$
 $C_2 = C_1 / K_c$

4. $|k_v| = 1 \Rightarrow T_{ep}$.
For given k_{vco}


Noise Analysis of CP-PLL

Extrinsic Noise Source

Intrinsic Noise Sources.

1. Supply Noise
2. Substrate Noise.
3. Ref. Noise.


1. Thermal Noise
2. flicker Noise.

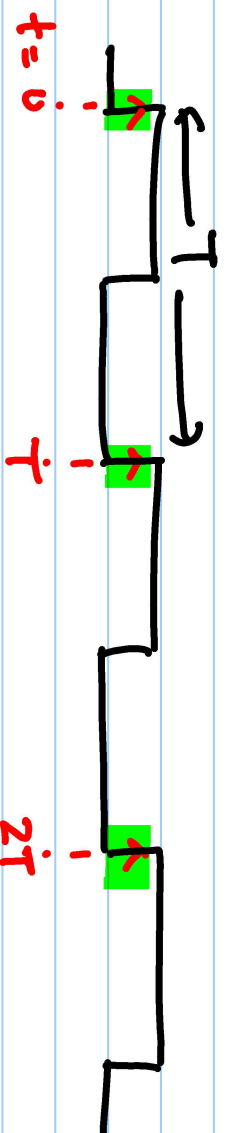

Jitter : any deviation in clocking events w.r.t absolute time.
 $(\Delta t) \rightarrow \Delta \Phi$

Noise Source




1. Resistor

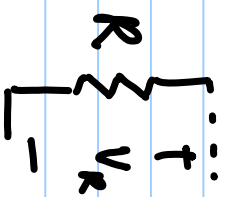


$$|S_R(f)| = \frac{4kTR}{R} \text{ (V}^2/\text{Hz)}$$

K: $1.38 \times 10^{-23} \text{ J/K}$

T: Temp. in Kelvin.

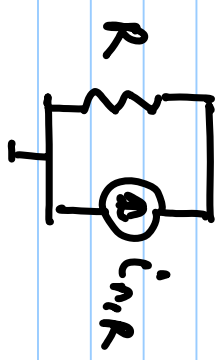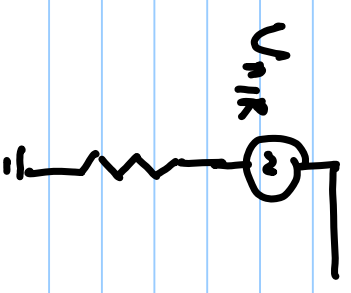
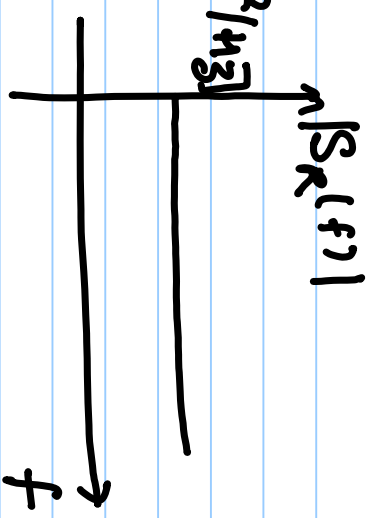


$$|S_{R,i}(f)| = \frac{4kT}{R}$$

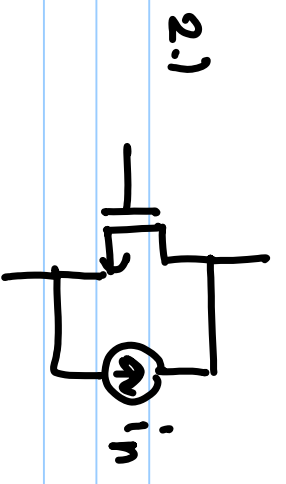


$$S_{i_n}(f) = 4kT \gamma g_m \quad [A^2/Hz]$$

$$\gamma: \frac{2}{3} - 2$$

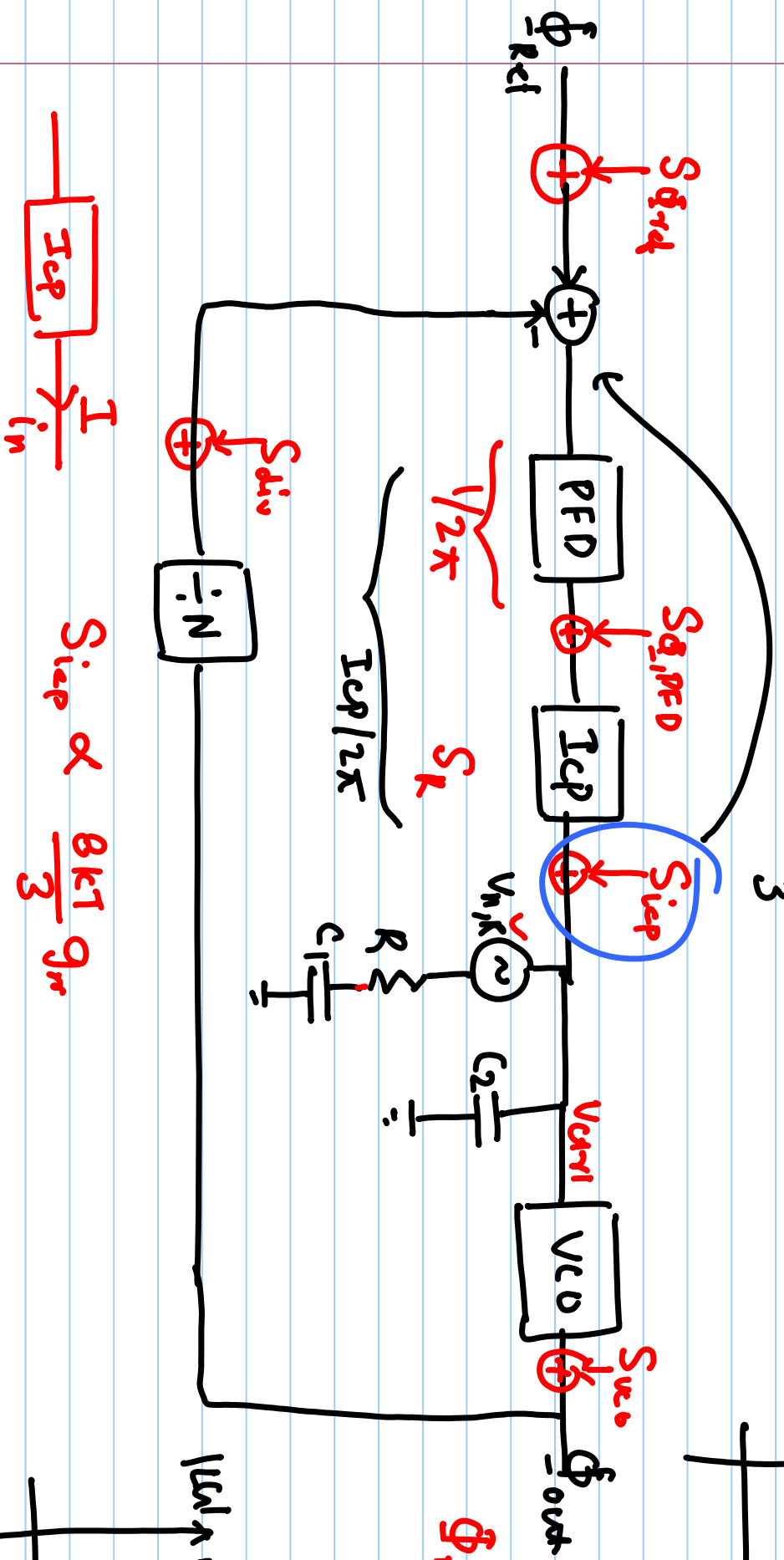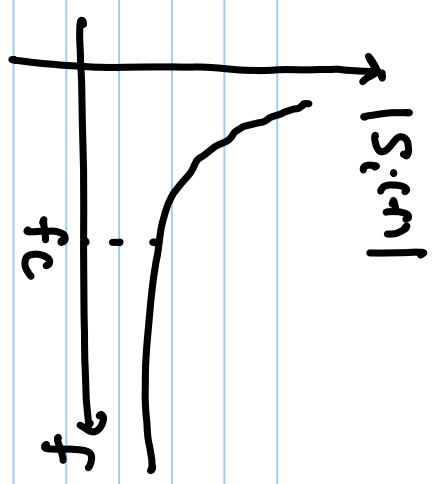

$\Phi_{n,out}$


$$S_{i_{cp}} \propto \frac{8kT}{3} g_m$$

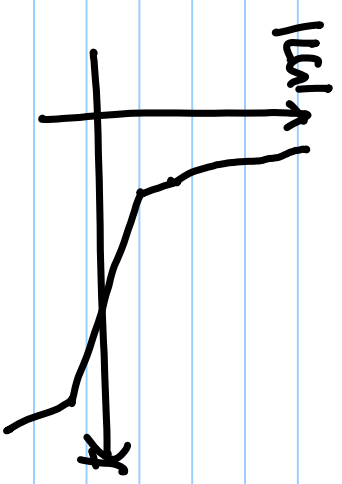

Noise Transfer Function (NTF)


$$L_n(s) =$$

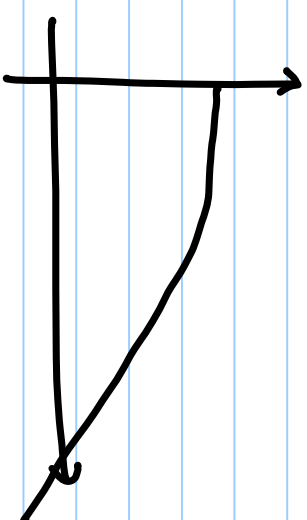1. $\Phi_{n,rd} : NTF_{rd} = \frac{\Phi_{n,out}}{\Phi_{n,rd}} = \frac{N_x L_n}{1 + L_n}$




2. $S_{n,PEB} : NTF_{PEB} =$

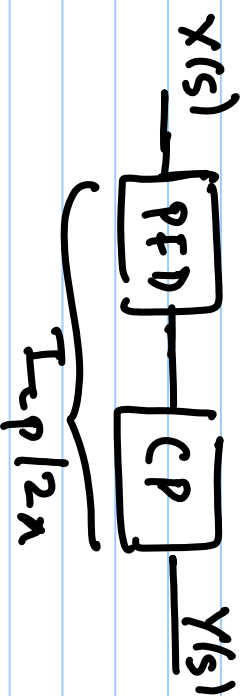3. $S_{n,Icp} : NTF_{Icp} = \frac{2K}{I_{cp}} NTF_{rd}$



$$\frac{I_{cp}}{2K} \cdot X(s) = Y(s)$$


$$X(s) = \frac{2K}{I_{cp}} Y(s)$$

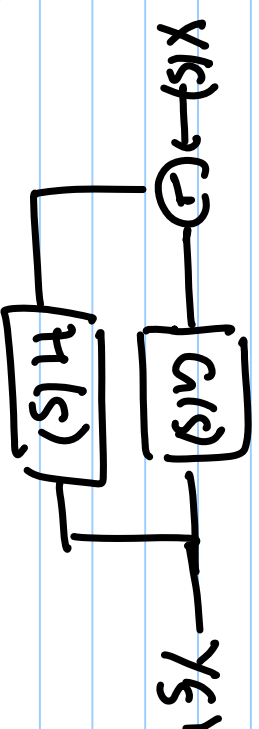

$$\frac{Y(s)}{X(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

$$L_n = G(s)H(s)$$
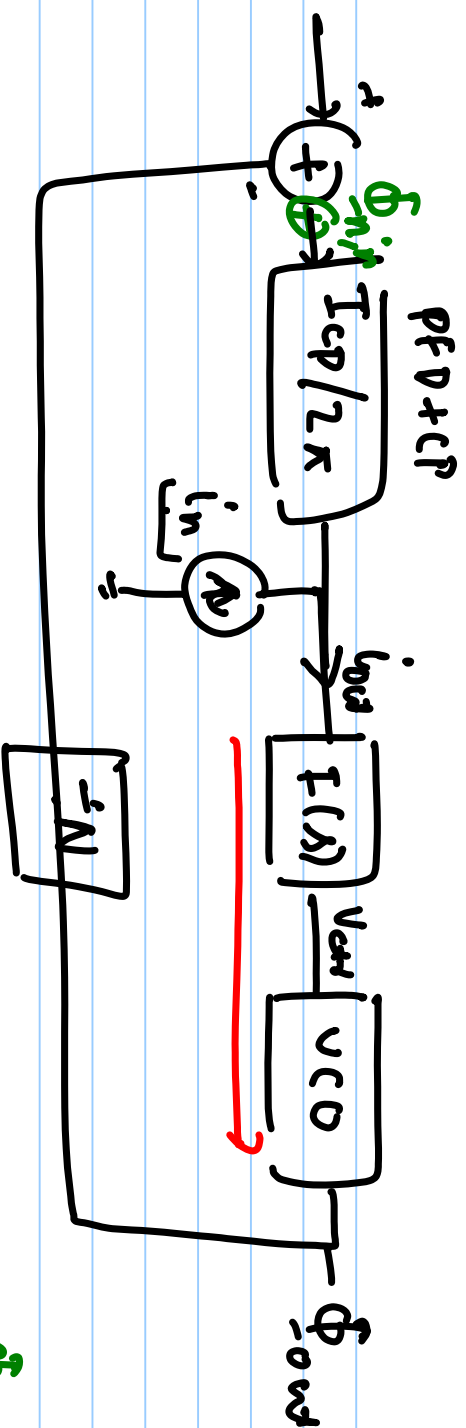
$$\frac{Y(s)}{X(s)} = \frac{L_n/H(s)}{1 + L_n}$$



$$\frac{\Phi_{out}}{I_n} = \frac{F(s) \frac{2\kappa K_{VCC}}{s}}{1 + L_n}$$

$$\Phi_{n,in} \times \frac{I_{cp}}{2\kappa} = I_n$$

$$\Phi_{n,in} = \frac{2\kappa}{I_{cp}} I_n$$


$$\frac{\Phi_{out}}{I_n} = \frac{\Phi_{out}}{\Phi_{n,in} \times \frac{I_{cp}}{2\kappa}} = \frac{2\kappa}{I_{cp}} \times \frac{\Phi_{out}}{\Phi_{n,i}} = \frac{2\kappa}{I_{cp}} \frac{N \times L_n}{1 + L_n}$$

$$= \frac{2\kappa \times N}{I_{cp}} \frac{\frac{I_{cp}}{2\kappa} \times \frac{1}{N} F(s) \frac{2\kappa K_{VCC}}{s}}{1 + L_n}$$

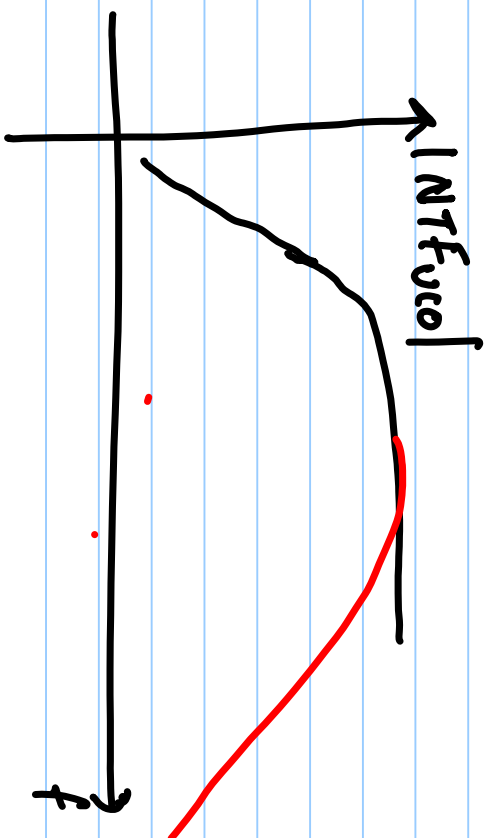
4. VCO Noise

$$NTF_{VCO} = \frac{\Phi_{n, out}}{\Phi_{n, vco}} = \frac{1}{1 + LC_n}$$

$$\frac{1}{1 + \frac{\alpha(1+s/\omega_2)}{s^3}}$$



5. Resistor Noise

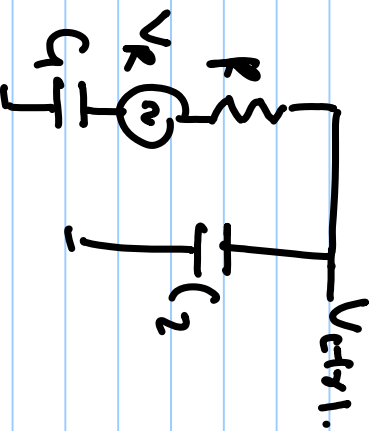

$$\frac{V_{err1}}{V_{n,R}} = \frac{1/sC_2}{R + 1/sC_1 + 1/sC_2} = H_R$$

$$NTF_R = \frac{\Phi_{out}}{V_{n,R}} = \frac{\Phi_{out}}{V_{err1}/H_R} = H_R \cdot \frac{\Phi_{out}}{V_{err1}}$$

$$\begin{aligned} NITR_R &= H_R \cdot \frac{2R_{K_{VCO}}}{\lambda} \cdot \frac{1}{1+L_R} \\ &= H_R \frac{2R_{K_{VCO}}}{\lambda} NITR_{VCO} \end{aligned}$$