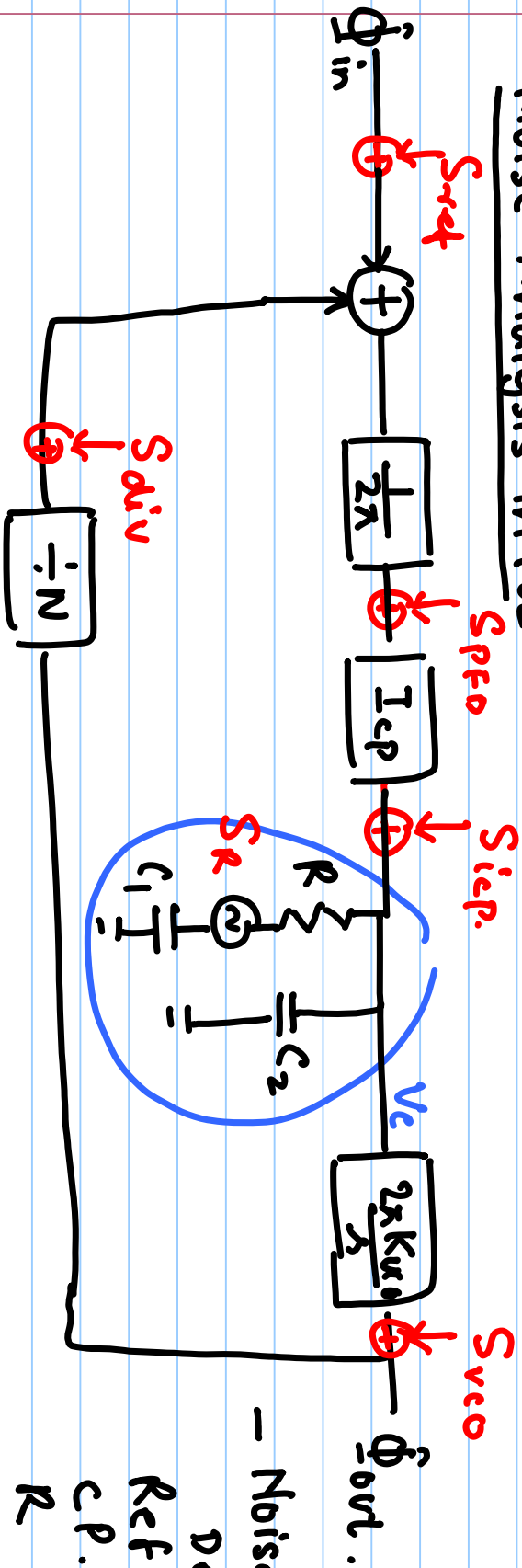


Lecture # 21

Noise Analysis in PLL




- Noise Power Spectral Density

Ref. c.p.
R

Noise Transfer functions (NTF)

$$\text{Ref. } NTF_{req} = \frac{N \times L_n}{1 + L_n} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} NTF_{vco} = \frac{1}{1 + L_n} \gamma$$
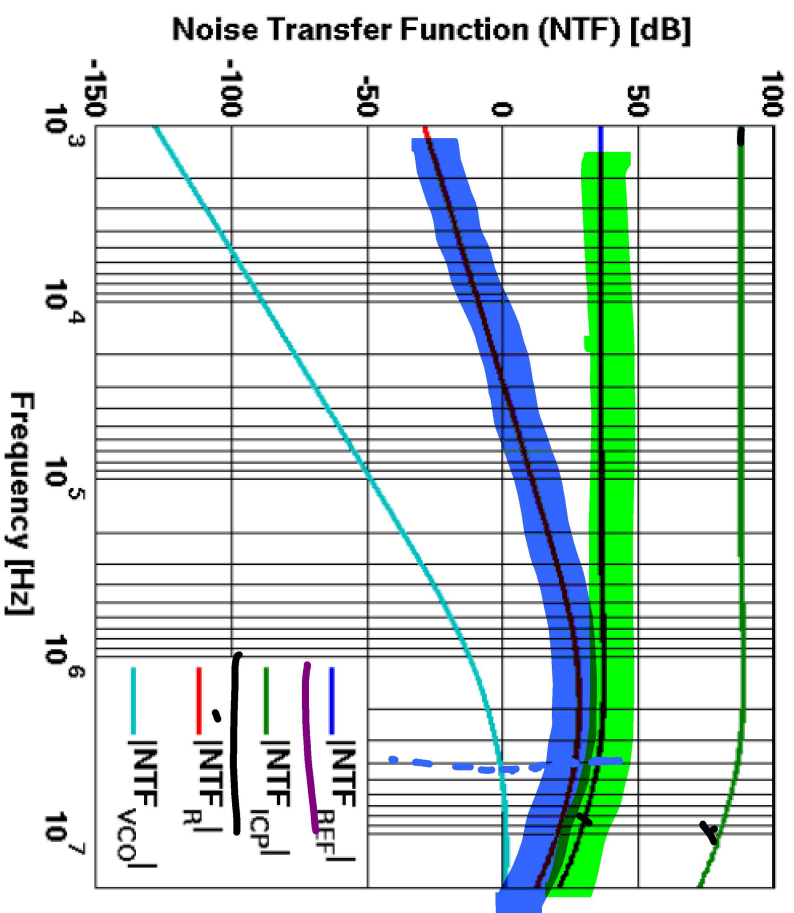
$$NTF_{cp} = \frac{2\pi}{I_{cp}} NTF_{req} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} NTF_R = H(s) \frac{2\pi K_{vco}}{s} NTF_{vco}$$



$$f_{\text{ref}} = 40 \text{ MHz}$$

$$K_{\text{VCO}} = 100 \text{ MHz/V}$$

$$R = 1 \text{ k}\Omega$$

$$\omega_{\text{M}_N} = 2\pi f_{\text{ref}} / 10 = 2\pi \times 4 \text{ Mrads}$$

$$\angle \Phi_m = 70^\circ, N = 64$$

$$C_1, C_2, T_{\text{cp}}$$

$$\underline{L_{\text{ca}}}$$


$$f_{\text{out}} = 64 \times 40 \text{ MHz}$$

$$= 2.56 \text{ GHz}$$

$$S_{\text{total}} = S_{\text{ref}} |NTE_{\text{ref}}|^2 + S_{\text{icp}} |NTE_{\text{icp}}|^2 + S_{\text{R}} |NTE_{\text{R}}|^2 + S_{\text{vco}} |NTE_{\text{vco}}|^2$$


Total Noise Power ($\overline{\Phi}_{n,\text{total}}^2$)

$$\overline{\Phi}_{n,\text{total}}^2 = \int S_{\text{total}} \cdot df \quad \left| \begin{array}{l} \text{trapz command} \\ \text{in Matlab.} \end{array} \right.$$

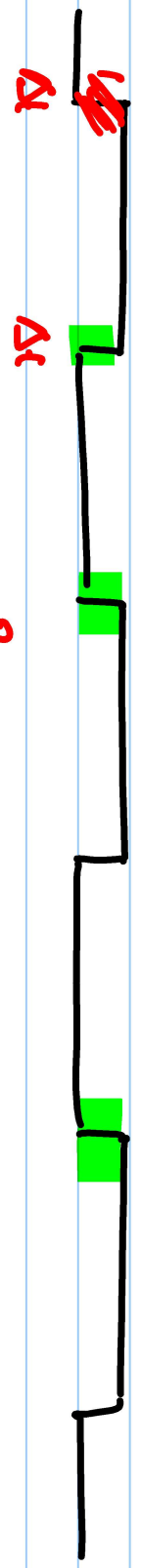

$$\Delta t \rightarrow \left(2k \cdot \frac{\Delta t}{T_{\text{vco}}} \right)^2$$

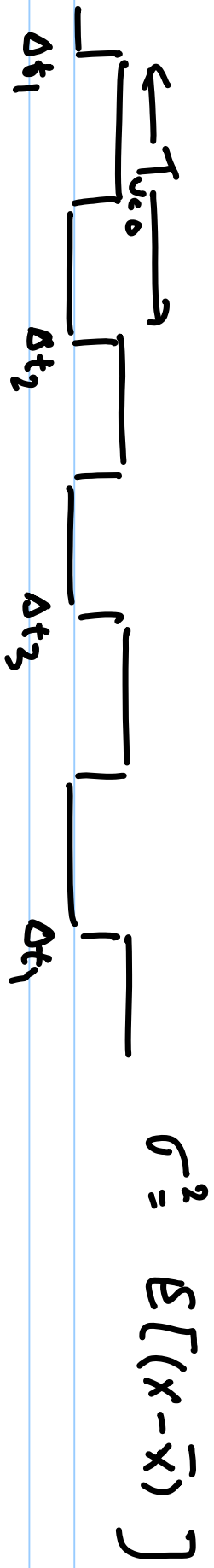
$$\sigma_{\Delta t}^2 = \left(\frac{T}{2k} \right)^2 \overline{\Phi}_{n,\text{total}}^2 \Rightarrow \sigma_{\Delta t} = \frac{T}{2k} \sqrt{\int S_{\text{total}} \cdot df}$$




$$\sigma_{\Delta t}^2 = \frac{1}{N} \sum_{k=0}^{N-1} (\Delta t(k) - \bar{\Delta t})^2$$

$\sigma_{\Delta t}$: r.m.s jitter at o/p clock.

$$\sigma_{\Delta t} = 0.8 \text{ ps}$$

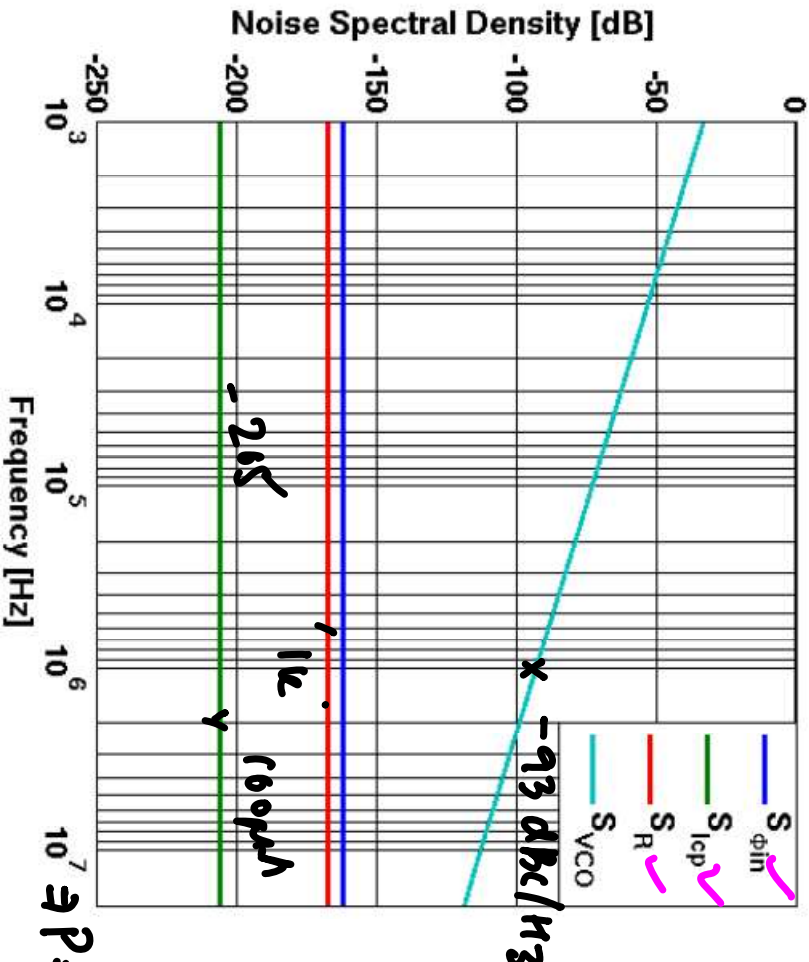

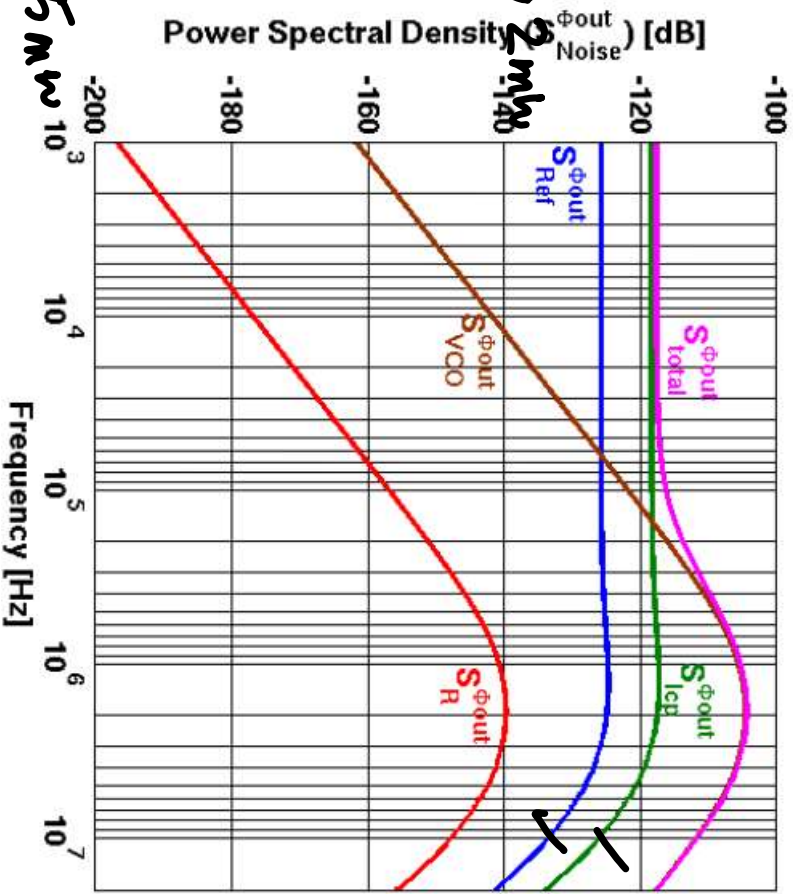$-93 \text{ dBc/Hz} \rightarrow 2 \text{ mHz}$



$$AP = 5 \text{ mW}$$



$$P = 5 \text{ mW}$$

$\omega_n, \beta_m, K_{vco}, R \rightarrow C_1, C_2, I_{cp}$

Noise contribution of all blocks.

$\sigma_{oi} \text{ @ } 0 \text{ dB} \rightarrow L_{ps}$



Power const! $\rightarrow 3 \text{ ps}$

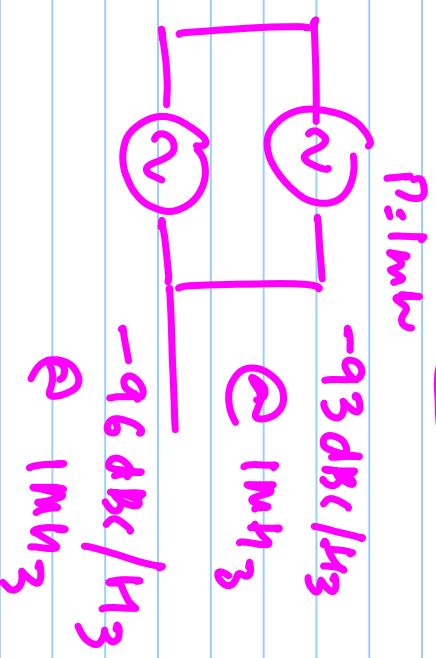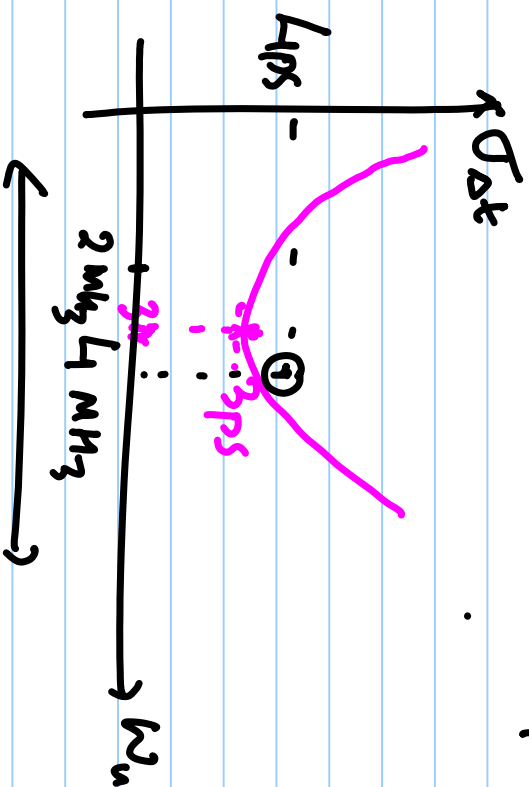

$$\left(\frac{2\pi}{I_{cp}} \right)^2 \frac{20kT}{3} g_m$$

$$\frac{4R^2}{I_{cp}^2} \times \frac{8kT}{3} \times \frac{2I_{cp}}{V_{ov}}$$

VCO Phase Noise

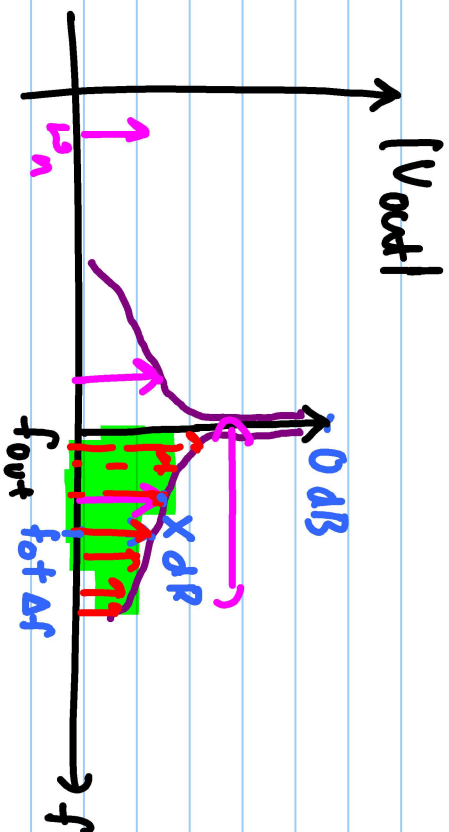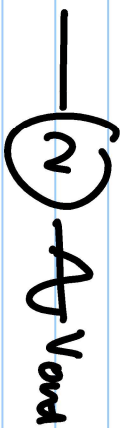

(0-X) dBc/Hz @ Δf

$$V_{out} = \sin(\omega_0 t + K_{VCO} \int V_c \cdot dt) \quad -93 \text{ dBc/Hz @ } 1 \text{ MHz}$$

$$= \sin(\omega_0 t + K_{VCO} \int A_n \sin(\omega_n t) \cdot dt)$$

$$= \sin(\omega_0 t + \underbrace{K_{VCO} A_n}_{\omega_n} (-\cos(\omega_n t)))$$

$$= \sin(\omega_0 t - \alpha \cdot \cos(\omega_n t))$$

$$= \sin(\omega_0 t) \cdot \cos(\alpha \cdot \cos(\omega_n t)) - \cos(\omega_0 t) \cdot \sin(\alpha \cdot \cos(\omega_n t))$$

$$= \sin(\omega_0 t) \cdot 1 - \cos(\omega_0 t) \cdot \alpha \cdot \cos(\omega_n t)$$

$$= \sin(\omega_0 t) - \frac{\alpha}{2} \left[\cos(\underbrace{\omega_0 + \omega_n}_t) + \cos(\underbrace{\omega_0 - \omega_n}_t) \right]$$