
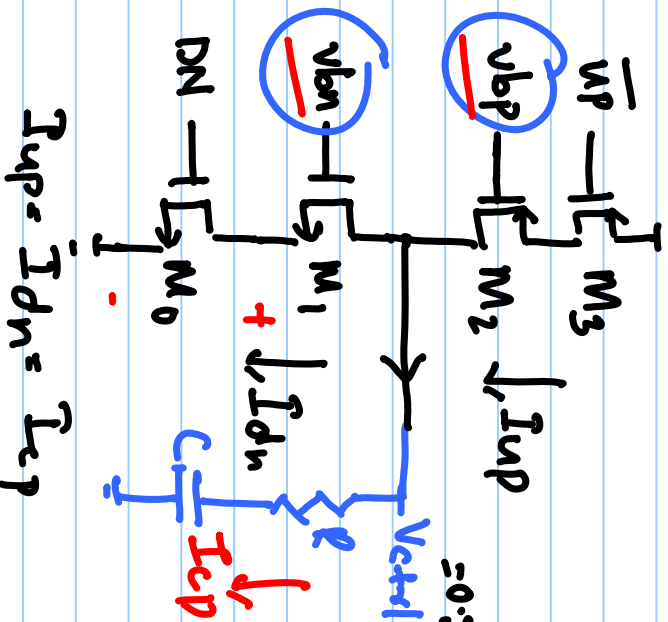


# Lecture #28

## Charge - Pump

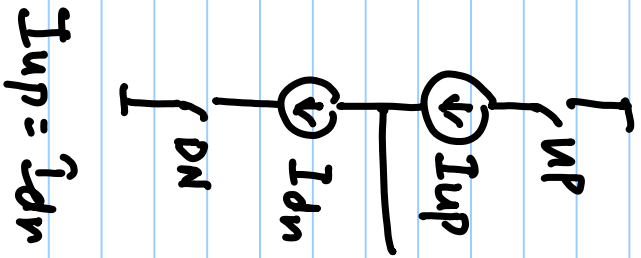1. Source - switched
2. Gate - switched
3. Drain - switched


$$I = \frac{kN}{2L} (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$$




$I_{up} = I_{dn} = I_{cp}$

$X$


$I_{cp}, I_{cp}/2$



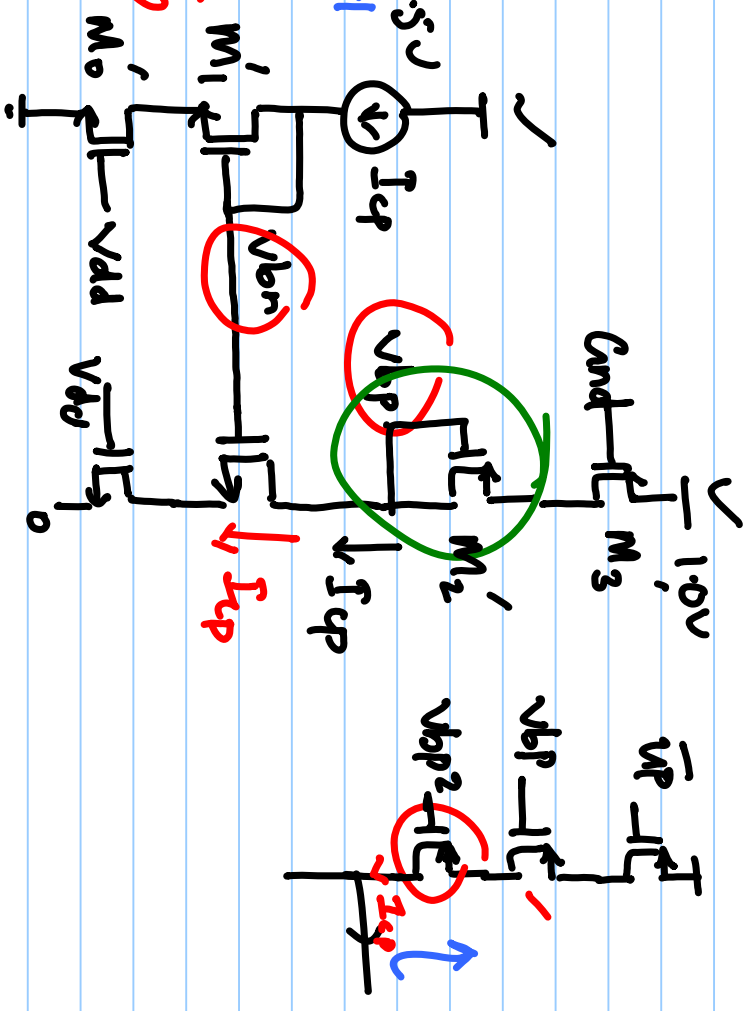


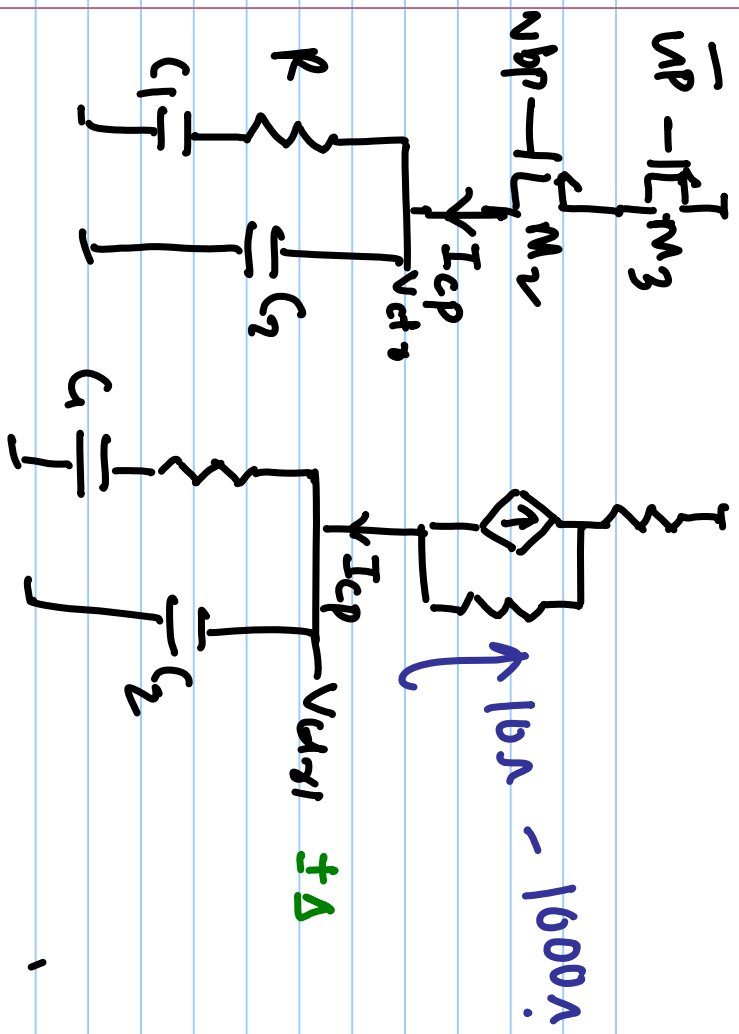



$$A_{v1} = \frac{1}{2} \left( \frac{1.0}{0.06} \right) \cdot \frac{1}{2} \left( \frac{4.0}{0.24} \right)$$

$$C_{gd1} < C_{gd2}$$

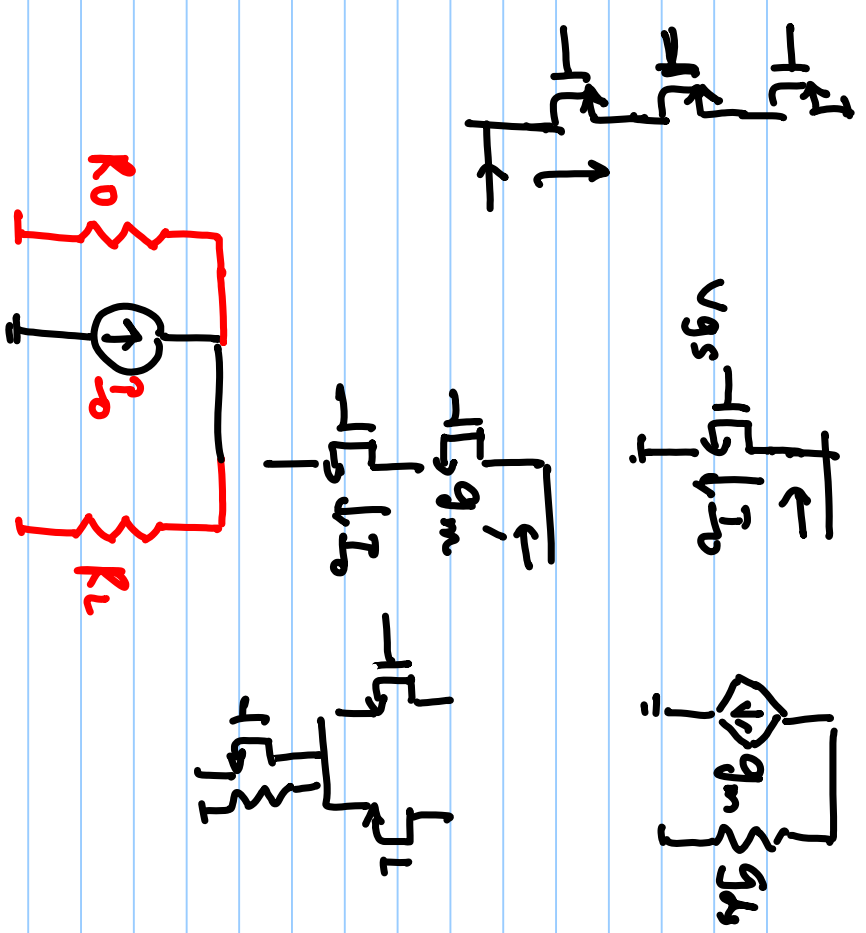

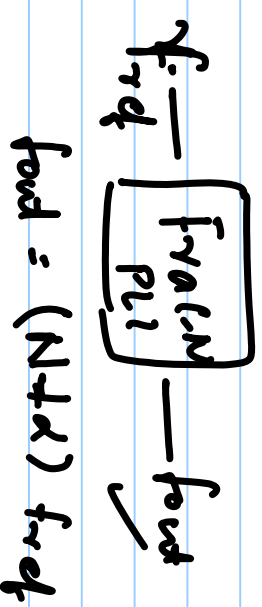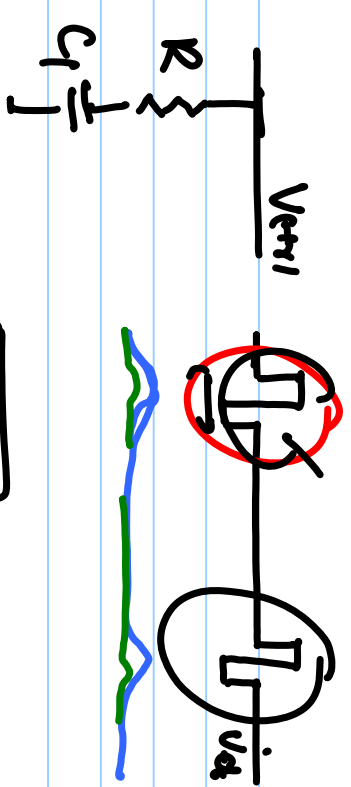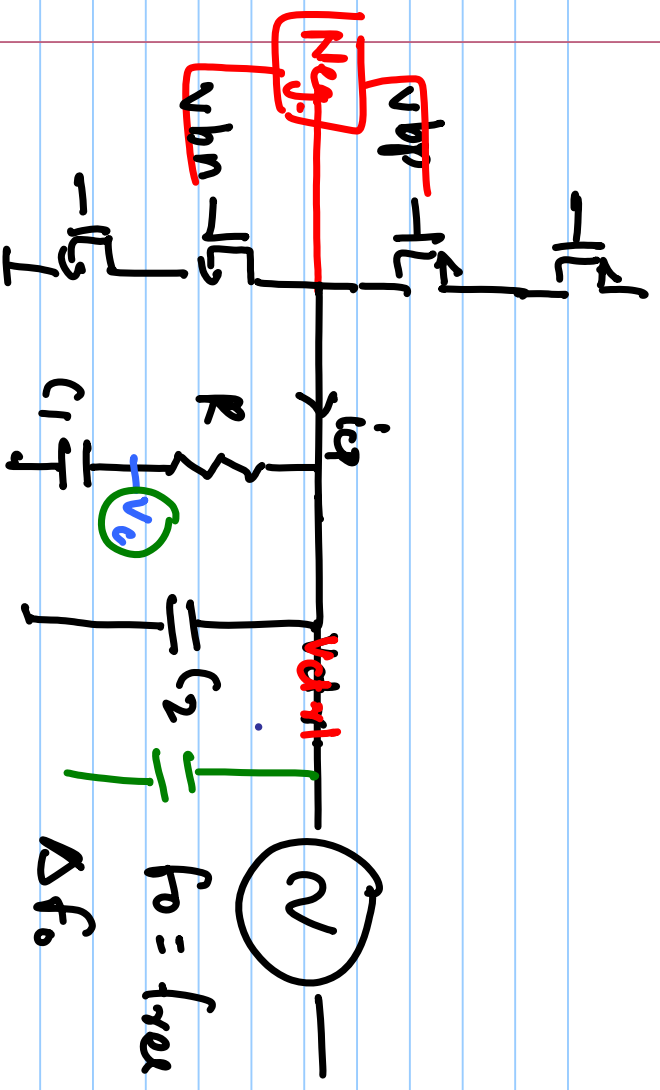

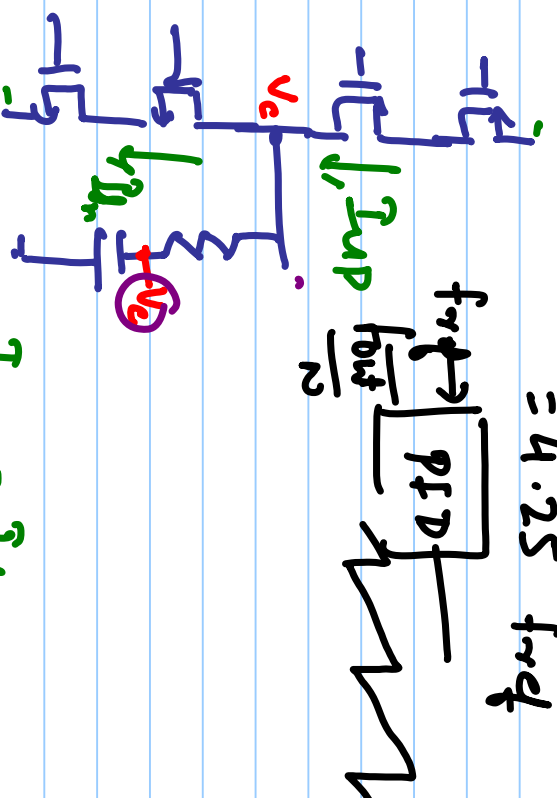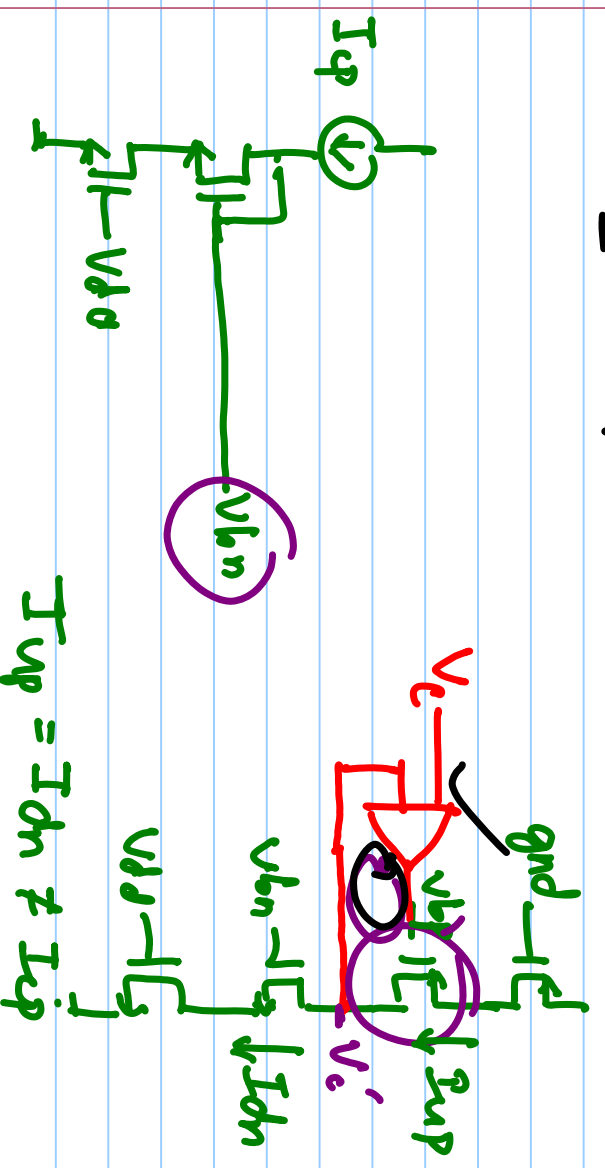$f_{out} = (N+K) f_{pd}$   
 $= 4.25 f_{pd}$



$$V_c = 0.5$$

$$f_{\text{out}} = 2.5 \text{ GHz}$$

$$\pm 0.25 \text{ V}$$

$$\pm 0.5 \text{ GHz}$$

$$0.675$$

$$2.75 \text{ GHz}$$

$$\sqrt{20 \mu\text{A}} \quad 18 \mu\text{A}$$

$$\sqrt{0.5} \rightarrow 0.625$$

$$\sqrt{20 \mu\text{A}} \quad 22 \mu\text{A}$$

$$I_{\text{up}} = I_{\text{dn}}$$

# Differential CP

