
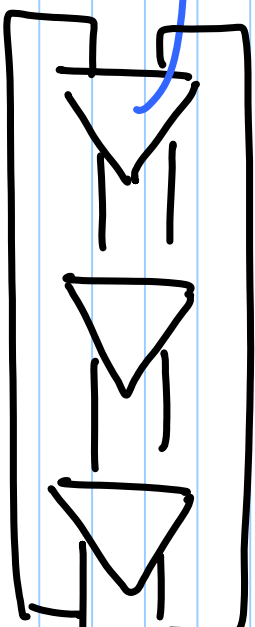


Lecture #33

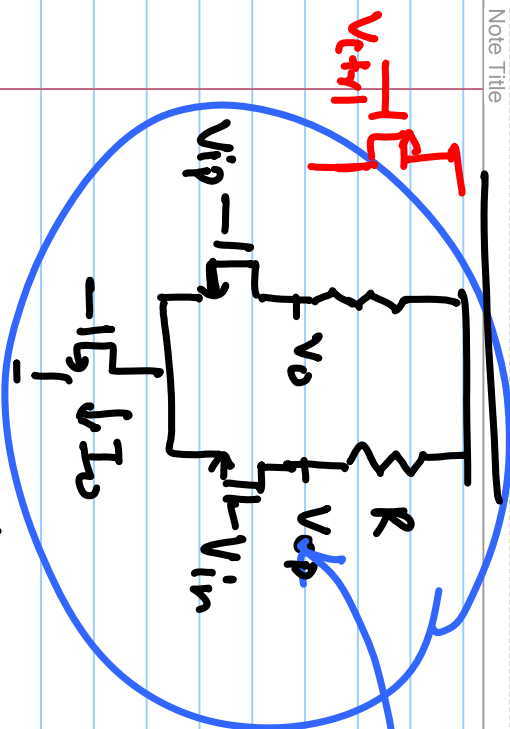

$$I = \frac{k_n}{2} (V_{gs} - |V_{tp}|) V_{SD} - \frac{V_{SD}^2}{2}$$


$$R \approx \frac{V_{SD}}{I} = \frac{k_n}{2} \frac{1}{(V_{gs} - |V_{tp}|)}$$

$$f_{osc} \propto \frac{1}{RC}$$

$$f_{osc} \propto -V_{cm}$$

$$V_{out} = I_0 R \propto \frac{1}{f_{osc}}$$

$$I_0 \propto \frac{1}{R}$$


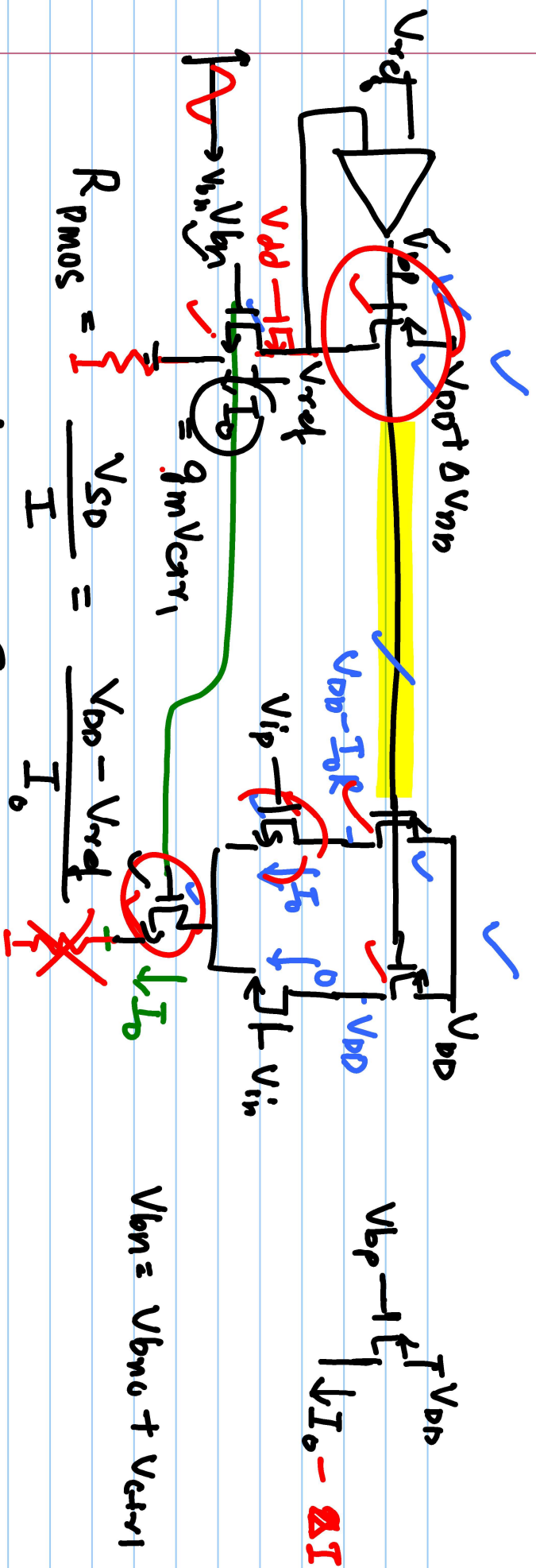


$$R_{PMOS} = \frac{V_{SD}}{I} = \frac{V_{DD} - V_{ref}}{I_0}$$


$$f_{osc} \propto \frac{1}{R} = \frac{I_0}{V_{DD} - V_{ref}} = \frac{g_m V_{ctrl1}}{V_{DD} - V_{ref}}$$

$$V_{out} = I_0 R = \frac{V_{DD} - V_{ref}}{I_0} \cdot I_0 = V_{DD} - V_{ref}$$

$$\Delta I = g_m V_{ctrl1}$$

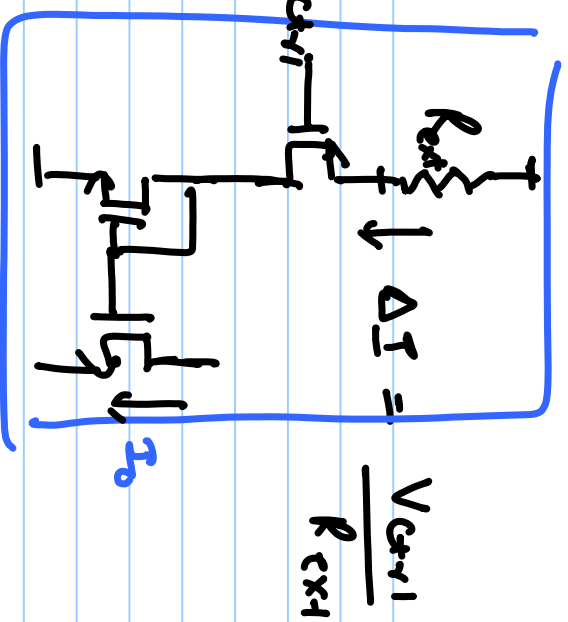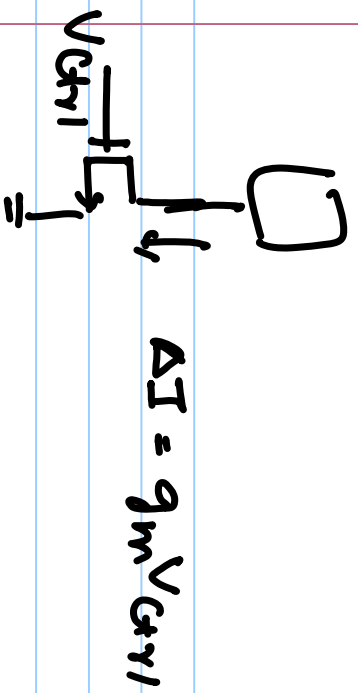

Power Supply Noise Rejection

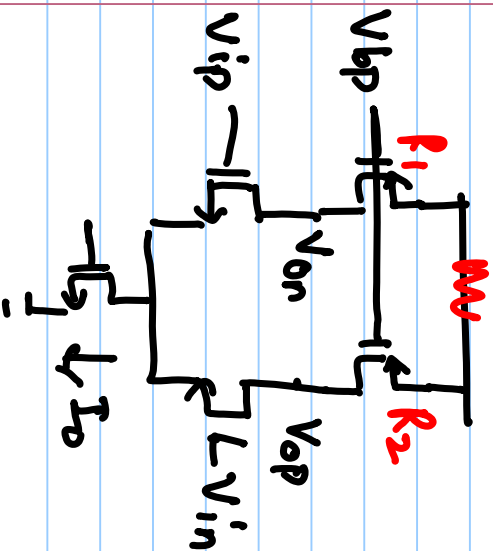


$$V_{op} = V_{DD} - \left(\frac{I_0 - \Delta I}{2}\right) R_2$$

$$V_{on} = V_{DD} - \left(\frac{I_0 + \Delta I}{2}\right) R_1$$

$$V_{op} = (V_{DD} + \Delta V_{og}) - \left(\frac{I_0}{2}\right) R_2 (1, \checkmark)$$

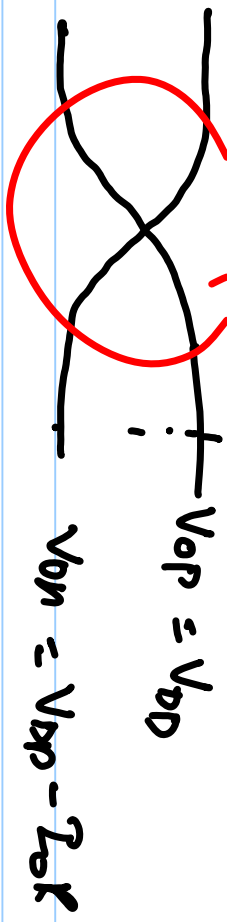
$$V_{on} = (V_{DD} + \Delta V_{on}) - \left(\frac{I_0}{2}\right) R_1 (1, \checkmark)$$



$$V_{op} = (V_{DD} + \Delta V_{DD}) - \left(\frac{I_0}{2} - \Delta I\right) R \left(\frac{I_0}{2} - \Delta I, V_{op} + \Delta V_{op}\right)$$

$$V_{on} = (V_{DD} + \Delta V_{DD}) - \left(\frac{I_0}{2} + \Delta I\right) R \left(\frac{I_0}{2} + \Delta I, V_{on} - V_{op}\right)$$



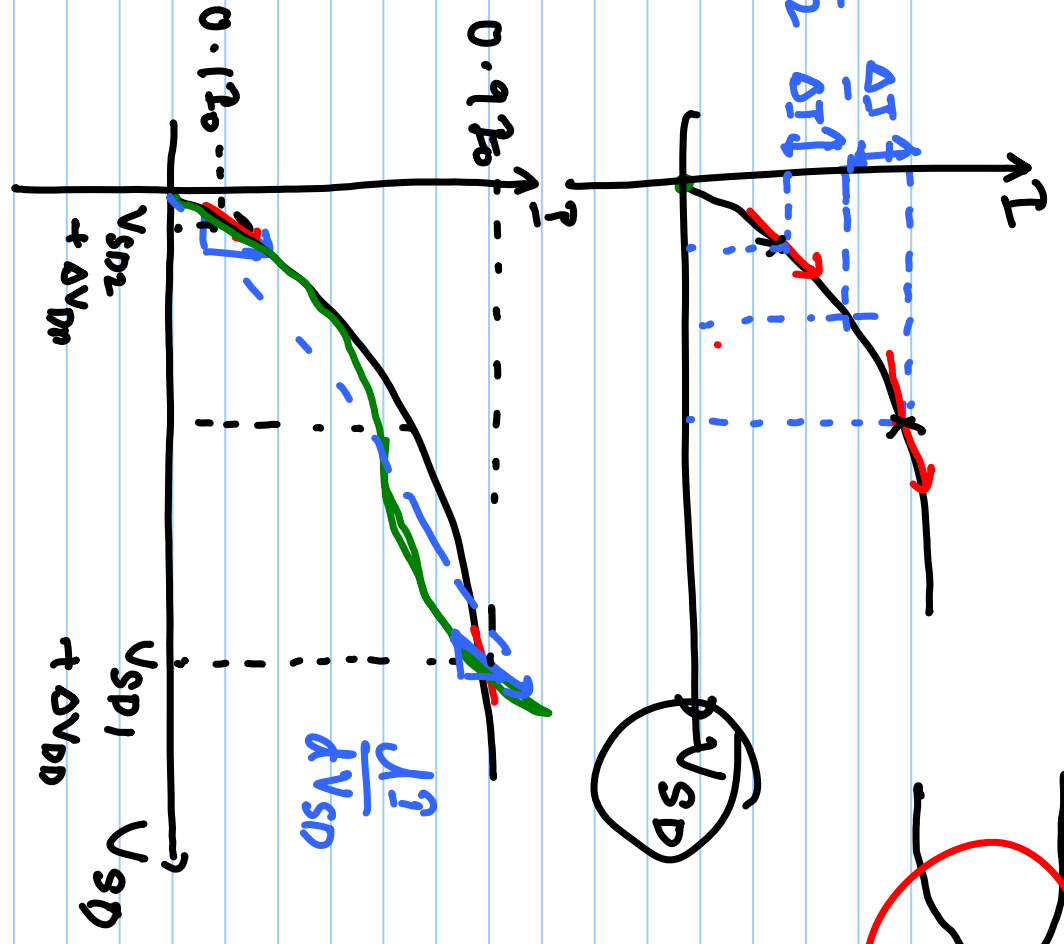
$$V_{op} - V_{on} = \Delta I \left[R \left(\frac{I_0}{2}, V_{SD1}\right) - R \left(\frac{I_0}{2}, V_{SD2}\right) \right]$$



$$I = \frac{K \mu C}{L} \left((V_{DD} - V_{tp}) - V_{SD} - \sqrt{\frac{V_{SD}^2}{2}} \right) V_{on} - I_0$$

$$V_{op} = V_{DD} + \Delta V_{DD}$$
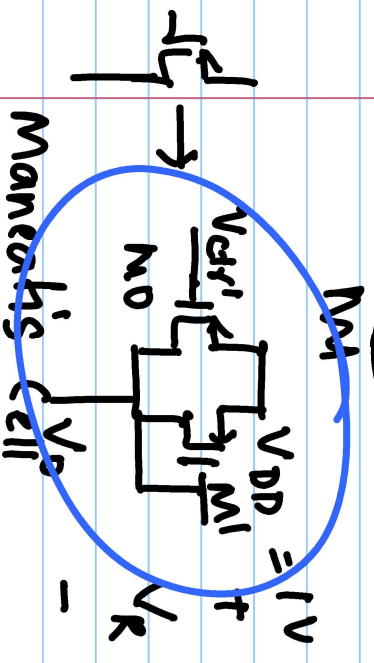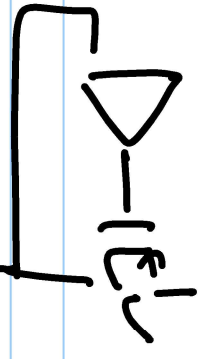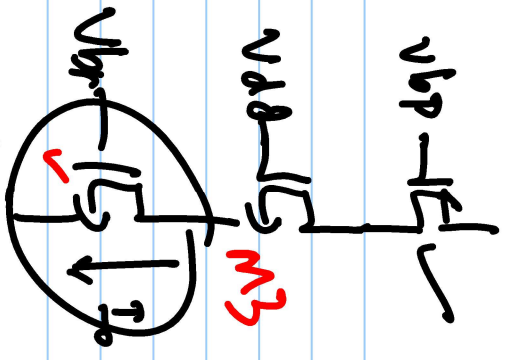
$$V_{on} = V_{DD} - I_0 \cdot R \left(\frac{I_0}{2} + \Delta I, V_{SD1} + \Delta V_{DD} \right)$$



Maneathis cell
 $V_R = 0, V_D = V_{DD}$
 $V_R = 10mV, V_D = 0.99V$

