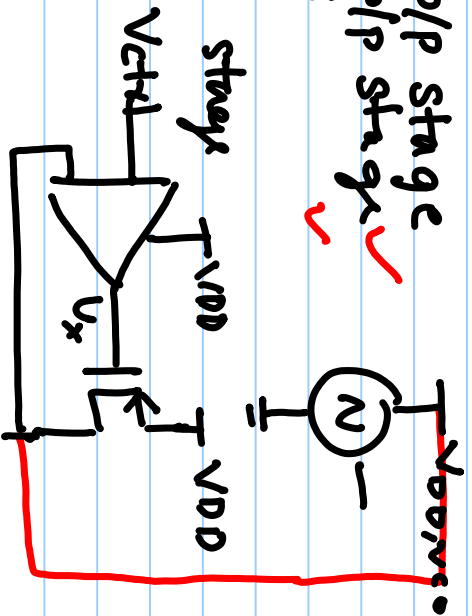



Lecture # 36

Power Supply regulation of VCO (Ring Osc.)

1. NMOS i/p amp + NMOS o/p stage
2. NMOS i/p amp + PMOS s/p stage
3. PMOS i/p + NMOS o/p stage
4. PMOS i/p + PMOS stage





$$\frac{V_{DD, VCO}}{V_{DD}} =$$

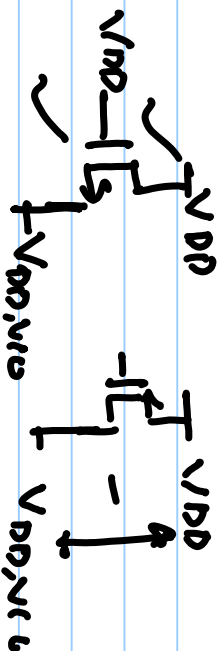


* Max. supply $\leq V_{DD}$

$V_{DD, VCO}$ for NMOS

NMOS i/p amp. + PMOS o/p stage.

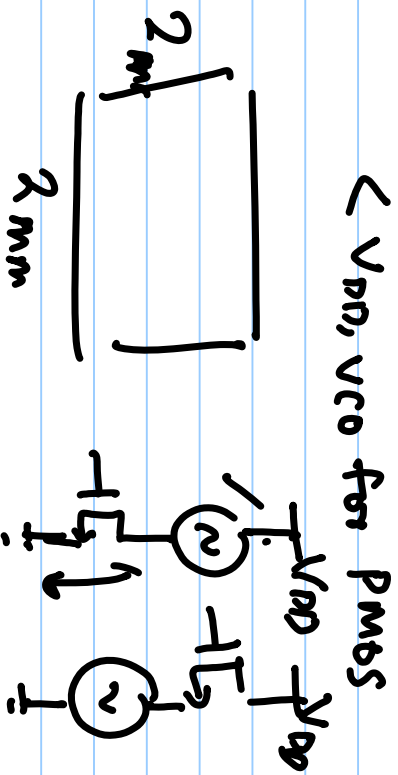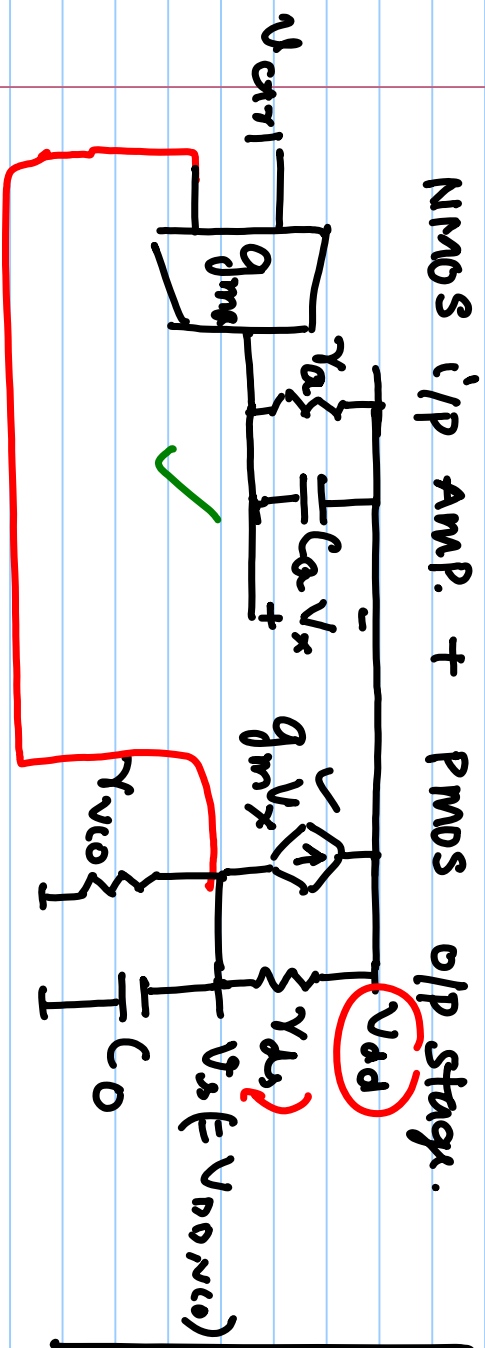

$$\sqrt{\Phi_{out}(s)} = \underbrace{\Phi_{out}(s)}_{V_2(s)} \cdot \underbrace{\frac{V_2(s)}{V_{dd}(s)}}_{|G_{dd}(s)|}$$

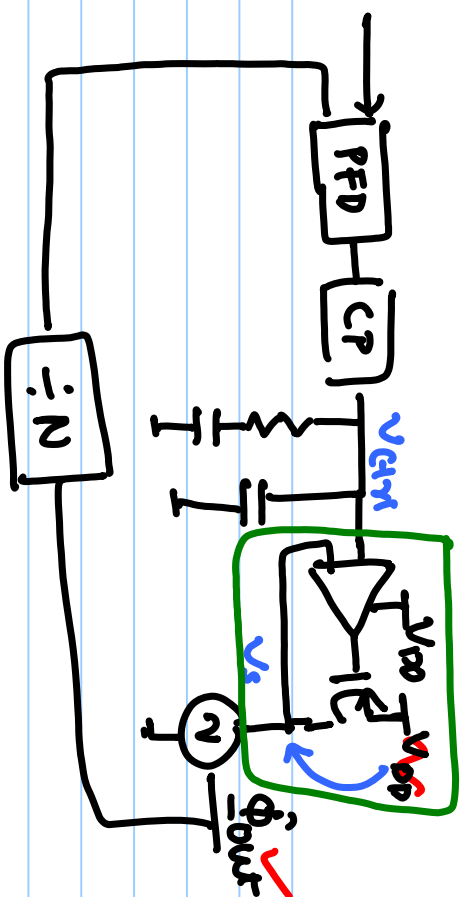

$$\frac{V_2(s)}{V_{dd}(s)} = \frac{S_{Vdd}}{(1+s/\omega_2) (1+L_{reg})}$$

$$S_{Vdd} = \frac{\gamma_{vco}}{\gamma_{vco} + \gamma_{ds}}, \quad \omega_2 = \frac{1}{(\gamma_{ds} || \gamma_{vco}) C_0}, \quad \omega_A = \frac{1}{\gamma_a C_a}$$

$$L_{reg} = \frac{A_a \cdot A_0}{(1+s/\omega_a) (1+s/\omega_0)}, \quad A_a = g_m \gamma_a, \quad A_0 = g_m (\gamma_{ds} || \gamma_{vco})$$



$$\frac{V_{s2}(s)}{V_{dd}(s)} = \frac{S_{VDD} (1+s/\omega_a)}{A_a A_o + (1+s/\omega_a) (1+s/\omega_o)} \quad \checkmark f(\omega_{reg})$$


$$\frac{V_s}{V_{DD}} = \frac{S_{VDD}}{A_a A_o + 1}$$

$$\frac{V_s(s)}{V_{s+1}(s)} = \frac{L_{nreg}}{1+L_{nreg}}$$

$$\frac{\Phi_{out}(s)}{V_{s2}(s)} = \frac{2\pi K_{VCO}}{s} \frac{1}{1+L_{npi1}}$$


$$L_{npi1}(s) = \frac{I_{cp}}{2\pi N} \frac{1+sRC_1}{s^2 C_1 (1+sC_1(s_2))} \times 2\pi K_{VCO}$$
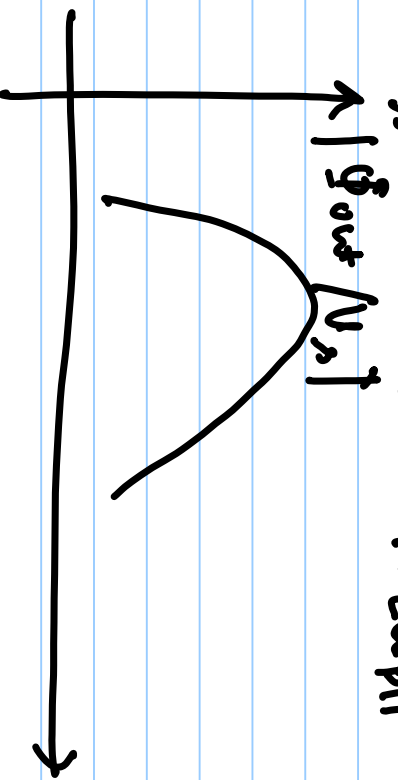
$$\times \left(\frac{L_{nreg}}{1+L_{nreg}} \approx \frac{1}{1+s/\omega_{reg}} \right)$$




* $\omega_{reg} < \omega_{pi10}$
 Φ_m

— Noise contribution, — VCO noise

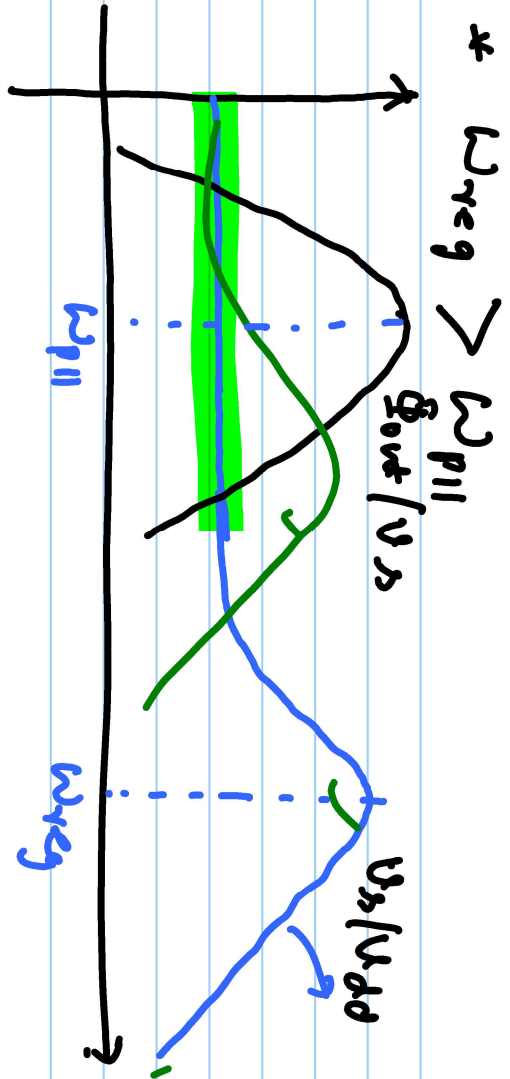

$\omega_{reg} = 10 \times \omega_{p11}$

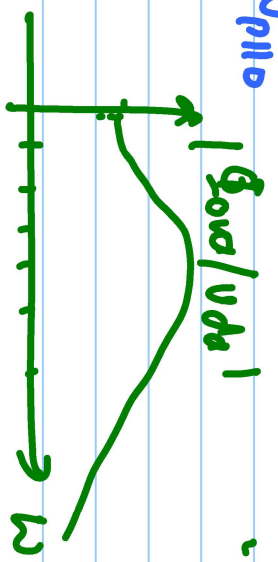

$\frac{\Phi_{out}}{U_{ad}} =$

