
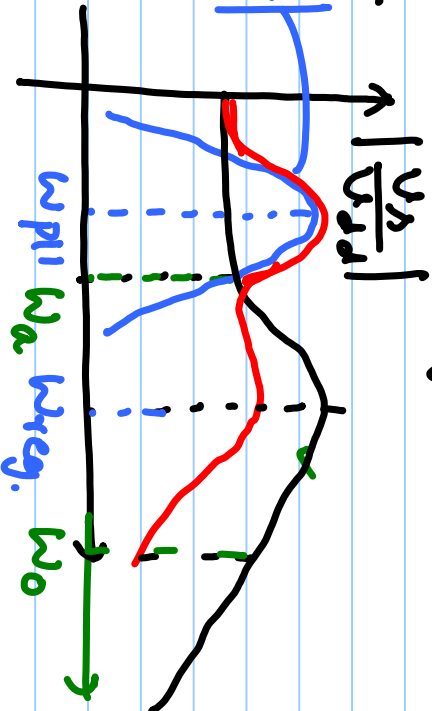

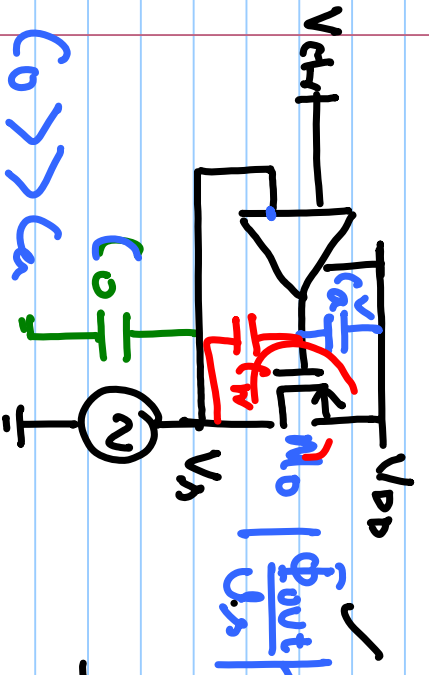
# Lecture # 37

Power Supply Regulation for ring oscillators.




$$\frac{V_3}{V_{DD}} = \frac{S_{vdd}}{(1 + LC_{reg})(1 + \frac{s}{\omega_0})}$$

$$\frac{\Phi_{out}}{V_{DD}} = \frac{V_3}{V_{DD}} \times \frac{\Phi_{out}}{V_3}$$


$\omega_{reg} > \omega_{PII}$

$$\omega_0 = \frac{1}{(r_{vcol} | Y_{ds} ) C_o}$$

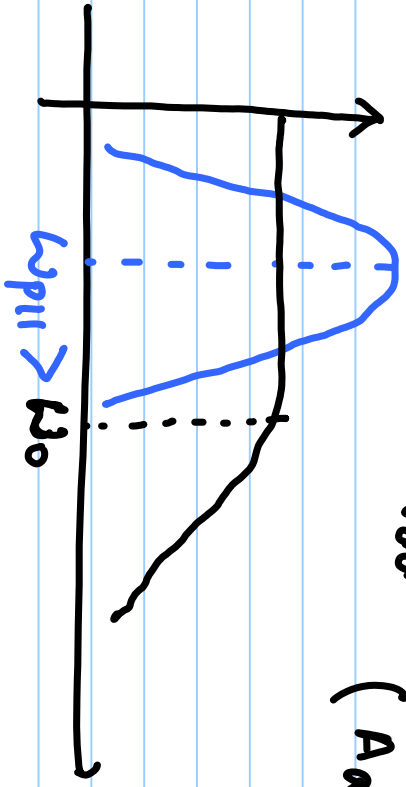
- $\omega_a < \omega_0$
- $\omega_0 < \omega_0'$
- $\omega_a > \omega_0$




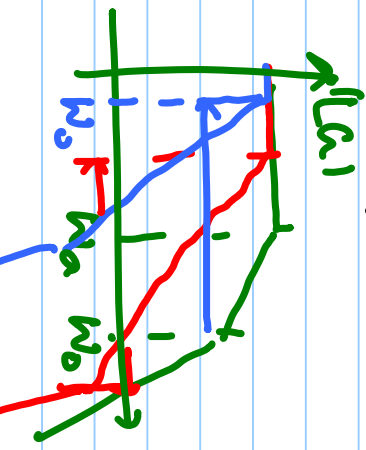
$$\frac{V_3}{V_{DD}} = \frac{S_{vdd} (1 + s/\omega_a)}{(A_a A_o + (1 + \frac{s}{\omega_a})(1 + \frac{s}{\omega_0}))}$$



# Replica-based regulation

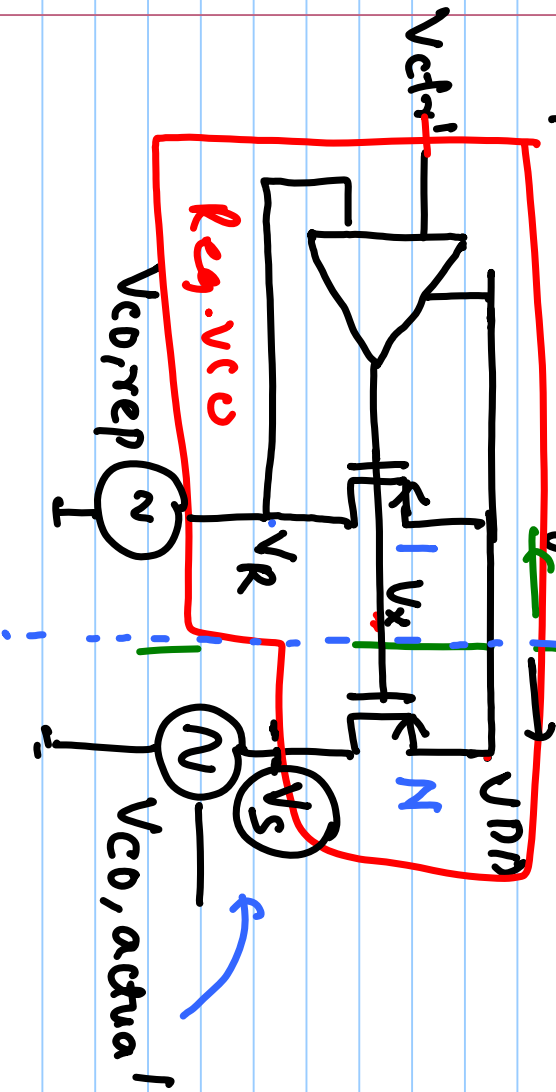



$$\frac{V_s}{V_{DD}} =$$

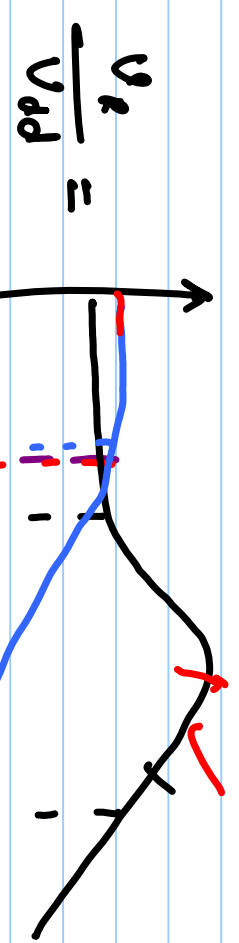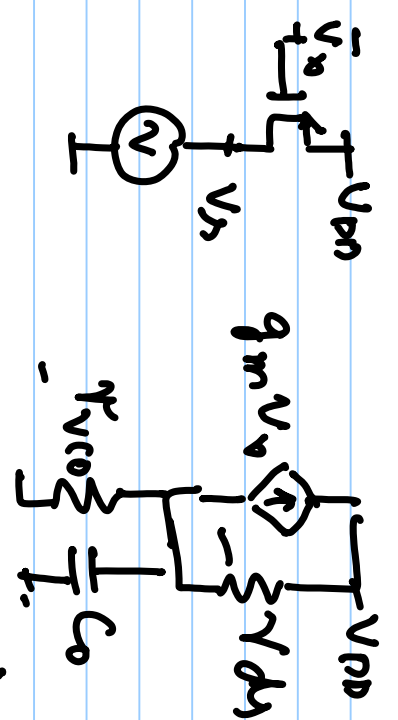

$$\omega_0' = \frac{1}{(r_{vcol} r_{ds}) C_0}$$

$$V_s = f(V_{DD}, V_r)$$

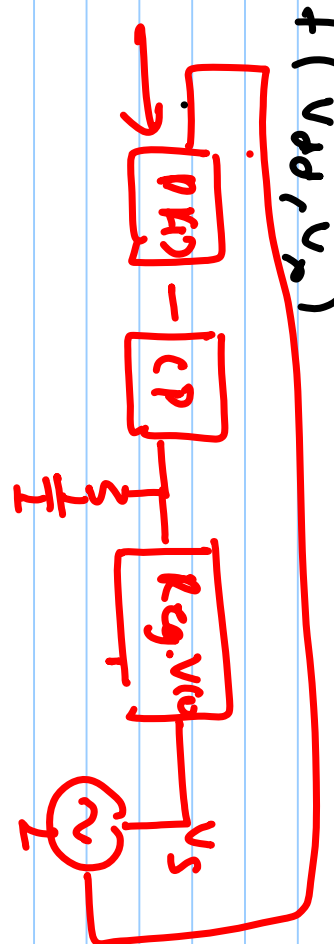


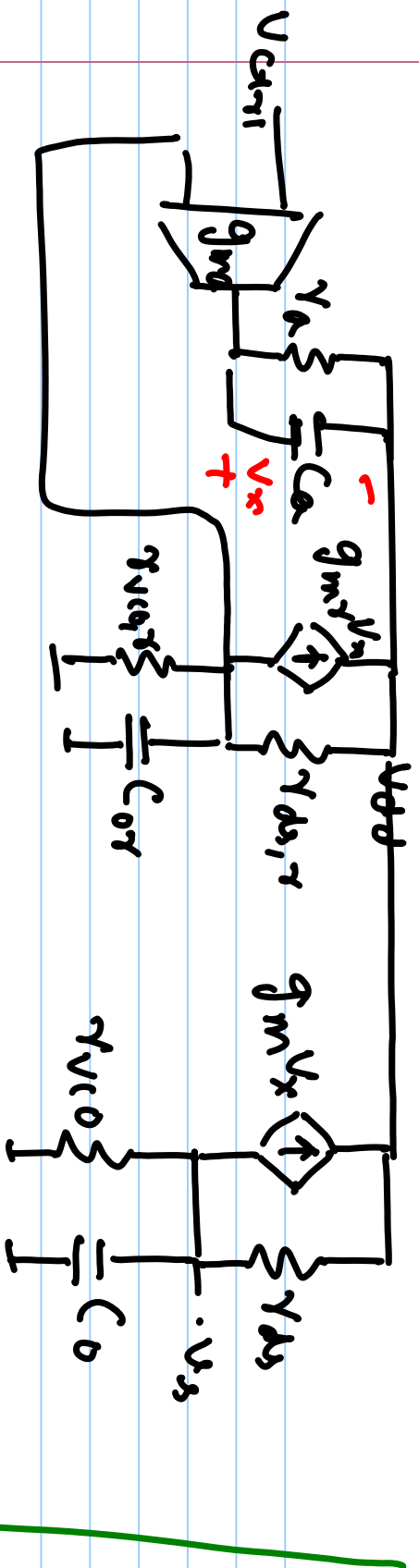

$$-g_m v_x + (V_{DD} - v_s) \frac{r_{ds}}{r_{ds}} = v_s (1 + \beta (r_{ds} r_{ov}))$$

$$v_s \left( \frac{1}{r_{ds}} + \frac{1}{r_{ov}} + \beta (r_{ds} r_{ov}) \right) = \frac{V_{DD}}{r_{ds}} - g_m v_x$$
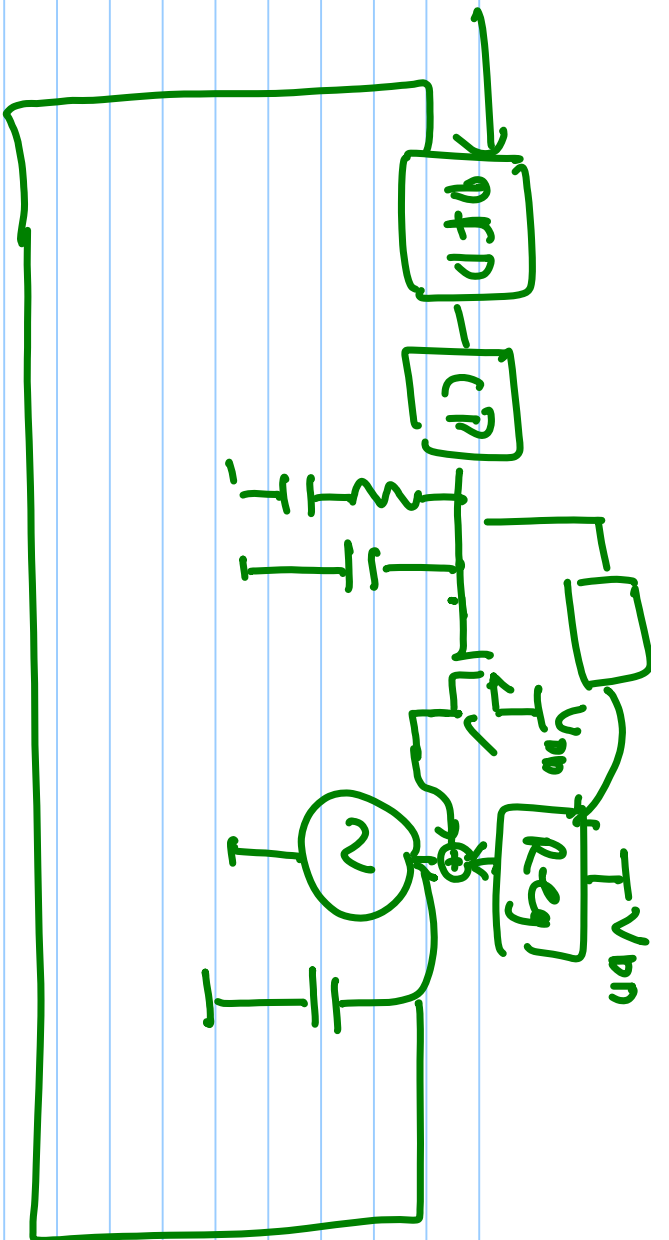
$$\frac{v_s}{V_{DD}} = \frac{r_{ov}}{r_{ds} + r_{ov}} \times \frac{1}{\left( 1 + \beta (r_{ds} r_{ov}) \right)} - \frac{g_m}{1 + \beta (r_{ds} r_{ov})} \frac{v_x}{V_{DD}}$$



NMOS o/p stage

— Max. freq. is limited.

$$- \frac{V_s}{V_{DD}} \approx \frac{1}{g_m r_{ds}}$$

$$V_{DD} \approx \frac{V_{th}}{1 - \frac{V_s}{V_{DD}}}$$


$V_{th} = 0.3V$


$$V_s < 0.7$$

$$- \frac{V_s}{V_{DD}} \approx \frac{1}{g_m r_{ds}}$$


$V_s < 1.0V$

Native device,  $V_{th} = 0$

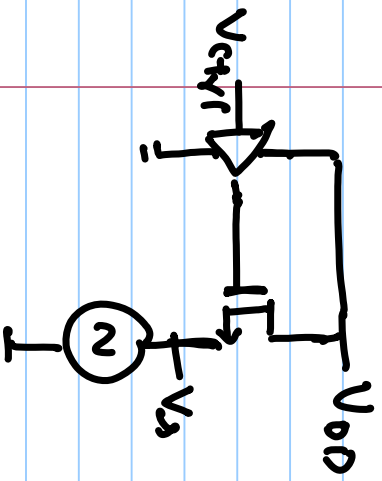

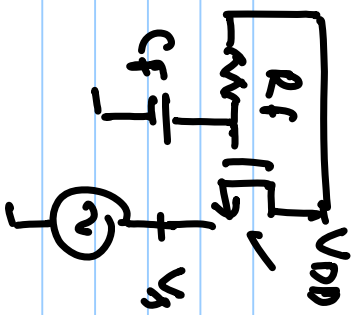
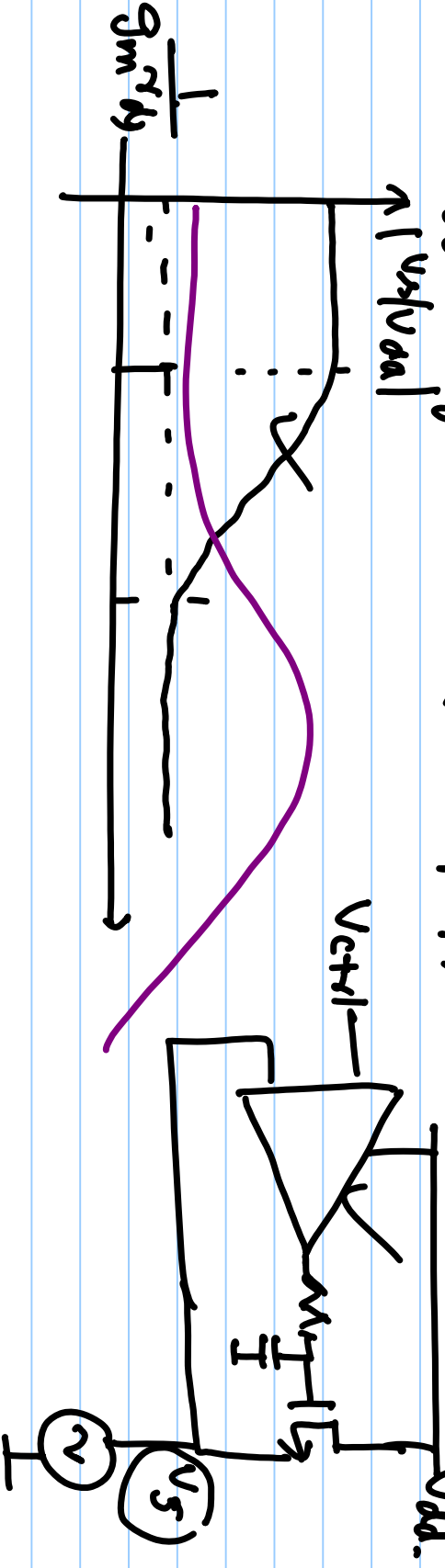
$$V_s \approx \frac{V_{DD}}{g_m r_{ds}} + \frac{1}{(1 + \beta C_f R_f)}$$



### Cascaded regulator

