

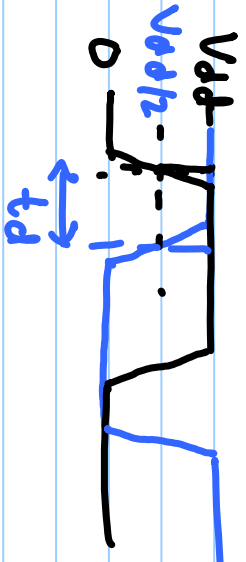
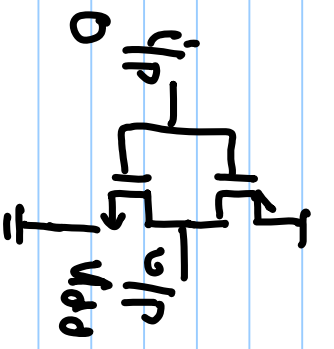
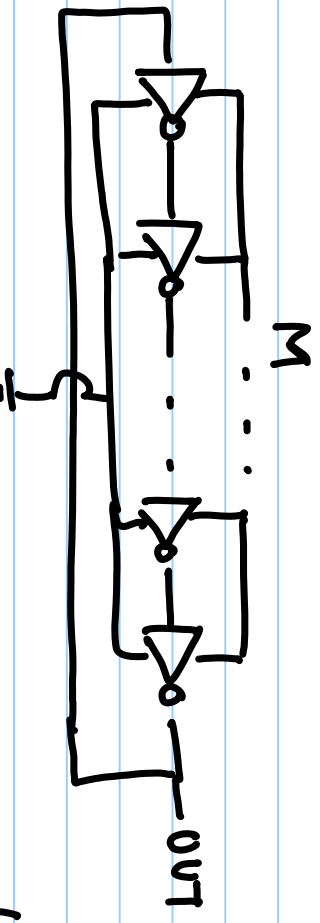


Lecture # 38

Phase noise in ring oscillators.

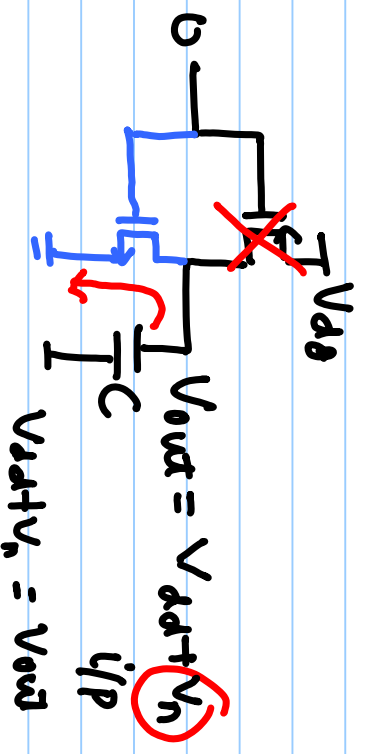


$$T = \frac{1}{2M t_d}$$

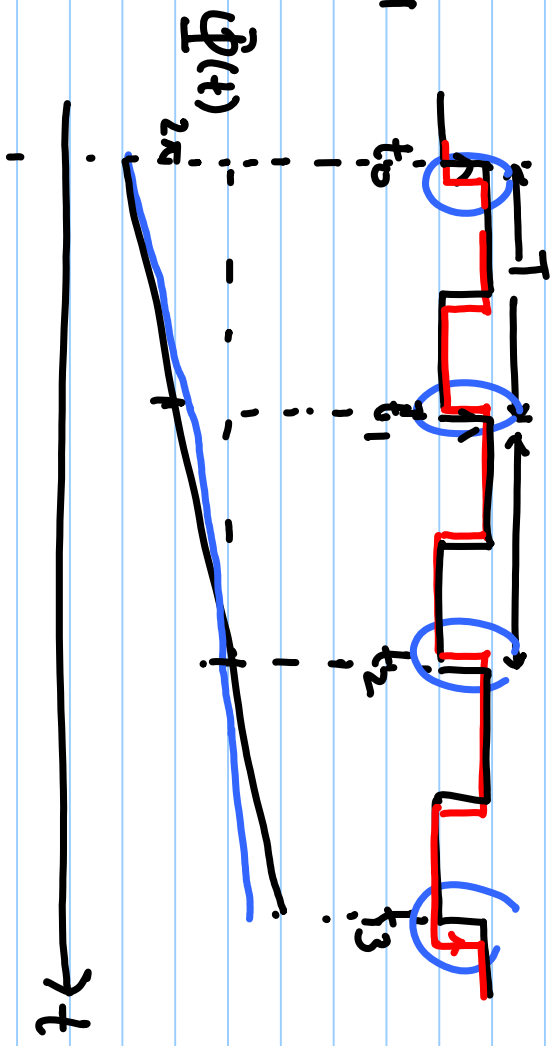


$$V_{out} = V_{dd} + v_n$$

$$v_{gs} + v_n = v_{out}$$

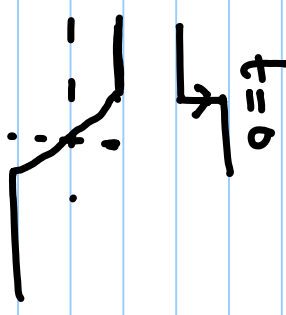
$$\overline{v_{out,n}^2} = \frac{KT}{C}$$



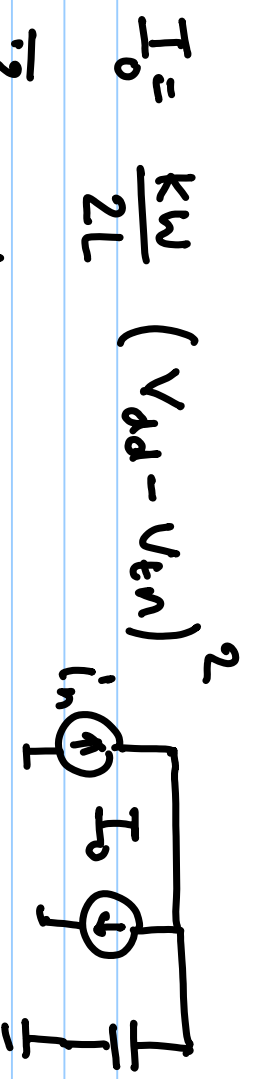

$$\frac{1}{C} \int_0^{t_{\text{tan}}} (I_0 + i_n) dt = \int dV_{\text{out}} = V_{\text{DD}} + v_n$$
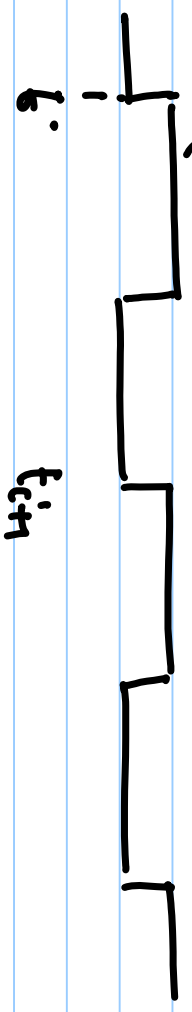
$$\frac{\overline{i_n^2}}{\Delta f} = 4kT Y_n g_m$$



M inverters

$$\sqrt{\tau_c} = \frac{1}{2\pi f_0} (\Phi(t_{i+1}) - \Phi(t_i)) \quad , \quad f_0 = \frac{1}{T_0}$$

freq. domain.

$$\sqrt{S_{\tau_c}(f)} = \frac{1}{(2\pi f_0)^2} S_{\Phi}(f) |1 - e^{-j2\pi f T_0}|^2 = \frac{S_{\Phi}(f)}{4\pi^2 f_0^2} |e^{-j\pi f / f_0} - e^{j\pi f / f_0}|^2$$

$$\sqrt{\sigma_{\tau_c}^2} = \int_0^{\infty} S_{\tau_c}(f) df = \frac{S_{\Phi}(f)}{4\pi^2 f_0^2} 4 \sin^2(\pi f / f_0)$$

$$\sigma_{\tau_c}^2 = E[(x - \bar{x})^2] \checkmark$$

$$\Phi(kT_0) = 2\pi f_0 (kT_0) + \sum_{i=1}^K \frac{2\pi}{T_0} \cdot \Delta t_i \quad \left| \quad \frac{x(t)}{x^2(t)} = \int S_x(f) df \right.$$

$$\Phi(kH T_0) = 2\pi f_0 (kH T_0) + \sum_{i=1}^{kH} \frac{2\pi}{T_0} \Delta t_i$$

$$\begin{aligned} \check{\Phi}(kH T_0) - \check{\Phi}(kT_0) &= 2\pi f_0 T_0 + \frac{2\pi}{T_0} \cdot \Delta t_{kH} \\ &= 2\pi f_0 (T_0 + \Delta t_{kH}) \end{aligned}$$

$$S_{\check{\Phi}}(f) = \frac{S_{\Phi}(f)}{4\pi^2 f_0^2} \quad \check{\Delta} \sin^2(\pi f / f_0)$$

$$\sigma_{\check{\tau}}^2 = \int S_{\check{\Phi}}(f) \frac{\sin^2(\pi f / f_0)}{(\pi f_0)^2} df$$

Phase Noise & Jitter in CMOS Ring Osc. by Abidi



$$V_{out} = A \sin(\omega_0 t + \check{\Phi}(t))$$

$$\sin(\omega_0 t + \int K_{vco} A_m \sin(\omega_m t) dt) \quad \check{\Phi}(t)$$

SSB (Single Sideband) Phase Noise.

$$L(f) = \frac{S_{\phi}(f)}{2} = \left(\frac{S_w}{f^2} \right)$$

-90 dBc/Hz

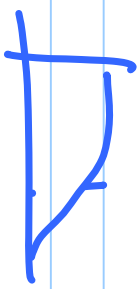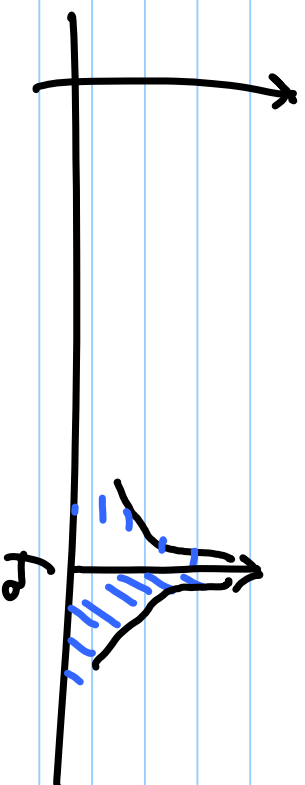

f: w.r.t carrier freq.
S_w: oscillator constants.

$$\sigma_c^2 = \int_{-\infty}^{\infty} \frac{2S_w}{f^2} \frac{\sin^2(\pi f/f_0)}{\kappa^2 f^2} df = \frac{2S_w}{f_0^4} \int_0^{\infty} \frac{\sin^2(\pi f/f_0)}{(\kappa f/f_0)^2} df$$

$$\kappa = \pi f/f_0 \Rightarrow \sigma_c^2 = \frac{2S_w}{f_0^4} \frac{f_0}{\kappa} \int_0^{\infty} \frac{\sin^2 \alpha}{\alpha^2} d\alpha$$

$$\sigma_c^2 = \frac{S_w}{f_0^3} \frac{2}{\kappa} \times \frac{\pi}{2} = \frac{S_w}{f_0^3}$$

$$L(f) = \sigma_c^2 \frac{f_0^3}{f^2}$$

M: no. of inverters in ring osc.

$$f_0 = \frac{1}{M(t_{dn} + t_{dp})} \int_0^{t_{dn}} \int_0^{t_{dn}} (I_N + i_n) dt = \frac{V_{dd}}{2} \checkmark$$

$$= \frac{2}{M C V_{dd}} \left(\frac{1}{I_N} + \frac{1}{I_p} \right)^{-1} \langle t_{dn} \rangle = \frac{C V_{dd}}{2 I_N}$$

$$\sigma_{t_{dn}}^2 = \left\langle \left(\frac{1}{I} \int_0^{t_{dn}} i_n dt \right)^2 \right\rangle \checkmark$$

$$\int_0^{t_{dn}} i_n dt = \frac{C V_{dd}}{2} - \int_0^{t_{dn}} I_N dt$$

$$t_{dn} = \frac{C V_{dd}}{2 I_N} - \frac{1}{I_N} \int_0^{t_{dn}} i_n dt \checkmark$$

$$\sigma_{t_{dn}}^2 = \frac{4 e^2 \gamma_N t_{dn}}{I_N (V_{dd} - V_{tn})}$$

$$= \frac{1}{M C V_{dd}} \times \frac{1}{2}$$

$$f_0 = \frac{I/c}{M V_{dd}}$$

$$T_0 = M(t_{dn} + t_{dp})$$

$$\sigma_T^2 = M(\sigma_{t_{dn}}^2 + \sigma_{t_{dp}}^2)$$

$$\sigma_f^2 = \frac{M \mu R T}{I (V_{DD} - V_t)} t_{dn} (Y_N + \gamma_P) \quad \Bigg| \quad \begin{array}{l} V_{tn} = V_{tp} \\ I_N = I_P = I \end{array}$$

$$+ (\quad) \quad t_{dn} = t_{dp} = \frac{C V_{DD}}{2I}$$

$$\bar{v}_n^2 = \frac{kT}{C}$$