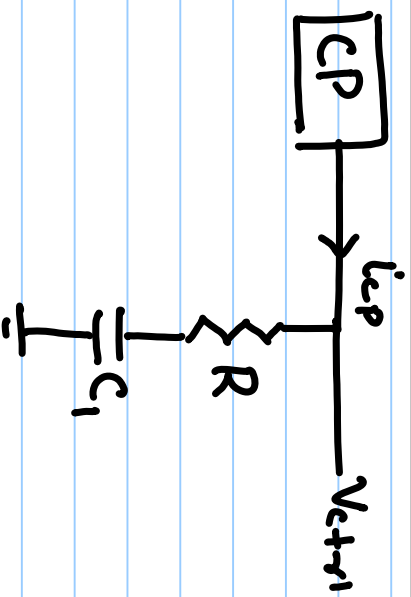


Lecture # 41

Dual-path loop filter. (nPLF)




$$V_{c+1}(s) = I_{cp} \left(R + \frac{1}{sC_1} \right)$$

$$= I_{cp} (1 + sRC_1)$$

$$= I_{cp} (R) + I_{cp} \left(\frac{1}{sC_1} \right)$$

Prop. Int.
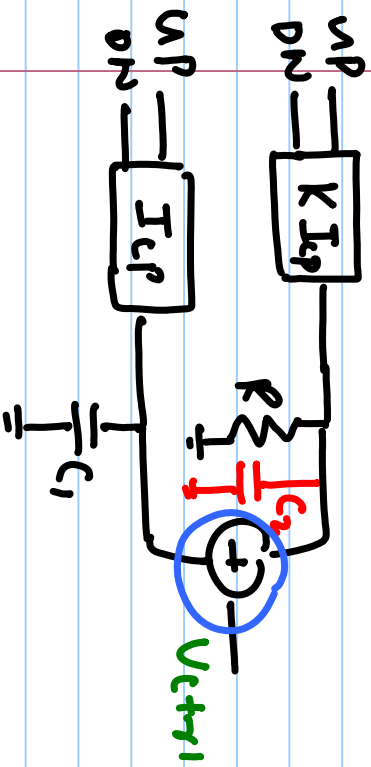
$$\omega_z = \frac{K_I}{C_1 K_P} = \frac{1}{RC}$$



$$V_{c+1}(s) = \underbrace{K_P + \frac{K_I}{sC_1}}_{\text{Prop.}} \underbrace{I_{cp}}_{\text{Int.}}$$

$$= \frac{sC_1 \cdot K_P + K_I}{sC_1}$$

$$= I_{cp1} R + I_{cp2} \frac{1}{sC_1}$$

$$\omega_z = \frac{I_{cp2}}{I_{cp1}} \frac{1}{RC_1} = \frac{s I_{cp1} \cdot RC_1 + I_{cp2}}{sC_1}$$

$$RC_1 \rightarrow 0.1 C_1 \Rightarrow I_{cp1} = 10 I_{cp}$$

$$V_{c_{t+1}}(s) = KI_{cp} \left(\frac{R}{1+sRc_2} \right) + I_{cp} \frac{1}{sC_1}$$

$$= \frac{I_{cp}}{sC_1} \left[\frac{sKRc_1 + 1 + sRc_2}{1 + sRc_2} \right]$$

$$= \frac{I_{cp}}{sC_1} \left[\frac{1 + sR(c_2 + Kc_1)}{1 + sRc_2} \right]$$


$$\omega_2 = \frac{1}{R(c_2 + Kc_1)}, \quad \omega_{p1} = 0, \quad \omega_{p2} = \frac{1}{Rc_2}$$

— More current in CP ✓


$$S_{icp}(f) = \frac{8KI}{3} (g_{m1} + g_{m2}) \frac{I_{KST}}{I_{ref}}$$

$$NTF = \frac{2\pi}{I_{cp}} \frac{L_u}{1 + L_u}$$


1.

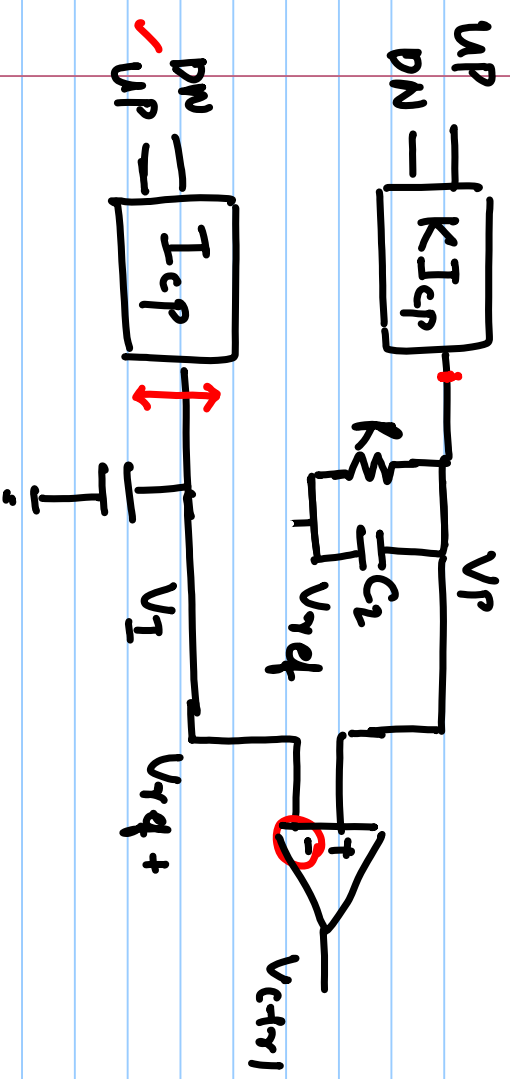

- Power } OPAMP
- Noise }

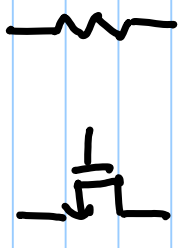



2

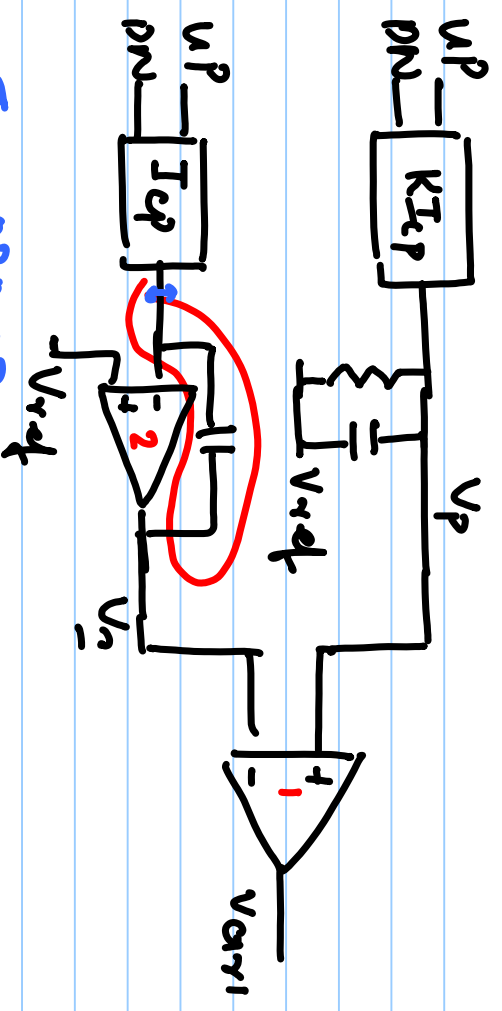

- Two OPAMP
- Added Noise.

3.

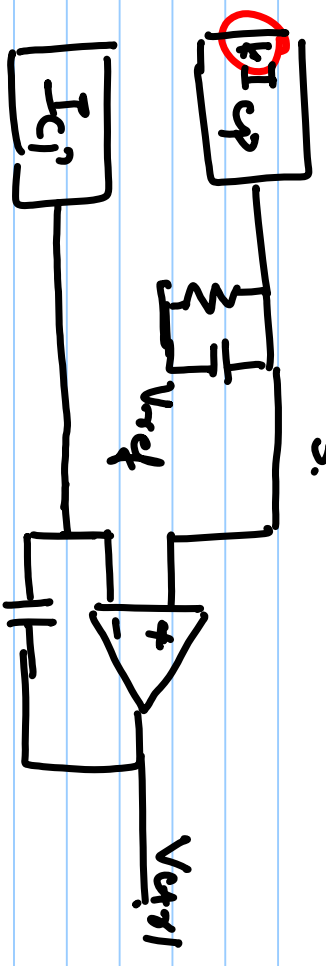


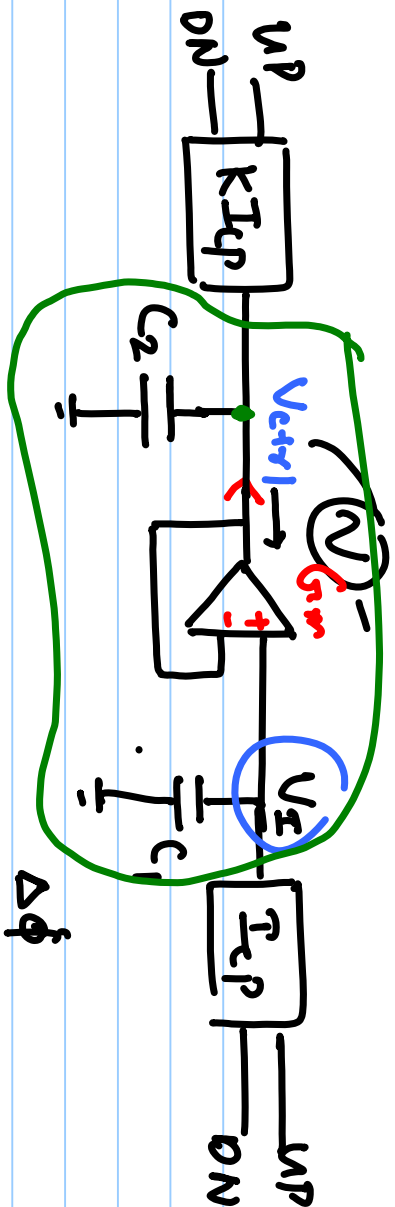



$$V_{ch2}(s) = [G_m (V_I - V_{ch1}) + k_{Icp}] \times \frac{1}{sC_2}$$

$$V_{ch1} \left(1 + \frac{G_m}{sC_2} \right) = \frac{G_m}{sC_2} \times \frac{I_{cp}}{sC_1} + \frac{k_{Icp}}{sC_2}$$



$$= \frac{I_{cp}}{sC_2} \left(\frac{G_m + sC_1 k}{sC_1} \right)$$
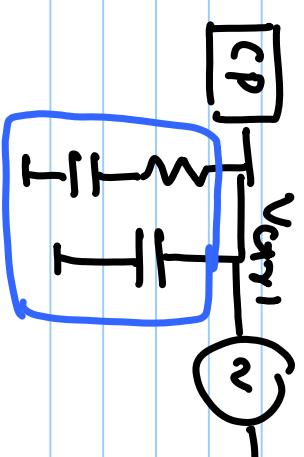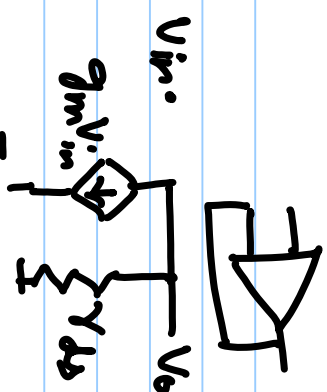
$$\frac{V_{ch1}}{I_{cp}} = \frac{(G_m + sC_1 k)}{sC_1 (G_m + sC_2)}$$



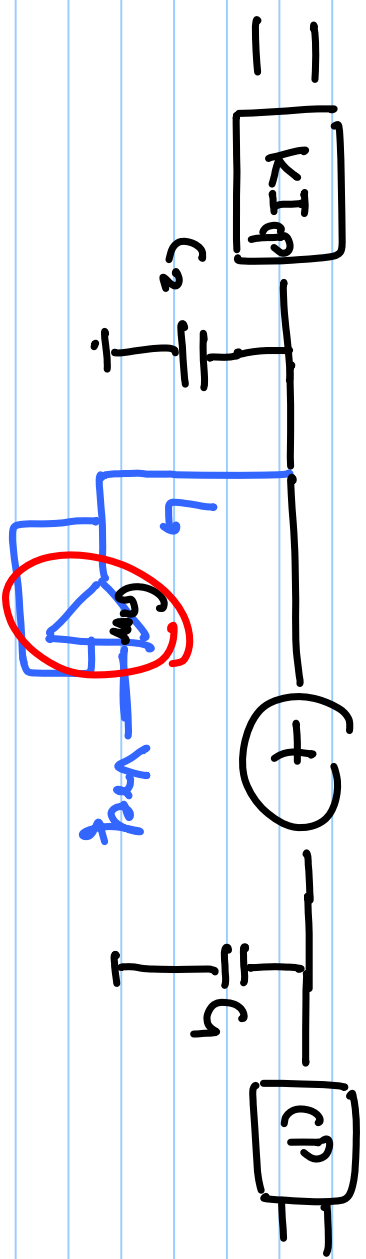

$$R = \frac{1}{G_m}$$

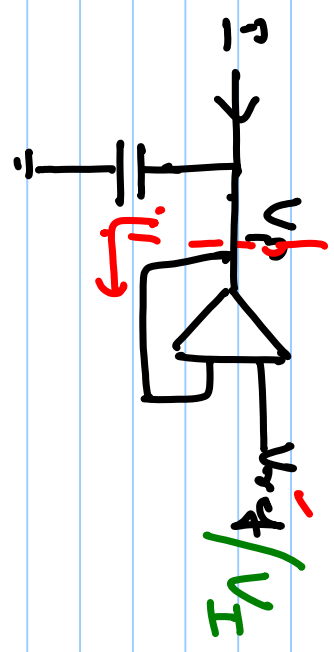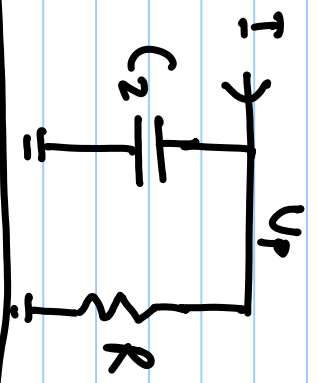


$$V_{cp} = I_{cp} \cdot R + I_{cp} \frac{1}{sC_1} = k_p + \frac{k_i}{sC_1}$$

$$k_2 = \frac{k_i}{k_p C}$$

$$V_{cp}(s) = I_{cp} \cdot R + \alpha \cdot I_{cp} \frac{1}{sC}$$

$$\alpha < 1$$

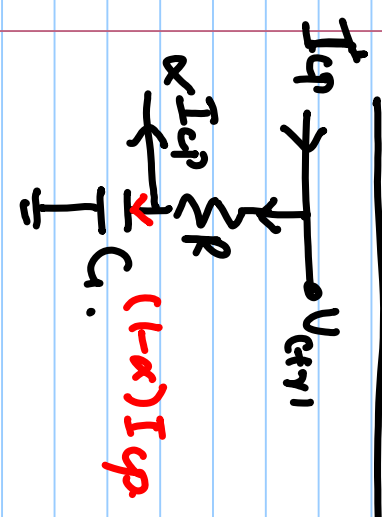


$$V_{em}(s) = I_{cp} \cdot R + (1-\alpha)I_{cp} \cdot \frac{1}{sC}$$

$$= \frac{I_{cp}}{sC} \left(sRC + (1-\alpha) \right)$$


$$= \frac{I_{cp}(1-\alpha)}{sC} \left[\frac{sRC}{1-\alpha} + 1 \right]$$

$$C_{new} = \frac{C}{1-\alpha}, \quad ; \alpha < 1$$


$$I_{cp} = i_c + K i_c$$

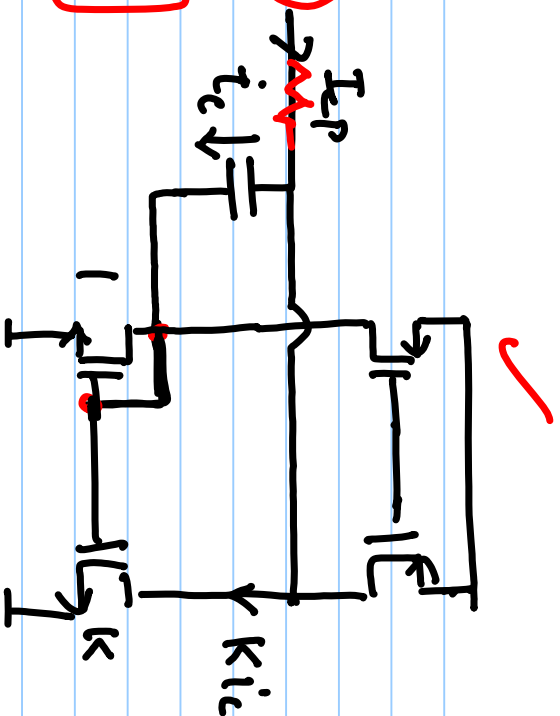

$$= \left(\frac{1}{1-\alpha} \right) C$$

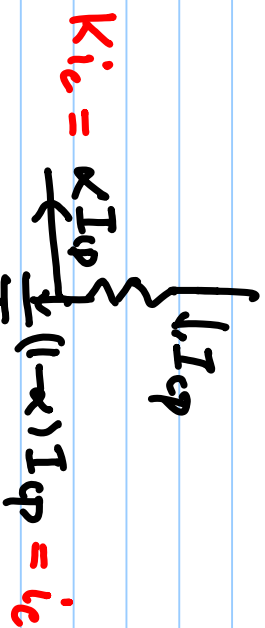
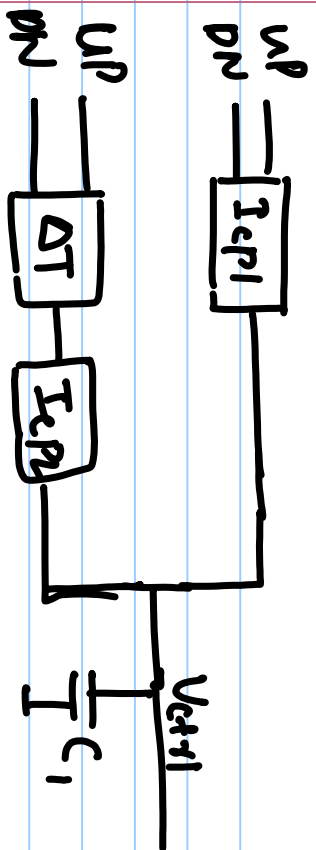
$$\frac{K i_c}{i_c} = \frac{\alpha I_{cp}}{(1-\alpha) I_{cp}}$$



$$(1 + \lambda RC) e^{-\lambda \cdot \Delta T}$$

$$V_{cp1}(s) = \frac{I_{cp1}}{\lambda C_1} + \frac{I_{cp2} e^{-\lambda \cdot \Delta T}}{\lambda C_1}$$

$$= \frac{1}{\lambda C_1} \left[I_{cp1} + I_{cp2} (1 - \lambda \cdot \Delta T) \right]$$

$$= \frac{1}{\lambda C_1} (I_{cp1} + I_{cp2}) \left[1 - \frac{I_{cp2} \cdot \Delta T}{I_{cp1} + I_{cp2}} \lambda \right]$$

$$= \frac{1}{\lambda C_1} (1 - \alpha) I_{cp1} \left[1 + \frac{\alpha \Delta T}{1 - \alpha} \lambda \right]$$

$$I_{cp2} = -\alpha I_{cp1}$$

$$\lambda_2 = \frac{1 - \alpha}{\alpha \cdot \Delta T}$$