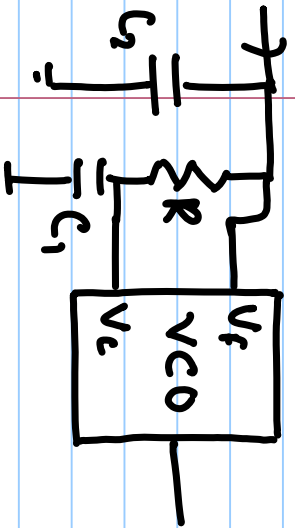


Lecture # 43

Split-tuned PLLs.



V_f : K_{VCO}^f

V_c : K_{VCO}^c

$$K_{VCO}^f = \frac{K_{VCO}^c}{K}$$


$$LG(s) = K \frac{I_{CP} K_{VCO}}{s^2 (K_C + C_2) (1 + sR K_C C_1)} \left| \begin{array}{l} K_{VCO}^c \\ K_{VCO}^c = \frac{(K-1) K_{VCO}}{K} \end{array} \right.$$

$$\frac{(R + \frac{1}{sC_1}) \times \frac{1}{sC_2}}{R + \frac{C_1 + C_2}{sC_1 C_2}}$$

$$\text{Old } LG(s) = \frac{I_{CP} K_{VCO}}{s^2 (C_1 + C_2) (1 + sR C_1)} \frac{(1 + sR C_1)}{(1 + sR (C_1 + C_2)) C_1 C_2}$$

$$\omega_{2, \text{new}} = \omega_{2, \text{old}} = \frac{1}{RC_1}$$
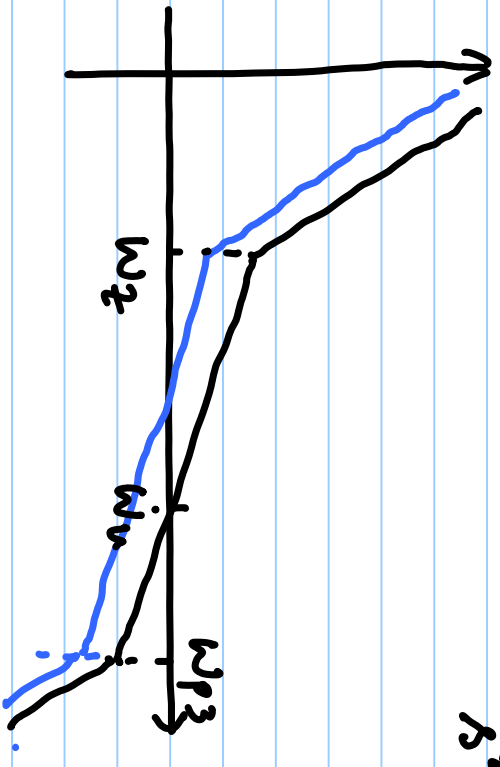
$$\omega_{p3, \text{new}} = \omega_{p3, \text{old}} = \frac{1}{RC_1 C_2 / (C_1 + C_2)}$$




$$L_n(s) \approx \frac{I_{cp} K_{vco}}{s^2 C_1} \frac{(1 + s/\omega_2)}{(1 + s/\omega_{p3})}$$

- $K_{vco} \rightarrow K_{vco}/k$

- $C_1 \rightarrow KC_1$

- $I_{cp} \rightarrow KI_{cp}$

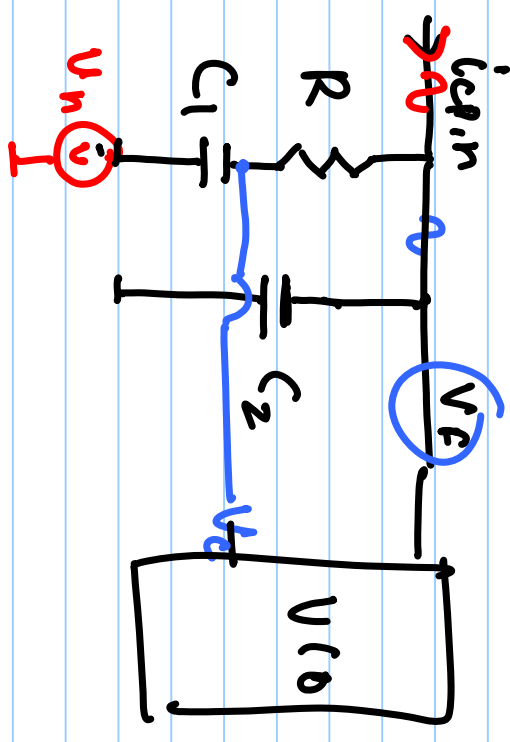


$$NTF_R = \frac{K_{vco}}{s} \frac{1}{1 + L_n}$$

\swarrow K_{vco}/k

$$\frac{V_f}{I_{cp}}$$
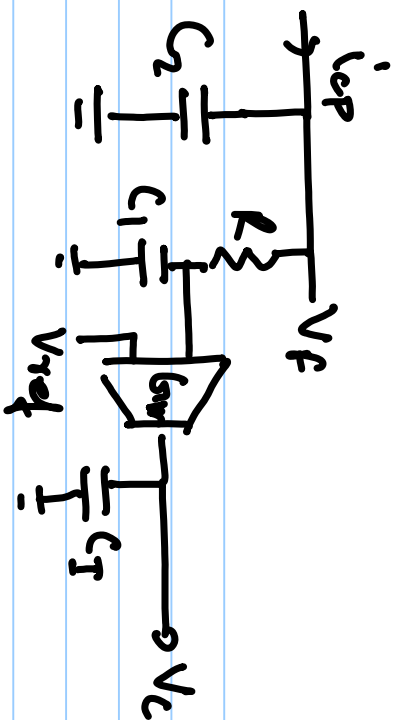
$$\frac{V_f}{I_{cp}} = \frac{V_f}{I_{cp}} \times \frac{1}{1 + sK_1}$$



$$\frac{V_F}{I_{cp}} = F(s)$$


$$\frac{V_C}{I_{cp}} = F(s) \times \frac{1}{1+sRC_I} \times \frac{g_m}{sC_I}$$

$$L_G(s) = \frac{I_{cp} F(s)}{2r} \left[K_{vco}^f + \frac{K_{vco}^c}{(1+sRC_I)} \times \frac{g_m}{sC_I} \right] \times \frac{2r}{s}$$

$$= \frac{I_{cp}}{2r} \frac{2r F(s)/s}{(1+sRC_I)} \cdot \left[K_{vco}^f sC_I (1+sRC_I) + K_{vco}^c \cdot g_m \right] \times \frac{1}{sC_I}$$

$$\underbrace{s^2 RC_I C_I K_{vco}^f + sC_I K_{vco}^c + K_{vco}^c g_m}_{=0}$$
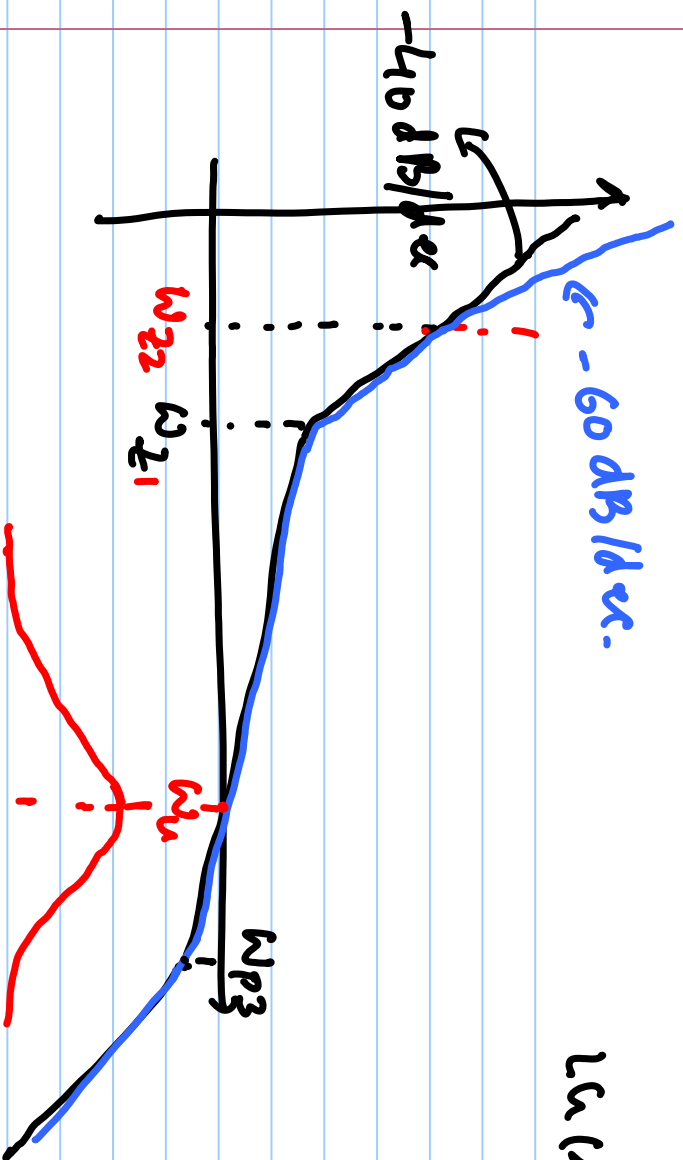
$$s \approx \frac{K_{vco}^c g_m}{K_{vco}^c C_I} = \omega_{z2}, \quad s \approx \frac{1}{RC_I} = \omega_{z1}$$



- G_m contributes noise

$$|G_v(s)| \approx I_{CP} \frac{(s + \omega_{z1})(s + \omega_{z2})}{(s + \omega_{p3})}$$


$$\approx \frac{3 C_I (C_1 + C_2) (s + \omega_{z1})}{(s + \omega_{p3})}$$

$$\omega_{z2} \ll \omega_{z1}$$

$$\frac{K_{VCO}^c G_m}{K_{VCO}^f C_I} \ll \frac{1}{R_C}$$

$$\boxed{\text{PFD}} + \boxed{\text{I}_{cp}} - \boxed{\text{I}_{cp}} - \boxed{\text{I}_{cp}}$$

Digital PLL.

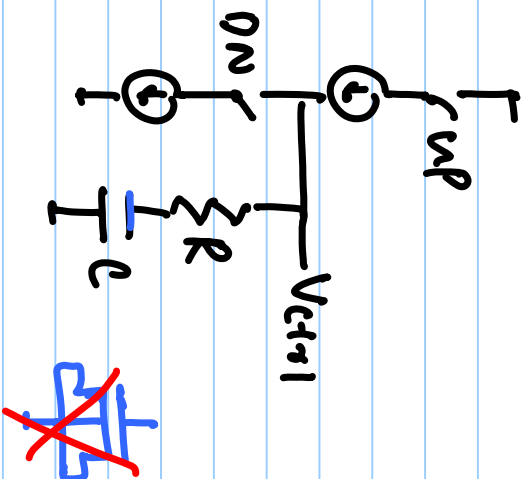

$$\frac{V_{ctl1}(s)}{\phi_{err}} = I_{cp} \left(R + \frac{1}{sC} \right)$$

Prop. Integral

$$s \rightarrow \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \quad I_{cp} \cdot C$$


$$V_{ctl1}(z) = I_{cp} \left(R + \frac{T}{2C} \frac{1+z^{-1}}{1-z^{-1}} \right)$$

$$= \frac{I_{cp}}{2C} \frac{2CR(1-z^{-1}) + T(1+z^{-1})}{1-z^{-1}}$$


$$\frac{V_{ctl1}(z)}{\phi_{err}(z)} = \alpha + \frac{\beta}{1-z^{-1}}$$

$$= \frac{I_{cp}}{2C} \frac{(2RC+T) + (T-2RC)z^{-1}}{1-z^{-1}}$$
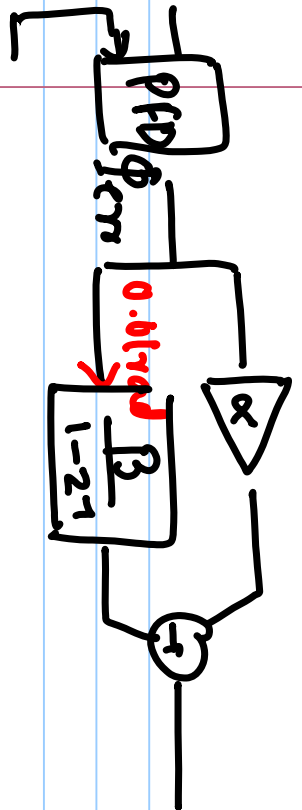
$$V_{ctl1}(n) = \alpha \phi_{err}(n) + \dots \quad (11)$$


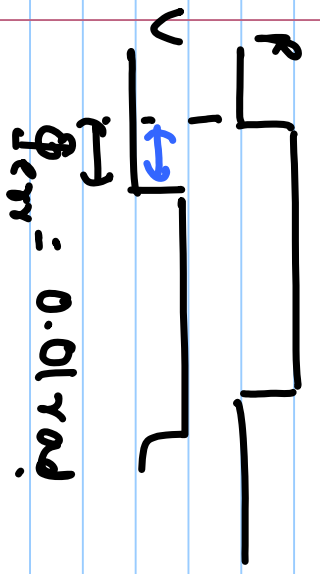
$$\frac{V_{GH1}(z)}{\Phi_m(z)} = \frac{(\alpha + \beta) - \alpha z^{-1}}{1 - z^{-1}} \quad (2)$$




$$\alpha + \beta = \frac{I_{cp}}{2C} (T + 2RC)$$

$$\alpha = \frac{I_{cp}}{2C} (2RC - T)$$

$$\beta = \frac{I_{cp}}{2C} \times 2T$$
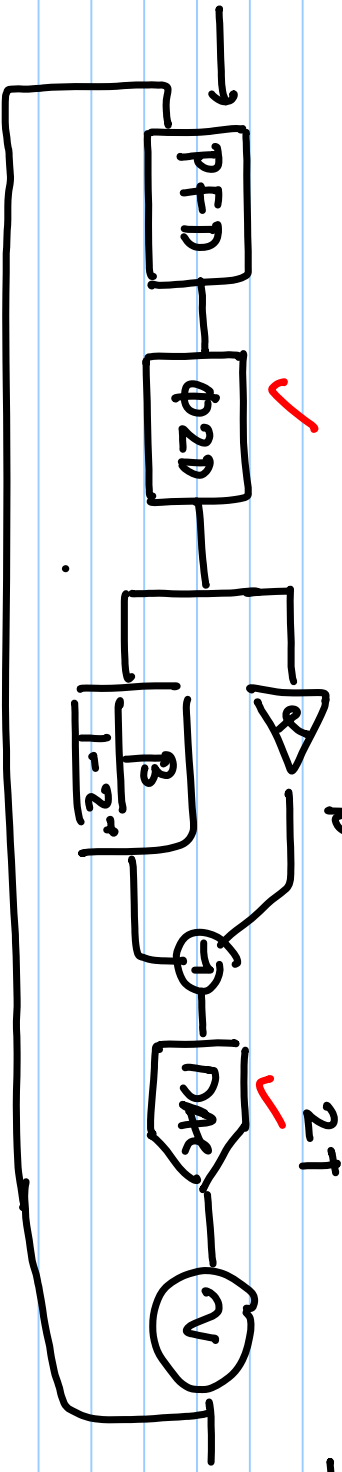
$$\frac{\alpha}{\beta} = \frac{(2RC - T)}{2T} = \frac{RC}{T} - \frac{1}{2}$$



$$L_{CL}(s) = \frac{I_{CP}}{2\pi} \times \frac{2\pi K_{VCO}}{s} \frac{(1+sRC)}{sC}$$

$$\angle L_{CL} = -180^\circ + \tan^{-1}(\omega/\omega_z)$$

$$\phi_m = \tan^{-1}(\omega_u/\omega_z)$$

$$\frac{1}{RC} = \omega_z = \frac{\omega_u}{\tan(\phi_m)}$$


ω_z

$$\frac{\alpha}{\beta} = \frac{RC}{T} - \frac{1}{2}$$

$$= \frac{f_{ref}}{\omega_z} - \frac{1}{2}$$

$$\frac{\alpha}{\beta} \approx \frac{f_{ref}}{\omega_u} \cdot \tan(\phi_m) - \frac{1}{2}$$

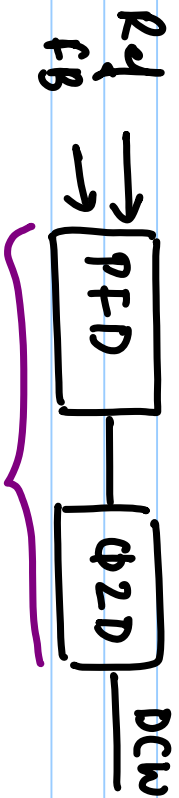Large $\phi_m \Rightarrow \alpha \approx \beta$



DCW: Digital Control Word.

TDC : Time to Digital Converter.

