
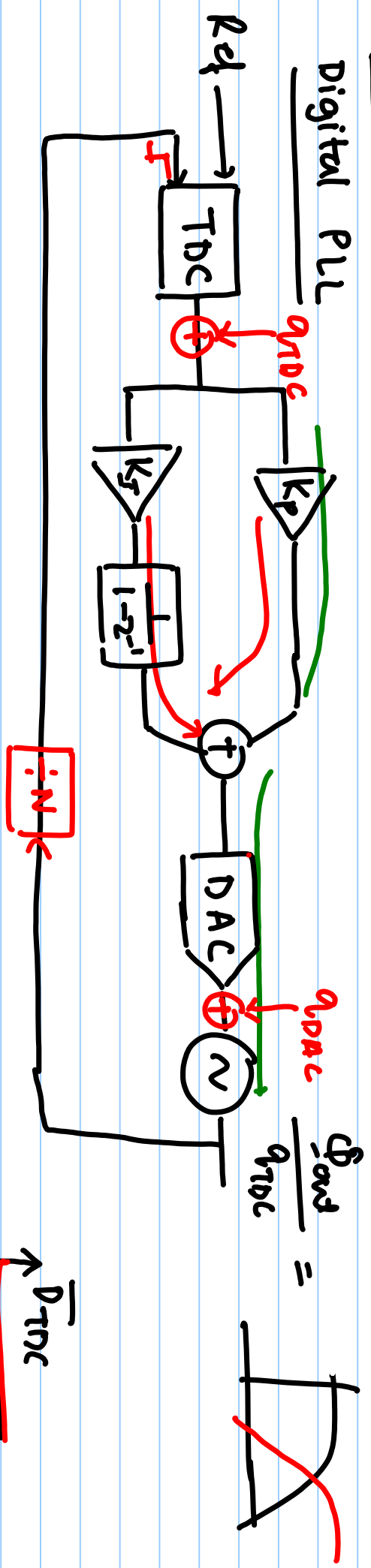


Lecture # 45

Digital PLL



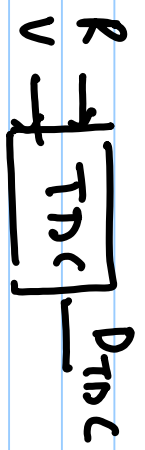


$$\frac{\phi_{avg}}{a_{TDC}} = f$$





$$TDC_{USB} = \frac{T_{ref}}{N}$$

$$D_{TDC} = \pm TDC_{USB}$$

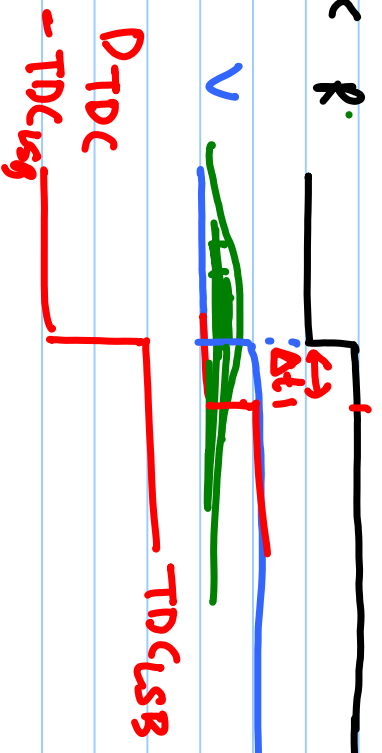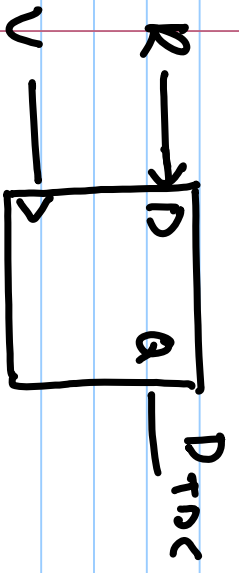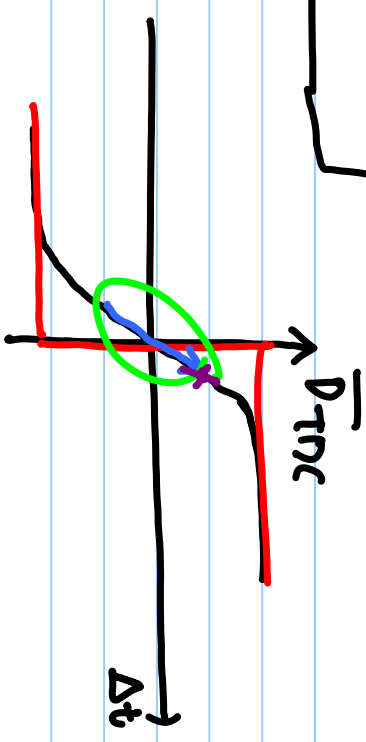


$$D_{TDC} = P(D_{TDC} = +TDC_{USB})$$

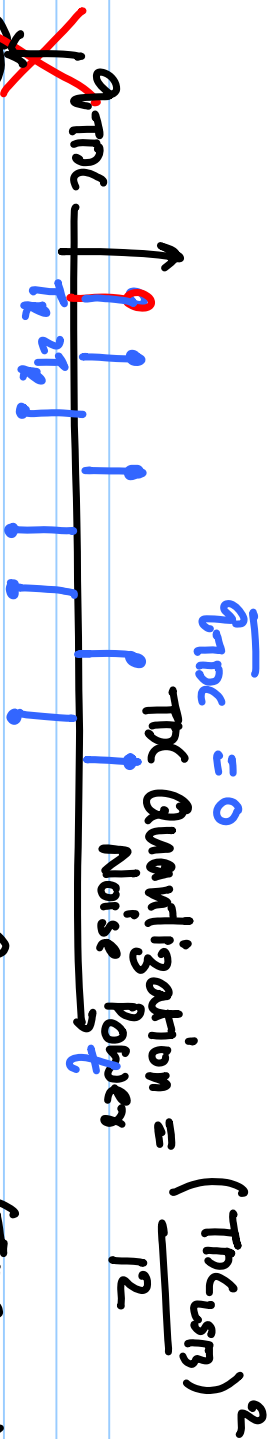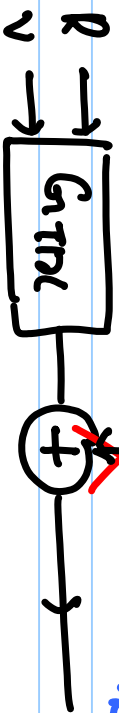- $\times TDC_{USB}$
- $+ P(D_{TDC} = -TDC_{USB})$
- $- TDC_{USB}$


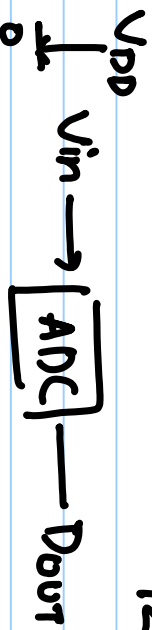
$$S_{TDC} = \frac{(TDC_{LSB})^2}{12} \times \frac{1}{f_{req}}$$




- q_{TDC} is low pass filtered
- $q_{TDC} \propto$ # delay elements in TDC

$$LSB = \frac{V_{DD}}{2^N - 1}$$

- Quantization Noise $\leq \pm \frac{LSB}{2}$

$$\overline{q_{TDC}} = 0$$
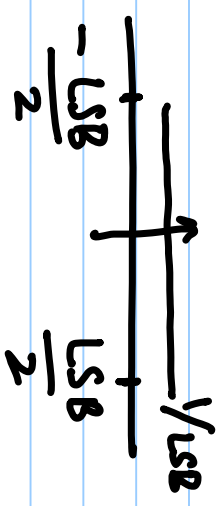
$$E[q_{TDC}^2] = \int_{-\frac{LSB}{2}}^{\frac{LSB}{2}} x^2 f(x) dx$$



Large cap. area in integral path \longrightarrow Digital loop filter




(Prop. + Integral)

$\downarrow \omega_{TDC}$


large ω_{TDC} through prop. path

$$NTF_q = \frac{(K_p + K_i \frac{f_{ref}}{s}) \frac{2\pi K_{vco}}{s}}{1 + L_n}$$

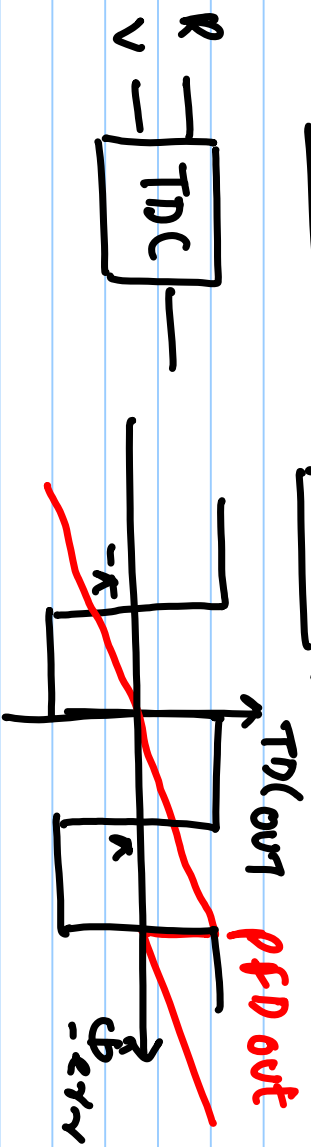
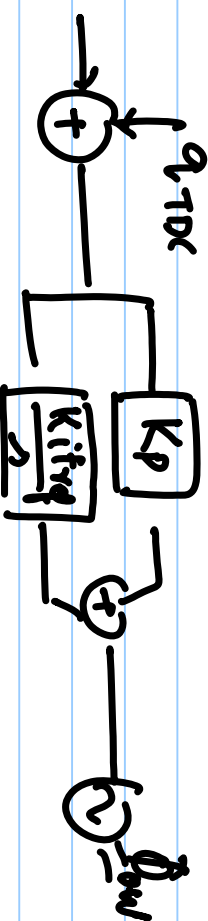
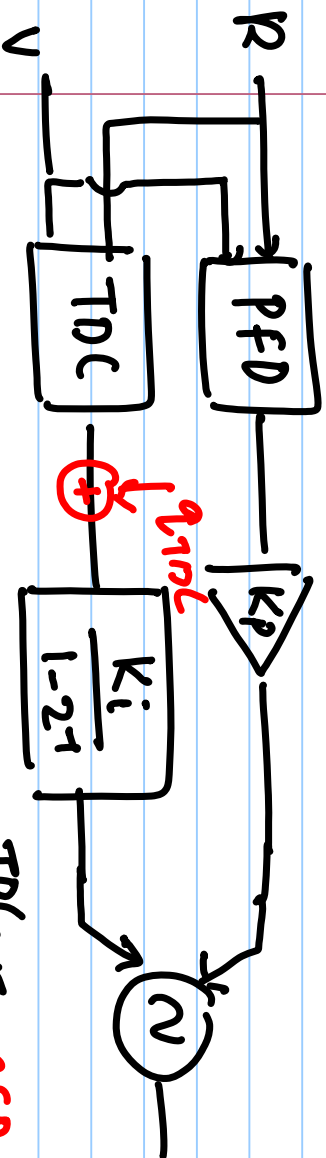
$$\frac{\alpha}{\beta} = \frac{f_{ref}}{\omega_{vco}} \tan(\delta_m) \approx \frac{1}{2}$$




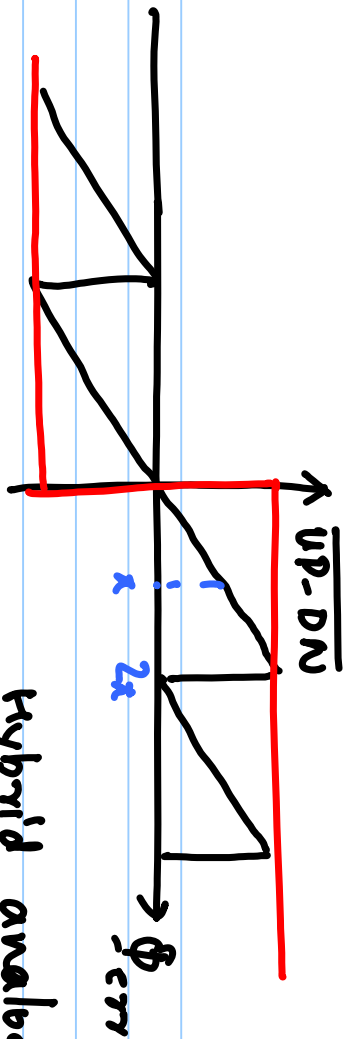
NTF_{prop} NTF_{int} = $\frac{K_i f_{ref}}{s \cdot K_p}$ NTF_{prop}



Hybrid analog/digital PLL

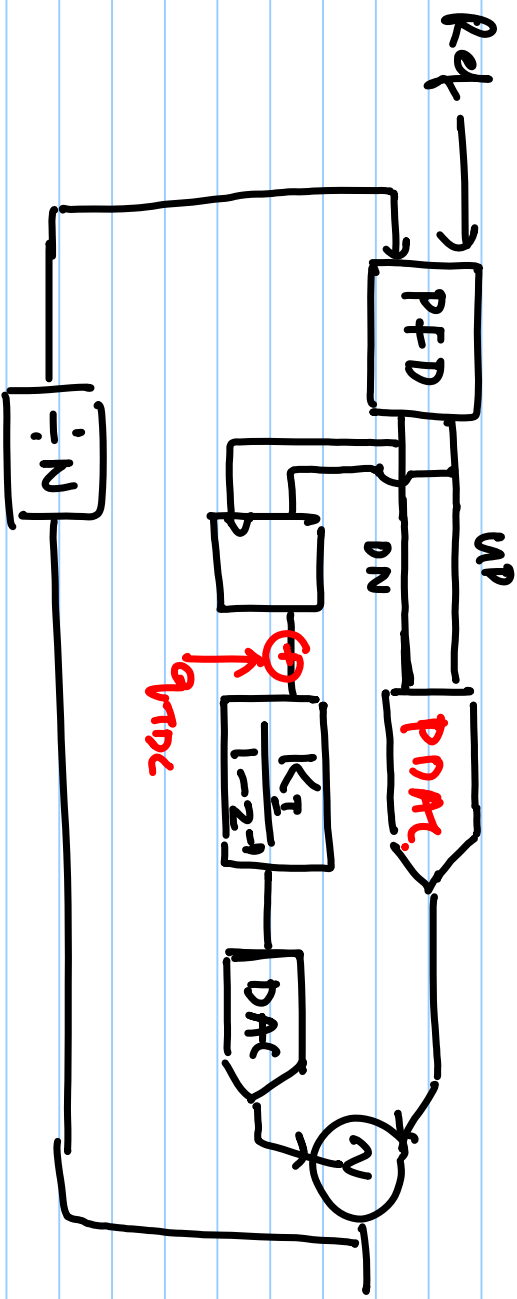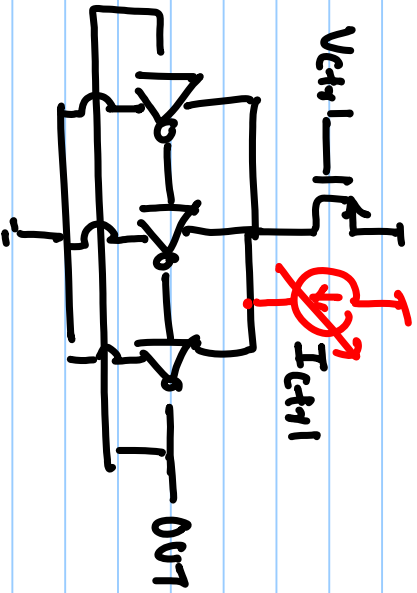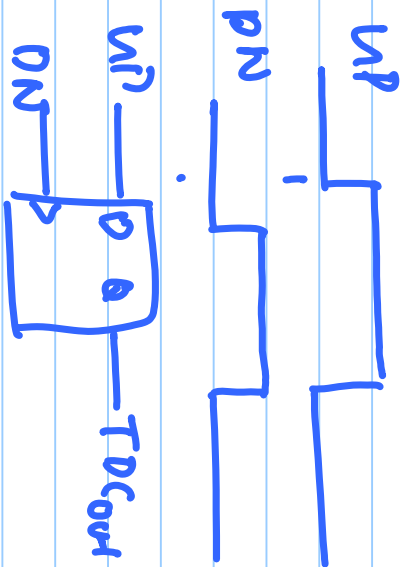


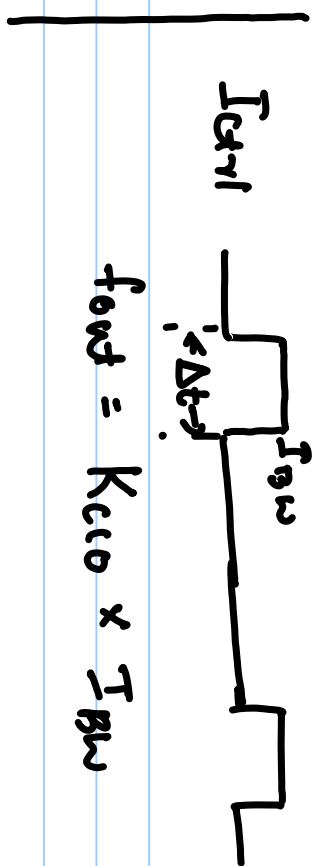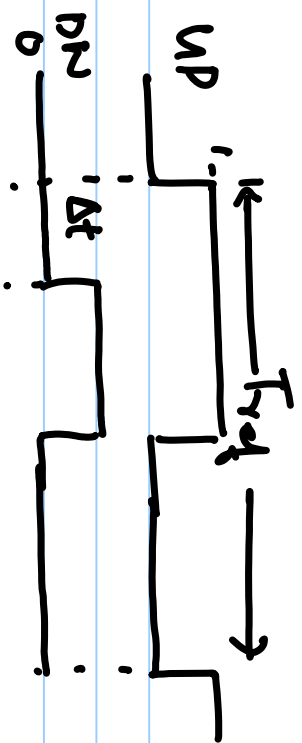$K_{VCO} \rightarrow$ OUT freq
 $K_{DC} \rightarrow$ OUT freq
 $I_{CH1} \rightarrow$ OUT freq



$$f_{osc} = K_{c10} \times I_{BW}$$
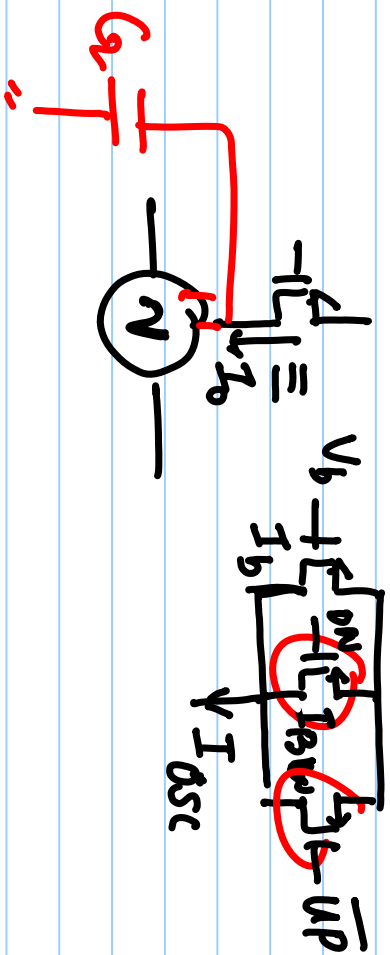
$$\overline{UP-DN} = \frac{\Delta b}{I_{rd}} \quad f_{osc} = K_{vco} \times \overline{UP-DN}$$



	UP	DN	
UP	0	0	I_{osc}
DN	0	0	$I_b + I_{BW}$
	1	0	$I_b + 2I_{BW}$
	1	1	$I_b + I_{BW}$
	1	1	$I_b + I_{BW}$

$-I_{GM}$
 $+I_{GM}$