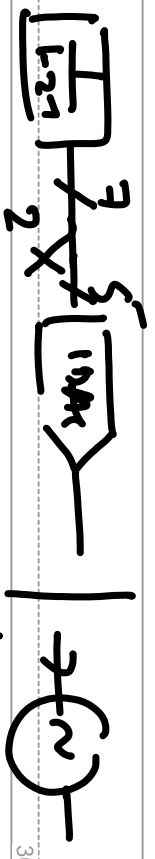


Lecture #46




1.5693 mA

$\omega_{p1}, \omega_{p2} = 0 \text{ } \omega_{50\mu\text{m}}$

$\omega_z = -\frac{K_i f_{ref}}{K_p}$

$[K_{ecc0}] = 413/A$

1.550 mA - 1.600 mA

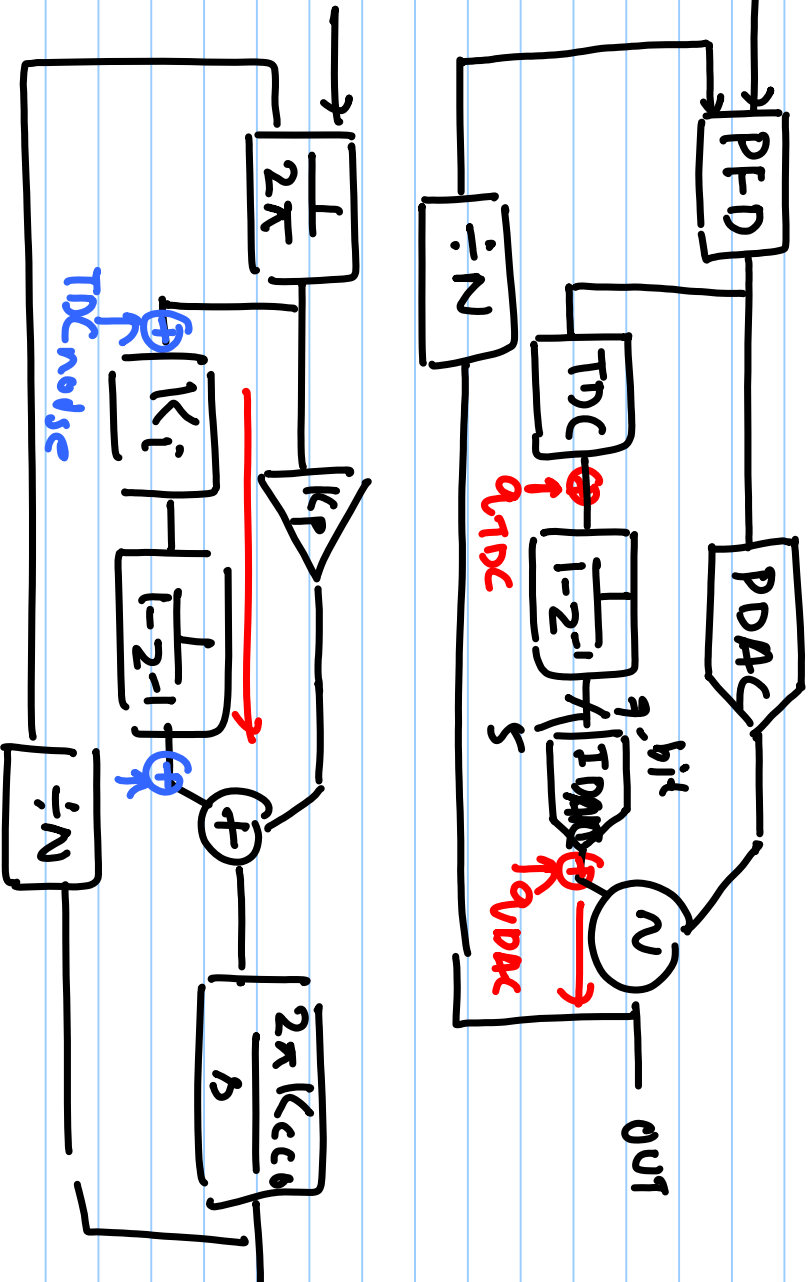

$$L_G(s) = \frac{1}{2K} \left(K_p + \frac{K_i}{1-s^{-1}} \right) \frac{1}{N} \times \frac{2\pi K_{ecc0}}{s}$$

$$= \frac{K_{ecc0}}{N s} \left(K_p + \frac{K_i f_{ref}}{s} \right) = \frac{K_{ecc0}}{s^2 N} \left(s K_p + K_i f_{ref} \right)$$


$$z = e^{T s / f_{ref}}$$

$$1 - z^{-1} = 1 - (1 - s T / f_{ref})$$


For DAC noise. $|H_n(\omega_n)| = 1$ $\omega_n = \frac{K_{CCO} k_p}{N}$

$$NTF_{DAC} = \frac{2\pi K_{CCO} / \lambda}{1 + L_n} = \frac{2\pi K_{CCO} / \lambda}{1 + \frac{K_{CCO}}{\lambda^2 N} (\lambda k_p + k_i f_{ref})}$$



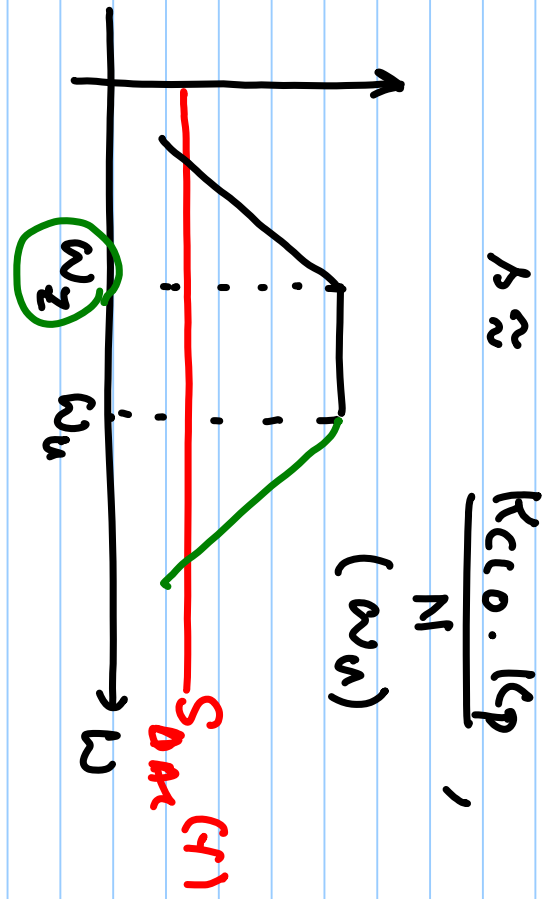
$$= \frac{2\pi K_{CCO} \cdot N \cdot \lambda}{\lambda^2 N + \lambda K_{CCO} \cdot k_p + K_{CCO} k_i f_{ref}}$$



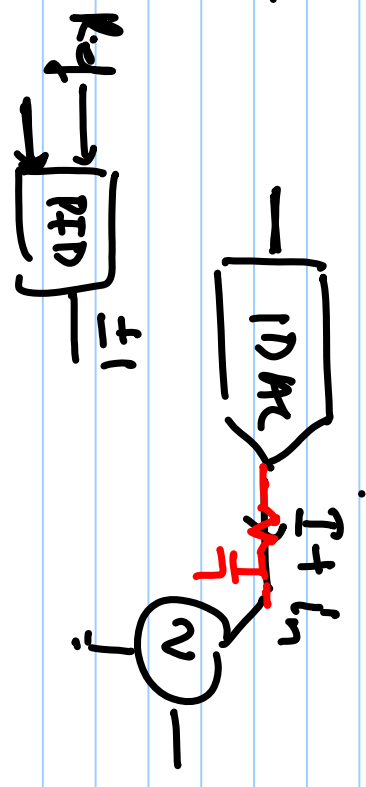$\lambda \approx \frac{K_{CCO} \cdot k_p}{N}$, $\frac{k_i f_{ref}}{k_p}$ (ω_z)



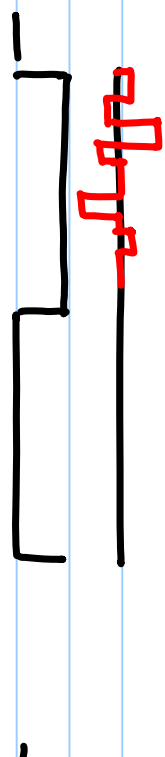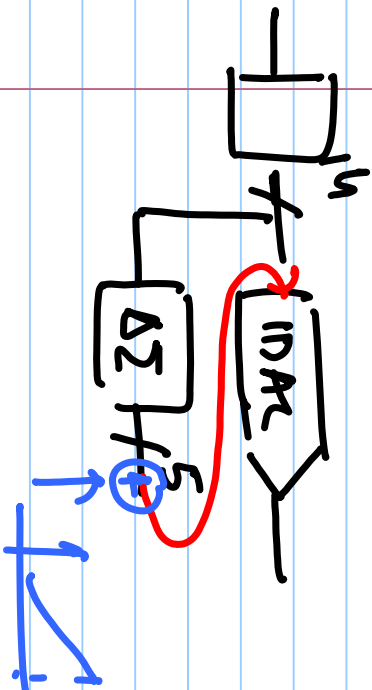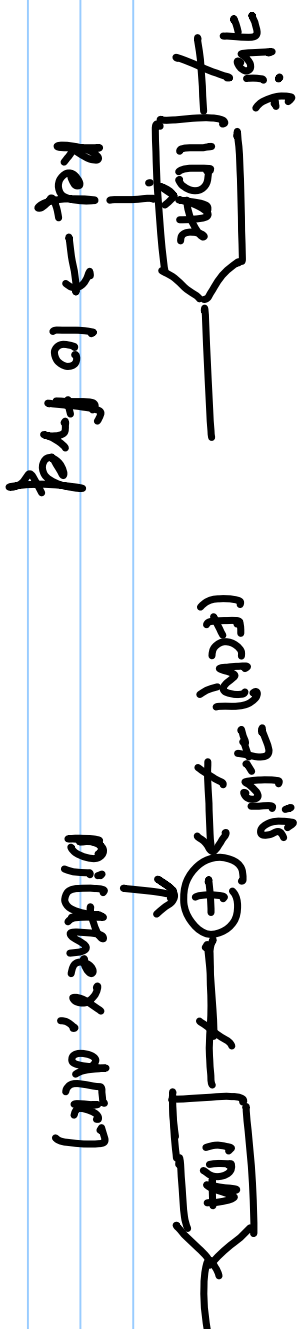- LSB of DAC \rightarrow Spur
- Non-uniform seg. of DAC
- Low-pass filter DAC ofp




TDC Noise


$$NTF_{rx} = \frac{K_i f_{rd}}{s} = \frac{2\pi K_{c0}/s}{1 + L_h} = \frac{2\pi K_{c0} \cdot K_i f_{rd} N}{s}$$

Poles: $\omega_{p1} = \omega_z$ (PLL loop)


$\omega_{p2} = \omega_u$ (PLL loop)

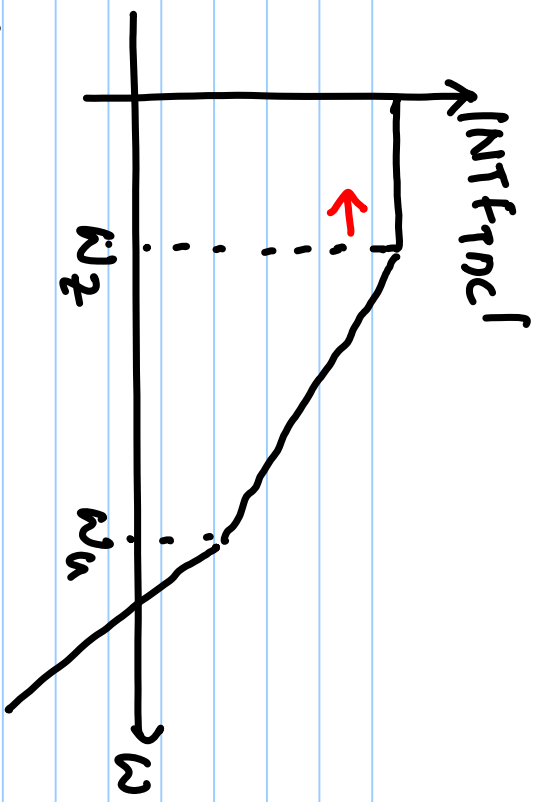

Noise BW = ω_{n2}
 -30dB/dec

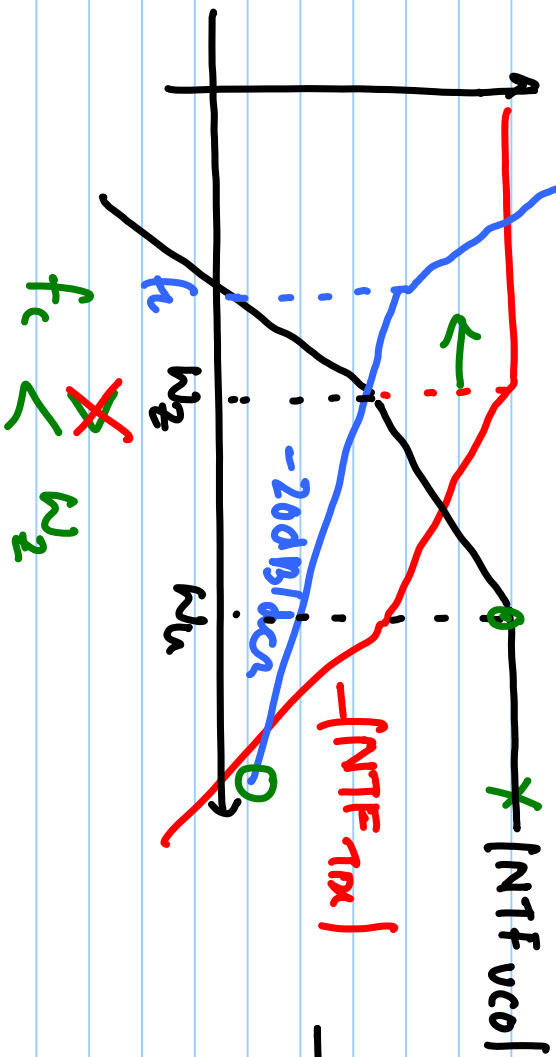

$\omega_c < \omega_{n2}$

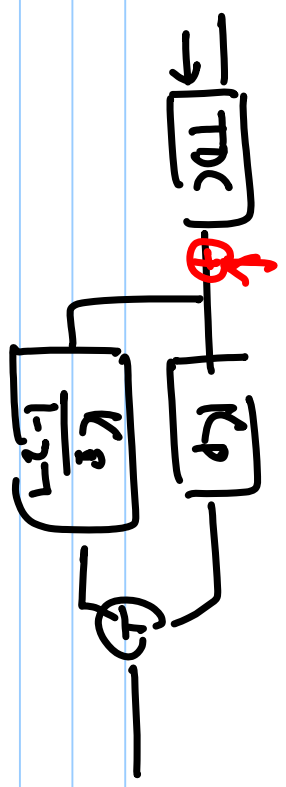


Noise BW = ω_n


$$NTF_{vco} = \frac{1}{1+L_n}$$

$\omega_{n2} \rightarrow 0$ — TDC noise reduces
 $\omega_{n2} \rightarrow 0$ — VCO flicker noise dominates

Fractional-N PLL

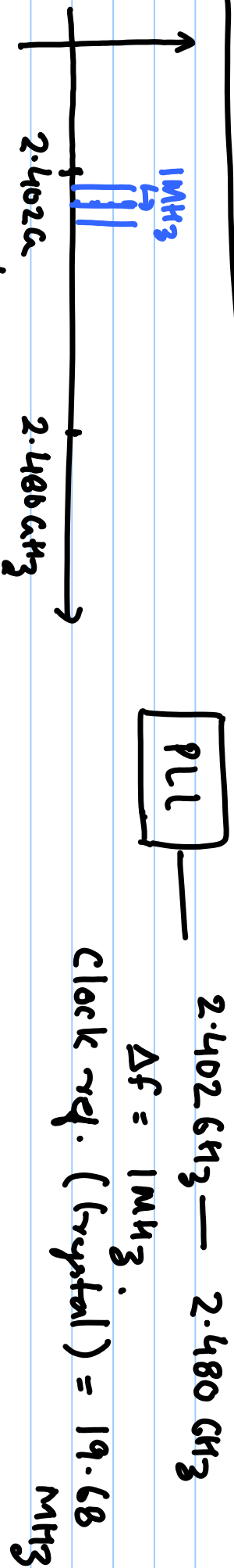

Ref - $[\div N_2]$ - f_{ref}
 19.68 MHz.

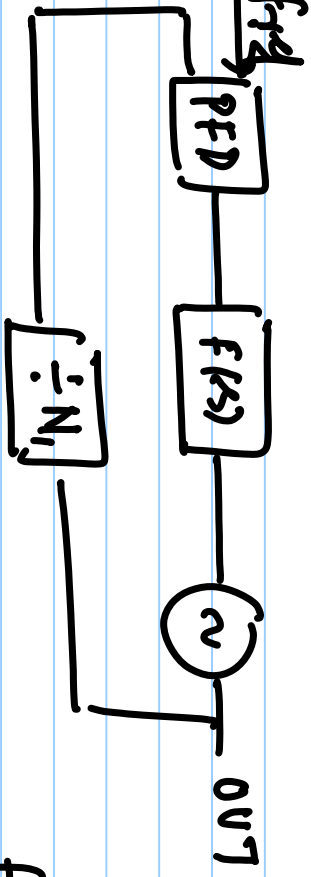

$$\frac{f_{out}}{N_2} = \frac{f_{out}}{N_1}$$

f_{ref} f_{out} N_1
 19.68 MHz 2.402 GHz 122.052846
 GCD (f_{out}, f_{ref}) = 868 kHz.
 $N_1 = 30256$

$$\frac{f_{out}}{f_{ref}} = \frac{N_1}{N_2} = \sqrt{\frac{240200}{1968}}$$

$$\frac{f_{ref}}{1968} = \frac{19680 \times 10^3}{1968} = 10 \text{ kHz}$$

$$80 \text{ kHz} \times 30280 = 2.402 \text{ GHz} ;$$

$$2.403 \text{ GHz}.$$

$$\Delta f = \frac{1 \text{ MHz}}{\frac{80 \text{ kHz}}{80 \text{ kHz}}} \longrightarrow 40 \text{ kHz}$$

$$N_1 = 60500$$