

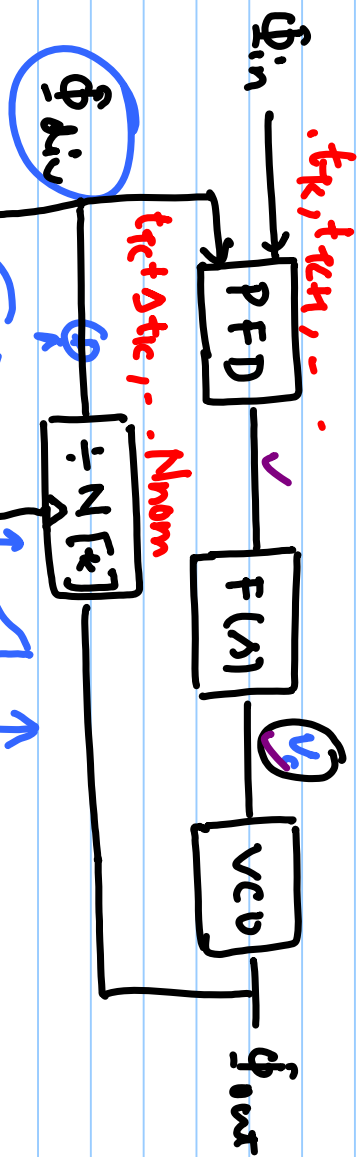


Lecture # 48

Fractional - N PLL

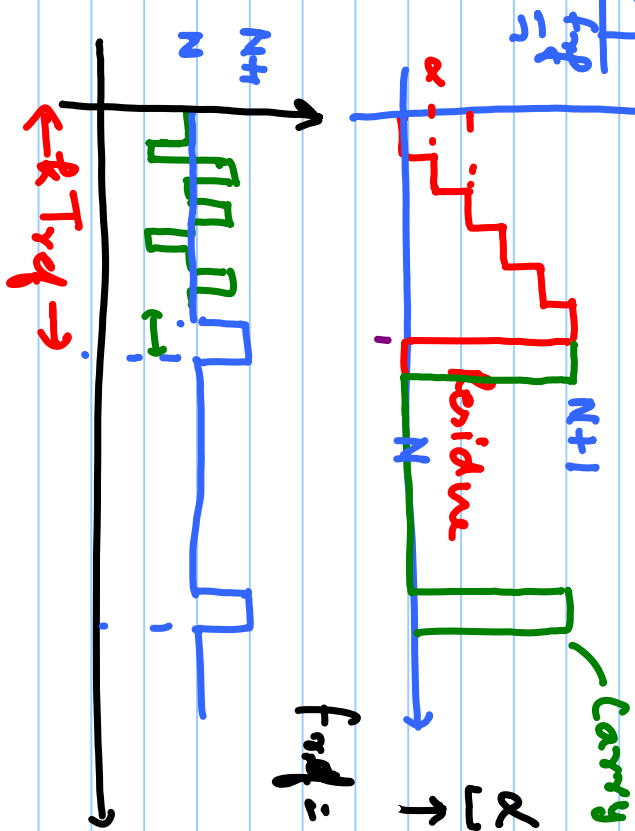

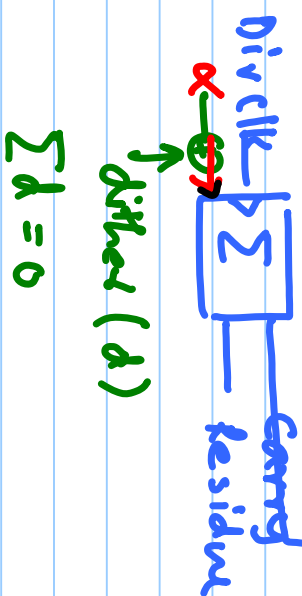$f_{out} = (N+d) f_{ref} = N_{nom} f_{ref}$
 $0 < \alpha < 1$
 $N_{div} \in [N-1, N, N+1]$







$f_{ref} = 40 \text{ MHz}$, $f_{out} = (16 + 0.001) \times 40 \text{ MHz}$
 $= 640 \text{ MHz} + 0.04 \text{ MHz}$
 α

3-bit LSB = $\frac{1}{2^3}$ (0, 0.125, 0.25, 0.5, 0.625, 0.75, 0.875)

$\alpha = 0.125$ $n = 3$ | 001 — [Σ] — 1-bit (Carry)
 Residue

$\alpha = 0.001$ $n = 10$ | 0000000000 — .1

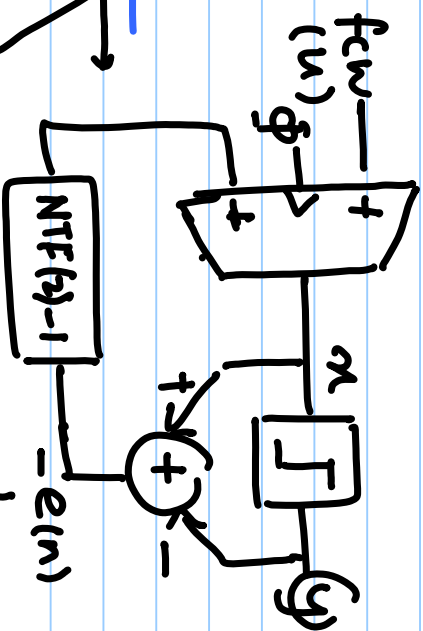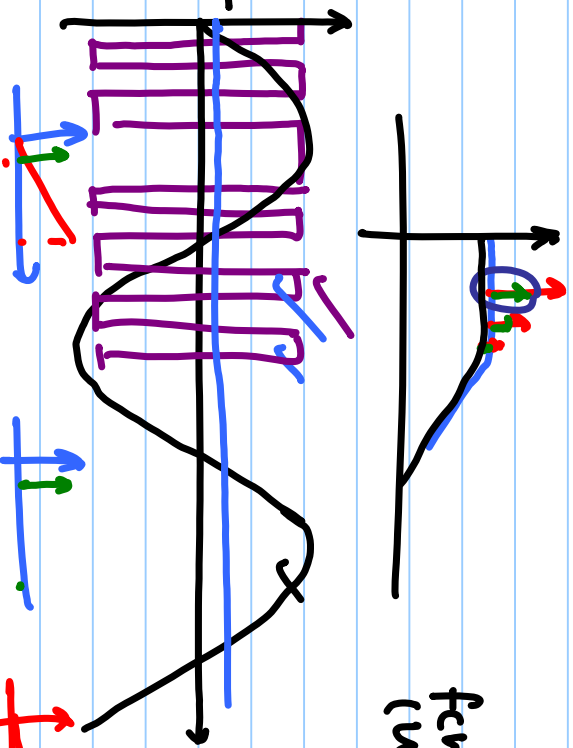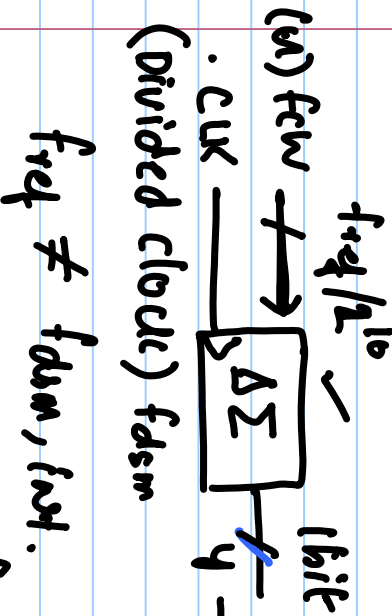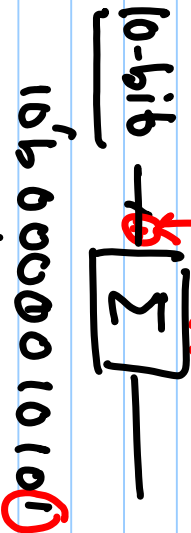Resolution of fractional freq, $\alpha = \frac{1}{\text{\# of bits in } f_{\text{res}}}$



OSR = $\frac{f_s}{2f_B}$

$Y(z) = \text{STF} \times U(z) + \text{NTF} \times E(z)$


Signal Transfer Fn. Noise Transfer Fn.

$$NTF(z) = (1 - z^{-1})^p$$

$$\checkmark NTF(z) = (1 - z^{-1})^2 =$$



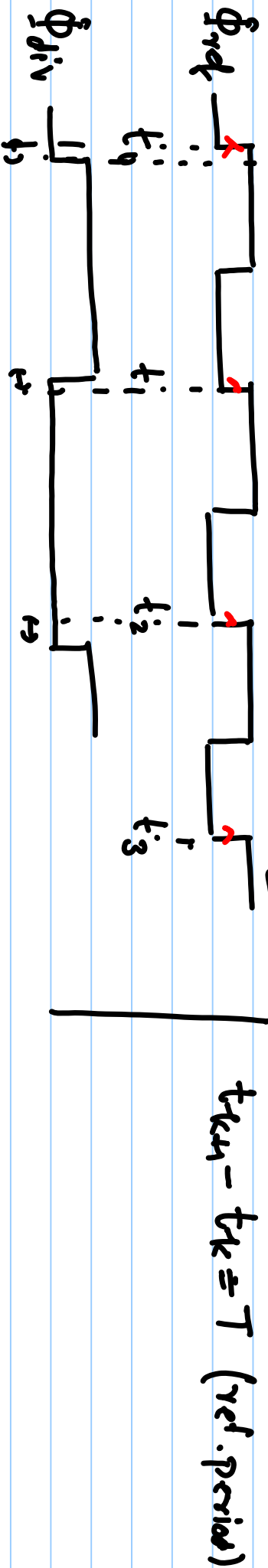1.) Ref. clock. has rising edge at $t = t_r$, $r \geq 0$



Time stamps for divided clock $t_r + \Delta t_r$.

$$\Phi_{err} = \frac{2\pi}{T} (t_r + \Delta t_r - t_r)$$

$$2) \Phi_{VCO} = 2\pi K_{VCO} \int V_{err} dt$$

from = $N_{nom} \cdot f_{ref}$

$$= \underbrace{2\pi}_{(N+r)}$$



$$\Phi_{\text{VCO}}(t_{r+1} + \Delta t_{r+1}) - \Phi_{\text{VCO}}(t_r + \Delta t_r) = \underline{2\pi N[r]}$$

$$= 2\pi f_{\text{nom}}(t_{r+1} + \Delta t_{r+1} - t_r - \Delta t_r) + \Phi_{\text{out}}(t_{r+1} + \Delta t_{r+1}) - \Phi_{\text{out}}(t_r + \Delta t_r)$$

$$= 2\pi f_{\text{nom}}(t_{r+1} - t_r) + 2\pi f_{\text{nom}}(\Delta t_{r+1} - \Delta t_r)$$

$$+ \Phi_{\text{out}}(t_{r+1} + \Delta t_{r+1}) - \Phi_{\text{out}}(t_r + \Delta t_r)$$

$$= \underbrace{2\pi f_{\text{nom}} \cdot T}_{\text{}} +$$

$$2\pi f_{\text{nom}}(\Delta t_{r+1} - \Delta t_r) = 2\pi(N[r] - N_{\text{nom}}) - (\Phi_{\text{out}}(t_{r+1} + \Delta t_{r+1})$$

$$- \Phi_{\text{out}}(t_r + \Delta t_r))$$