
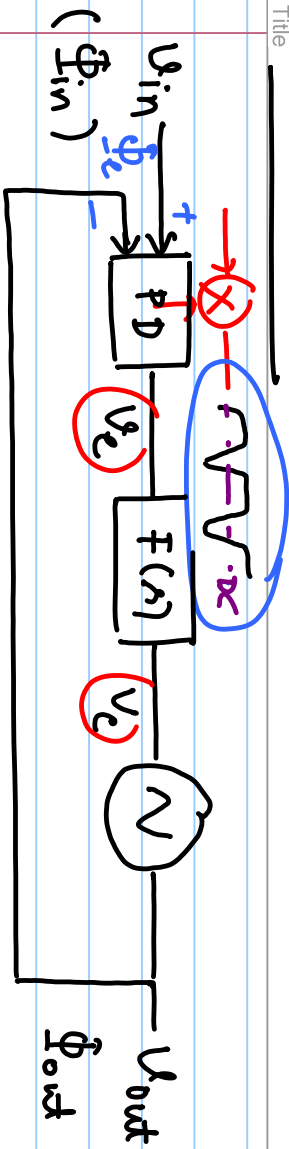


# Lecture # 6

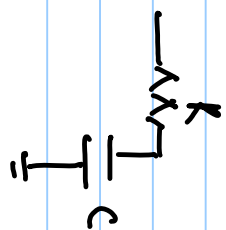

$\omega_{in}$  : Input freq.  
 $\omega_{out}$  : O/P freq.

Case 1:  $F(s) = \frac{1}{1+s/\omega_p}$



$\omega_{out} = \omega_{free} + 2\pi K_{vco} \cdot v_c$

at  $t=0$ ,  $v_c = 0$

$\Delta \omega = \omega_{in} - \omega_{out} = \omega_{in} - \omega_{free}$


$\Delta \omega > 2\pi K_{vco} \cdot K_{pd} F(0)$

Case 2:  $F(s) = \frac{1}{s}$

At  $\omega_{out} = \omega_{in}$   
 $t \rightarrow \infty$

$K = 2\pi K_{vco} \cdot K_{pd} F(0) \rightarrow \infty$

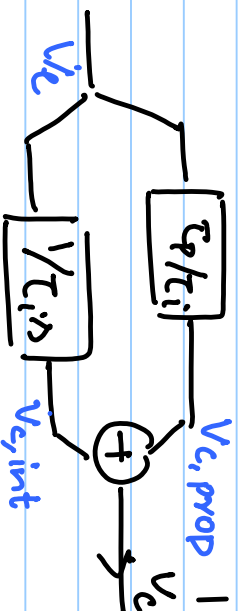Case 3:  $F(s) = \frac{1}{\tau_i s} + \frac{C_p}{\tau_i}$



$\Delta \omega_p < K \sqrt{\frac{2K_{vco}}{K} - 1}$


$K_{n1} = 2\pi C_{pd} K_{vco} F(0)$ ,  $K = 2\pi K_{pd} K_{vco} F(\infty)$

$$\Delta\omega = 2\pi K_{VCO} \cdot V_C = 2\pi K_{VCO} (V_{C,prop} + V_{C,int})$$

$= 0 \quad \neq 0$

$$\Delta\omega = 2\pi K_{VCO} \cdot V_{C,int} \rightarrow V_C = 0$$

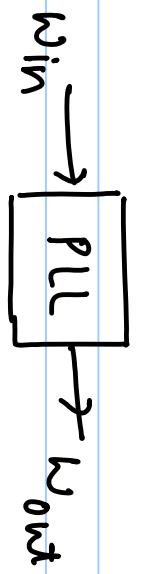1. Lock-in Range: <sup>( $\Delta\omega_L$ )</sup> Range of freq. ( $\Delta\omega$ ) PLL locks w/ cycle slipping.
2. Pull-in Range: <sup>( $\Delta\omega_P$ )</sup> Range of freq. PLL locks w/ cycle slipping.
3. Hold-in Range: <sup>( $\Delta\omega_H$ )</sup> Range of freq. PLL locks w/ cycle slipping.



$$t=0, \omega_0 = \omega_{out} = \omega_{in} \Rightarrow \Delta\omega = 0$$

$$\omega_{in} = \omega_0 + \Delta\omega \rightarrow \omega_{out} = \omega_0 + \Delta\omega$$



$$\omega_{in} = \omega_{out}$$

$$V_C = 0, V_C = \frac{\Delta\omega}{2\pi K_{VCO}} \rightarrow \frac{\Delta\omega'}{2\pi K_{VCO}}$$

Eg:  $\omega_{in} = \omega_{out} = 1 \text{ GHz}$

$$\Delta\omega_L = 50 \text{ MHz}$$

$$\Delta\omega_P = 200 \text{ MHz}$$

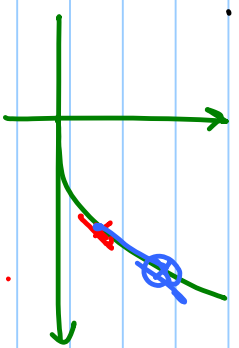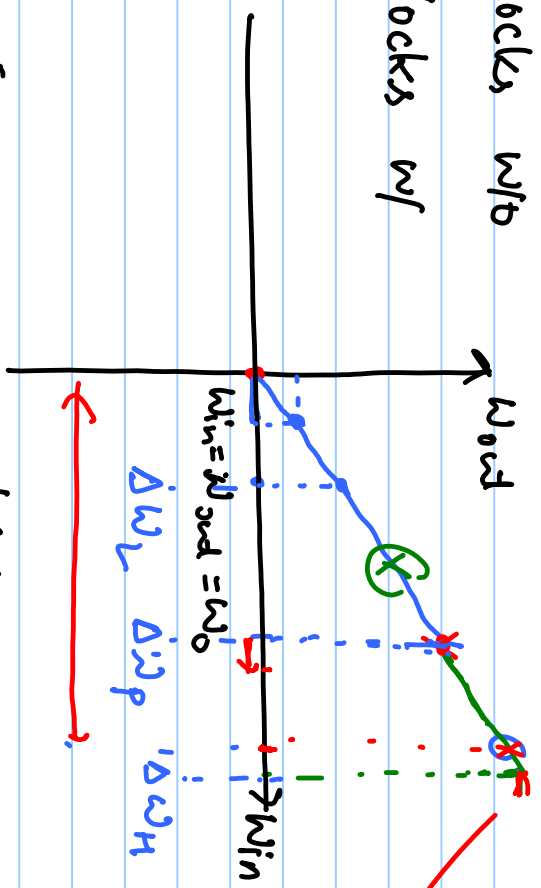

$$\Delta W_L = 10 \Delta W_1$$


$$\Delta W_P = 50 \Delta W_1$$

$$\Delta W_H = 70 \Delta W_1$$

at  $t=0$ ,  $\omega_{in} = \omega_{out}$

Case 1  $t < t_1$ ,  $\omega_{in} = \omega_0 + 49 \Delta \omega_1 \rightarrow \omega_0 + 50 \Delta \omega_1 < \Delta W_P$

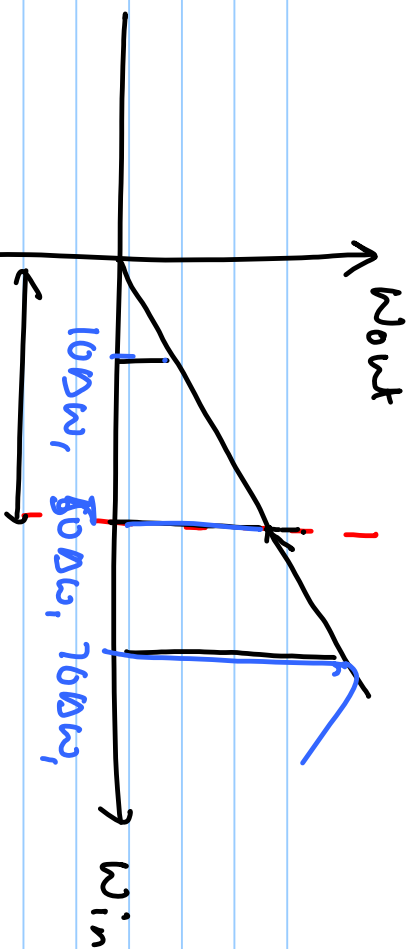Case 2  $t \geq t_1$ ,  $\omega_{in} = \omega_0 \rightarrow \omega_0 + 50 \Delta \omega_1$



$$\Delta W > \Delta W_P$$



$$\Delta W = 50.1 \Delta W_1$$

$$50 \Delta W_1 \rightarrow 50.001 \Delta W_1$$

$\Phi_e$	$V_e$	$V_e$	$\Delta W$
	0.47	$\chi_e?$	50 $\Delta W_1$
		$V_e$	50.001 $\Delta W_1$

$$V_c = V_{c,prop} + V_{c,int}$$
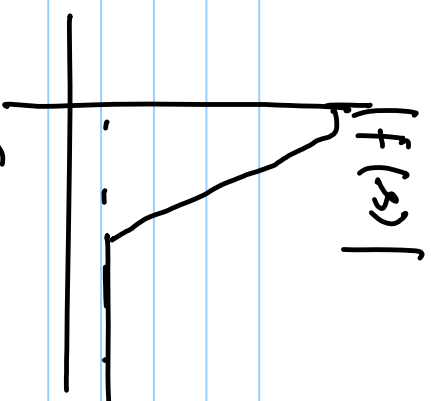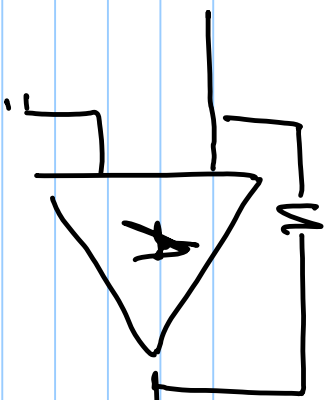
$$V_c = \frac{T_P}{T_i} V_e + V_{c,int}$$



$$\Delta \omega = 60 \Delta \omega_1 \rightarrow V_c = \frac{60 \Delta \omega_1}{2\pi k_{vco}} \rightarrow (V_e) \rightarrow (\phi_e)$$

