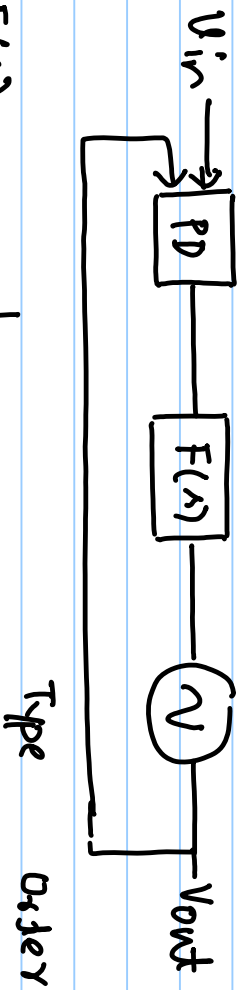


# Lecture #7



Case 1:  $F(s) = \frac{1}{1+s/\omega_p}$

Type	1	2
Order	1	2

Case 2:  $F(s) = \frac{T_i}{T_i s} + \frac{1}{T_i s}$


Type	2	2
Order	2	2

Freq. acquisition ranges

1. Lock-in range
2. Pull-in range
3. Hold-in range


Open loop gain =  $LC = K_{pd} F(s) \frac{2\pi K_{uc0}}{s}$

Type	Order
# of integrators	# of poles

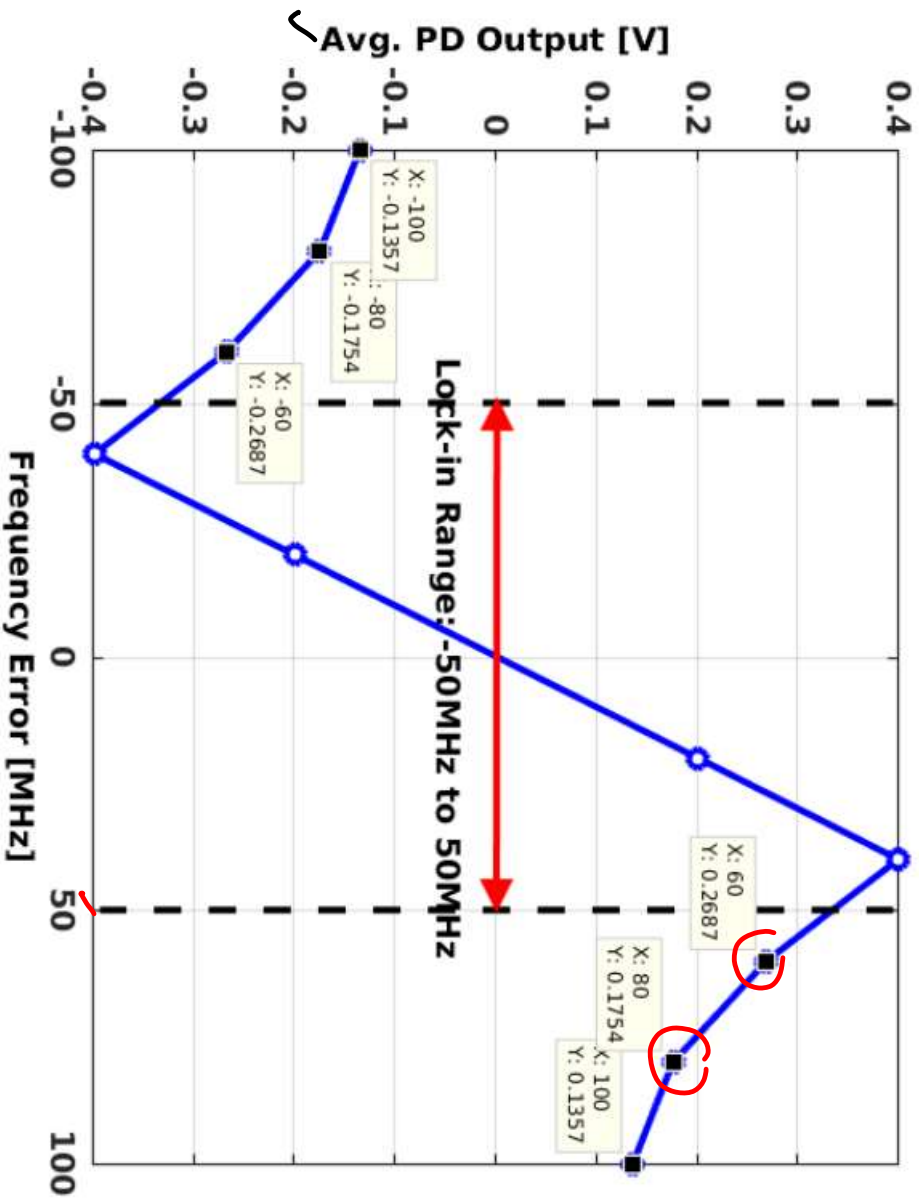


Type-I Order-2 PLL

$$K_{VCO} = 100 \text{ MHz/V}$$

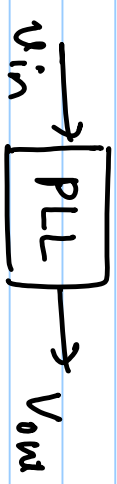


$$f_{in} = 1 \text{ GHz}, \quad f_{out} = 1 \text{ GHz}$$

$\Delta \omega_{in}$

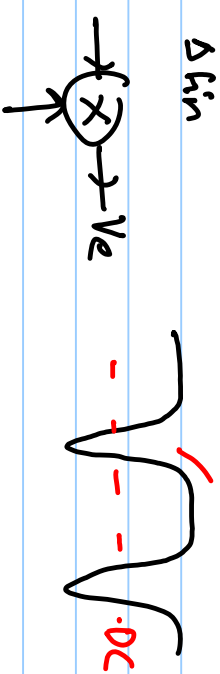
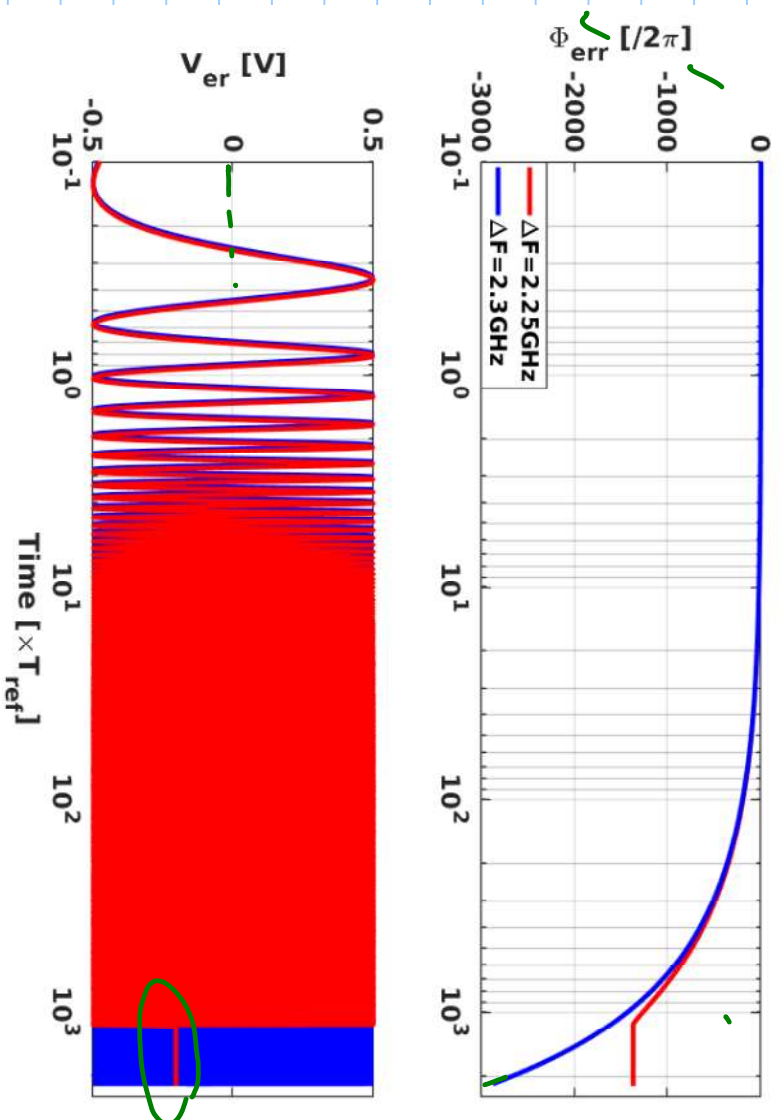
$$\frac{\Delta \omega}{2\pi k_{pd} k_{vco}} \leq 1$$



$$V_{er} = \frac{1}{2} \sin(\Phi_{er})$$

## Type-II Order-2

$$\Delta f_1 = 2.25 \text{ GHz}$$


$$\Delta f_2 = 2.3 \text{ GHz}$$



$$\Delta \omega \leq K \sqrt{\frac{2K_{DC}}{K} - 1}$$

$$f_{in} = 1 \text{ GHz}, \quad f_{out} = f_{ref} = 1 \text{ GHz}$$

$$\Delta f = 2.25 \text{ GHz}$$
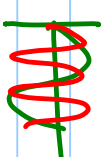
$$\Phi_{ref}(f) = (\omega_{in} - \omega_{ref}) \cdot t$$



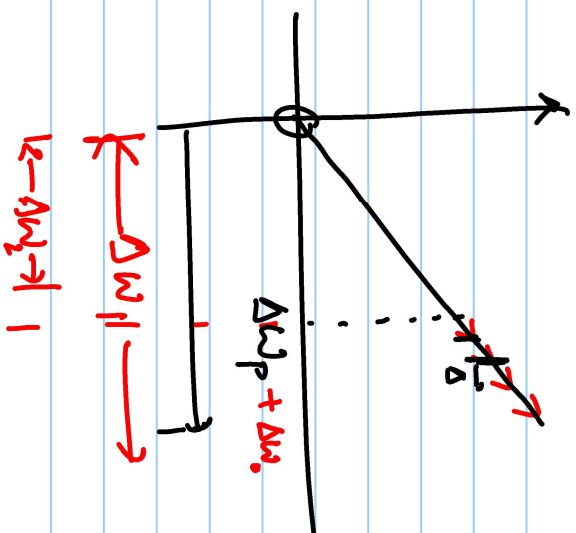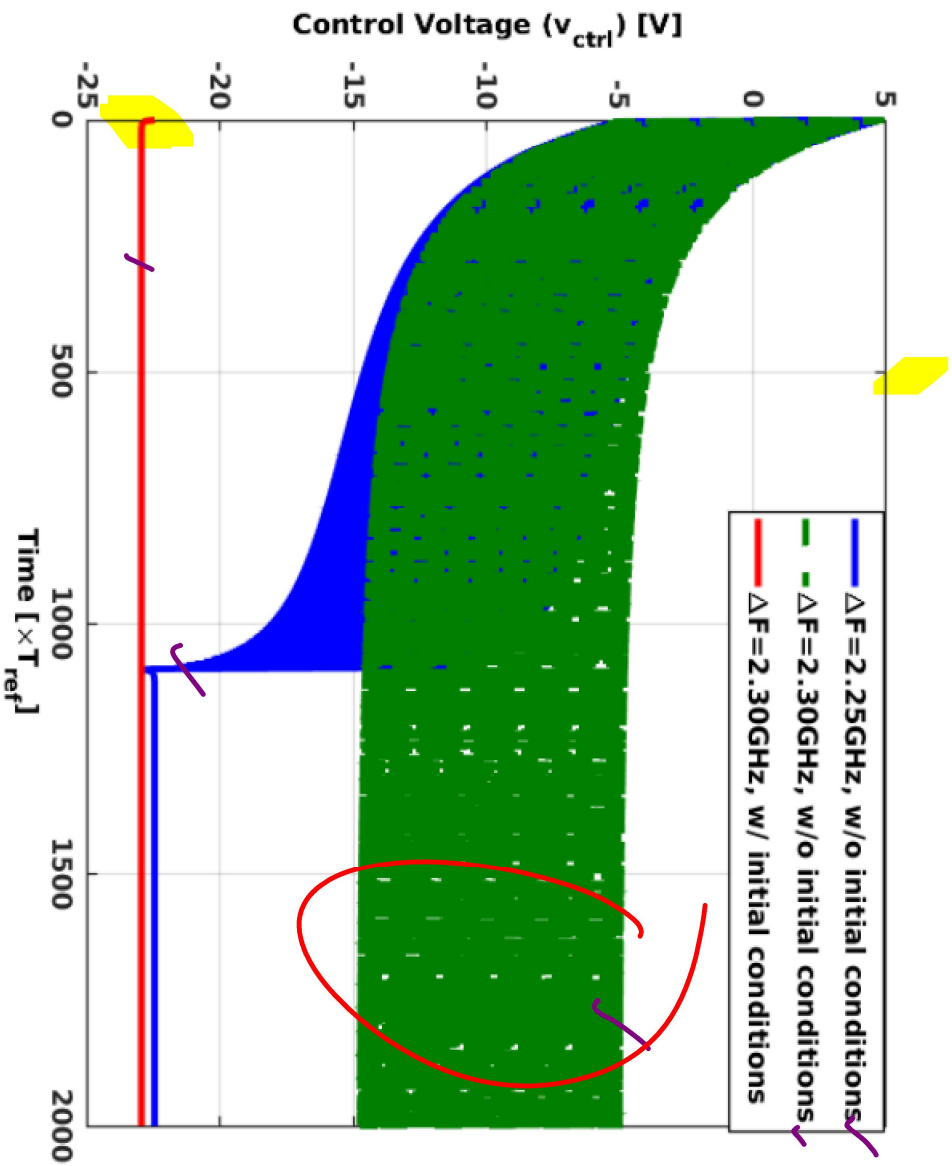




$$L_n = \frac{K_{pd} F(s) 2\pi K_{vco}}{s}$$

$$\lim_{t \rightarrow \infty} \dot{\Phi}_e(t) = \lim_{s \rightarrow 0} s \dot{\Phi}_e(s) = 0.6$$


$$\lim_{t \rightarrow \infty} V_e(t) =$$
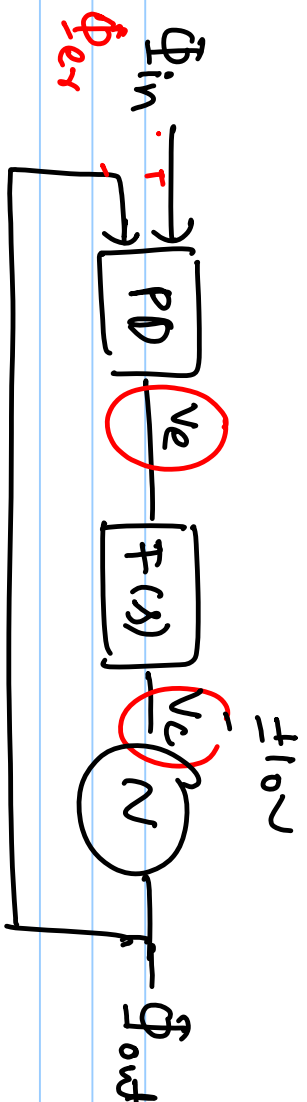
$$\lim_{t \rightarrow \infty} V_e(t) = 110$$



$$\frac{\Phi_{owl}(s)}{\Phi_{in}(s)} = \frac{L_n}{1+L_n}$$
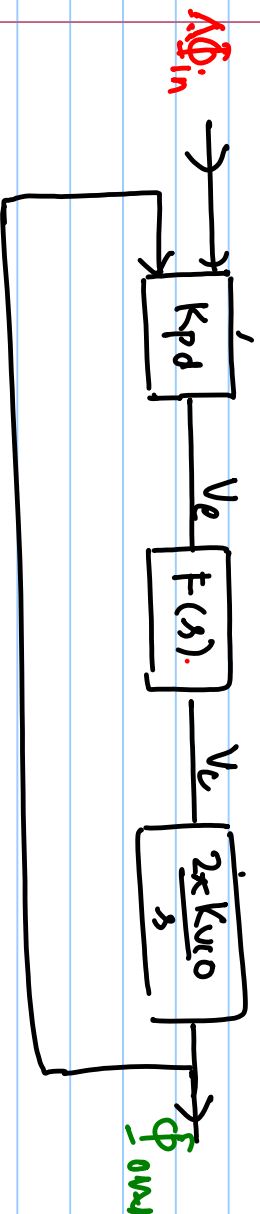
$$\frac{\Phi_{owl}(s)}{\Phi_{in}(s)} = \frac{1}{s} \frac{L_n}{1+L_n}$$




$$\Phi_e = \pi/3$$


$$V_e = \frac{\sqrt{3}}{2} \times \frac{1}{2}$$

$$F(s) \Big| =$$
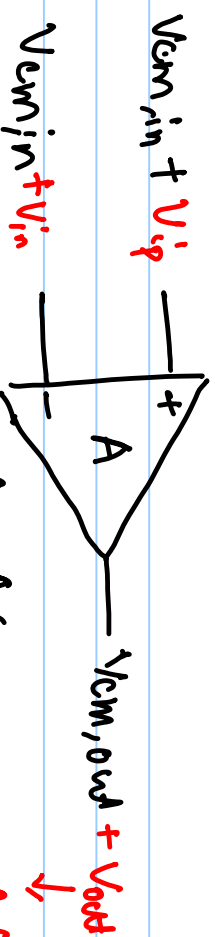
$$V_{owl} = \sin(2\pi f_{F_{vco}} t + 2\pi K_{vco} \int V_e dt)$$


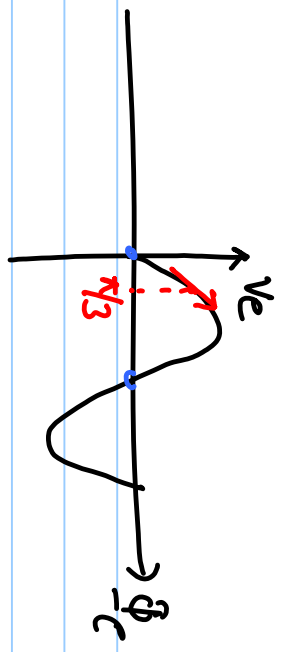
$$A = \frac{A_0'}{1 + s/\omega_p} = A(V_{ip} - V_{in})$$



$$\Delta V_c = K_{pd} \times \Delta \Phi_{in}$$

$$\Delta V_c = F(s) \times \Delta V_c$$

$$N_{D,out} = K_{uo} \cdot \Delta V_c$$

$$B_{D,out} = \frac{2 \times \Delta V_{out}}{s}$$

$$V_c = V_{cst} + K_{pd} \cdot \Delta \Phi_{in}$$

