
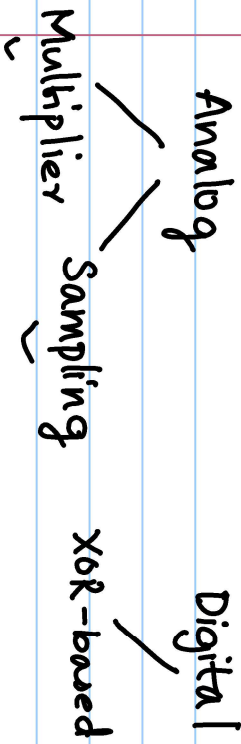



Lecture # 9

Phase Detectors

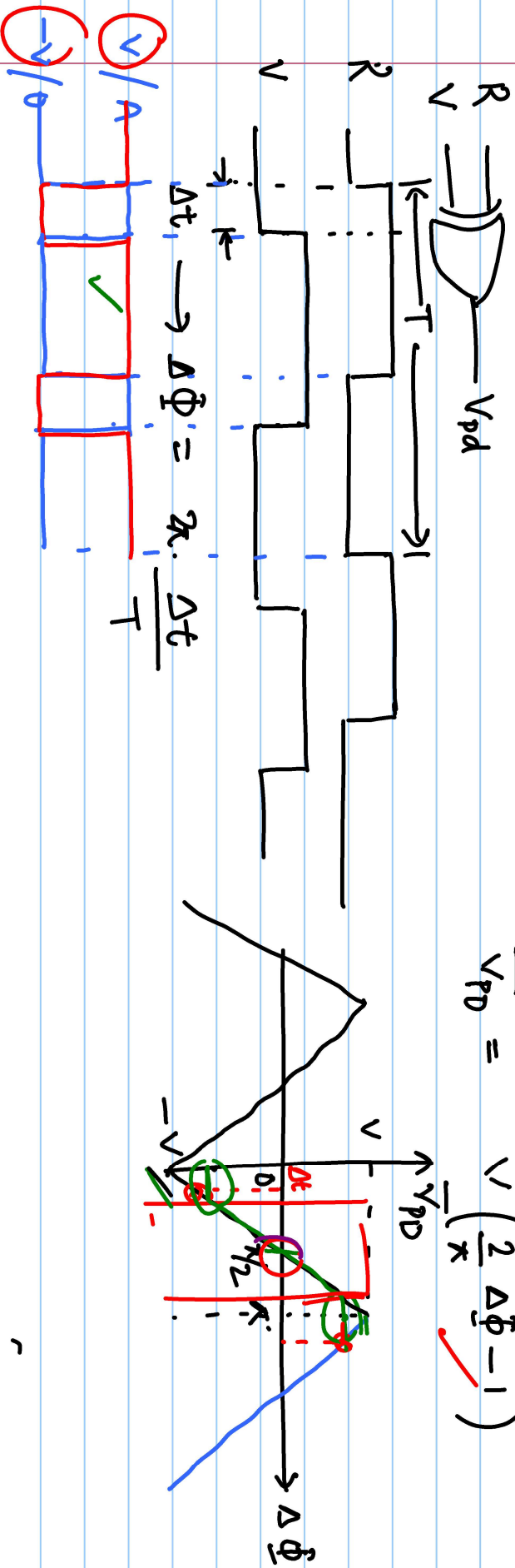

XOR-based PD



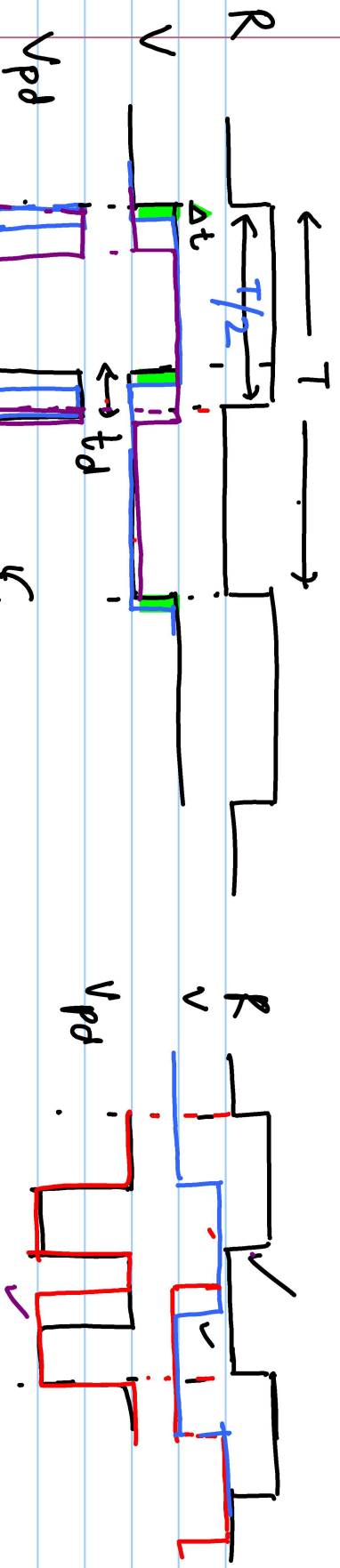


$$1) \overline{V_{pd}} \Big|_{\Delta t=0} = \frac{1}{T} (V \times t_d - V (T - t_d)) = \frac{V}{T} (2t_d - T) = \underline{V \left(\frac{2t_d}{T} - 1 \right)}$$

$$2) \overline{V_{pd}} \Big|_{\Delta t < t_d} = \frac{1}{T} (V \times \Delta t + V (t_d - \Delta t) - V (T - t_d)) =$$

$$\frac{2V \Delta t}{T} < \frac{2V t_d}{T}$$

$$\Delta \phi < \Delta \phi_0$$

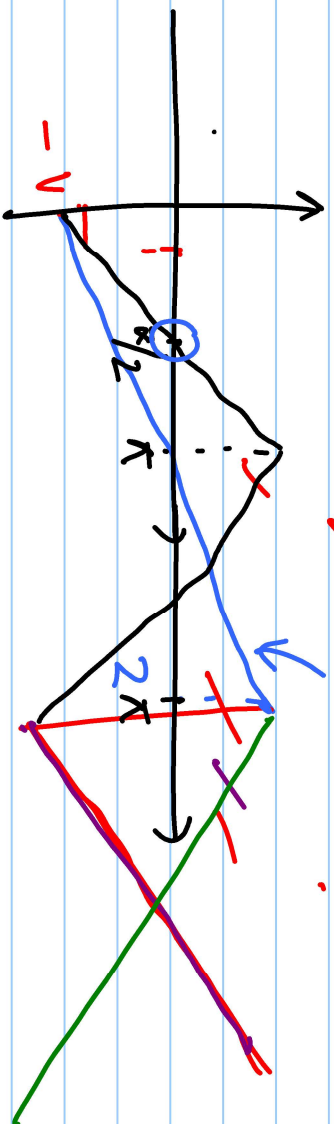


∴

$$V_1 = \sin(\omega_0 t + \phi_1)$$

$$V_2 = \sin(\omega_0 t + \phi_2)$$


$$\phi_2(0) - \phi_1(0)$$

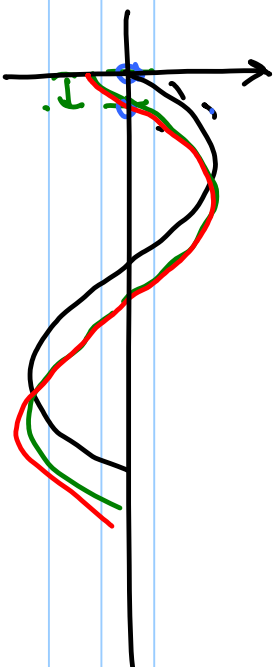

$$\phi_1(t) = \omega_0 t + \phi_1(0)$$

$$\phi_2(t) = \omega_0 t + \phi_2(0)$$
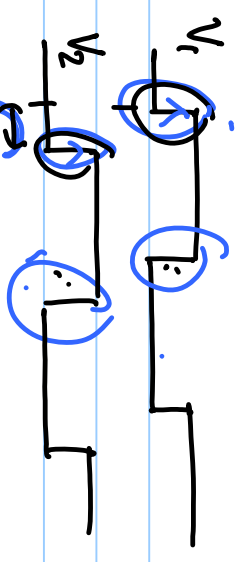
$$\begin{aligned} \phi_1(t) - \phi_2(t) &= \phi_1(0) - \phi_2(0) = \phi_{\text{eff}}(\Delta t) \\ &= 2\pi \cdot \frac{\Delta t}{T} \end{aligned}$$




$$V_1 = \sum \sin(n\omega_0 t + \phi_{n1}(0))$$

$$V_2 = \sum \sin(n\omega_0 t + \phi_{n2}(0))$$

$$\Delta \phi = 2\pi \cdot \frac{\Delta t}{T}$$

SR-FlipFlop based PD

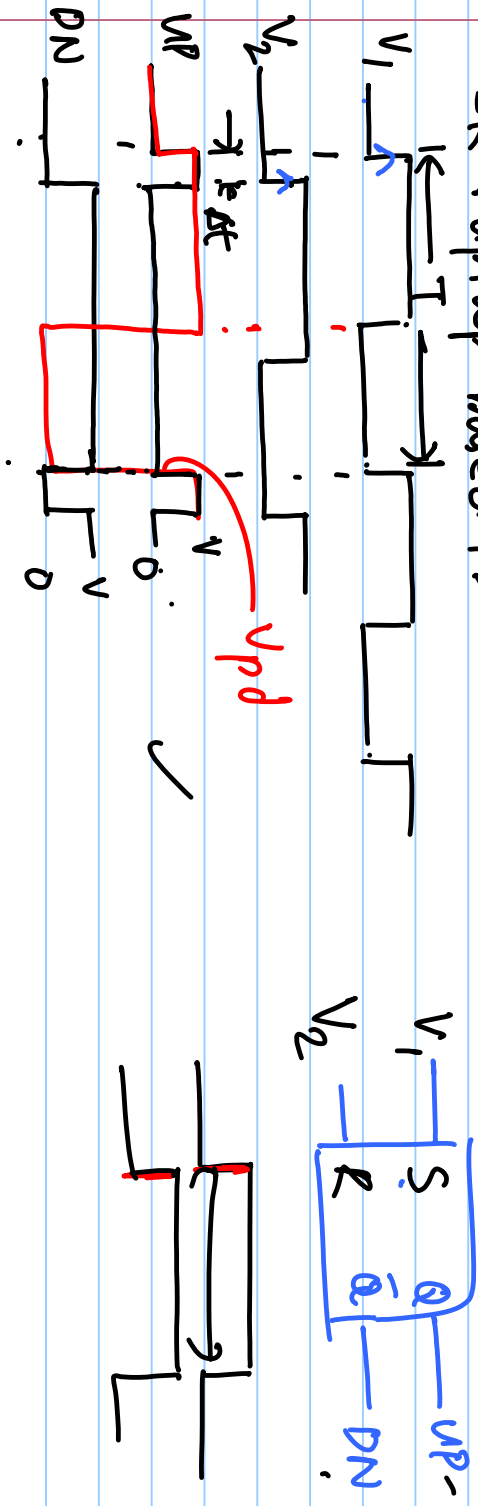

$$V_{PD} = WP - DN$$

$$\begin{aligned} \overline{V_{PD}} &= \overline{WP - DN} = \frac{V_r \Delta t - (T - \Delta t)V}{T} = \frac{V}{T} (2 \cdot \Delta t - T) = V \left(2 \frac{\Delta t}{T} - 1 \right) \\ &= V \left(\frac{2 \cdot \Delta t}{2\pi} \cdot 2\pi \frac{\Delta t}{T} - 1 \right) = V \left(\frac{1}{\pi} \Delta \Phi - 1 \right) \end{aligned}$$

