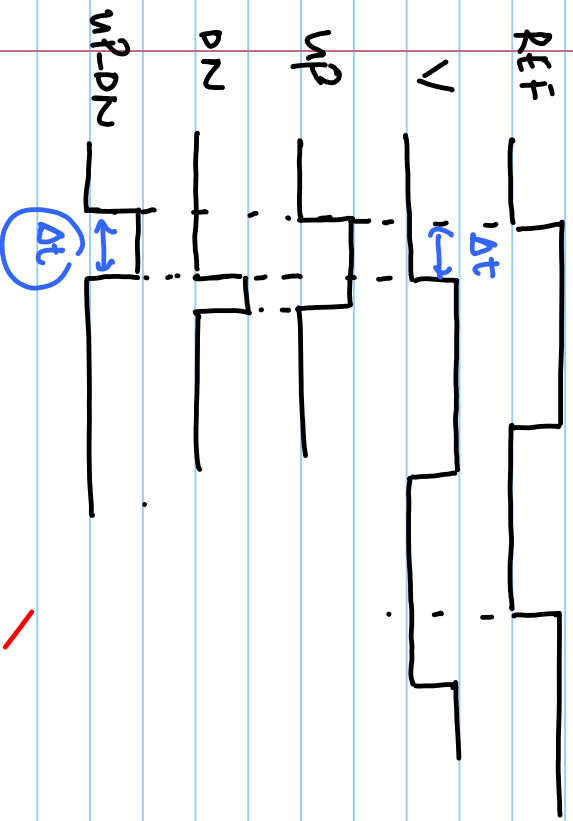


Lecture # 13






$$V_{err1} = V (1 - e^{-t/RC})$$

$$= V (1 - e^{-\Delta t/RC})$$

$$\approx V \left(1 - \left(1 - \frac{\Delta t}{RC} \right) \right) = V \cdot \frac{\Delta t}{RC}$$

Voltage-loop phase error to V_{err1}

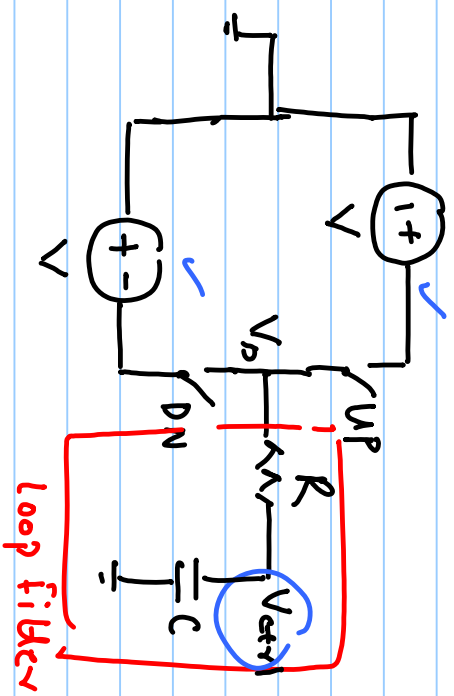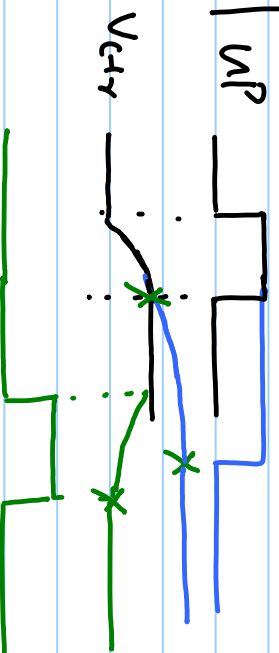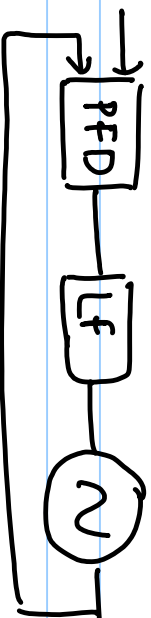

A

Current-based $\Phi_c \rightarrow V_{str1}$

$$V_{str1}(\Delta t) = \frac{I_{cp} \cdot \Delta t}{C}$$

$$= \frac{I_{cp}}{C} \frac{T}{2\pi} \frac{2\pi \cdot \Delta t}{T}$$

$$= \frac{I_{cp}}{2\pi} \cdot \frac{T}{C} \Phi_c$$

$$V_{str1}(n+1T) = V_{str1}(nT) + \frac{I_{cp} \cdot \Delta t(nT)}{C}$$





T: Rq period

$$= V_{str1}(nT) + \frac{I_{cp}}{2\pi} \frac{T}{C} \Phi_c(nT)$$

$$V_{str1}(nT) = \frac{I_{cp}}{2\pi} \frac{T}{C} \Phi_c(nT)$$

$$V_{str1}(z) = \frac{I_{cp}}{2\pi} \frac{T}{C} \frac{\Phi_c(z)}{z-1}$$

Charge-pump.

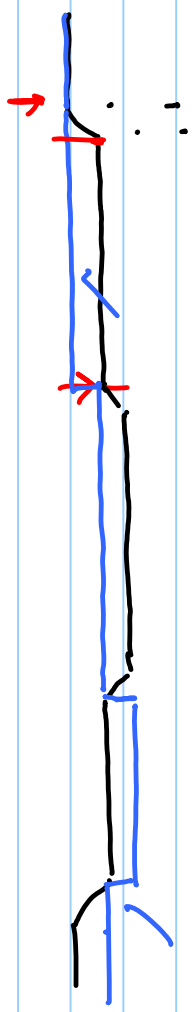
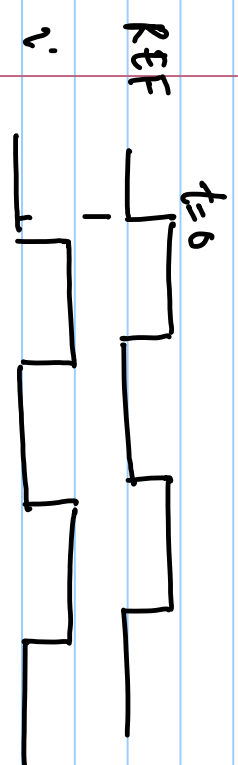
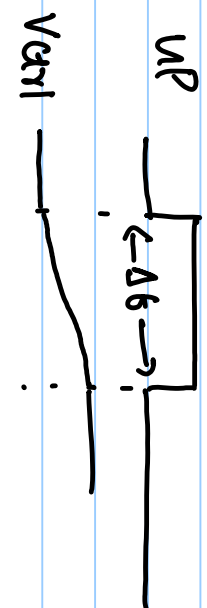
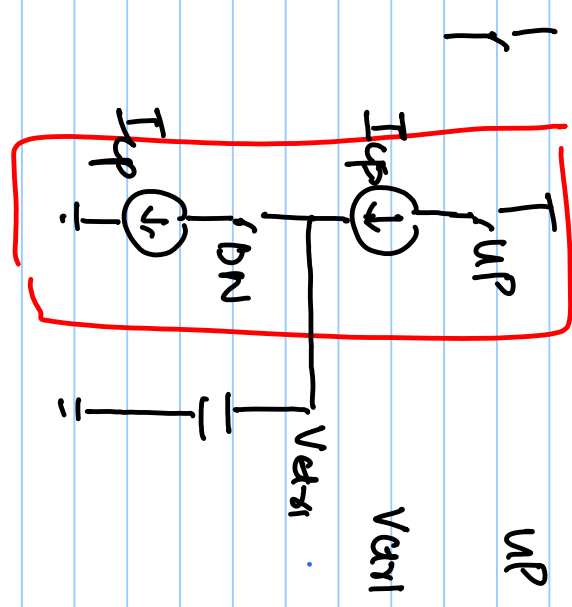


$z = e^{sT}$




$$V_{CM}(s) = \frac{I_{CP}}{2R} \frac{1}{C(sT)} \Phi_c(s)$$


; $sT \ll 1$
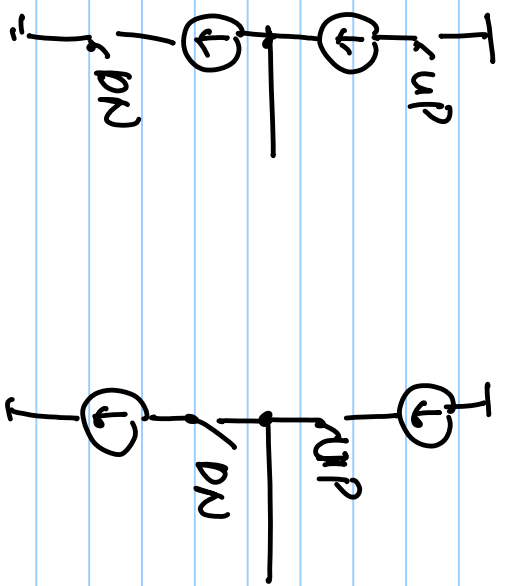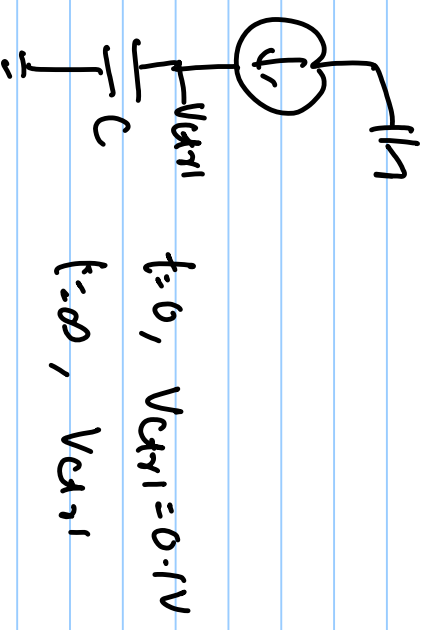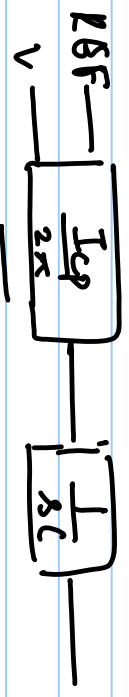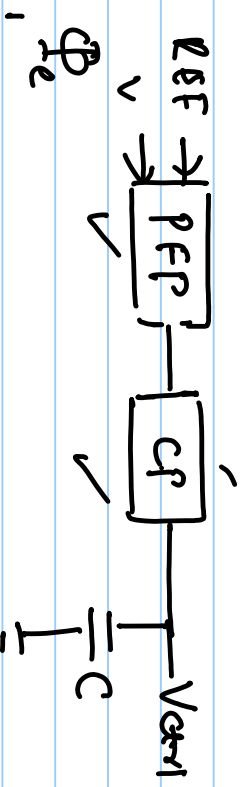
$$V_{CM}(s) = \frac{I_{CP}}{2R} \frac{1}{sC} \Phi_c(s)$$



$t=0, V_{CM}=0.1V$
 $t=\infty, V_{CM}$

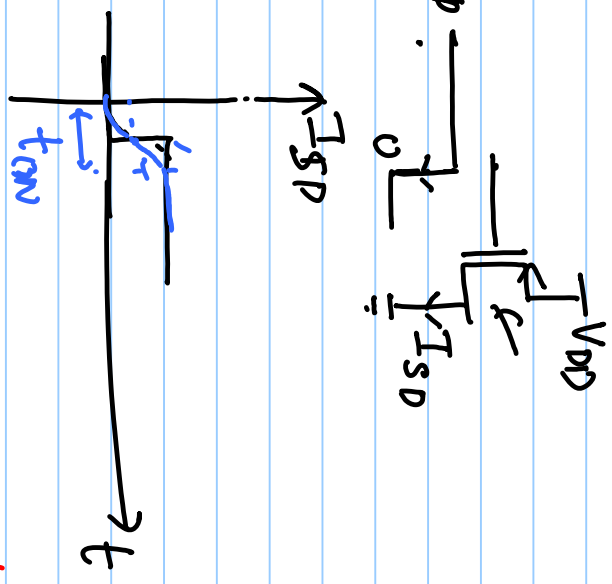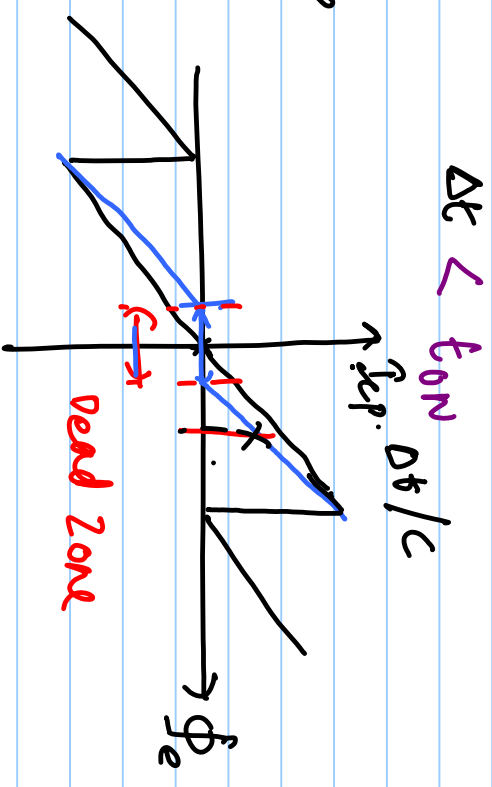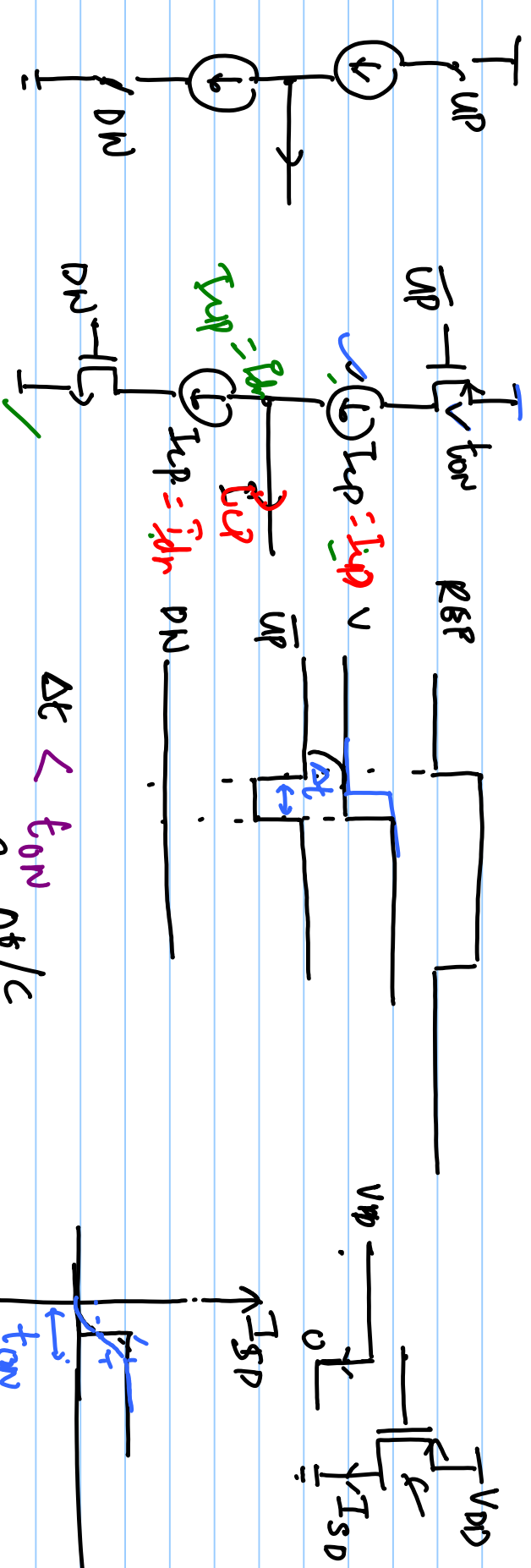

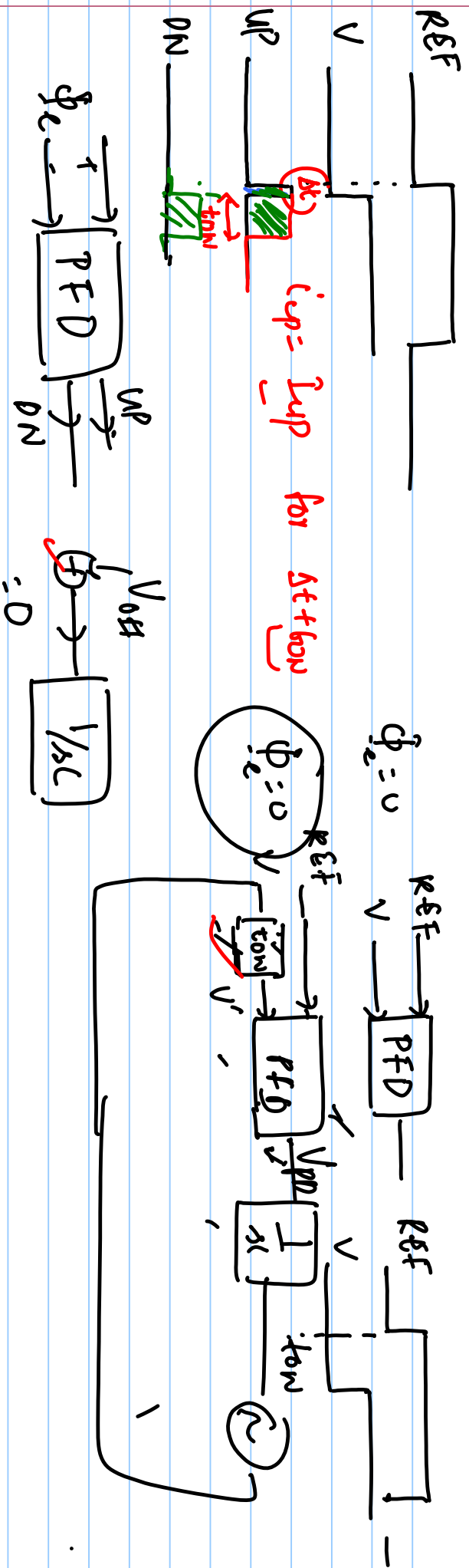

$$\Delta V_{out} = \frac{I_{cp} \cdot t_{on}}{C}$$