

# Lecture # 18

Note Title

06-09-2018



$$\left. \frac{\Phi_{out}}{\Phi_{in}} \right|_{\omega_{loop}} = L_u = \frac{1}{2\pi} I_{cp} \frac{1}{s(C_1+C_2)} \frac{(1+sRC_1)}{(1+sRC_1C_2)}$$

$$M_u \leq \frac{\omega_{ref}}{10}$$



$$|L_u| M_u \approx 1$$


$$\Rightarrow \frac{I_{cp}}{\omega_u^2 (C_1+C_2)} \frac{M_u \cdot R C_1 \cdot K_{vco}}{N} = 1$$

$$\omega_{out} = N \omega_{ref}$$

$$\omega_{in} = \sin(\omega_{in} \cdot t)$$
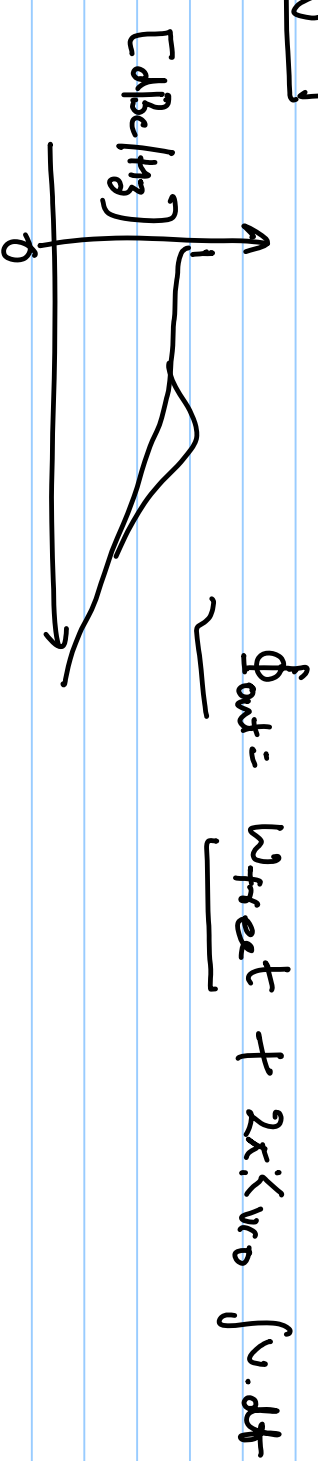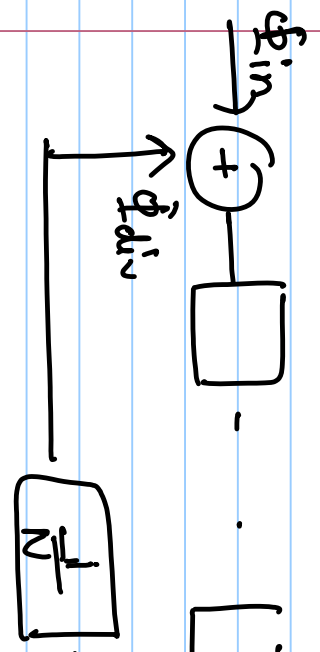
$$\omega_{out} = \sin(\omega_{out} \cdot t)$$



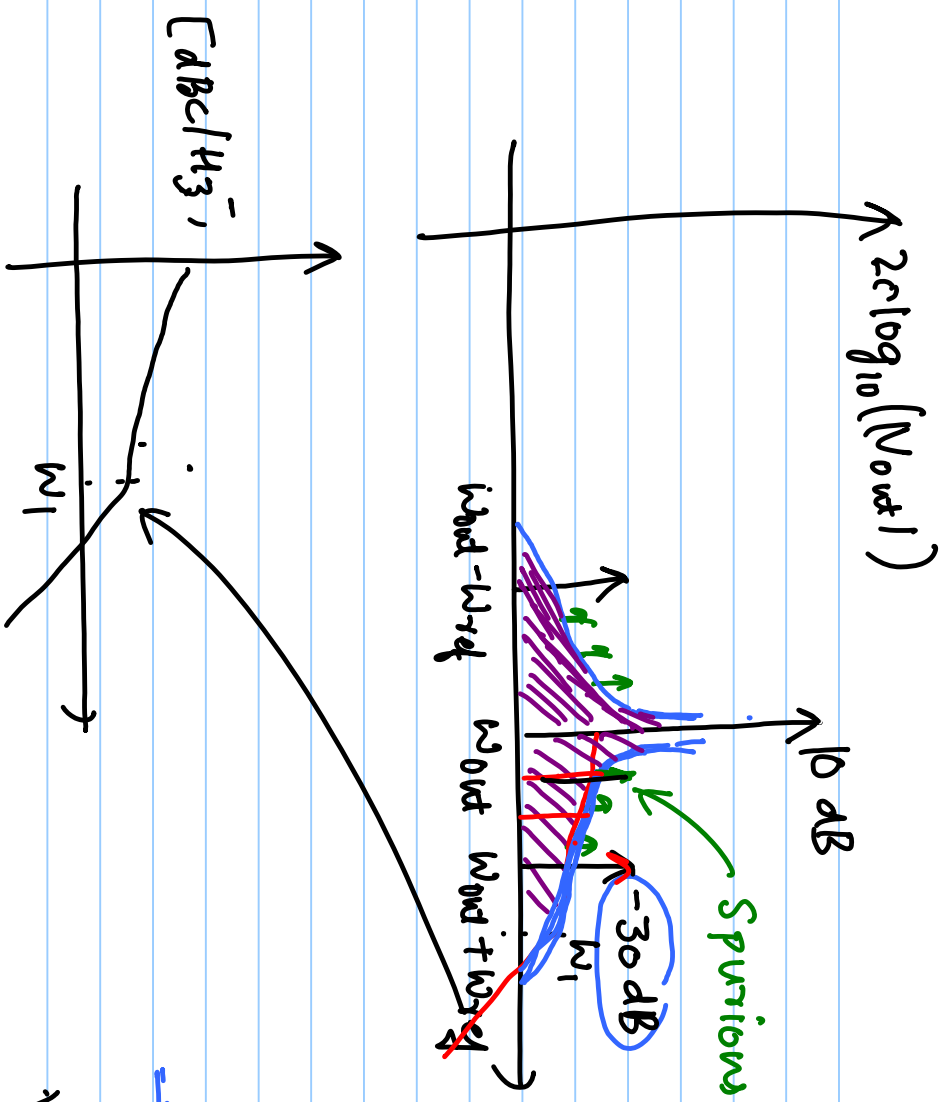

Ref. spur =  $N_{sig}$  of voltage signal

$\ominus \omega_{out} \pm \omega_{ref}$

$= -30 - (10) = -40$   
[dBc]





Fractional - spur

$$V_{c1} + V_{c2} = \sin(\omega_0 t + 2\pi K_{vco} (V_c) / \omega_0) + \sin(\omega_0 - \omega_{ref})$$

$V_{c1} = a_1 \sin(\omega_{ref}/\omega_0 \cdot t)$

$V_{c2} = a_2 \sin(\omega_{ref}/\omega_0 \cdot t)$

$\omega_{ref} = \omega_{sig}/20$

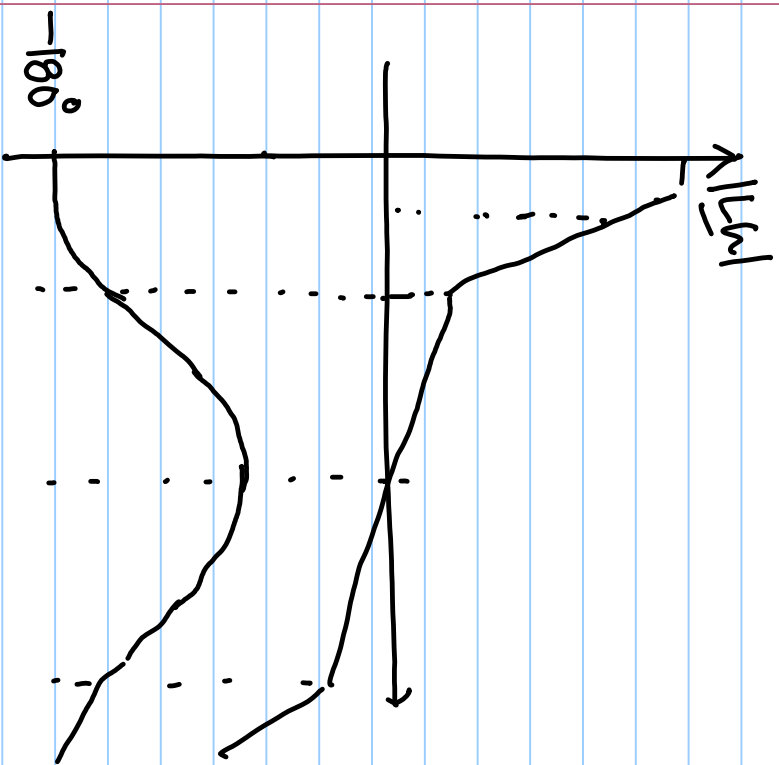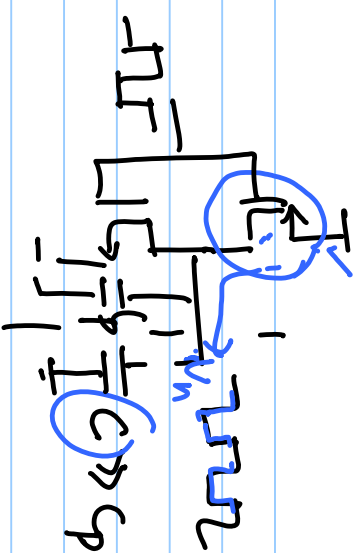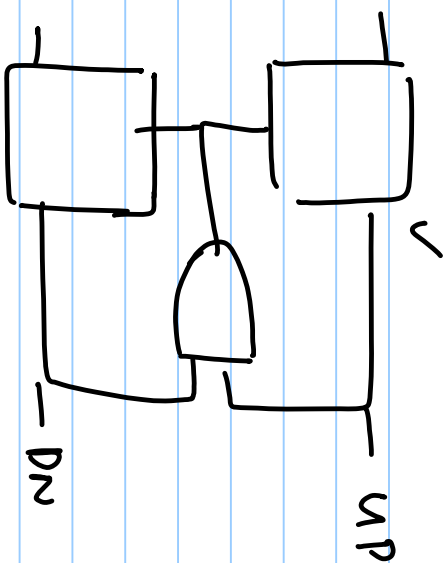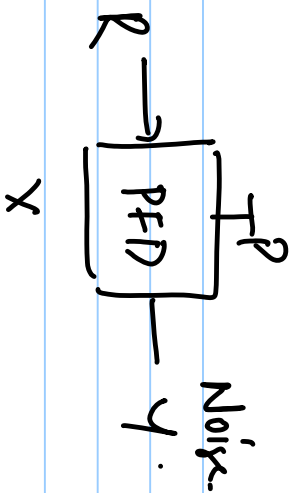

$$|L_u(\omega)| = A \angle 180^\circ = -A$$

$|L_u| > 1$  ,  $\angle L_u = 180^\circ$  Sustained Oscillations

