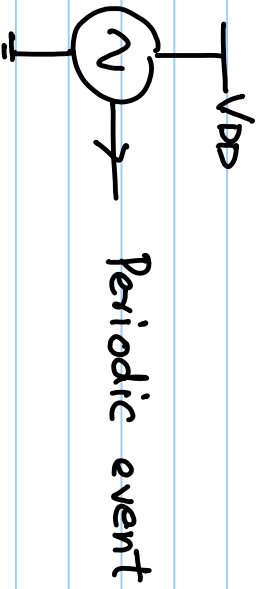




Lecture # 19

Oscillator VCO: Voltage Controlled Oscillator
 CCO: Current "



Crystal Oscillators (f_0)

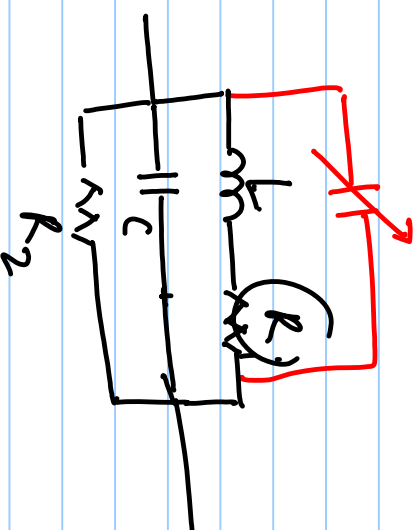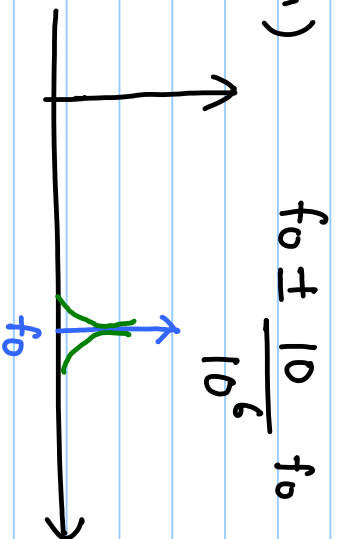- Frequency Stable (10-100 ppm)
- Excellent phase noise
- low frequency
- low tunability.
- Large form-factor.





Tuned Oscillators


- L, C (1 peak no freq. limitation)
- Frequency stability moderate.
- Phase noise is good.

- large size $M_0 = \frac{1}{\sqrt{LC}}$
- $56 \text{ Hz} \rightarrow 2f_0 \rightarrow 10 \text{ MHz}$

$2X$

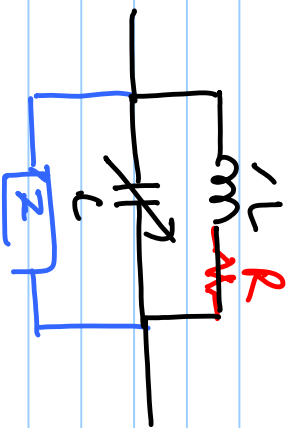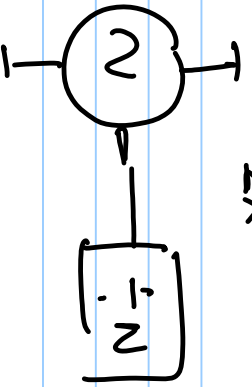





$$M_0 = \frac{1}{\sqrt{LC}}$$

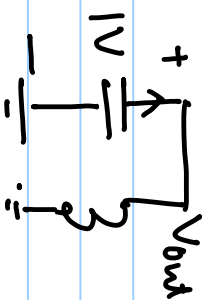

at $t=0$, $V_{out} = 1V$

$$-C \frac{dV}{dt} = -I_L$$


$$V = L \frac{dI_L}{dt}$$

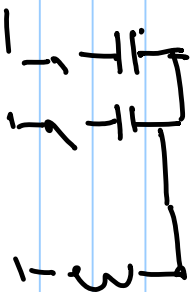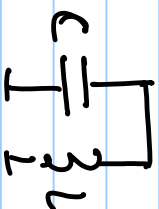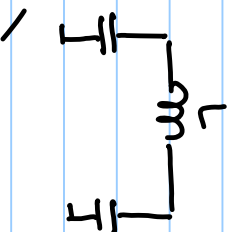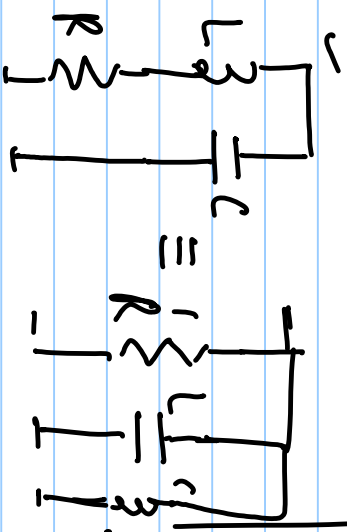

Ring Oscillators.



- Wide frequency range ✓
- Small form factors ✓
- Phase noise is poor.
- Frequency stability is poor.

$$f_0 = \frac{1}{6td}$$

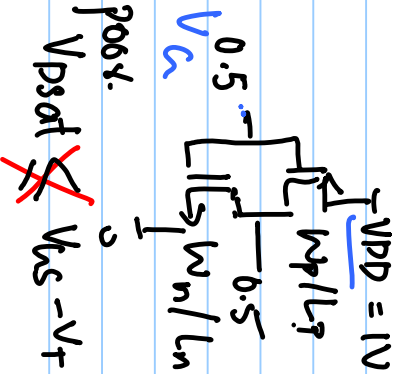

$$V_{DD} > V_{TN} + |V_{TP}| \quad \checkmark$$
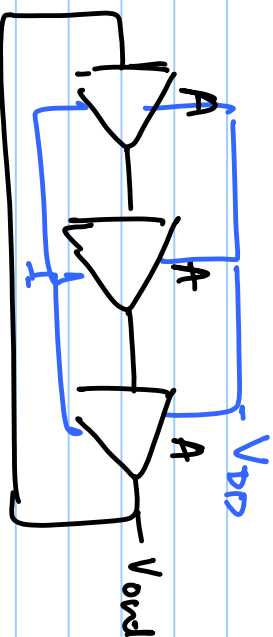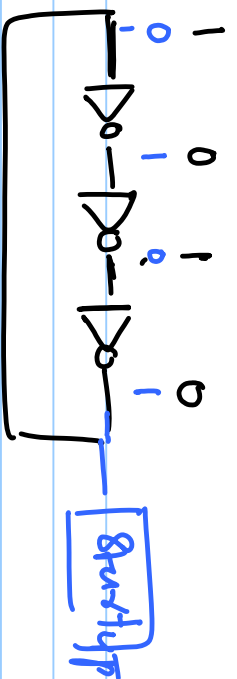
$$0 \leq V_G \leq V_{DD} \quad \checkmark$$



$$A = \frac{-A_0}{(1 + s/\omega_p)}$$

$$L_G = \left[\frac{-A_0}{(1 + s/\omega_p)} \right]^3$$

$$|L_G(\omega_{osc})| = 1$$


$$\angle L_G(\omega_{osc}) = 2\pi m$$

Small-signal swing Oscillators


Large signal swing Osc.



$$A(s) = \frac{-A_0}{1+s/\omega_p}$$

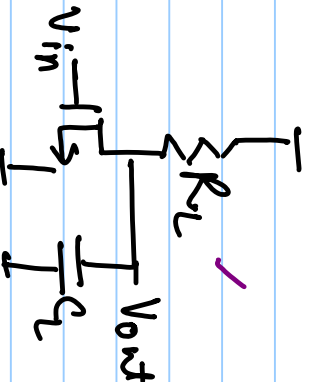
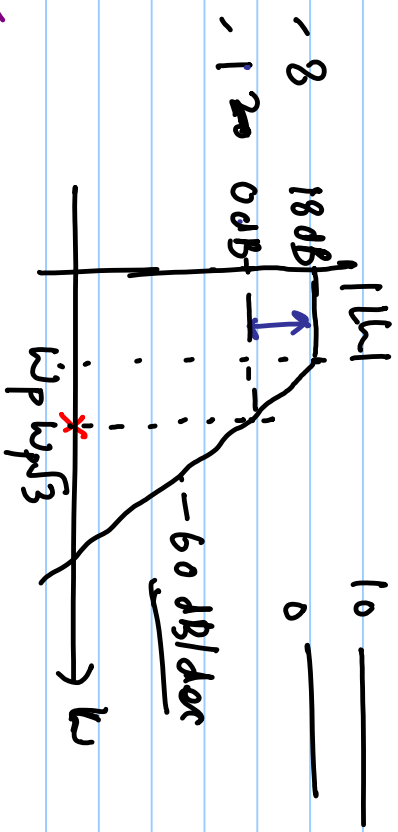
$$\frac{v_{out}}{v_{in}} = \frac{-g_m R_L}{1+s R_L C_L}$$



$$L_A(s) = \left[\frac{-A_0}{1+s/\omega_p} \right]^3$$

$$|L_A(\omega)| = 8 \rightarrow 18 \text{ dB}$$

$$|L_A(\omega_{osc})| = 1 \rightarrow 0 \text{ dB}$$

$$|L_A(\omega_{osc})| = 1 \Rightarrow \frac{A_0^3}{8} = 1 \Rightarrow A_0 = \underline{2}$$

$$\angle L_A(\omega_{osc}) = 2n\pi \checkmark$$

$$-180^\circ - 3 \tan^{-1} \left(\frac{\omega_{osc}}{\omega_p} \right) = 2n\pi \Rightarrow \tan^{-1} \left(\frac{\omega_{osc}}{\omega_p} \right) = 60^\circ \rightarrow \underline{\omega_{osc} = \omega_p \sqrt{3}}$$