
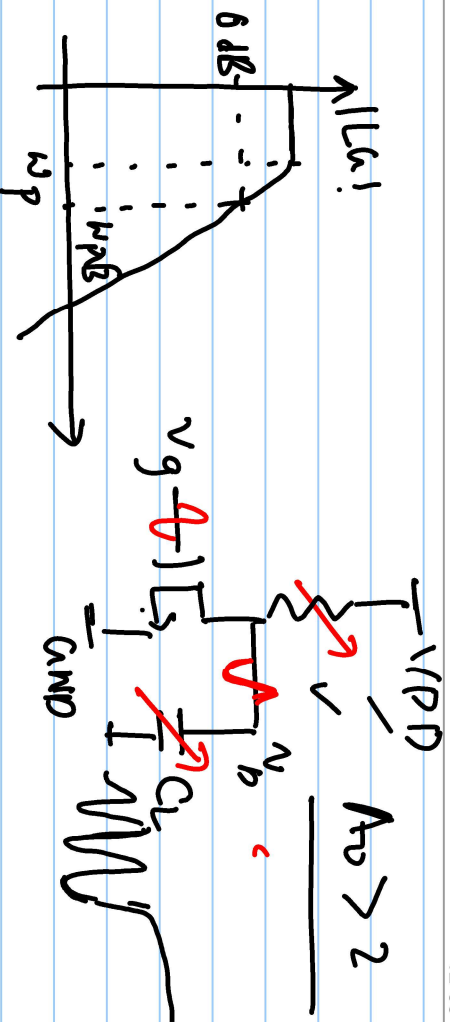


Lecture # 20

Small-swing oscillators:

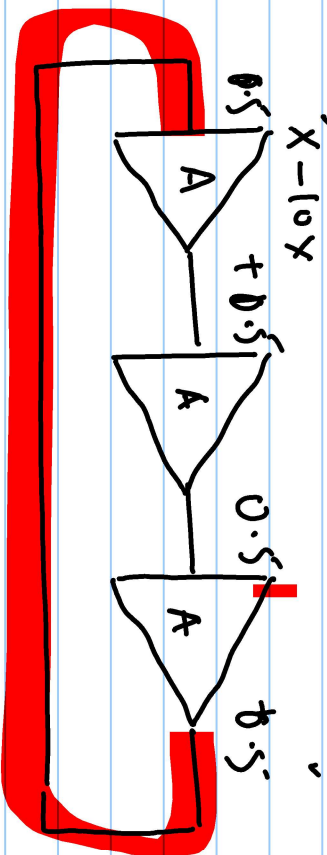



$$A(s) = \frac{-A_0}{(1+s/\omega_p)}$$

$$L_u = \left[\frac{-A_0}{1+s/\omega_p} \right]^3$$

Condition for sustained oscillations:

$$|L_u(\omega_{osc})| = 1 \quad \omega_{osc} = \omega_p \sqrt{3}$$
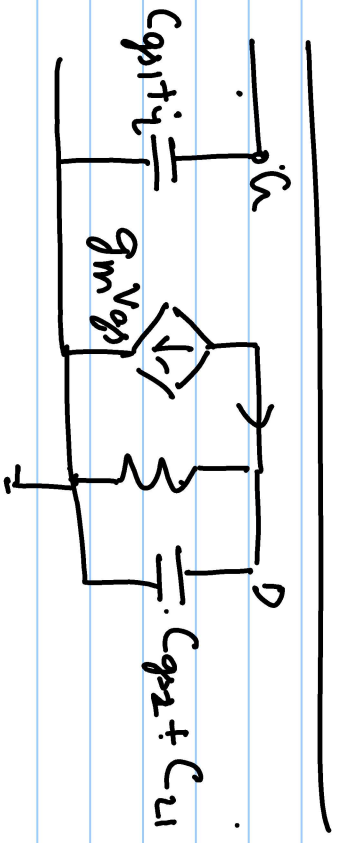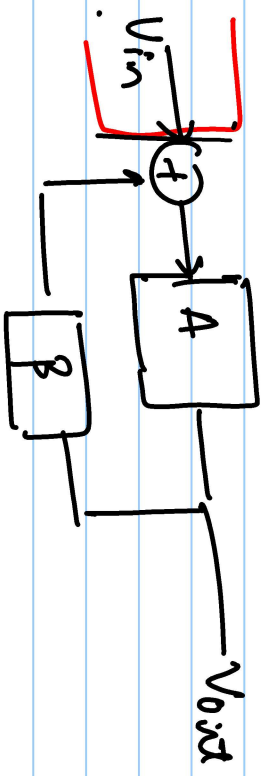
$$\angle L_u(\omega_{osc}) = 2\pi \quad A_0 = 2$$




/

$$\frac{L_R}{1+L_R} = \frac{-A_0^3 (1+s/\omega_p)^3}{1 - (-A_0^3) \frac{1}{(1+s/\omega_p)^3}}$$

$$= \frac{-A_0^3}{(1+s/\omega_p)^3 + A_0^3}$$
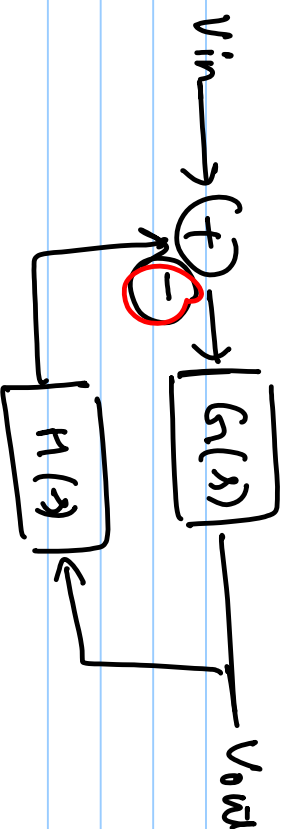
$$\frac{V_{out}}{V_{in}} = \frac{G(s)}{1+G(s)H(s)}$$



$$[V_{in} - H(s)V_o] G(s) = V_{out}$$

V_{out}

$$\left(1 + \frac{s}{\omega_p}\right)^3 + A_0^3 = 0$$

$$\frac{s}{\omega_p} = -1 + A_0^3 (-1)^{1/3}$$

$$s = \omega_p \left[-1 + A_0^3 e^{j(\pi/3 + 2k\pi/3)} \right] \quad k=0, 1, 2$$

$$s_1 = \omega_p \left[-1 + A_0^3 e^{j\pi/3} \right] = \omega_p \left[-1 + A_0^3 \left(\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) \right]$$

$$= \omega_p \left[(-1 + \frac{A}{2}) + j \cdot \frac{A\sqrt{3}}{2} \right]$$

$$= e^{j2\pi/3}$$

$$= \cos(2\pi/3) + j \cdot \sin(2\pi/3)$$

$$s_2 = \omega_p \left[-1 + \cancel{A_0} e^{j(\pi/3 + 2\pi/3)} \right]$$

$$= \cos(\pi_0 + 3\pi_0) + j \cdot \sin(\pi_0 + 3\pi_0)$$

$$= \omega_p \left[-1 + (-A_0) \right]$$

$$= -\frac{1}{2} + j \cdot \frac{\sqrt{3}}{2}$$

$$s_3 = \omega_p \left[-1 + A_0 e^{j(\pi/3 + \pi/3)} \right]$$

$$(-1)^{1/3} = (e^{j\pi})^{1/3}$$


$$= [e^{j(\pi + 2n\pi)}]^{1/3}$$

$$= \omega_p \left[-1 + A_0 (e^{j(2\pi/3)}) \right]$$

$$= e^{j(\pi/3 + 2n\pi/3)}$$

$$= \omega_p \left[-1 + A_0 \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right) \right]$$
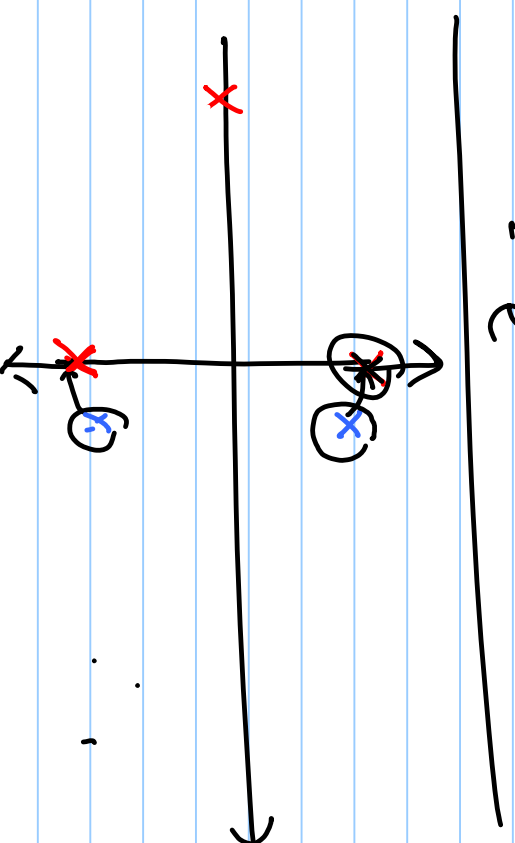
$$= \omega_p \left[\left(-1 + \frac{A_0}{2} \right) - j \frac{\sqrt{3} A_0}{2} \right]$$



$$\omega_{osc} = \sqrt{3} \omega_p = \frac{\sqrt{3}}{RC} \quad R = (R_o || r_{ds})$$

$$A_o = g_m (R_o || r_{ds}) = 2$$



V_{out}

Oscillator,

1. Amplitude ✓
2. Frequency
3. Power consumption.
4. Phase noise
5. PSRR ✓

Stability


Tunability

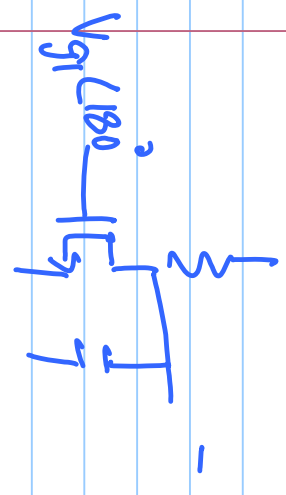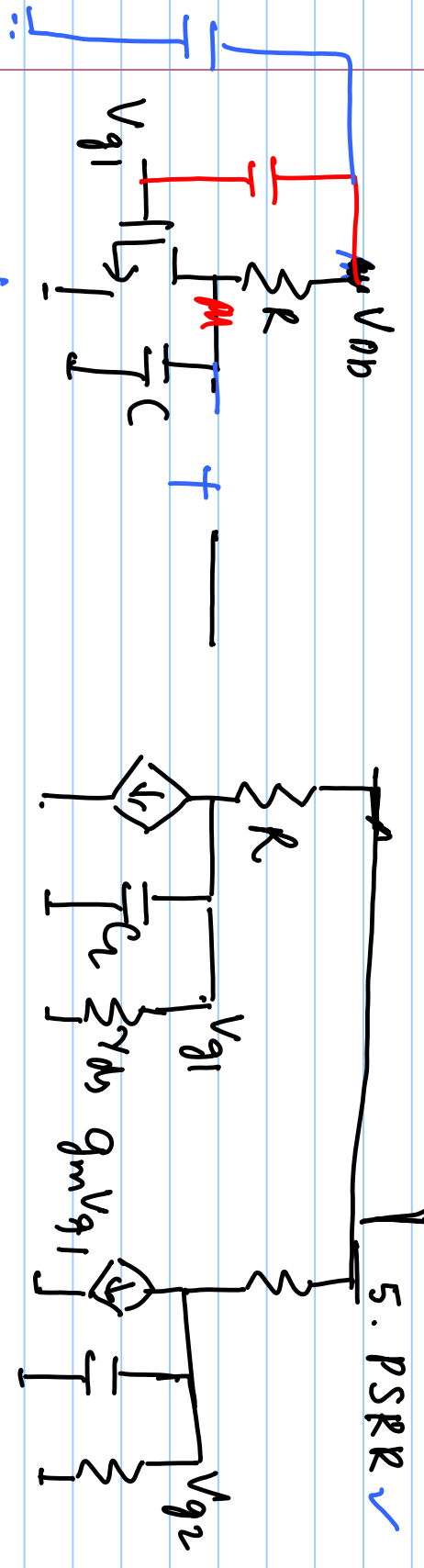

$$V_{on} = V_{DD} - I_0 \cdot R_L$$

$$V_{op} = V_{DD}$$


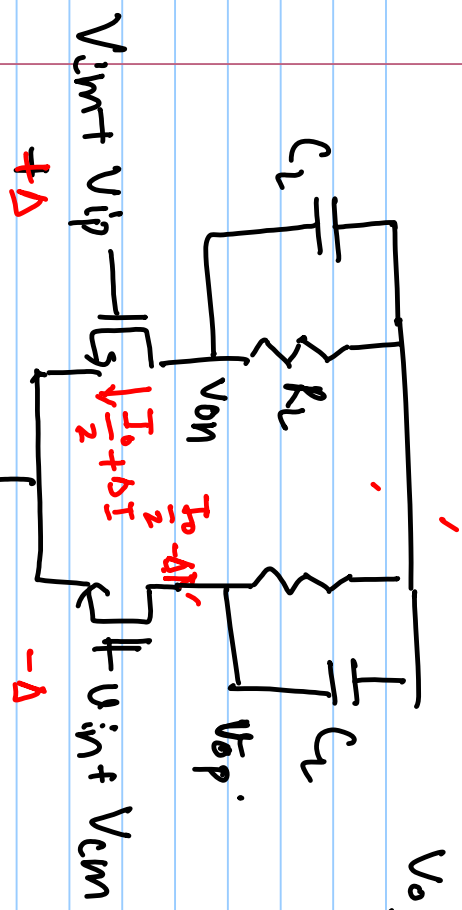
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{V_{op} - V_{on}}{V_{ip} - V_{in}} = \frac{g_m R_L}{1 + s C_L R_L}$$





$$+ 2 \cdot (2I_0) \cdot R_L = 2 \cdot \frac{I_0}{2} \cdot R_L$$

$$\omega_{p1} = \frac{1}{R_L C_L}$$

$$\omega_{osc} = \sqrt{3} \omega_p$$

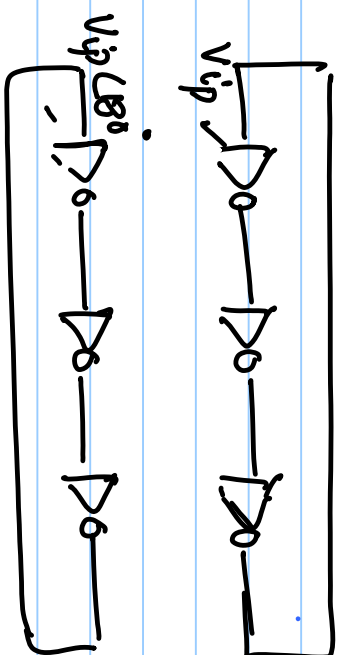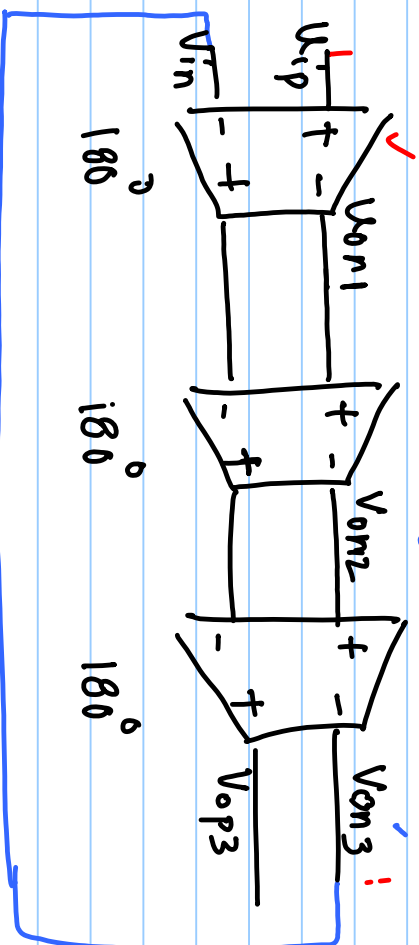

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

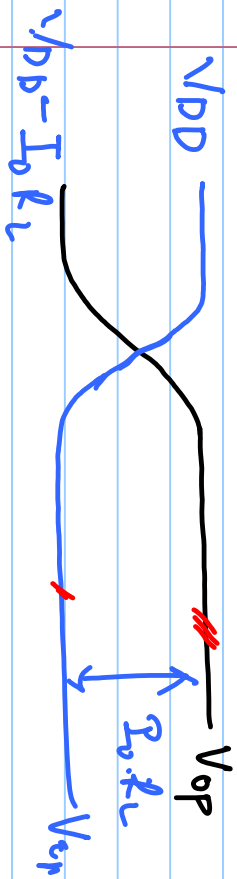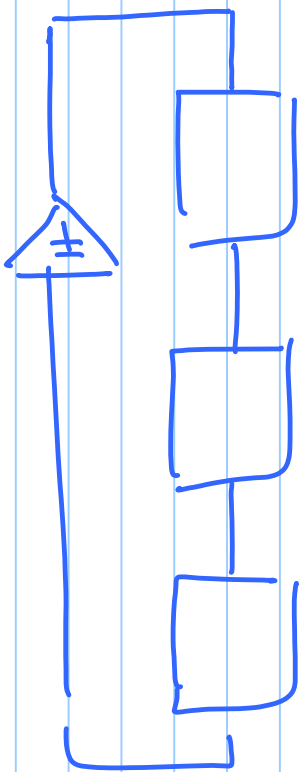

$$V_{out, max} = |V_{op} - V_{on}|_{max}$$

$$= g_m R_o \left| \frac{V_{ip} - V_{in}}{V_{in}} \right|_{max}$$

$$= 2 g_m R_i$$