
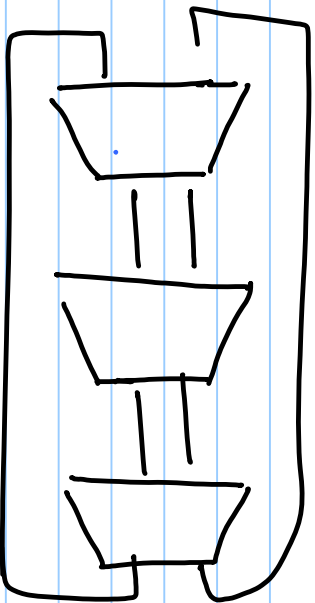


# Lecture #21

## Small swing Oscillators.

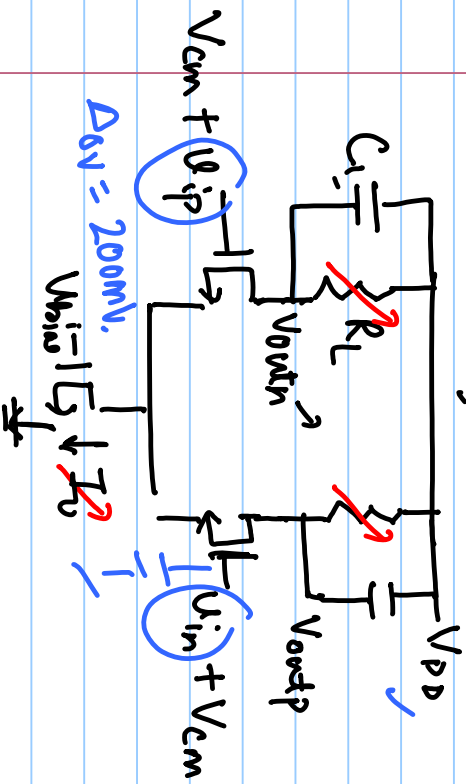

$V_{outp} = V_{DD}$   
 $V_{outn} = V_{DD} - I_0 R_L$

$$A(\omega) = \frac{g_m R_L}{1 + s R_L C_L} = \frac{A_0}{1 + s/\omega_p}$$

$$\omega_{osc} = \sqrt{3} \omega_p = \frac{\sqrt{3}}{R_L C_L}$$

Amplitude =  $I_0 R_L$

$I_0 \rightarrow 2 I_0$        $R_L \rightarrow 2 R_L$   
 $I_{0k1} \rightarrow 2 I_{0k1}$        $C_L \rightarrow C_L/2$




1. Oscillation amplitude
2. " frequency.

$f_{out} \xrightarrow{R} 2 f_{out}$   
 $V_{out} \xrightarrow{R} V_{out}/2$

$\omega_{out1} = \frac{1}{R C}$        $V_{out} = I_0 \cdot R$


$\omega_{out2} = \frac{1}{R/2 \cdot 2C}$        $V_{out} = 2 I_0 \cdot R/2$

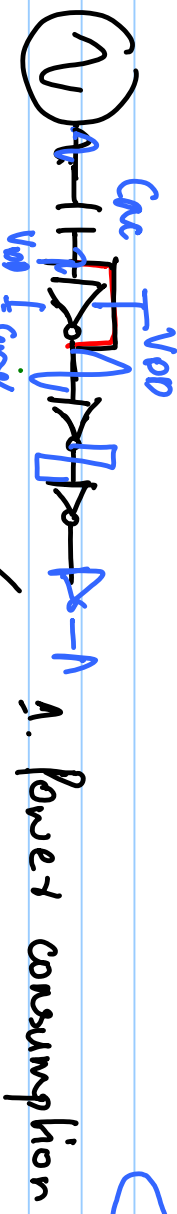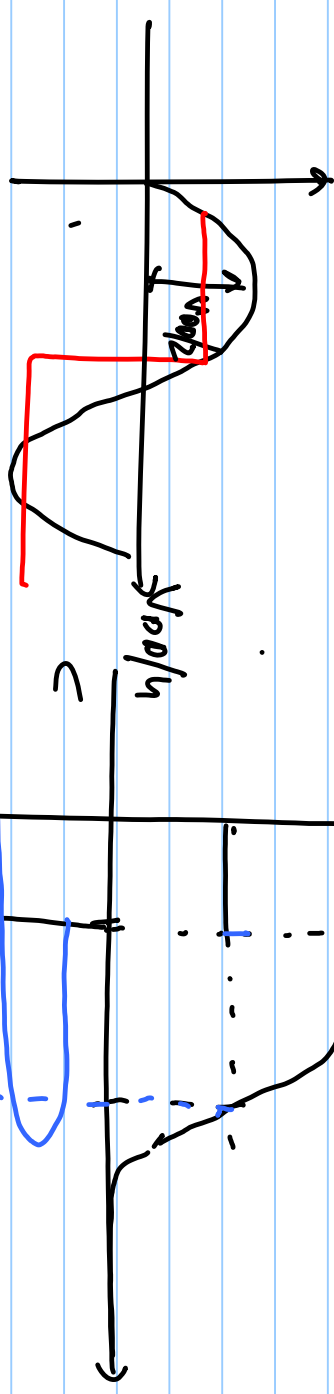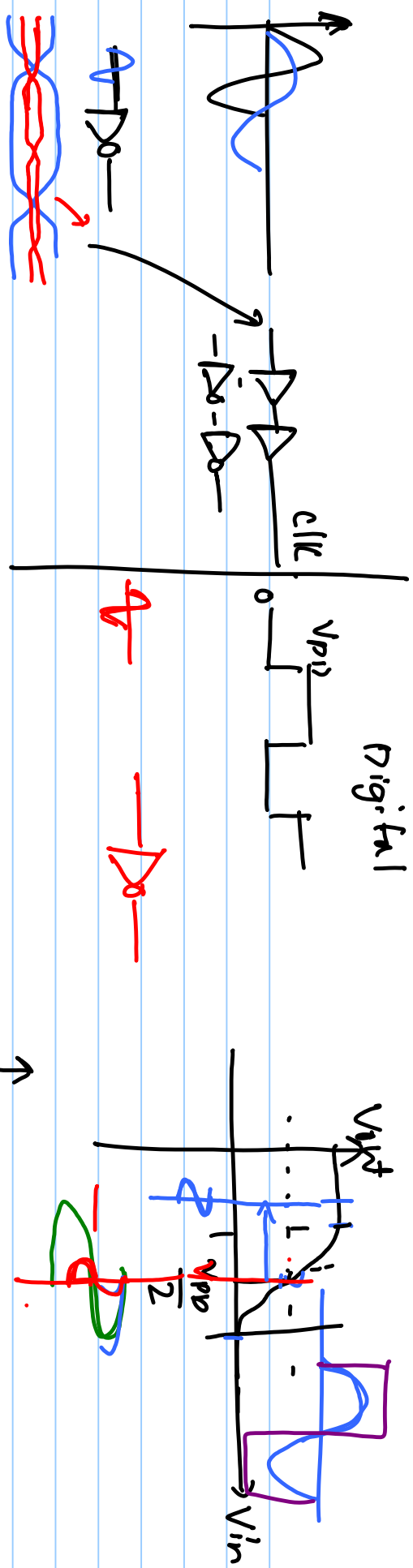$\omega_{out3} = \frac{1}{2R \cdot C/2}$        $V_{out} = \frac{I_0}{2} \cdot 2R$



1. Power consumption

2.

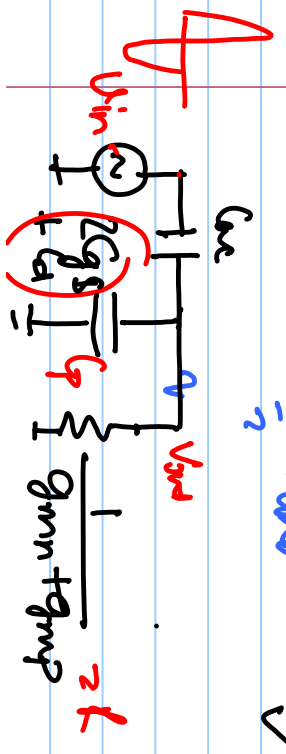

0, 1  
0, VDD  
L100mV, 600mV. Digital.

$$\frac{V_{out}}{V_{in}} = \frac{(R_{11} \frac{1}{s_{cp}})}{(R_{11} \frac{1}{s_{cp}}) + \frac{1}{s_{dec}}}$$


$$\approx \frac{C_{out}}{C_{in} + C_{cp}}$$

$$f_1 \quad A_1 \quad n \quad W_p = \frac{\sqrt{3}}{K_C}$$






$$f_2 \quad A_2$$

$$A = \beta_0 \cdot K$$

(IV) 1

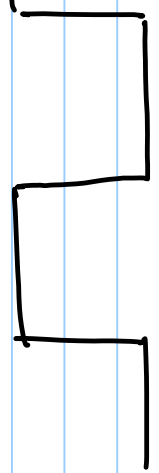




Digital

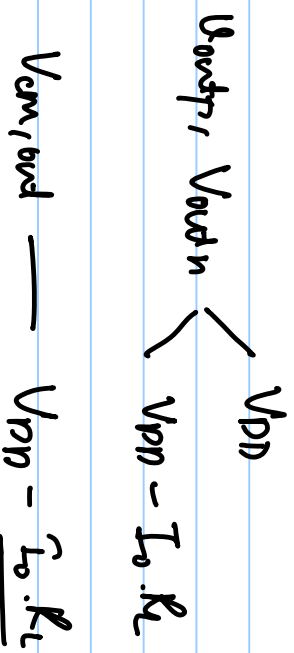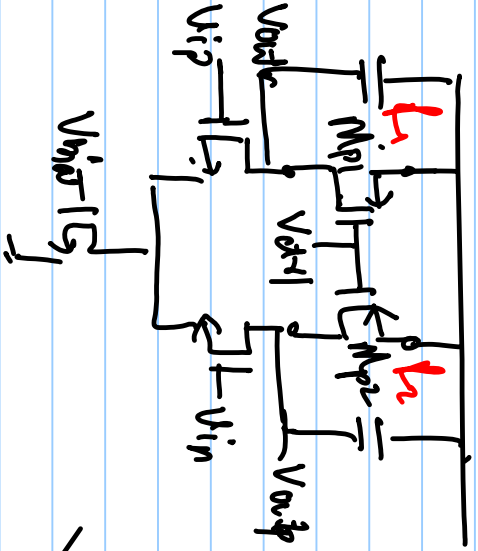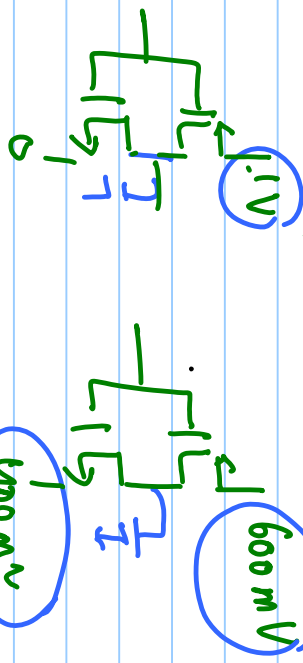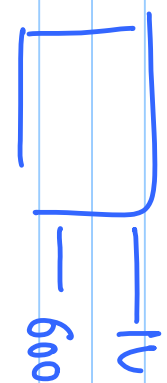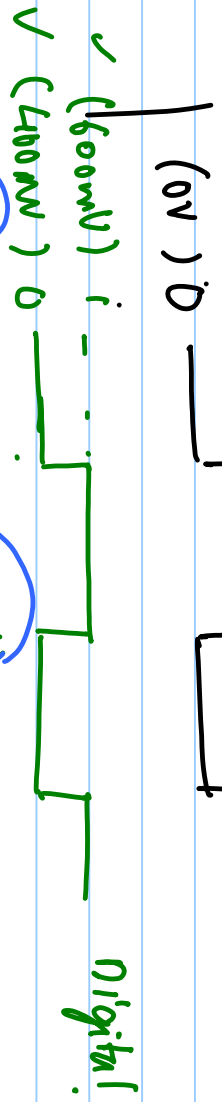

$$\frac{I_0}{2} = \frac{K_n}{2} \left( (V_{DD} - V_{GS1} - |V_{THP}|) (V_{DD} - V_{GS1}) - \frac{V_{GS1}^2}{2} \right)$$

$$R_{eq} = \frac{1}{\frac{g_m}{2} \left( (V_{DD} - V_{GS1}) - (V_{TP1}) - \left(\frac{V_{SD}}{2}\right) \right)} = \frac{V_{SD}}{(I_0/2)}$$

$$I_0 = \frac{K_M}{2} \left[ (V_{DD} - V_{GS1} - |V_{TP1}|) (V_{DD} - V_{DS1}) - \frac{(V_{DD} - V_{DS1})^2}{2} \right]$$

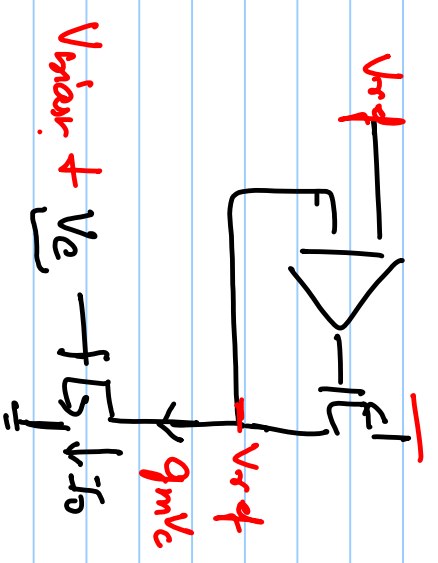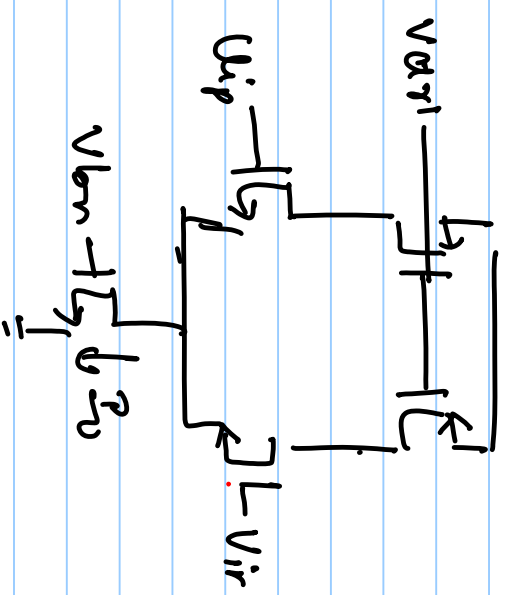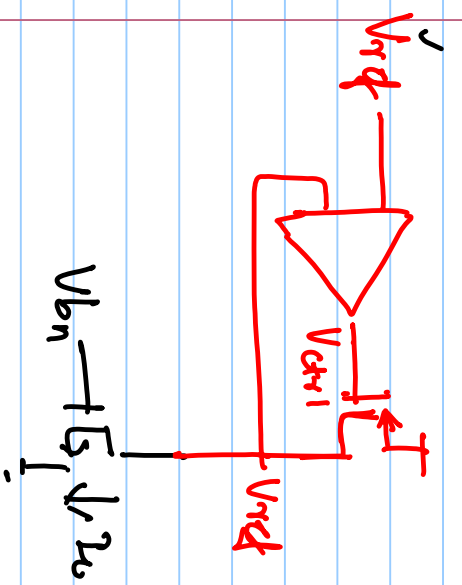

$$R_{eq} = \frac{\sqrt{3}}{K_L} = \frac{\sqrt{3} (R_{total})}{C (V_{DD} - V_{GS1})}$$

$$R = \frac{V_{DD} - V_{GS1}}{I_0/2}$$

---

$$A_{mp} = (V_{DD} - V_{Tq})$$