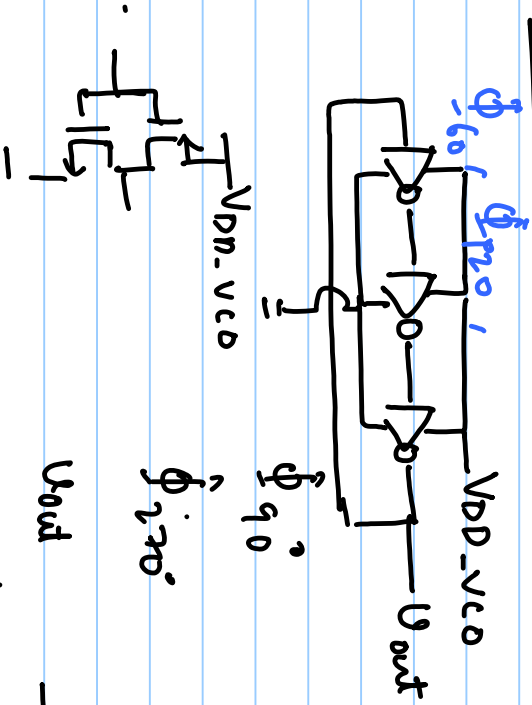



Lecture # 24







$$\phi_{60}: t_d/6$$



$$f_{out} = K_{VCO} \times V_{DD-VCO} \cdot I_{D0}$$
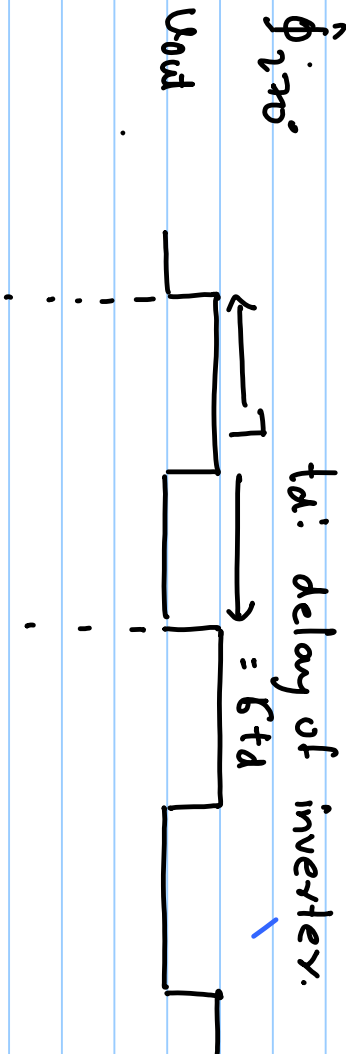
$$f_{out} = \frac{1}{2(Nt_d)} = \frac{1}{2(2M4).t_d}$$











t_d : delay of inverter.

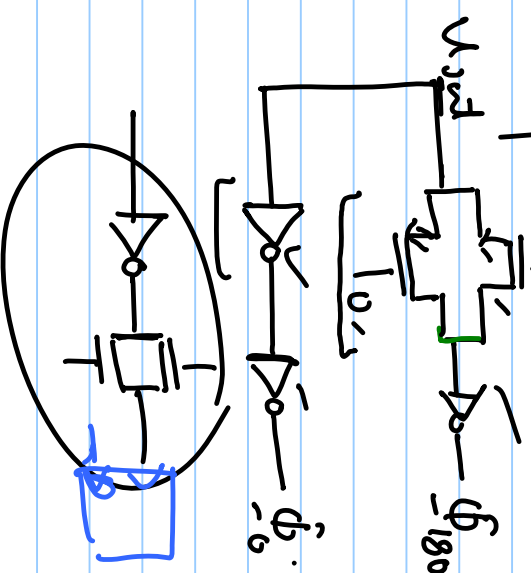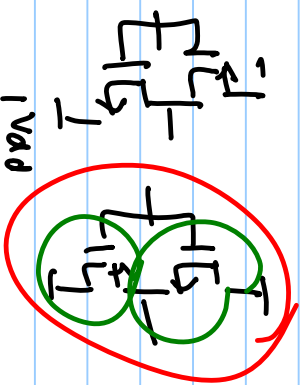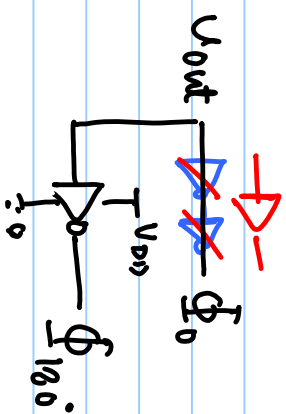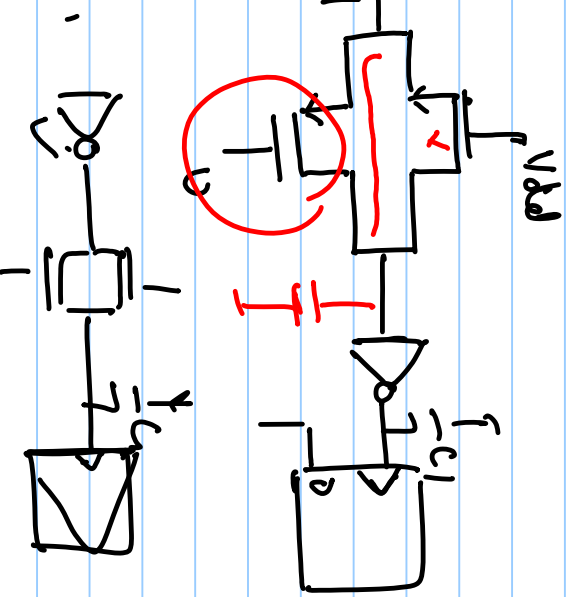






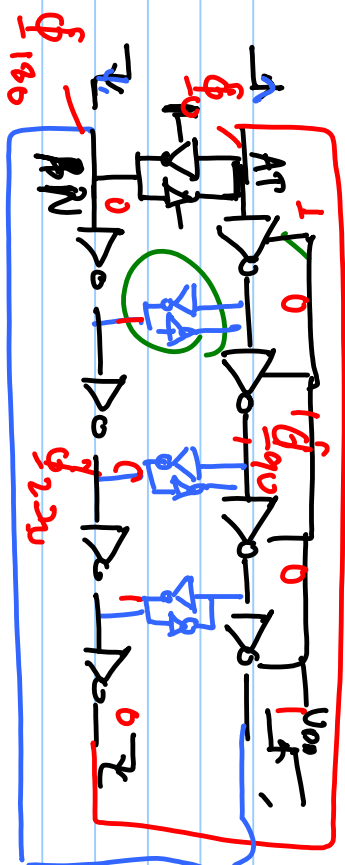
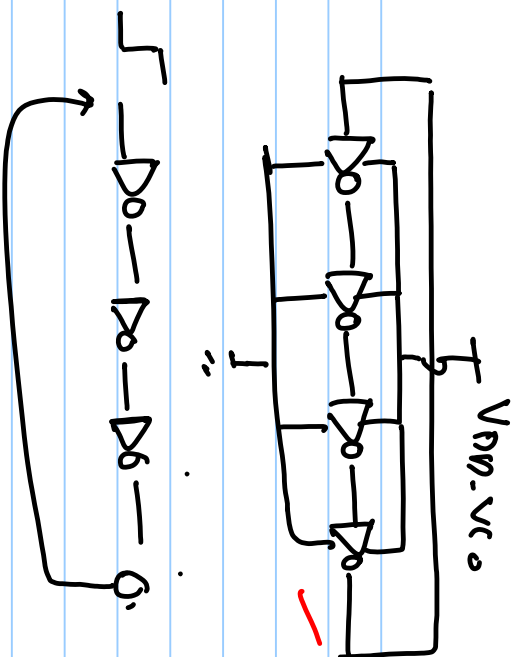


Pseudo-differential ring osci

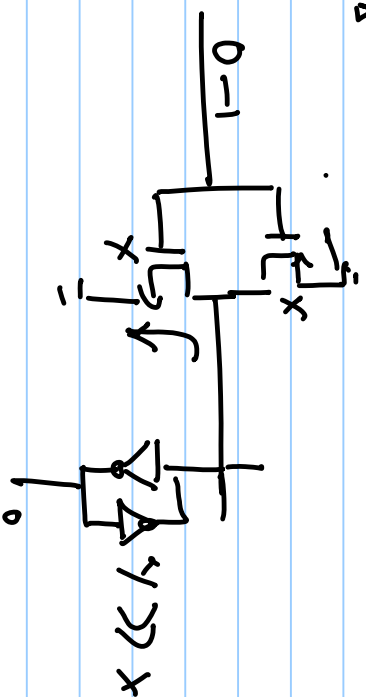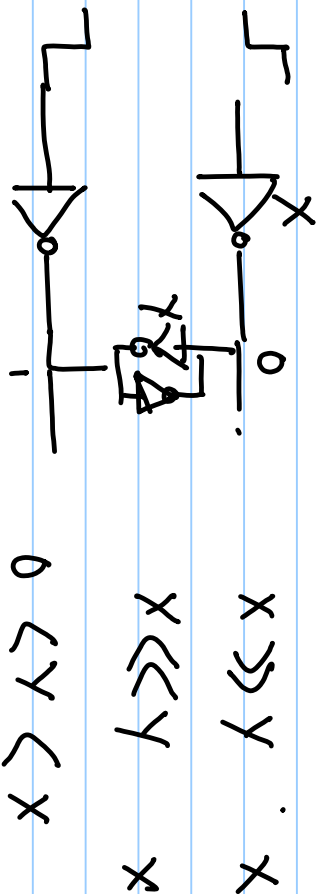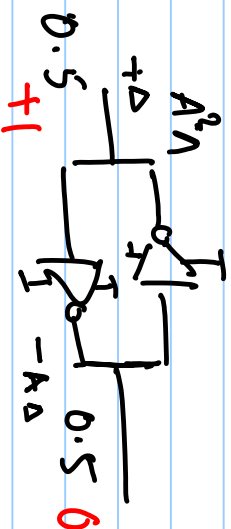

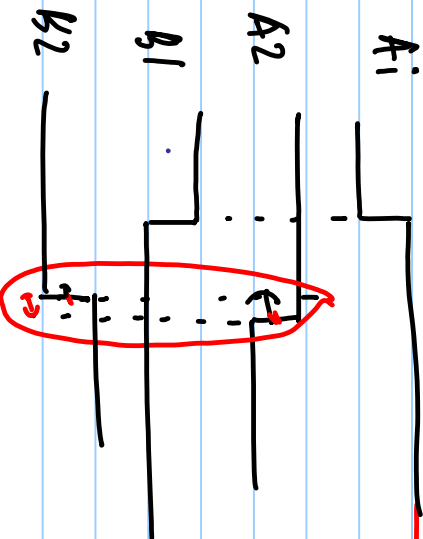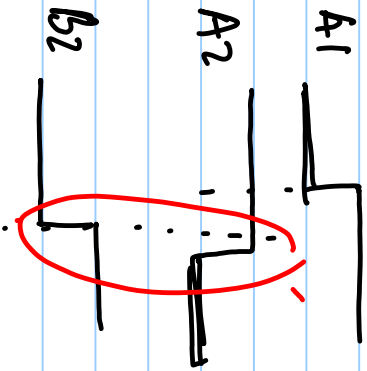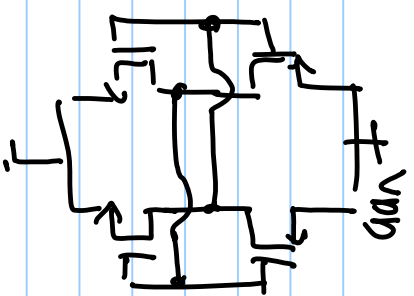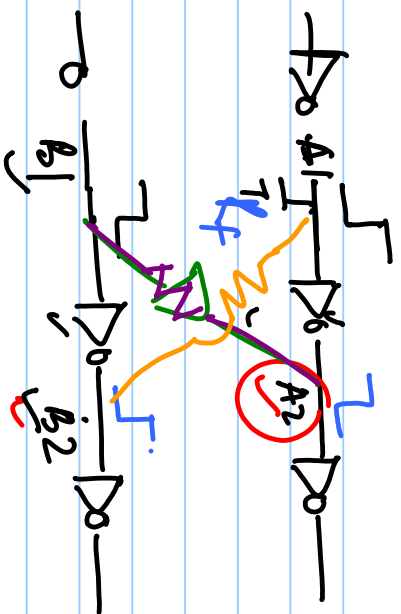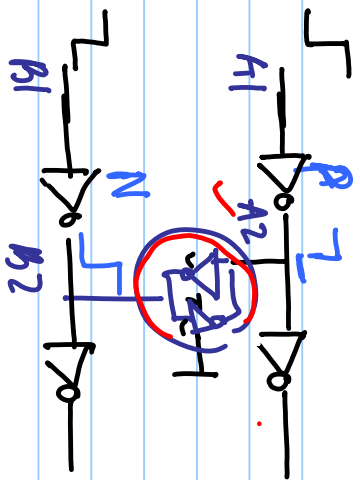

$R_f = 0$
 $R_f = 0$

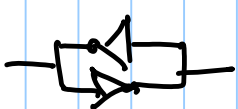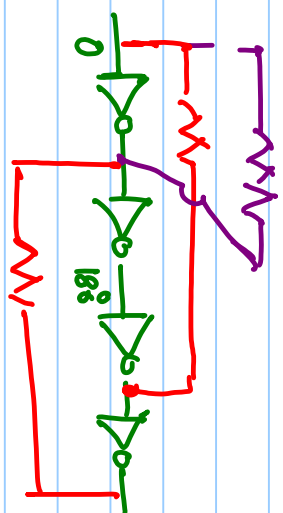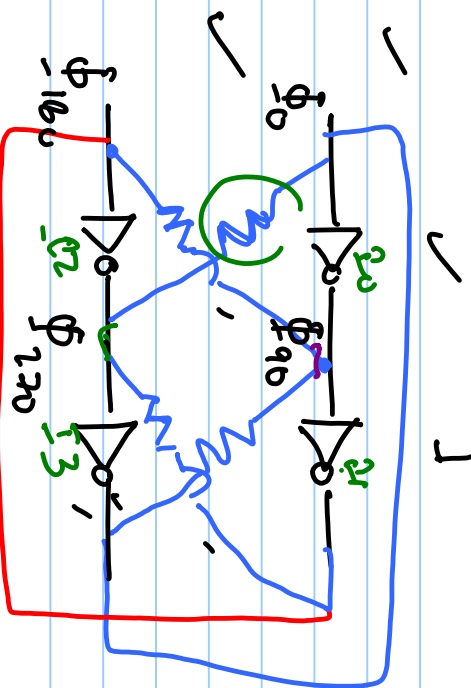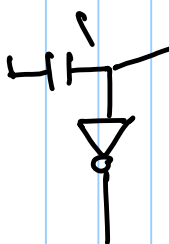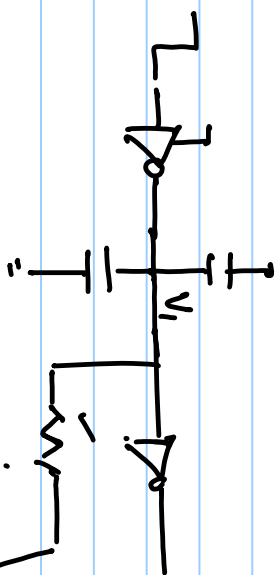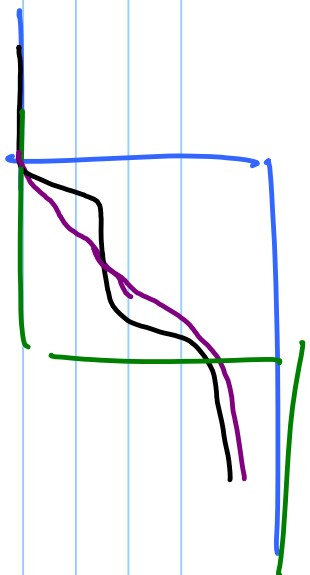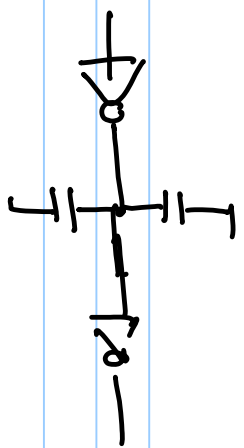

..