

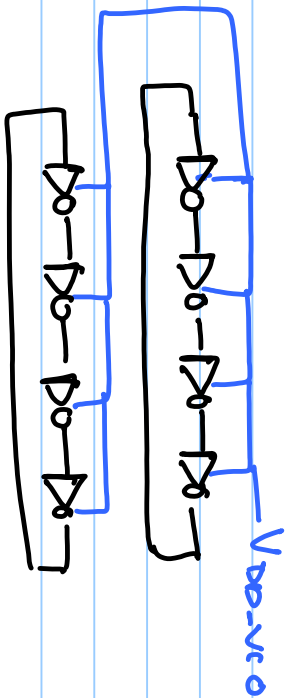


Lecture # 25

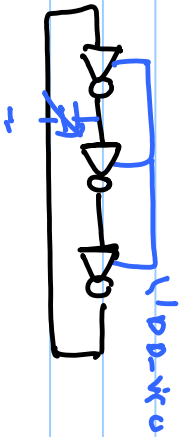



$V_{DD-VCO} \rightarrow t_d$ of inverter \rightarrow freq. of osc.

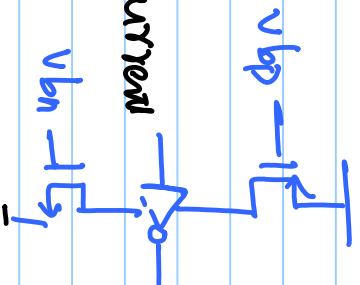$t_d \sim V_{DD-VCO}$
 ~ capacitor ~
 Current starved inverter — headroom for current source.




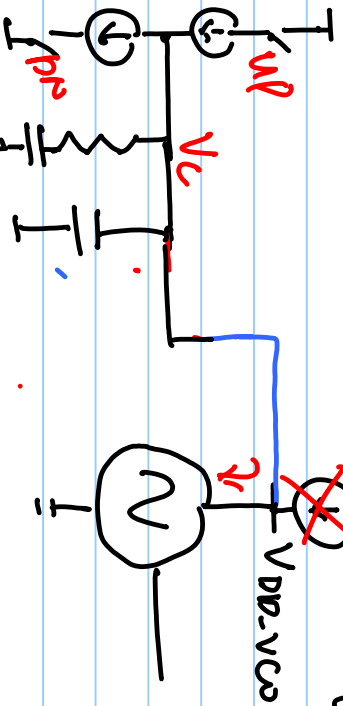
$V_{DD-VCO} (V_{eff}) : f_{vco} = K_{vco} \cdot V_{eff1}$
 [Hz/V]



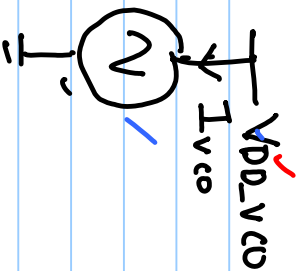


$$f_{out} = 16\text{Hz}$$
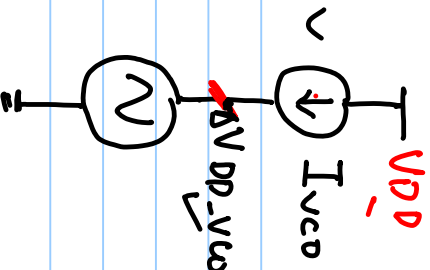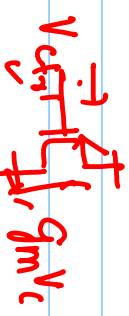
$$K_{VCO} = \frac{df_{out}}{dV_{DD_VCO}}$$




$$f_{out} = 16\text{Hz}$$
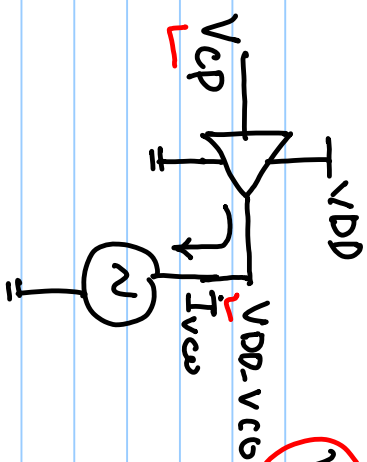
$$K_{VDD} = \frac{df_{out}}{dV_{DD_VCO}}$$



$$f_{out}$$

$$K_{VCO}$$

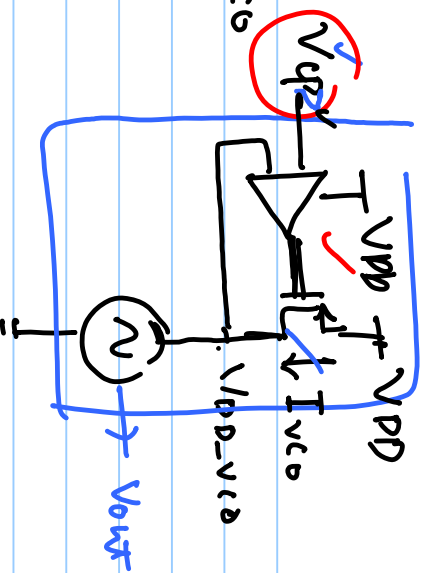

$$f_{out}$$

$$K_{VCO}$$

K_{VCO} : Voltage Controlled Osc.


K_{VDD} : Current Controlled Osc.

Process Corners




SS : slow-slow $V_{DD_VCO} \uparrow$

ft :

ft : fast-fast $V_{DD_VCO} \downarrow$

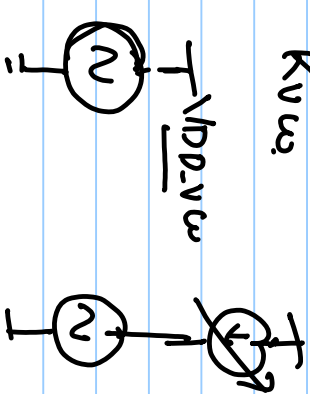

$$ft'$$

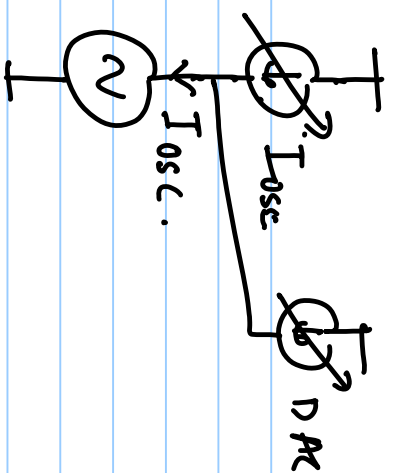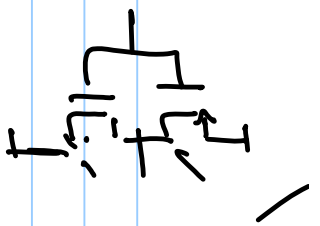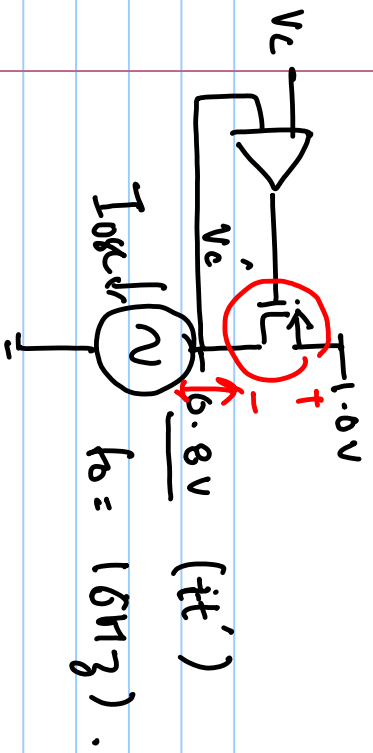



V_c'
 SS $> 0.8V$ $0.85V$
 ff $< 0.8V$ $0.75V$
 tt

K_{VIO} 0.8Ω
 K_{VCO} 0.75
 I_{mA}


0.8 I_{mA}

$10GHz$

V_{CP} Digital Word

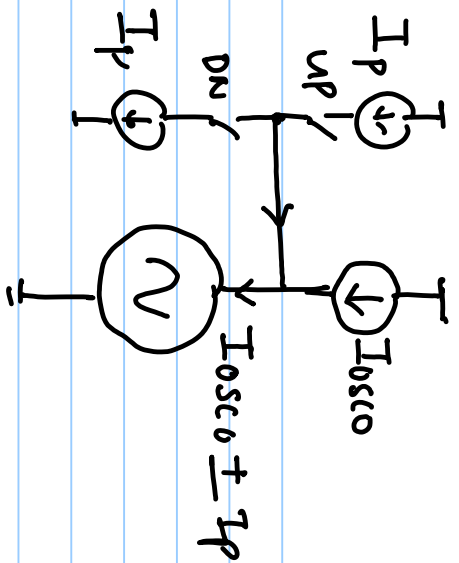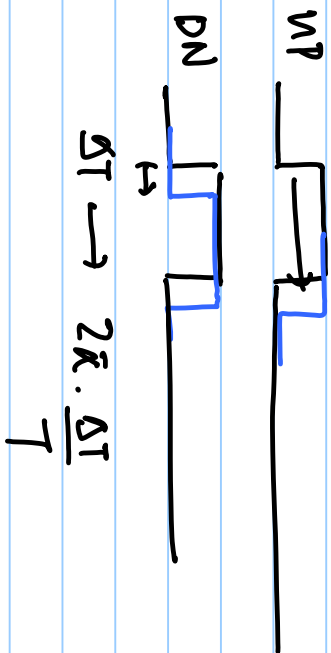

$$f_{osc} = f_0 + K_{c10} \cdot I_p$$



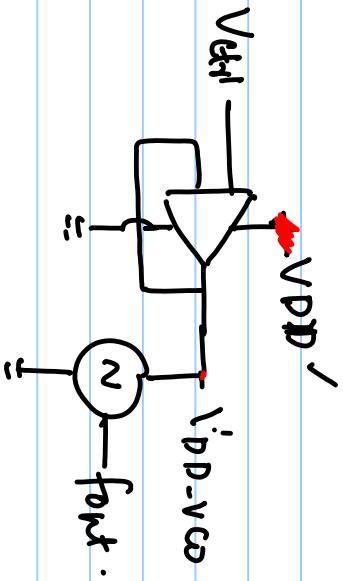


$$\frac{f_{osc}}{V_{DD-Vc0}} = K_{v10}$$

$$10 \times 10^9 \times 10^{-2} = 10^9$$

$$\frac{V_{DD-Vc0}}{V_{DD}} =$$

$$\frac{\Phi_{osc}}{V_{DD}} = PSRR$$

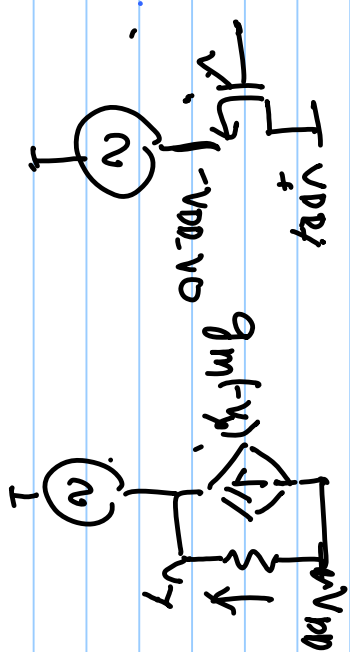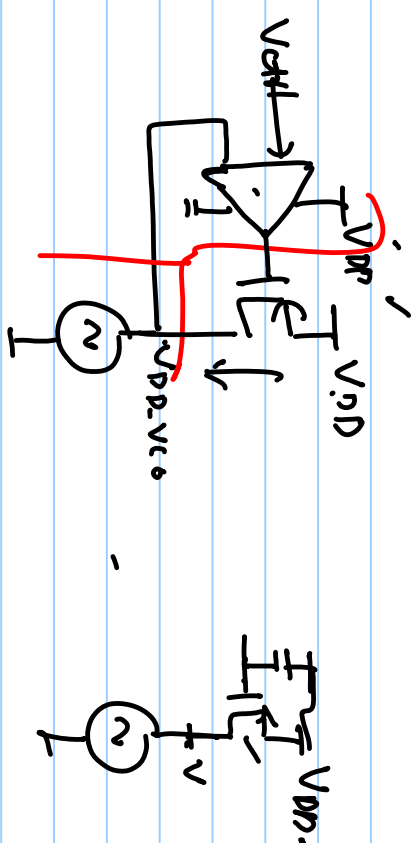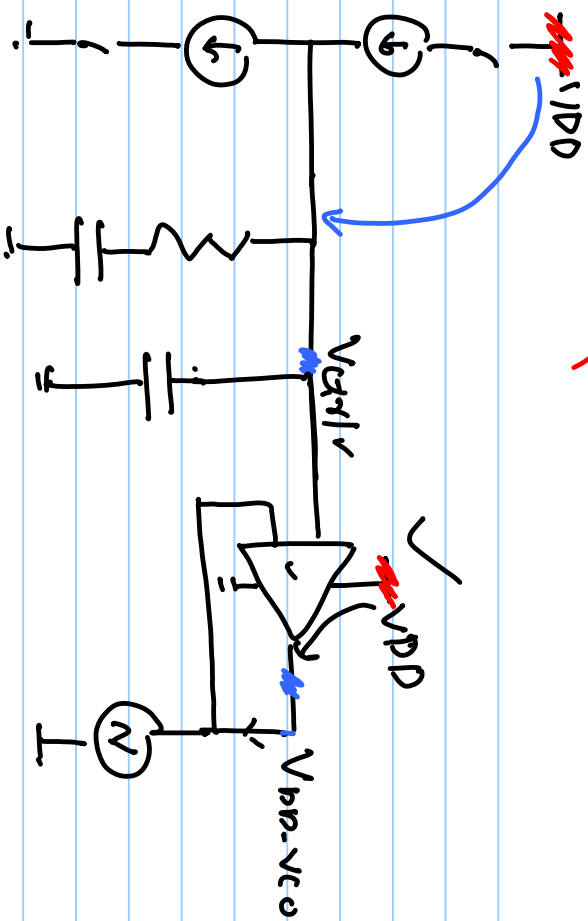

$$\frac{V_{out} - V_x}{r_{ds}} + g_m(-V_x) = \frac{V_x}{r_{osc}}$$

$$\frac{1}{g_m} \approx \frac{V}{(1+g_m r)} \approx \frac{V_x}{V_{DD}} = \frac{1}{r_{ds} r_{osc} + g_m}$$