
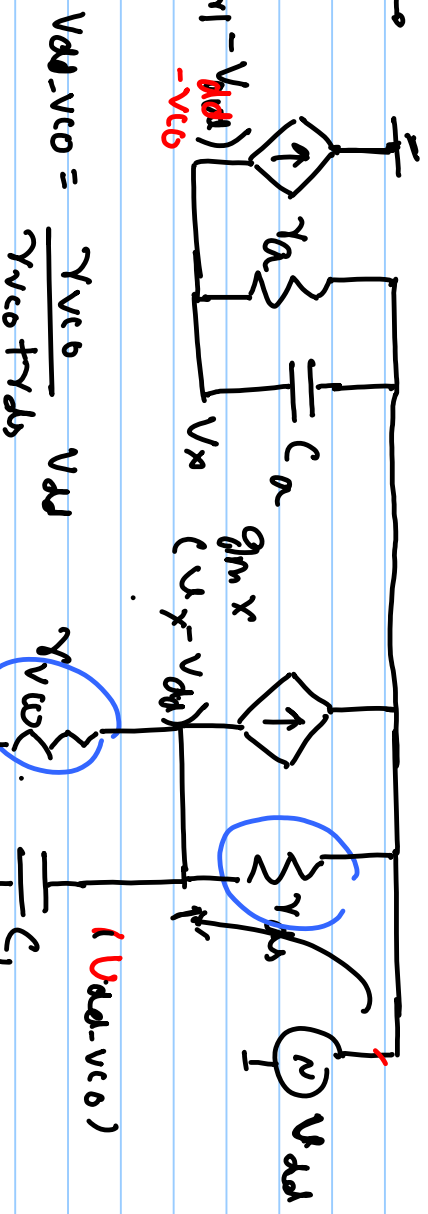
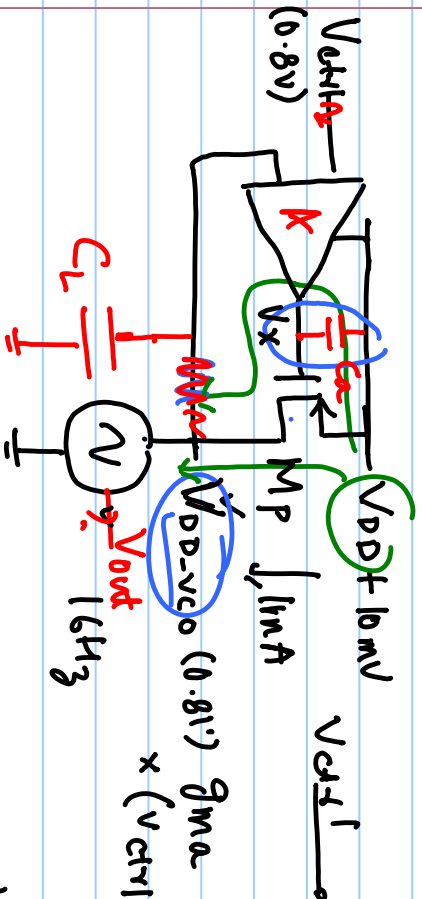


# Lecture # 27

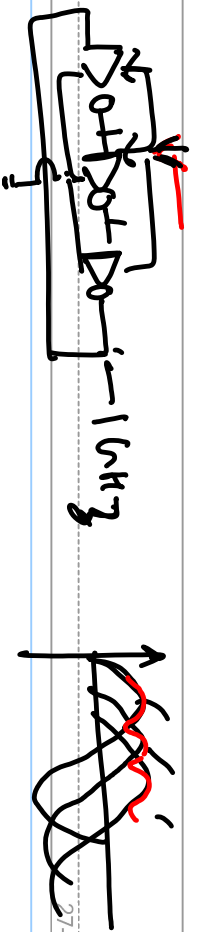

Ca: mostly from Mp.

Ya: o/p imp. of amplifier.

Yco:  $\approx V_{DD-VCO} / I$

CL:

$$V_{DD-VCO} = \frac{V_{VCO}}{r_{VCO} + r_{ds}} V_{DD}$$

$V_{G1} \rightarrow V_x, I_{VCO} \rightarrow V_{DD-VCO} = V_{G1}$  [V]

$V_{G1} \rightarrow V_{DD-VCO} \rightarrow \phi_{ow}$

$V_{DD}$

$V_{ov}$

$$L_{margin} = \frac{A_a A_b}{(1+s/\omega_a)(1+s/\omega_b)}$$

$V$ ;  $A_a = g_m r_a$

$A_b = g_m (r_{ds} || r_{VCO})$

$$\omega_{pt} = \frac{1}{r_a C_a}$$


$$\omega_{p3} = \frac{1}{r_o C_L}$$

$$V_{out} \rightarrow V_{dd-vco} \quad \left| \quad A_{f_{vco}} = K_{vco} \cdot V_{dd-vco} \right.$$

$$\frac{V_{dd-vco}(s)}{V_{out}(s)} = \frac{L_{vreg}}{1 + L_{vreg}} \approx \frac{1}{(1 + s/\omega_{reg})}$$

$$= \frac{1}{1 + \frac{1}{L_{vreg}}} = \frac{1}{1 + (1 + s/\omega_a)(1 + s/\omega_b)}$$

$A_a A_b$

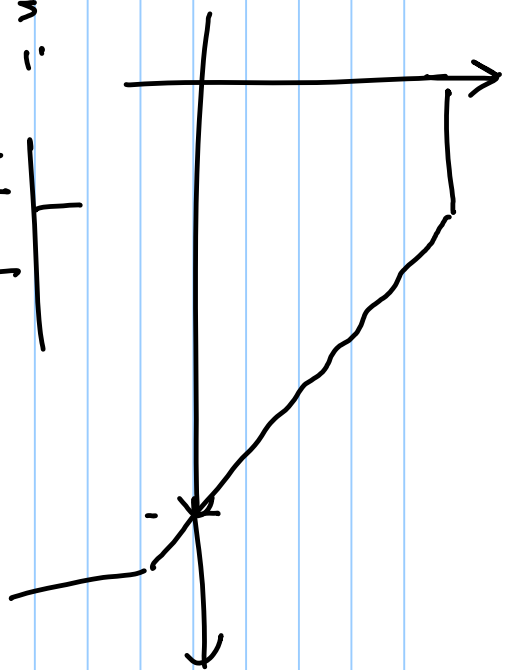

$$\text{DC gain} = \frac{1}{1 + \frac{1}{A_a A_b}}$$

$$1 + A_a A_b + s \left( \frac{1}{\omega_a} + \frac{1}{\omega_b} \right) + \frac{s^2}{\omega_a \omega_b}$$

$$\frac{\Phi_{out}(s)}{V_{out}(s)} = \frac{\Phi_{out}(s)}{V_{dd-vco}(s)} \times \frac{V_{dd-vco}(s)}{V_{out}(s)}$$

$$\omega_a \ll \omega_b$$

$$\omega_a \approx (1 + A_a A_b) \omega_a$$

$$= \frac{2\pi K_{vco}}{s} \times \frac{1}{(1 + s/\omega_{reg})}$$

$$\omega_x^2 + b\omega + c = 0$$

$$\omega_1 + \omega_2 = -b/a$$


$$\omega_1 \omega_2 = c/a$$

$$L_{u_{p11}} = \frac{I_{cp}}{2\pi} \left( R + \frac{1}{sC_1} \right) \frac{2\pi K_{vco}}{s} \left( \frac{1}{1 + s/\omega_{reg}} \right)$$

$L_{u_{p11}}$


$$H_{vdd} = \frac{V_{dd} - v_{ce}(s)}{V_{dd}(s)} = \frac{S_{vdd} (1 + s/\omega_a) \checkmark}{A_{aA_0} + (1 + s/\omega_a) (1 + s/\omega_0) \checkmark} \quad S_{vdd} = \frac{\gamma_{vce}}{\gamma_{vce} + \gamma_{ds}}$$
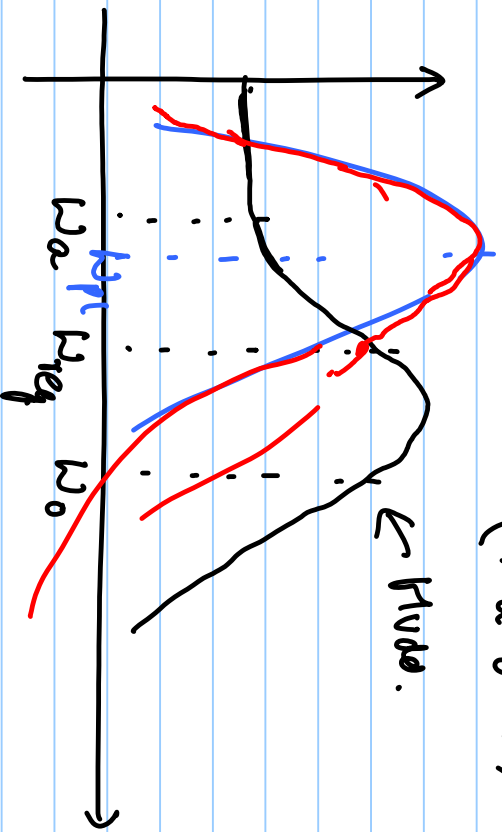
$$V_{ds} \text{ DC.} = \frac{S_{vdd} ( )}{(A_{aA_0} + 1)}$$



$$f_{ov} = K_{vce} \cdot V_r$$

$\omega_{reg} = \omega_0$

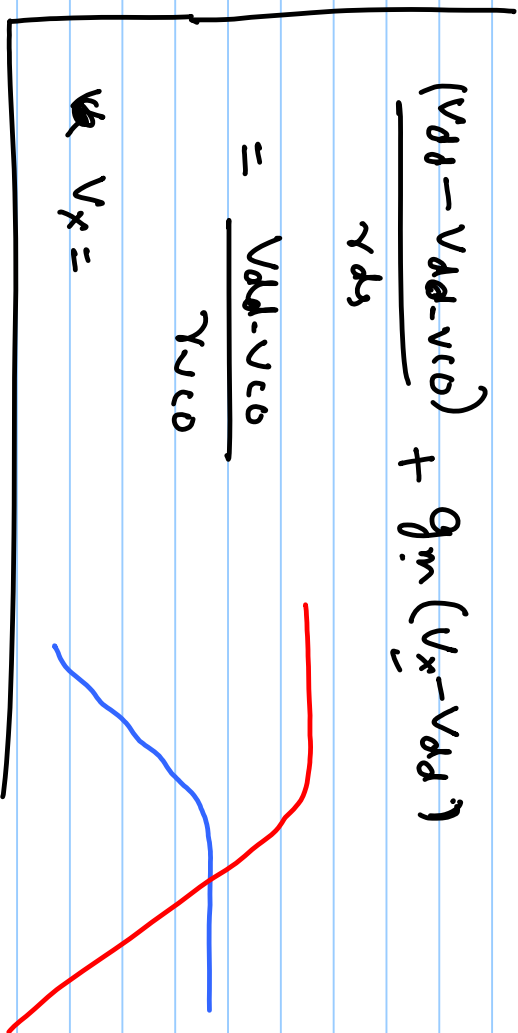

$$\begin{aligned} & \frac{(V_{dd} - V_{dd} - v_{ce})}{\gamma_{ds}} + g_{in} (V_x - V_{dd}) \\ & = \frac{V_{dd} - v_{ce}}{\gamma_{vce}} \end{aligned}$$

$V_x =$

