


Lecture # 48

Fractional -N PLL

$$f_{ref} \rightarrow \boxed{\text{PLL}} \rightarrow f_{out} = (N + \alpha) f_{ref}$$

$$0 < \alpha < 1$$
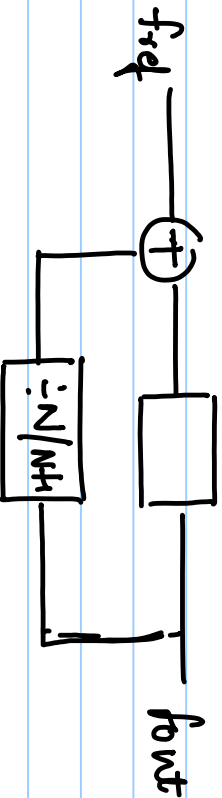
$$f_{out} = 4.25 f_{ref} \quad \text{BT: } \left(122 + \frac{51}{402} \right) f_{ref}$$



$$N = 4$$

$$N + 1 = 5$$

$$1223 \times 51 \text{ Trq}$$

$$122 \times 402 \text{ Trq}$$



$$T_{ref} = \frac{425}{100} T_{out}$$

$$4 T_{ref} = 17 T_{out}$$



$$1 T_{ref} = 4 T_{out}$$

$$2 \quad - \quad 4$$

$$3 \quad - \quad 4$$



$$4 \quad - \quad 5$$







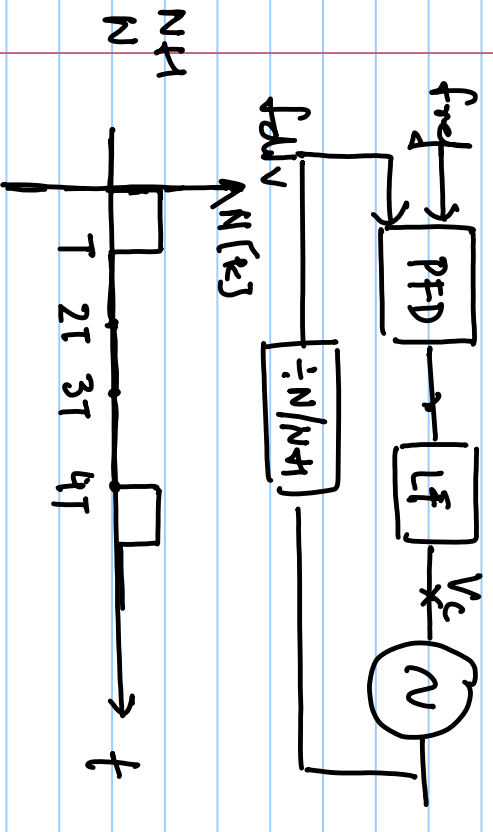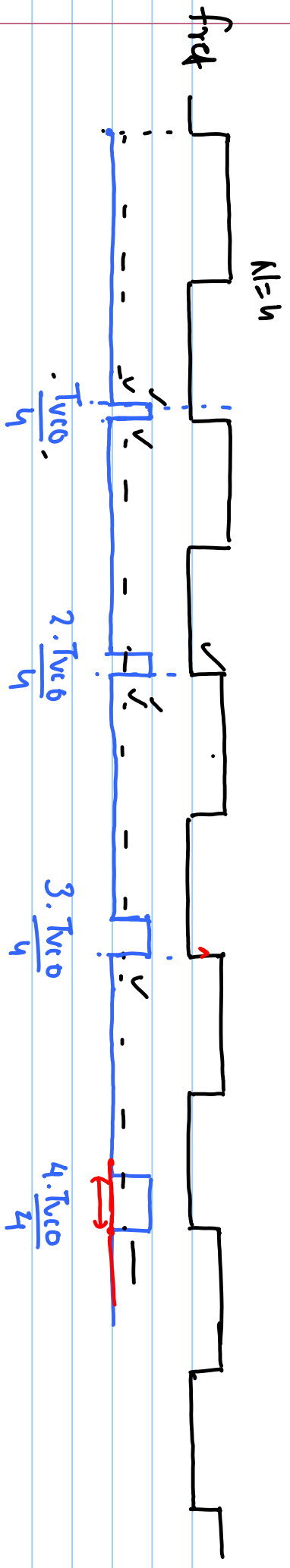

$f_{out} = 4 \cdot 25 \text{ v}$
 \rightarrow $\text{freq} / 4$ $\text{div} \pm \text{freq} / 4$

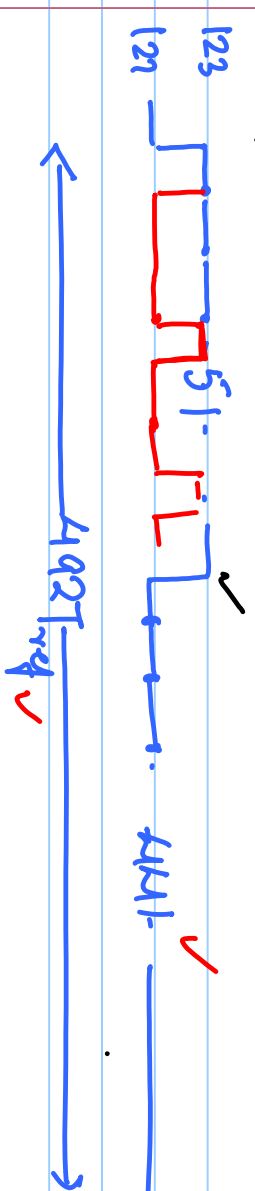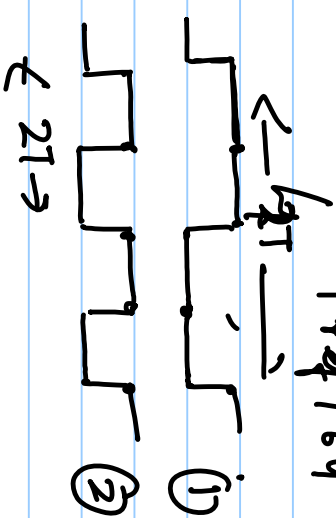$\cdot 125$
 $\cdot 0625$
 $\cdot 03125$ \uparrow $\text{div} \pm \text{freq} / 4$




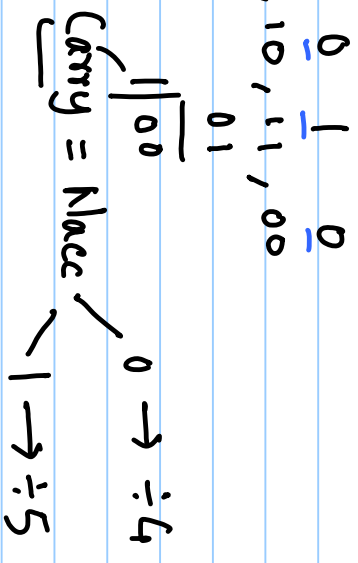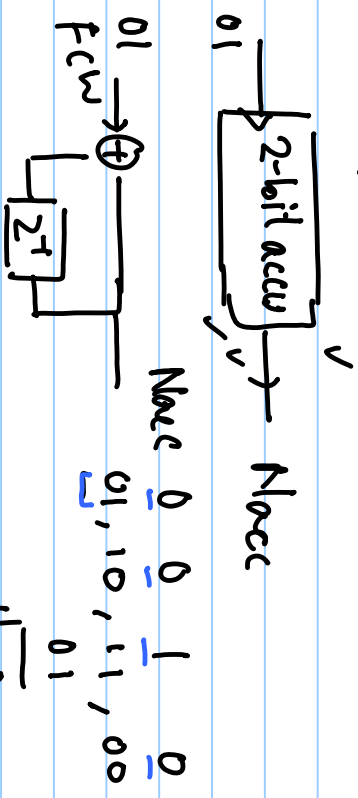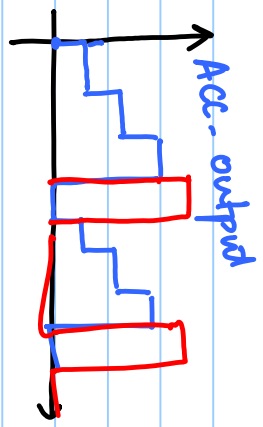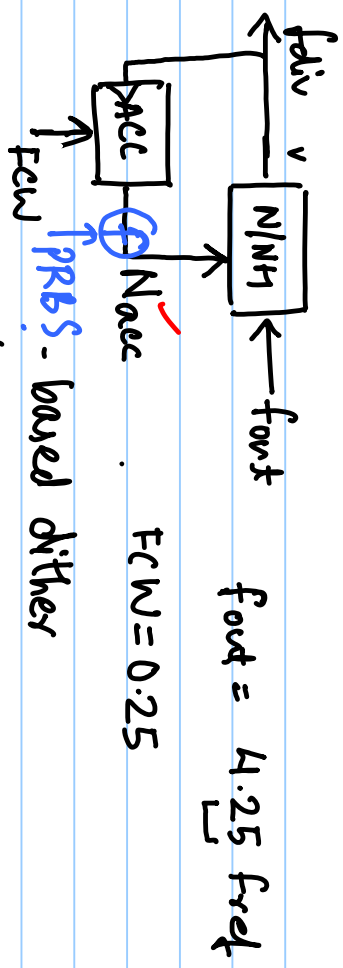

$$f_{cw} = .00000001$$




$$= \frac{1}{2^{28}}$$
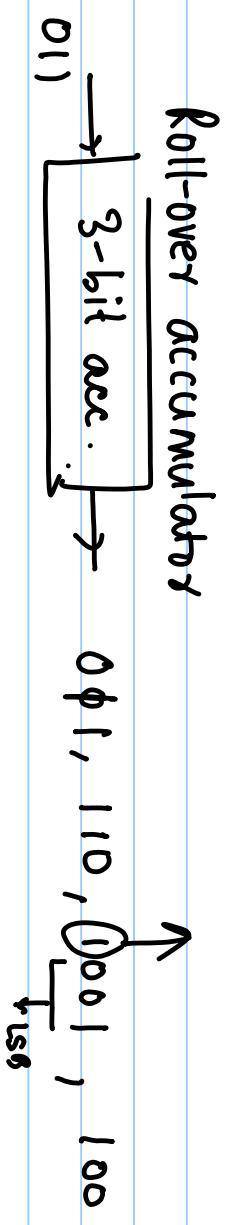
$$= \frac{1}{2} + \frac{1}{2^2} + \dots + \frac{1}{2^8}$$



Roll-over accumulator

Div-by- 4 4 4 5 4 4 4 5 4 4 4 5

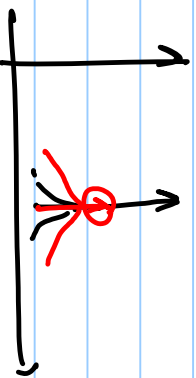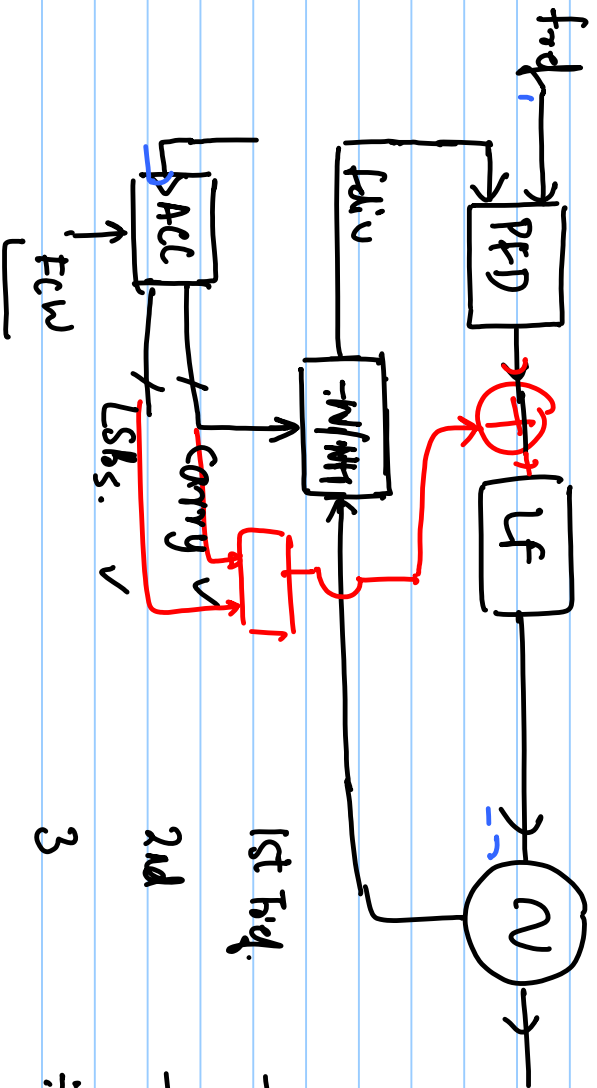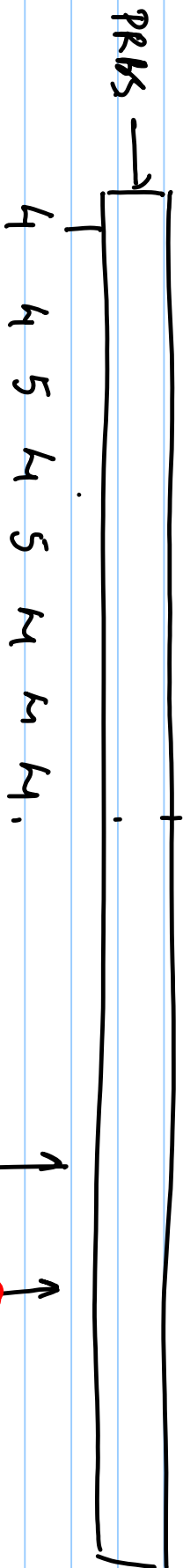

$f_{out} = (N + \alpha) f_{ref}$


$T_{req} = (N + \alpha) T_{out}$

1st Eq. $\div N$ Phase error = $-\alpha T_{out}$

2nd $\div N$ $\phi_e = -2\alpha T_{out}$

3 $\div (NH)$ $\phi_e = (3NH + 1) T_{out}$

= $(1 - 3\alpha) T_{out}$

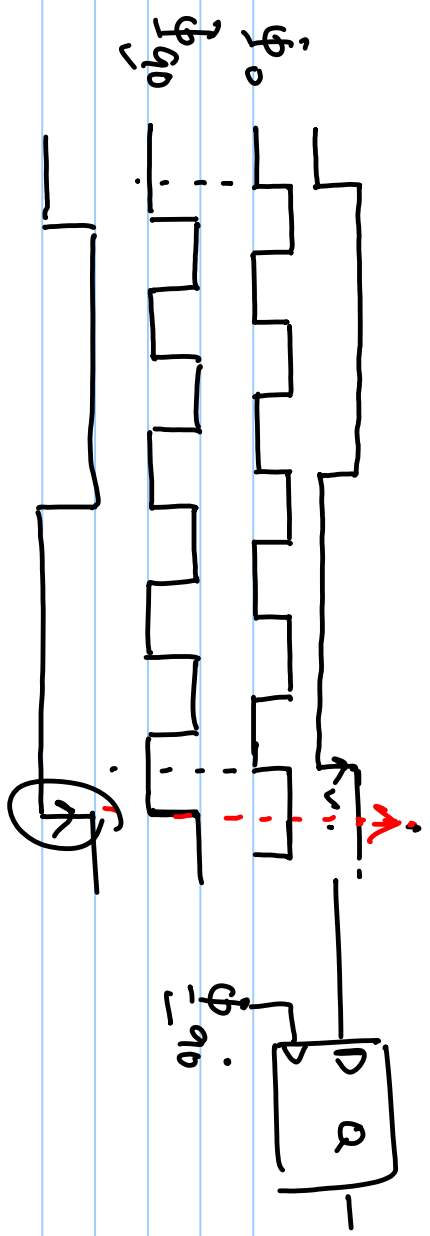

1