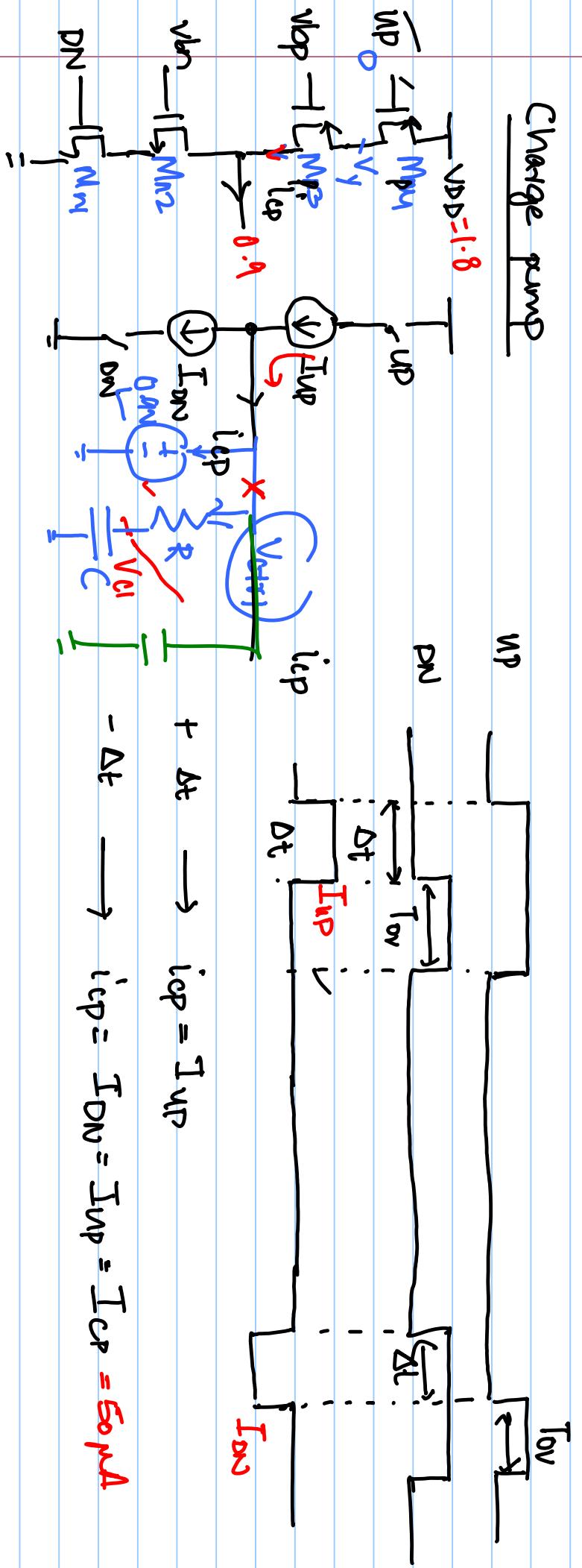


Lecture # 36Charge pump

$M_{N1}, M_{P1}$  as switches

$M_{N2}, M_{P2}$  as current sources in saturation.

$$V_{DS} = 0.85V \quad \left( \frac{0.21\mu m}{0.18\mu m} \right)$$


$$V_{DS} = 0.85V \quad V_{DS} < V_{GS}$$

$$V_{DS} = 0.85V \quad \left( \frac{W_P}{0.18\mu m} \right), \quad 50mA$$

$$V_{DS} = 0.85V \quad \left( \frac{W_P}{0.18\mu m} \right), \quad 50mA$$

$$I_{DS} = 50mA \quad \left( \frac{W_P}{0.18\mu m} \right), \quad 50mA$$
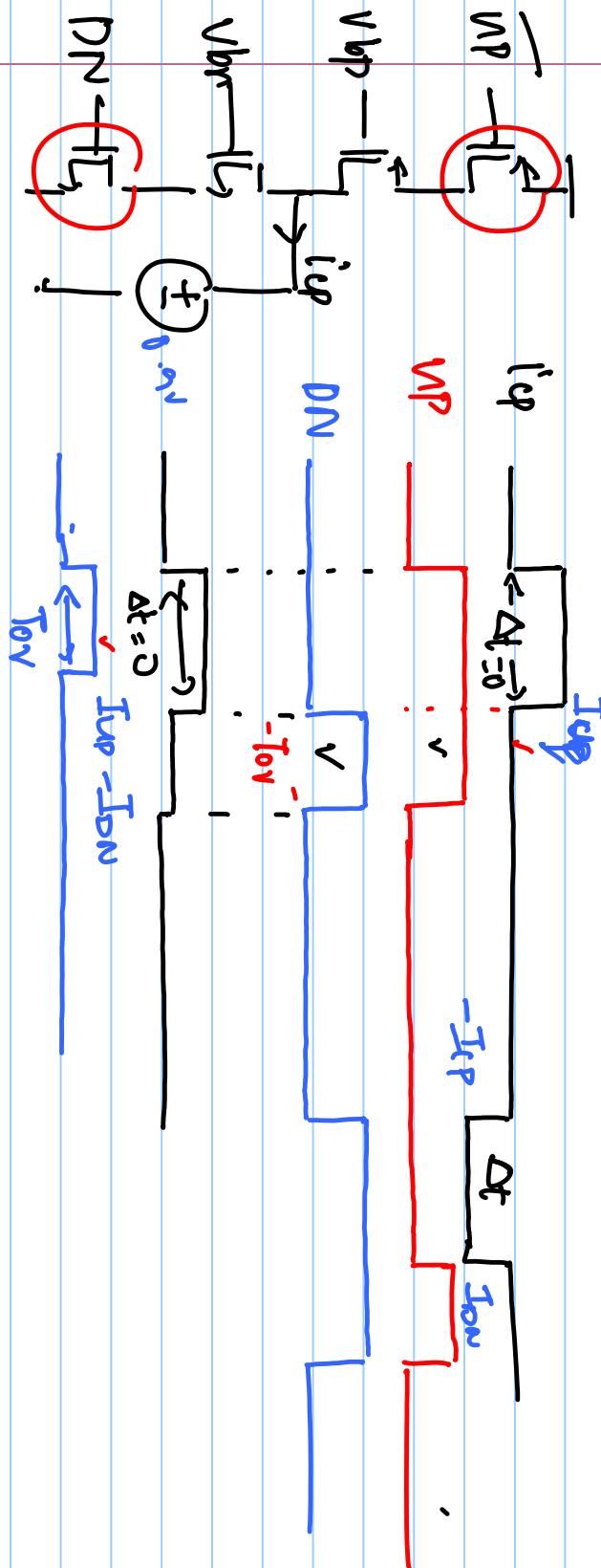
$$I_{DS} = 50mA \quad \left( \frac{W_P}{0.18\mu m} \right), \quad 50mA$$



$$I_{DN} \times T_{OS} = (I_{UP} - I_{DN}) T_{OV}$$

$$I_{DN} \times T_{OS} = (I_{UP} - I_{DN}) T_{OV}$$

$$I_{DN} = I_{UP} + \frac{\Delta I}{2}$$

$$T_{OS} = \left( I_{UP} - \frac{\Delta I}{2} \right) T_{OV} = \Delta I \cdot T_{OV}$$

$$T_{OS} = \frac{\Delta I}{\left( I_{UP} - \frac{\Delta I}{2} \right)} \cdot T_{OV}$$

$$I_{DN} = I_{UP} - \frac{\Delta I}{2}$$

$$I_{UP} - I_{DN} = \Delta I$$

$$V_{r1} = \int_C \int_{t_0}^t i_{UP} dt$$

$$V_R = i_{UP} \cdot R$$

$$V_R = (I_{UP} - I_{DN}) R$$

$$V_{ctrl} = f_{ther} + k_{vo} \cdot V_{ctrl}$$

$$I_{DN} = I_{UP} - \frac{\Delta I}{2}$$

$\omega_r$ : Reference freq. in rad.

$$f_{out} = f_{free} + k_{vo} \cdot \underbrace{V_{ch1}}_{\substack{\text{Fourier Series} \\ \text{V}_1}} \quad V_{ch1} = a_0 + \sum_n a_n \cos(n\omega_r t) + b_n \sin(n\omega_r t)$$

$$= f_{free} + k_{vo} [a_0 + a_1 \cos(\omega_r t)]$$

$$= (f_{free} + k_{vo} \cdot a_0) + k_{vo} \cdot a_1 \cos(\omega_r t)$$

$$\frac{V_{ch1}}{V_{ch1}} = \frac{1}{2} - \frac{V_{out}}{V_{ch1}}$$

$$V_{out} = \sin(2\pi \int f \cdot dt)$$

$$\begin{aligned} &= \sin \left( 2\pi \left( f_{free} + k_{vo} \cdot a_0 \right) t + 2\pi k_{vo} \cdot a_1 \int \cos(\omega_r t) \cdot dt \right) \\ &= \sin \left( \omega_0 t + \frac{2\pi k_{vo} \cdot a_1}{\omega_r} \sin(\omega_r t) \right) \end{aligned}$$


$$\underbrace{\omega_r}_{\beta}$$

$\rightarrow$  Bessel function.

$$\begin{aligned} V_{out} &= \sin \left( \omega_0 t + \beta \underbrace{\sin(\omega_r t)}_{\theta \approx 0} \right) \\ &= \sin(\omega_0 t) \cdot \cos(\beta \sin(\omega_r t)) + \sin(\beta \sin(\omega_r t)) \cdot \cos(\omega_0 t) \end{aligned}$$

$$\approx \sin(\omega_0 t) + \beta \cdot \sin(\omega_R t) \cdot \cos(\omega_0 t)$$
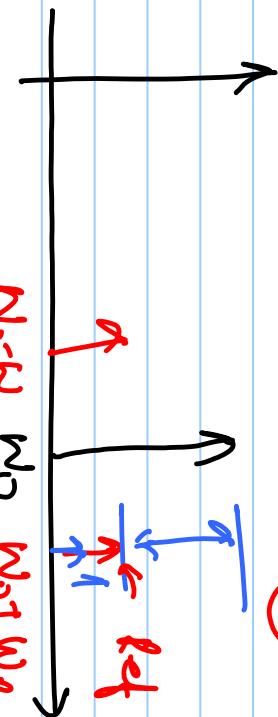
$$= \sin(\omega_0 t) + \left( \frac{\beta}{2} \right) \left[ \sin(\overline{\omega_0 + \omega_R} t) + \sin(\overline{\omega_0 - \omega_R} t) \right]$$



$$\overline{\omega_0} \quad \overline{\omega_0} \quad \overline{\omega_0 + \omega_R}$$

$$\text{Ref. Sprut} = 20 \log_{10} \left( \frac{1}{\beta/2} \right) \text{ dBc}$$

$$\beta = \frac{2\pi k v_o \cdot \chi}{N R} \alpha_1$$